# HiFi, Radio & Computers MESTA

FEBRUARY, 1979

AUST. \$1.40\* NZ \$1.40



**NEW "SUPER QUALITY" DISCS MADE FROM DIGITAL MASTERS ★ LOW COST EPROM BURNER**, SIMPLE TRAIN CONTROLLER

SPECIAL OFFER ON **TRANSISTORS: 20 FOR \$2.50** 



REVIEWED INSIDE: THE APPLE-II COMPUTER FREE LIFTOUT OG



ctual test, speakers should ced the same distance apart as you are away from them.

Here's the test. First, visit your Marantz dealer and listen to a pair of Marantz floor standing speakers placed in a normal listening position. Then, with your eyes closed, have the speakers turned until they're facing each other.
We're betting you won't be able to hear even a slight change in the sound ... because there won't be any! Unlike

conventional speakers that tend to beam certain frequencies in a narrow corridor (so you have to be directly in front of them to hear all the sound), the Marantz speakers disperse all the frequencies over a 180 degree listening pattern. Result: You'll hear the entire sound wherever you are in the room. Take the test at your Marantz dealer now.

Distributed by:

SUPERSCOPE (A'ASIA) PTY. LTD., P.O. BOX 604, BROOKVALE. NSW. 2100. Telephone: 939-1900

# ELECTROMICS

Austrolia

VOL. 40 No. 11 FEBRUARY, 1979

Australia's largest selling electronics & hi-fi magazine

STOP PRESS: Latest figures published by the Audit Bureau of Circulations (period April 1-September 30, 1978) show our circulation as in excess of 43,500 — documenting a lead of more than 15,000 over our nearest rival!



Built around a new Intersil evaluation kit, our new 3½-digit DVM features LCD readout, 10M input impedance, and four measuring ranges from 200mV to 200V. The details are on p54.

# 9kHz Whistle Filter . . .

Rid your AM/FM tuner of whistles with our new 9kHz whistle filter design. See page 58 for details.

# On the cover

The colour graphics display of the Apple II microcomputer system featured this month is nicely complemented by pretty Sungravure staffer Sharyn Keeble. For a detailed review of the Apple II by an experienced user, turn to p93. (Apple II system pictured is by courtesy of Computerland Australia.)

# FEATURES

rea lunes	
THE TELEVISION YOU CAN TALK TO! The TV set of the future	10 12
REMARKABLE NEW TV DISPLAYS Single-gun colour tube, LCD display	14 93
HIFI TOPICS AND REVIEWS	
DIGITAL RECORDING: DIRECT CUT QUALITY WITHOUT THE HASSLE	23 26
DIGITAL RECORDING REVIEWS Impressive quality and dynamic range	32
PROJECTS AND CIRCUITS	
BIPOLAR MODEL TRAIN CONTROLLER For model railroad enthusiasts	34
HIGH POWER 12-230V DC-AC INVERTER Design features overload protection	38
QUARTZ CRYSTAL CLOCK DRIVERFor Yaesu Musen clock	44
SPECIAL OFFER: 20 TRANSISTORS FOR \$2.50 Plus nine simple projects	54
9kHz WHISTLE FILTER FOR AM TUNERS Rid your tuner of heterodyne whistles	58
FAST/SLOW SCANNER FOR ICOM IC22S Scans 146-148MHz in 25kHz steps SIMPLE EPROM BURNER SUITS SC/MP & 2650 Program a 2708 in five minutes	60 84
EXPANDING THE MOTOROLA 6800 D2 KIT Backplane, card cage & power supply	96
A LOW-COST EPROM ERASER Simple, economical eraser for around \$30	101
AMATEUR RADIO, CB SCENE, DX	
CB SCENE: WHAT'S AHEAD FOR UHF CB? Success or obscurity?	105
AMATEUR RADIO Sydney Science Museum puts amateur station on display	109
BOOK REVIEWS Two books to assist the novice candidate	115 116
COLUMNS	
EDITORIAL The end of the cathode-ray tube?  FORUM They were worried about loudspeaker phase in the 1930s, but	3 16
THE SERVICEMAN When the data sheets are wrong, try mathematics	72
RECORD REVIEWS Classical	77770

# **DEPARTMENTS**

NEWS HIGHLIGHTS 4 — CIRCUIT & DESIGN IDEAS 69 — MICROCOMPUTER NEWS & PRODUCTS 90 — NEW PRODUCTS 118 — BOOKS & LITERATURE 123 — INFORMATION CENTRE 125 — MARKETPLACE 126 — NOTES & ERRATA 124, 125

RECORD REVIEWS Devotional, popular and jazz ...... 79



It's no wonder your records are flat.
Before they're pressed, about half of the music's dynamic range has been squeezed out.

The vice is the recording process. Live music's dynamic range can be more than 100dB, but the studio recorders have only 58dB of useable dynamic range capacity. So the engineer has to compress the signal, making the loud sounds quieter and quiet ones louder. And that's where the live gets squeezed out of it. Your con-

ventional discs offer less than 50dB of dynamic range.

You can undo much of the damage. Just add a dbx 3BX Dynamic Range Expander to your system, and you'll restore most of the missing dynamic range in your records, tapes and FM broad-

casts. The 3BX unsqueezes all kinds of music, making every-

thing sound richer, clearer and fuller than you've ever heard. And with dramatically less noise as well.

The 3BX works equally well with bud-

get-priced equipment and state-of-the-art systems. You won't need an audio engineer's ears to hear

the remarkable improvement in the quality of your recorded music.

But we suggest you hear it for yourself. Take your favorite record or tape to your dbx dealer and ask for a demonstration. Once you hear the 3BX in action, you'll wonder how you ever listened to music without it.

OX

SUPERSCOPE (Australasia) Pty Ltd P.O. Box 604 Brookvale, NSW 2100. Tel. 939 1900

3BX three band dynamic range expander





# **Editorial Viewpoint**

# The end of the cathode-ray tube?

**EDITOR-IN-CHIEF** Neville Williams M.I.R.E.E. (Aust.) (VK2XV)

**EDITOR** 

Jamieson Rowe B.A. (Sydney), B.Sc (Technology, NSW) M.I.R.E.E. (Aust.) (VK2ZLO/T)

> ASSISTANT EDITOR Philip Watson A.M.I.R.E.E. (Aust.) (VK2ZPW)

SCIENCE FEATURES Greg Swain, B.Sc. (Hons, Sydney)

> PRODUCT REVIEWS Leo Simpson

TECHNICAL PROJECTS David Edwards, B.E. (Hons, Tasmania) lan Pogson (VK2AZN/T)

> GRAPHICS Robert Flynn

PRODUCTION Danny Hooper

ADVERTISING MANAGER Selwyn Sayers

CIRCULATION MANAGER Alan Parker

One of the stories I think you'll find particularly interesting this month is the one starting on page 14, describing two new video displays which have been developed by Matsushita Electric in Japan. One of the displays is a new single-gun colour cathode-ray tube (CRT), while the other is a monochrome liquid-crystal display (LCD) panel which forms the heart of a tiny receiver.

The new colour tube is quite intriguing, as Matsushita has been able not only to produce a tube with only one electron beam and gun in contrast with the usual three, but also to do away with the conventional electron mask behind the phosphor screen. Until now, all colour tubes have had to have three electron beams and a mask of some sort to ensure that each beam only hit the dots or stripes of phosphor corresponding to the appropriate colour.

The new tube uses a multiplexing technique to fit all three resultant colour signals onto the single electron beam. Then it uses stripes of ultra-violet emitting phosphor so that the beam itself generates a feedback signal, which is used to ensure that the right colour signals are modulating the beam when it is over the various colour phosphor stripes.

This is certainly an ingenious approach, and one which seems to have many advantages: reduced power consumption, greater reliability and freedom from comvergence problems to name only a few. But somehow I personally find the little LCD monochrome display even more impressive — not so much for what it is at the moment, but for what it is likely to portend in the future.

To be sure, there have been LCD panels and other types of flat-screen video display under development in laboratories for quite a while now, and each one was signalled as the "beginning of the end" for the conventional CRT. But now, it seems, Matsushita has come up with a fully practical LCD panel, and is about to put it into production sets. It looks as if the writing really is up on the wall (panel?),

finally, as far as the CRT is concerned.

Perhaps in a way it will be sad to see the demise of the CRT, as it was after all the device which first made possible fully electronic television. Yet nowadays it is something of an embarrassment, its need for very high voltages making it scarcely compatible with modern solid state circuitry. Its departure, when it comes, will no doubt be a tremendous step forward in display technology.

- Jamieson Rowe

Registered for posting as a publication — Category B.

Printed by Magazine Printers Pty Ltd, of Regent Street, Sydney and Masterprint Pty Ltd of Dubbo, NSW, for Sungravure Pty Ltd, of Regent St, Sydney

**Editorial Office** 

57 Regent St, Sydney 2008 Phone (02) 699 3622 Postal Address: PO Box 163, Beaconsfield 2014.

**Advertising Offices** 

Sydney — 57 Regent St, Sydney 2008. Phone (02) 699 3622 Representative: Narcisco Pimental.

Melbourne - 392 Little Collins St, Melbourne 3000. Phone (03) 602 3033 Representative: Keith Watts

Adelaide - Charles F. Brown & Associates Ltd. 254 Melbourne St, North Adelaide 5006 Representative: Tom Duffy, (08) 267 4433 Perth — 454 Murray Street, Perth 6000

Representative: Ashley Croft, (09) 21 8217.

Subscriptions

Subscription Dept, John Fairfax & Sons Ltd, GPO Box 506, Sydney 2001

Enquiries: Phone (02) 20944, ext 2589.

Circulation Office

21 Morley Ave, Rosebery, Sydney 2018 Phone (02) 663 3911.

Distribution

Distributed in NSW by Sungravure Pty Ltd, 57 Regent St. Sydney; in Victoria by Sungravure Pty Ltd, 392 Little Collins Street, Melbourne; in South Australia by Sungravure Pty Ltd, 101-105 Weymouth St, Adelaide; in Western Australia by Sungravure Pty Ltd, 454 Murray Street, Perth; in Queensland by Gordon and Gotch (A'asia) Ltd; in Tasmania by Ingle Distributors, 93 Macquarie St, Hobart; in New Zealand by Gordon and Gotch (NZ) Ltd, Adelaide Rd, Wellington.

Copyright. All rights reserved

Devices or arrangements shown or described herein may embody patents. Information is furnished without responsibility for its use and without prejudice for patent rights. All manuscripts, photographs and other material submitted to Electronics Australia for publication must be accompanied by a stamped, addressed envelope. Contributions are submitted at the sender's risk, and responsibility for loss cannot be accepted by Electronics Australia.

\*Recommended and maximum price only



# **News Highlights**

# The computer you can ring and talk to! similar Assemble to the similar and talk to!

Researchers at Bell Telephone Laboratories have taken a major step in enabling people to speak directly with computers. They've devised an experimental system that can automatically provide directory assistance in response to a spoken request. The caller simply spells out the first five letters of the last name and then the initials.

The new system, which can comprehend most American dialects and some foreign accents, is able to understand a large number of people it has never heard before. This demonstrates one potentially simple and inexpensive

way to make the value of computers more directly accessible to the public.

Though this experimental system is still in the research stage, it does bring closer the day when people can simply ask a computer for information or services, such as booking an airline flight or filing a memo

or filing a memo.

The "ear" of the system is based on an automatic word recognizer devised a few years ago at Bell Labs. To recognize a spoken word, the computer quickly compares it with a file of stored reference patterns — representing the words in the computer's vocabulary — until it finds the closest match. The computer then produces a list of likely candidates in order of their

similarity to the spoken word.

A self-correcting strategy is also built into the system. If the computer makes a mistake in recognizing a letter, it's likely to look for a name that isn't in the directory. So when it fails to find a name, it knows it's made an error.

The system builds up the name letter by letter, from left to right, checking the stored telephone directory after each addition to make sure the combination of letters exists. When it fails to find a match, the computer immediately substitutes the next letter in its list of likely candidates and checks the directory again. The system works backward and forward along the sequence of letters in the name, substituting one at a time until it finds a perfect match.

The combined efforts of the word recognizer and the self-correcting strategy make the system right about 97 times out of 100.

# Writing aid/switch for the disabled

A typewriter that not only types, but can be used for switching electrical appliances on or off has been developed by a British company especially for the disabled.

Called "Popstar", it consists of a standard electric typewriter that fits into a special case. Using a hand or finger controlled joystick, a suck/blow unit or pressure pads for the hand, elbow or foot, a striker is moved up or down and from side to side along the keyboard to the appropriate key and then depressed. A variable speed adjustment enables the striker's movements over the keys to be increased or decreased to suit the skill and level of attainment of the user.

In addition to its use as a typewriter the equipment will also operate four pieces of electrical equipment simultaneously. The electrical appliances are simply plugged into the Typewriting for the disabled — Popstar can be operated using pressure pads, a joystick, or a suck/blow unit, and can be used to turn mains equipment on and off.




back of the equipment to a total loading of 13 amps. Because no special wiring is required, any appliance with a standard plug can be used. This could include an electric heater, a lamp, radio or television and an electrical door release.

The equipment is robust yet completely portable, needs no special installation and is expected to bring the benefit of communication and control to thousands of people to whom it has previously been denied. It is available in 220-240V and 110-120V versions.

Readers requiring further information should contact Rehabilitation Products Ltd, Pettaugh Lane, Gosbeck, Ipswich, Suffolk England. New audio/video equipment

from Japan

- Sony Corp has stretched the playing time of its pulse-code modulated (PCM) audio disc from 30 minutes to 2½ hours. The increased playing time was brought about in two ways: the disc rotates more slowly (450rpm vs 1800rpm), and has a higher recording density. Sony is currently investigating two more refinements. One would replace the player's helium-neon laser with a solid-state version; the other would slow the disc as the pickup moves towards the outer tracks, increasing playing time another 50 per cent.
- JVC has unveiled a new grooveless capacitive pickup "Video/Audio High Density Disc System". The player plays a 30cm plastic disc which contains up to two hours (both sides) of colour programs with sound. Alternatively, it can be used to play digitally recorded "super hifi" audio (PCM) discs, also developed by JVC. JVC says that no special components are required for player construction, and that both discs and players are economical to manufacture.
- Universal Pioneer recently put the finishing touches to its version of the

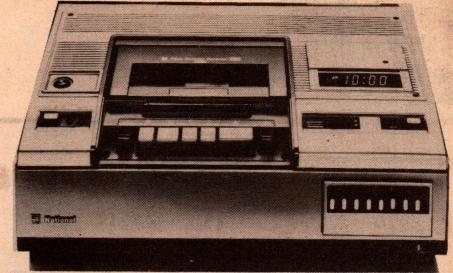

Recently released onto the Australian market, National's VHS VCR system is said to incorporate all the very latest features available in home video cassette recorders. These features include: a one-step 'M'-shaped tape loading system with a shorter tape path and quicker threading for faster response than conventional systems; a direct drive, quartz-locked head motor; and a one-piece, lightweight diecast chassis.

MCA-Philips optical video disc system and shipped several samples to MCA. The company is a joint venture between Pioneer Electric and MCA, and aims to start full-fledged exports

early in 1979. The discs are about the same size as ordinary audio discs, and give about 1 hour of colour programming. They can also be used for PCM recording and playback.

# "Projects & Circuits" aids the blind

For most people, pouring tea or coffee into a cup is a fairly simple operation, performed without any conscious effort. But how does a blind person perform this otherwise simple task? In particular, how does he know when the cup is full?

Obviously, it is a serious problem for blind people and, until recently, the Royal Blind Society of NSW imported a simple electronic device, from England, which solved this problem very well.

Unfortunately, the supply of these devices dried up, and the Society put the problem to their voluntary technical adviser, Mr D. A. H. Champion; a retired electrical engineer.

Mr Champion found that it was not possible to duplicate the English model, due to the lack of some special components. Then he came across a simple water level alarm circuit in our "Projects and Circuits" handbook (p89), originally contributed by Mr A. Mann of Victoria

Mr Champion obtained Mr Mann's permission to use the idea, and the result is the device in the picture. Most of the circuit is in the plastic box, including a small buzzer, with a sensor which hangs on the cup. The sensor

consists of two wires, insulated except at the tip, which complete a circuit through the liquid.

Two sensors are provided, of different lengths, one for cups and one for jugs, saucepans, etc. Their operating level can be adjusted by bending. No switch is needed and the battery should have a very long life.

Mr Champion builds the units on a voluntary basis, for the cost of components, and the Royal Blind Society sells them at a nominal price.



# \$172M FOR UK MICROELECTRONICS

Britain's microelectronics industry is to recieve a £100 million (\$172 million) boost over the next three years, according to an announcement by Prime Minister James Callaghan. This will bring the total sum committed to microelectronics by the government and private industry to more than £400 million (\$688 million)

Mr Callaghan emphasised the crucial role which microelectronics would play in the industrial future of the nation and said Britain was now

on the threshold of the most rapid industrial change in its history. He saw the development of an efficient microelectronics industry as a major element in future economic growth, and stressed the speed at which full adoption of the new technology must take place.

Government sources claim that Britain's investment stake in microelectronics is now bigger than that of either France or West Germany, and approaching the level of Japanese investment.

# **NEWS HIGHLIGHTS**

# New tuning system with non-volatile memory

EPM (Electronic Program Memory) is the name SGS-Ates has given to its new tuning system for radio and television receivers. The system features nonvolatile semiconductor memory for digital storage of tuning voltage.

EPM is a modular system with many options and can be used with or without remote control. Station search can be either automatic, semi-automatic or manual.

The heart of the system is the M 193, an LSI N-channel MOS circuit which includes non-volatile memory for 16

channels (no battery back-up is required). A special structure developed by SGS-Ates for the memory cells (NV-RAM) is the key to the exceptional information retention capability of the memory which is said to outperform similar devices.

Ancillary circuits for the kit include the M 190 16-key encoder and latch (for use in TV sets where a remote control system is not included), the M 191 onscreen tuning bar generator and the M 192 channel number decoder and LED display driver.

# Experimental telephone powered by light

Bell Laboratories researchers in the United States have devised a highly efficient light detector and transmitter to demonstrate the feasibility of operating telephones solely with the power of light transmitted over glass fibres.

They also devised a highly efficient means of converting electrical energy to sound energy for "ringing". Accomplishing this was very important since "ringing" takes much more power than any other function in a telephone.

The detector converts more than half of the light power to electrical energy — the highest photodetector efficiency yet reported. Moreover, the same detector doubles as a light source, greatly simplifying the problem of coupling separate detector and transmitter devices to the same end of a hair-thin fibre.

In a laboratory setup, a light-powered phone was connected to a simulated telephone company office over a one-kilometre length of glass fibre. The laboratory demonstration showed that light signals from a small semiconductor laser chip have enough energy to carry a range of telecommunications signals as well as power all the electronics in the telephone.

So, unlike various phones used today, a light-powered model would need no electricity (and no copper wire) from a telephone company office. Nor would it require any power from a wall outlet or self-contained battery.

# Electronic ruler with calculator



National Panasonic has developed a unique electronic ruler incorporating an 8-digit calculator with memory functions.

The ruler will measure straight or curved lines by means of a small wheel fitted to one end, and the resultant measurement can be fed directly into the calculator as a basis for computations. It is convenient for measuring distances on maps or charts, and in warehousing, textile, carpentry and engineering activities.

The electronic ruler, designated Model JE-8210 U, is available from electrical retailers, discount houses and department stores throughout South Australia for around \$64.00. Distribution will probably be extended to other states at a later date.

Further information from National Panasonic (Australia) Pty Ltd, 57-69 Anzac Parade, Kensington 2033.

# Vicom to distribute Jostykit

Vicom International Pty Ltd has been appointed Pacific area distributor for Jostykit of Denmark.

Jostykit is a leading manufacturer of high quality kits throughout Europe and is renowned for the attention given to aethestic design and presentation. The kits include comprehensive instruction booklets giving precise directions for assembly and testing together with circuit diagrams, drawings of components and soldering techniques.

Attractive Scandanavian-style extruded aluminium cases and knobs are available for most of the kits to give them a professional finish. About 40 different kits are now available and the range will later be extended to about 100 kits covering audio, laboratory, amateur radio and other interests.

# **News Briefs:**

# Australia buys Canadian satellite ground station

The Australian Department of Science is to spend \$C4.5 million with a Canadian company — MacDonald, Dettwiler and Associates Ltd — for a satellite ground station to handle data from the current Landsat earth resources technology satellites. The ground station is currently being installed near Alice Springs, and is expected to be operational by the end of 1979.

Landsat data has a variety of practical applications in the fields of agriculture, forestry, land use, mapping, geology, water resources, oceanography, and the environment. There are currently three Landsat satellites in orbit, and additional satellites are in the planning stages.

# NS to form joint company with Saint-Gobain

National Semiconductor Corporation has announced that it has reached a preliminary agreement with Saint-Gobain-Pont-A-Mousson to form a joint venture company in France to manufacture integrated circuits. Under the terms of the agreement, the new company will be 51 per cent owned by Saint-Gobain and 49 per cent by NS. Initial capitalisation will be 70 million French francs.

Your new distributor for

# HEWLETT IND PACKARD



# **CEMA ELECTRON**

If your needs are high efficiency lamps and displays, opto-couplers, microwave diodes and transistors, then Hewlett Packard has the product. Cema Electronics is the source.

# **CEMA ELECTRONICS PTY. LTD.**

21 Chandos Street, Crows Nest, N.S.W., Australia 2065. Telephone 439 4655. Telex 22846. P.O. Box 578. **MELBOURNE OFFICE:** 

208 Whitehorse Road, Blackburn, Victoria, Australia 3130. Telex 32295. Telephone 871 5311.



BRISBANE:

ADELAIDE:

CANBERRA:

PERTH:

WOLLONGONG:

**NEW ZEALAND:** 

22 Ross Street, Newstead, Qld.

Telephone 52 4261

170 Sturt Street, Adelaide, S.A.

Telephone 51 6483

Ortex (062) 824995

Macelec (047) 29 1455

Reserve Electronics (09) 275 2377 Cema Electronics (N.Z.) Ltd., 7-9 Kirk

Street, Grey Lynn, Auckland. Telephone 76 1169


PAPUA NEW GUINEA: Daltron Electronics, Boroko, Papua New

Guinea. Telephone 25 6616

# OWERSCOPE

A NEW CLASS OF OSCILLOSCOPE DEDICATED TO MEASUREMENT IN THE FIELD OF

# **POWER CONTROL**

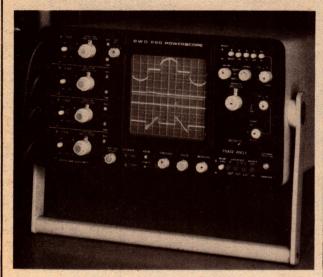

Safety engineered for DIRECT measurement of waveforms in AC and DC power lines

- 4 Channel differential input. 100mV to 200V/div. DC to 7.5 MHz.
- Common mode rejection 350V RMS (+500V)
- Maximum Input 660V RMS or ±1000V (3kV peak transient overload)
- 0° to 359° phase measurement with digital readout.
- 0°, 120°, 180° and 240° zero reference by push button selection.
- 100nSec to 10Sec/div. time base with phase delay trigger.
- Hazard-free operation with insulated controls, panel and probes.
- Powered-by single or two phase AC, DC, or optional battery pack.
- Supplied with 4 x 1:1 probes and 4 x 10:1 probes (3kV rating).

# OSCILLOSCOPES made to measure

# **ELECTRONICS PTY. LTD**

Miles St., Mulgrave, Vic. 3170 P.O. Box 325, Springvale, Vic. 3171 Phone (03) 561 2888 Cables: 'Oscilloscope Melb'

Telex: 35115

PS 881


DISTRIBUTORS N.S.W: (02) 888 8111 N.T: (089) 85 2249 QLD: (07) 52 7255 S.A: (08) 42 6666 (08) 212 3111

TAS: (003) 23 1843 W.A: (092) 25 3144


# NOW THE SENSATIONAL

1070 DYNAMIC

SPECTRUM'

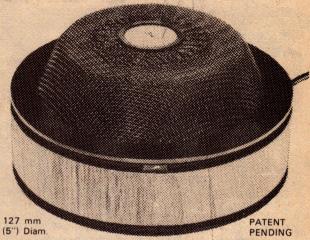

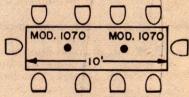The latest addition to the ASTATIC Studio. Entertainment, Paging, Public Address range of American Microphones — Famous since 1912.



The Sound Man's "Dream" for conventions. Vertically oriented carioid dynamic microphones.

- ☆ Special tailored frequency response
- A humbucking coil to minimize hum induction pick-up
- A superior mechanical shock-mounting system
- the lt is revolutionary and it really performs.

AND...two of the range of outstanding ASTATIC High Frequency entertainment and public address microphones.



# NOMIS ELECTRONICS PTY. LTD...

689 SOUTH RD., BLACK FOREST, ADELAIDE 5035. Phone (08) 293 4896

DISTRIBUTION: A limited number invited for some areas in N.S.W., Qld., Tasmania and W.A.

# **NEWS HIGHLIGHTS**



# Statement by Minister for Mines and Energy

The NSW Minister for Mines and Energy, Mr P. D. Hills, MP, has released the following statement regarding electrical safety standards:

"Few people would question the right of the public to expect that all electrical goods offered for sale in the market place are electrically safe and will remain so through their normal working life.

"The New South Wales Government therefore looks to all sections of industry engaged directly and indirectly in the supply of electrical goods to

the public to accept responsibility for ensuring that articles they handle comply with recognized electrical safety standards.

"Many appliances and some items of equipment have been specifically 'prescribed' under the Electricity Development Act in New South Wales and are required to be examined and approved by the Electricity Authority of New South Wales or an approvals body in another State, and to carry an approval marking, prior to sale.

"As the responsible Minister I also look to the Electricity Authority to monitor the general safety standard of electrical goods of different types offered to the public and to recommend application of legislative control

"I have been concerned to learn through reports of recent Electricity Authority inspections of electrical and electronic equipment of the type featured in the columns of some publications that many of the items examined do not comply with safety standards published by the Standards Association of Australia. Several cases have also been reported by the Authority of products which come within the scope of prescribing definitions being offered for sale without approval.

"In particular it appears not to be realised that the prescribing definition for 'Extra Low Voltage Transformer' includes a number of regularly advertised items such as power supplies of different types, antenna boosters and

"Most sections of the electrical industry supplying consumer goods have developed a safety awareness through knowledge of S.A.A. safety standards and regular contact with regulatory authorities on approvals matters.

"However it is clear that the popular electronics (hobby/enthusiast) section of the industry is giving insufficient attention to safety requirements.

"It seems clear to me that the first need is for people operating in this section of the industry to be better informed of their responsibilities and obligations in the electrical safety area. In New South Wales closer contact with the Electricity Authority would certainly assist in this regard and I have asked the Authority to give priority to fostering that contact in its safety en-

"Through these columns I also make a general appeal to manufacturers, importers and retailers in New South Wales to co-operate with the Authority and assist in ensuring that all popular electronics goods offered to the public

fully comply with Australian safety standards."

Editorial Note: Guidance and technical advice may be obtained by contacting your state regulatory authority. These are:

The Electricity Authority of New South Wales, 50 Miller St (PO Box 456),

North Sydney 2060. Telephone 92 4171.

The State Electricity Commission of Victoria, Monash House, 15 William St (GPO Box 2765Y), Melbourne 3001. Telephone 615 0433.

The State Electricity Commission of Queensland, Cnr Gregory Terrace and Warry Sts (GPO Box 10), Brisbane 4001. Telephone 52 2701.

The Electricity Trust of South Australia, 220 Greenhill Rd (PO Box 6),

Eastwood 5063. Telephone 223 0383. The State Energy Commission of Western Australia, 365 Wellington St

(GPO Box L921), Perth 6001. Telephone 25 0561. The Hydro-Electric Commission, Tasmania, 4-16 Elizabeth St (GPO Box

355D), Hobart 7001. Telephone 30 1101.

# Laser pin-points wafer defects

An experimental laser-scanning method that can detect microscopic defects in silicon wafers has been developed by IBM scientists. The method has potential importance, because even one such defect can cause the failure of a complete circuit containing thousands of transistors.

The surface of the silicon wafer is scanned with a laser beam. As it scans, the beam excites and frees electrons, some of which travel to the surface of the wafer and are detectable as a voltage. This voltage remains steady as long as the surface being scanned is

perfect.

When the beam passes over a defect, however, some of the excited electrons recombine in it, and the surface voltage drops. After the beam passes the defect, the surface voltage returns to normal. These voltage changes are registered on the screen of a cathode ray tube, forming pictures that can be interpreted as representing various defects such as scratches, cracks, dislocations, precipitates, and other imperfections.

The method takes a minute or less per wafer and can spot imperfections as small as 1 micrometre. Because the method is non-destructive, it can be used to examine silicon wafers for defects before devices are fabricated on them. It also offers the possibility of examining wafers at several stages in the circuit-manufacturing process in order to determine which steps need adjusting to improve the process yield.

# Sodium/sulphur battery for rail cars

A significant step forward has been made in the development of sodiumsulphur (Na/S) batteries for transport applications with the recent press announcement by British Rail that a 10kWh battery has been successfully activated. Initial tests have shown that the battery is safe, reliable and can be easily and quickly assembled. It is built from 176 cells and has a capacity of 288

ampere-hours at 45 volts.

The Na/S battery, which operates at 350°C, has a practical energy density of five times that of conventional lead-acid batteries. The UK Atomic Energy Authority's Harwell Research Establishment has been engaged on work involving the Na/S battery since 1972. During the last three or four years the battery has been developed jointly by British Rail, Chloride Silent Power Ltd (Runcorn), and Harwell in a collaborative national program.

British Rail's long-term intentions are to use Na/S batteries for light-weight

rail cars on branch lines.

The TV set of the future could guard your home, summon emergency services, and do your shopping. You could tell it when you're bored, and one day you may even vote with it from the comfort of your armchair.


# The television you can talk to!

# by SUE THOMAS

The television of the future will guard your home, do your shopping and entertain you. What's more, you will be able to talk to it!

Just press one of the buttons on the console, and you can vote on a local talent show, or book a restaurant. In time, you may even be able to elect the next prime minister, all from the comfort of home.

How will this be done? Well, the system is called "Qube" and Ronald Castell, Vice President of Marketing at Warner Cable Corporation, the people

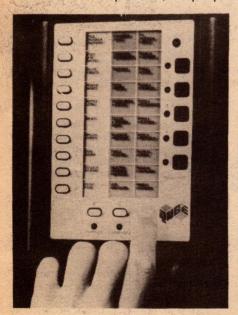

The 30-channel Qube home console. By pushing the appropriate buttons, viewers can choose programs and tell the television company what they think.

behind the project, says: "For the first time, viewers will be able to actively participate in the program they are watching."

So far, Qube has only been tested in one American town, Columbus, Ohio, but it's getting good reactions. One satisfied customer said: "You're just more part of it. It's a lot more fun knowing you're the one doing the judging.".

And judge they do. Every day on the community channel there is an amateur talent contest. Viewers can vote from their armchairs, and it's their vote that

Each performer has 40 seconds to do their thing before the audience is commanded: "Touch Now". The verdict is flashed on the screen. The people have spoken. The majority rules, and if more than half the viewers don't like the act it's goodbye to the contestant.

Gustave Hauser, Chairman of Warner Cable, believes that "people like to be involved with television beyond watching it".

"Maybe it's a response to loneliness but they seem to welcome being asked questions that they can answer by pushing buttons," he added.

One viewer has a more basic theory with regard to the talent show. "The kids love to watch it," he said. "They like to hit number four button — that's the hook that gets the guy off the

And it doesn't stop there. A live show could be stopped before its time if more than half the viewers don't approve. That would be fine if you're one of them, but not so funny if you're one of 49% who was loving every minute.

Qube families pay a small monthly subscription for the talk-back system. Each family is supplied with a small computer terminal, about the size of a shoebox, which sits under the television set, and a pushbutton console for the viewer to hold.

This has three columns with ten buttons in each. The "T" column is the one to press for regular channels, "P" indicates that programs from this column cost extra, and "C" indicates a community channel. It's the "C" channel that Qube viewers find the most exciting because this is the one which invites response via the pushbutton console. This is the one you can talk to!

How does the system work?

A dual cable feeds TV signals via the receiver to the computer terminal. Four central computers sweep the terminal every six seconds and record such detailed information as which sets are on, and which channels are being watched. They tabulate viewers' responses to spoken or written questions and can even record the reactions of individual homes.

But it's this ability of Qube to record individual viewing patterns that has made a few wary people wonder if the era of "Big Brother" is close at hand. The implications of Qube are obviously more far-reaching than simply voting on a local talent show. For instance, it could revolutionize the world of politics.

And while the prospect of an instant election by television terrifies many politicians, Qube officials are eagerly awaiting the one who makes a statement, and then dares to ask: "How many of you believed what I just said?"

But it is just these political implications that are worrying some people. They fear that politicians could phrase certain questions to ensure getting the answer they want. And the politicians worry that the box in the

corner will reveal things about them they might not wish to be known.

For instance, the extensive choice in column P allows the viewer to be his own TV programmer. On button 10, the P is for porn and viewers can ogle at the Khama Sutra riding again and again should they wish — for a modest fee, of course. The computer will bill them at the end of the month.

Another popular channel is called "drive-in" where blood and guts abound in quantities that would turn weaker stomachs.

And for those parents who might lose sleep worrying that their ten-year-old could be turning on to more fleshy temptations when left alone, there is the security of the Qube key which disconnects all pay programming.

But some people are worried as to whether they will be able to watch a few suspect films unnoticed.

"Would it not be possible," they ask, "for Qube to tabulate every pervert in the proximity who is tuned to channel P10?" Qube executives say no, the computer never records individual names and addresses unless the viewer wishes.

But Gustave Hauser has a suggestion which would make the feeding of a political candidates' lust to a hungry public impossible. "If you're in a position where you could be blackmailed, don't watch blue movies," he said wryly.

Harlan Kleiman, Vice President for Qube programming, is less flippant: "We have a time bomb here. We have to be extremely careful and set up very strict rules. If we abuse them, we're fools."

Qube isn't completely ready for large scale application yet, but in the meantime it is being kept busy. The constant monitoring makes alternative rating systems a thing of the past.

The central computer which sweeps the cables every six seconds reports back instantly to programmers exactly which programs are being watched. It can track down information that advertisers would kill for.

Gustave Hauser is confident that the commercial aspect of Qube will be a success. "Advertisers who are getting involved with Qube see it as a whole new way of relating to viewers," he said. "What's different about their adverts is that they are more information and research orientated. For the first time the advertiser can use television to have a direct dialog with the consumer."

Market research would be made simple. Advertisers could flash questions on the screen — "Which of these products would you buy? Which slogan do you prefer?" Predetermined viewers could receive product samples and then be quizzed on response. Advertisers could conduct magazine readership surveys. Viewers could be paid to participate.

"We can do research 88 ways," boasts

But there is a risk, Kleiman warns. "We have to be careful not to exploit it. There's a bell curve of interest. We have to be careful of reaching the point where the viewer says 'We'll pay you anything but please, please don't ask our opinion any more!"

Qube is there to help as well as to gain. It even has its own friendly fraud catcher in the form of Jon Steinberg, nicknamed Mr Qubesumer. He reigns supreme on Qube C6, where his acts on behalf of the helpless shopper are the stuff heroes are made of.

Every week he compares the prices in all the major regional shopping centres, to save thrifty housewives the trouble. Regular as clockwork, he transmits the relative prices of goods ranging from baby food to bourbon. Other days in

medical service.

An elderly or housebound person within 150 feet of home can press a "panic button" necklace, and within seconds an ambulance will be rushing to the scene, equipped with the victim's medical history and "even the phone number of the mother-in-law in California," says Mike Korodi, Qube's general manager in Columbus.

Other benefits that Qube offers would be invaluable to the aged and handicapped. For one thing, shopping could be done without leaving the home. The TV displays goods. A touch of the button brings the goods of your choice — and the bill — to your home. Restaurant bookings could also be made, and bank statements could be called to the screen at the push of a button.

Qube can be educational too.



A family in Columbus, Ohio, watch television using the Qube two-way system. The home terminal unit can be seen on the table top, in front of the TV set.

the life of Mr Qubesumer include exposing frauds, like the time he demonstrated that a bowl of soup at a local restaurant cost twice as much as a cup, when both held the same volume, and warning unsuspecting citizens that their "vine-ripened" tomatoes were really "gassed pink" in a nearby warehouse.

Adding to its talents, Qube will shortly offer fire and burglar protection, made possible by the computer's six second sweep of all households. These systems are armed with ingenious trick-proof codes. For instance, if a burglar forces the house-owner to disconnect the alarm, the warning sirens stop, but the computer passes on a "better hurry" message to the local police station.

Also coming soon is an emergency

Viewers can have various courses channelled into the living room at their request, whether it be to study anthropology or correct a golf swing. The obvious advantage of Qube TV courses is 2-way communication.

The professor might ask, "Am I going too fast?" or even "Am I boring you stiff?" Personal contact is important, and Professor Qube begins by checking the register — "Nice to see you back Johnny."

No doubts that Qube is versatile. It allows viewers to learn, buy, boo and vote from the comfort of home.

You may be able to talk to your TV sooner than you think!

Copyright Syndicated Features Limited, London.

# RCA 'Gold Chip' devices: improving IC reliability

One problem with conventional integrated circuits is that they are prone to sudden failure in very humid environments due to moisture penetration. This can be solved by using hermetically sealed devices but, up until now, such devices have been expensive to produce. Now RCA has come up with a low-cost solution to the problem.

# by BRIAN DANCE

One of the major causes of equipment failure in extremely humid or wet areas is due to the penetration of moisture into conventional plastic encapsulated integrated circuits. In the past, aluminium has been universally used for the interconnections on all chips, but is easily attacked by moisture. The latter may penetrate through the plastic material (especially if the environment is either acidic or alkaline), or may enter at the interface between the package and the leads. This penetration is greatly accelerated by rapid temperature changes or by severe mechanical shock.

The water converts the very thin

enter. For example, chips can be sealed into a cavity formed in a ceramic dual-in-line case, the cavity being filled with an inert gas and the pin connections "frit-sealed" with glass. Unfortunately such hermetically sealed packages are expensive to produce and devices using them cost several times more than a similar device in a conventional plastic dual-in-line package.

Hermetically sealed devices are therefore used mainly in military equipment and in equipment used in difficult environments where reliability is more important than cost. The home constructor seldom meets integrated circuits of this type.

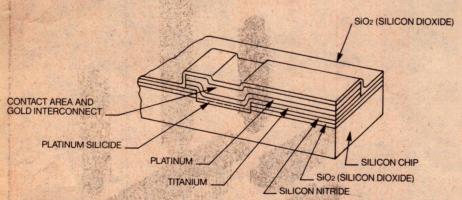


Fig. 1: Structure of a tri-metal device, showing different metal and passivation layers. Gold, platinum and titanium are the three metals used.

layers of aluminium on the chip into aluminium oxides and hydroxides, which have very low conductivity. Thus an open circuit can develop between elements on the chip of between one of the connecting leads and the chip, rendering the device useless.

It is, of course, possible to prevent this type of failure by using hermetically sealed packages which water cannot

# **Reducing the Cost**

In an effort to achieve high reliability and yet keep costs low, RCA has developed a process in which the hermetic sealing is accomplished not by sealing the device into a special package, but by sealing the chip of the microcircuit itself. This is done by depositing suitable metallic layers on the silicon chip.

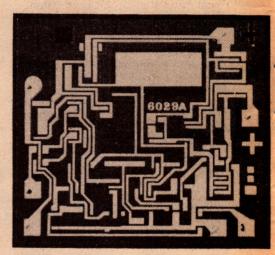


Fig. 2: \*Photomicrograph of CA741G chip shows gold metallization in areas where aluminium metallization normally exists (light areas in photo).

One of the main advantages of this new "hermeticity on a chip" process is that it can be carried out much more economically than hermetically sealing the microcircuit into a relatively expensive package. Indeed, the cost differential between the new process and that of conventional integrated circuit production is so small that RCA has been able to offer its new hermetically sealed devices for the same prices as devices manufactured by conventional techniques.

# The Tri-metal Process

Basically RCA's new "Tri-metal" process involves the application of three precious metals (titanium, platinum and gold) over the places where the individual transistors on the chip are interconnected. Thus corrosion failures are eliminated. Silicon nitride is used for passivation.

The device production follows the conventional procedure until the final oxide step. A layer of silicon nitride is applied at this point to hermetically seal the junctions. A standard masking operation is then used to open the contact windows. Platinum is sputtered over the wafer and is sintered into the areas where the contacts will be formed

so that it is converted into platinum silicide. Titanium and platinum layers are sequentially sputtered on the sur-

face of the wafer (Fig. 1).

The pattern of interconnections is defined in the platinum layer by the use of standard photoresist techniques. With photoresist masking, a gold layer is electrolytically plated on the platinum interconnecting runs to provide good conductivity. Finally a protective layer of silicon dioxide is deposited on the chip, as in conventional integrated circuit production.

## The Three Metals

The titanium is used to improve the adherence of the metals to the silicon nitride. The platinum acts as a barrier layer between the titanium and the gold layers, whilst the gold provides the high conductivity and a reliable metallization pattern.

# Types Available

RCA has made six device types available with hermetically sealed chip surfaces. These have the same characteristics as other standard devices, but a letter "G" is added to the device coding to identify the "hermetic-in-plastic devices"

One of the new devices is the CA741CG, this being equivalent to the standard 741C operational amplifier in an 8-pin dual-in-line case. The CA747CG contains two 741C type operational amplifiers in a single 14-pin dual-in-line case. CA741G and CA747G types are also available, these being equivalent to the 741 and 747 devices.

Another hermetically sealed chip is the CA324G, this being a quad operational amplifier. The four amplifiers in this device are especially convenient to use, since they have been designed to operate from a single supply voltage of any value between 3V and 30V, whereas most operational amplifiers require balanced positive and negative supplies. Electrically, the CA324G is equivalent to the 324 device and will operate linearly even if the input voltage falls to the negative supply line potential.

Another device is the CA339G, a guad voltage comparator which is electrically equivalent to the 339 device. Other Gold Chip devices include the CA3724G and the CA3725G high current NPN transistor arrays. Further devices will be added to the range in the near future and will include completely new devices as well as Gold Chip versions of established devices.

The new devices are called "Gold Chip" devices, the "Gold" signifying both high quality and the metal used in the final conducting layer. The new hermetic devices are manufactured at the RCA Plant in Findlay, Ohio. It is not intended that they should ever replace devices with conventional aluminium metallizing, since there are many

applications in which aluminium corrosion is not a problem.

# **Testing**

Samples of the new devices have been submitted to the Electronics Technology and Devices Laboratory of the US Army Electronics Command for testing at their tropical test centre, Panama Canal Zone. After nearly a million device operating hours, there has not been a single failure. The devices have also been tested in "pressure cooker" types of equipment where they are tested at high pressure and high temperature (202 kilonewtons/m<sup>2</sup> and 121°C for 250 hours). Again, there has not been a single failure.

Accelerated life tests thus far indicate a mean time before failure of about 30 million hours.


# **Applications**

The new Gold Chip devices are ideal for use in mobile communications equipment, such as 2-way radio equipment for police, fire, military and forest patrol use. They are also suitable for use under the bonnet of motor vehicles where sudden temperature and humidity changes occur.

Other applications include marine equipment, portable instruments and control and monitoring equipment at unattended locations where weather conditions may be extreme.
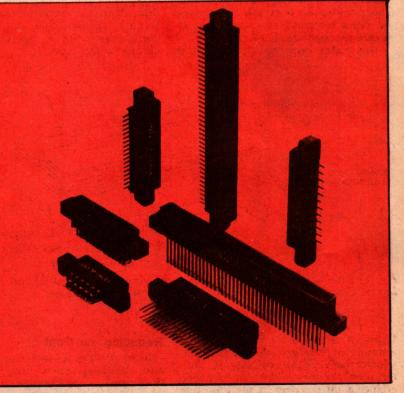
# **TEKA** printed circuit connectors ...

a new series of edgeboard connectors utilising the most advanced materials and finishes to furnish extremely high performance at low cost.





# C&K Electronics (Aust.) Pty Limited

Office 2/6 McFarlane Street Merrylands NSW 2160
PO Box 101 Merrylands 2160 Telephone 682 3144 Telex AA23404

Agents Melb. 598 2333/Adel. 269 2544/Bris. 36 1277/Perth 458 7111

Obligation free and comprehensive data is yours for the asking

PSST!... wanna buy a television receiver that you can put into your pocket? Or how about a portable colour model employing a single-gun colour tube? Matsushita has already developed these remarkable products, and will launch them onto the world market in the near future.

# Remarkable new TV displays

Two highly innovative TV receivers have been announced by Matsushita Electric Industrial Co Ltd, Japan. One is a pocket-size monochrome TV which uses a 6cm (diagonal) liquid crystal display (LCD) in place of a conventional cathode ray tube; the other is a portable colour TV using a single-gun, single-beam tube that has no shadow mask!

A shadow mask is an indispensable component in conventional 3-beam colour tubes.

Both new displays are compact in size and are designed for low power applications. Matsushita initially plans to use them in battery-powered portable TV receivers.

Marketing plans for the pocket TV with LCD have not yet been determined. Matsushita says it first plans to develop a more compact unit with even lower power consumption.

Single-gun, single-beam colour TV


receivers for both NTSC and PAL systems have now been completed and, according to Matsushita, will be ready for export towards the middle of this year.

# **Pocket TV with LCD**

The cigarette case-shaped pocket TV receiver measures a compact 118mm x 115mm x 34mm (L x W x D), and weighs in at just 640 grams. The new LCD flat-screen display is attached to the inside of the lift-up lid, measures 36 x 48mm, and comprises an array of 240 x 240 picture elements. Matsushita says that the number of picture elements, 57,600, is the highest ever for an LCD TV, and results in good picture quality.

Power consumption is said to be just 1.5W, and this allows three hours of continuous use with two lithium batteries (4.6V).

Matsushita claims to have solved the

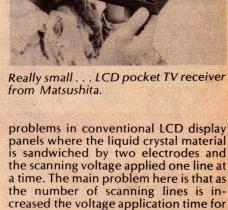

cuitry becomes bulky and complicated.
Matsushita has solved these problems by sandwiching the liquid crystal between a front glass electrode and an IC array. The TV signals are temporarily stored in capacitors and then discharged to drive each picture element. High density mounting and low power consumption are attained by using CMOS ICs in the drive circuitry.

The concept of a "display IC array" is

each line becomes shorter, resulting in

reduced contrast and response speed. Also, when the number of picture elements is increased, the drive cir-

The concept of a "display IC array" is a major technical advance, according to Matsushita. Production of the array required a great deal of research and development effort, and resulted in the development of a new photo-process technology capable of integrating more than 110,000 elements onto a silicon substrate. These elements include the





Single-gun, single-beam colour TV tube without shadow-mask (left), and two 10cm colour TVs using the tube.

57,600 capacitors which correspond to

each picture element.

The liquid crystal used in the new TV is of the dynamic scattering mode type, and is said to give a clear monochrome picture even when viewed at an angle. Other advantages of the LCD display include its low operating voltage and its excellent visibility in bright light.

# Single-gun, single-beam colour TV

Conventional colour TV receivers all employ a shadow mask in the picture tube — a thin steel plate which carries a pattern of holes or slots and which ensures that the beams from three electron guns strike the appropriate colour phosphors. This method has the disadvantage that power is wasted by the shadow mask (only about 40 per cent of the electrons get through the shadow mask), while the use of three separate electron guns increases power consumption even further and causes convergence problems.


Matsushita's new colour tube, on the other hand, uses only a single gun and has no shadow mask. Instead, the shadow mask is replaced by stripes of fluorescent material which emit ultraviolet light when struck by the electron beam. The emitted light is detected by a photomultiplier tube and the output signal used to multiplex colour infor-

mation onto the single gun.

According to Matsushita, the single-gun structure reduces power consumption by about 40 per cent when compared to a conventional tube of the same size. Power drain of a newly-developed colour receiver employing the tube is only 7W, as against 12W for a comparable earlier model. A further major advantage of the single-gun structure is that it eliminates convergence problems.



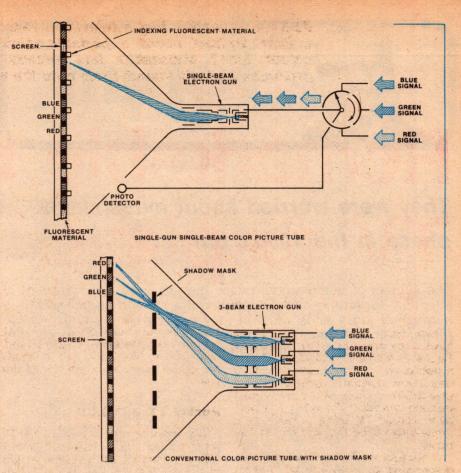Side-by-side comparison of compact TV displays. Colour receiver at right will be marketed later this year.



Basic structure of single-gun picture tube compared to conventional tri-gun tube. Indexing material is on back of black matric stripes.



# 3RD FLOOR, EQUITABLE LIFE BUILDING, 301 CORONATION DRIVE. BRISBANE 4064. PH. 36 1257.

# 3 HOURS VCR VIEWING



3 hours continuous recording/playback. 1-2-3 operation simplicity. Video head and azimuth recording system: key to perfect picture reproduction. The ingenious yet simple "M" loading system, low 35 watts power consumption.

## VIDEO EQUIPMENT -

Sony, Akai and JVC Colour and BW Portopacks. We have several BW Portopacks traded on colour sets. Also agents for JVC, National, Sony and Nec Umatic equipment. All formats and brands colour and BW recorders, editors, generators and blank video tapes available. New and used equipment. Trade and terms.

Specials. Also transfers from Super 8 film to video tape.

## VIDEO MOVIES

# FULL LENGTH FEATURES — MANY TITLES AVAILABLE AUSTRALIA WIDE


These movies suitable for all video players including U-matic, Philips, Grundig One, and two-hour machines, Betamax and VH(S).

Movies available in all classifications from G to R rating.

We require dealers and franchises in all states
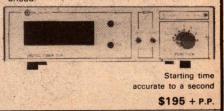
# SPECIAL CLOCK TIMERS

Can be set to switch equipment up to 4 days ahead.



FRANCHISEES REQUIRED FOR S.A., W.A., VICTORIA AND TASMANIA



# They were worried about loudspeaker phase in the 1930's but ...

The subject of audio signal phase has received a fair amount of attention during the past 12 months, but we find ourselves with a number of loose ends which it may be as well to tidy up. These range from one suggestion as to where it all began, to another which writes phase off as a non-issue!

The first suggestion, an historical reference, was brought to our notice by a reader H.S. of Bulimba, Qld, and is in the form of a photostat of pages 31 and 32 of "High Fidelity Techniques" by James R. Langham, Gernsback Publications Inc, New York, 1950. It refers, in turn, to a situation which obtained in early sound movie theatre practice, and which I retell, substantially as I've heard it through the years:

Around about the time that "talkies" were introduced, dynamic (i.e., moving coil) loudspeakers came into vogue and these made it possible for listeners, in both theatres and homes, to hear reproduced sound containing a substantial bass content.


Prior to that, with the old gooseneck horn and unbaffled cone speakers, bass had been implied rather than heard. With the arrival of dynamic speakers — and in a classic over-reaction — weight of bass became one of the criteria by which sound quality was judged!

Theatres were in a good position to give expression to this because they had — by the standards of the day — very powerful amplifiers, large and efficient loudspeakers, and a fair amount of room behind the screen to deploy loudspeaker enclosures. What should be more natural than to mount the woofer at the small end of a large, folded exponential horn with a mouth aperture large enough to stand in? Separate drivers, usually in smaller horns, were provided for the midrange and treble.

The efficiency was high, the bass was ponderous and the sound on most material very impressive — again, by the standards of the day.

But there were some sounds that didn't fare too well: percussive sounds, like the tap dancing of Fred Astaire and his contemporaries. Apart from the problem of picture/sound synchronisation, the sound itself seemed to be dismembered, with the "click" obviously leading the "thump".

Here I must confess that I am relying entirely on what I have been told. My own experience of talkies during the period was largely confined to country situations, involving the local Mechanics' Institute and such places. There were no large horns and the audience had to grapple with more elementary acoustic problems: like subjectively differentiating between the sound from the loudspeakers and echoes bounced off the galvanised iron

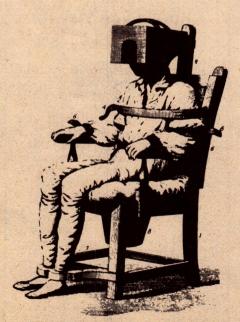

"You're right, you know. It certainly tightens up the phase response!"

roof - or the noise of passing trains!

However, in more "refined" situations, it was soon realised that the problem of Fred Astaire's hoofbeats arose from the very different path length for the high frequency components, compared with the bass energy working its way through a long, convoluted horn.

As Langham points out in the aforementioned textbook, the movie industry smartly settled for the alternative of a much shorter bass horn expanding rapidly from a large "throat" that often accommodated four 15-inch drivers. This greatly reduced the disparity in path length and in bass/treble timing or phase.

Again, according to Langham, quite a few private hifi enthusiasts (pre 1950) had to learn the same lesson. Their ponderous horns, built into the corner of the room, or down the unused chimney, were magnificent on some programs, but . . . and I quote:

"On organ records it isn't at all bad—the bass notes come booming out beautifully. But play that one section of Tchaikowsky's Fourth, with all the pizzicato strings, and it sounds crummy!"

In so saying, one can almost hear the cheers of the present day champions of linear phase loudspeaker systems—those units where the tweeter and midrange units have been set back by a few centimetres to equalise the path lengths to the listener's ears. Seemingly, the observations dating back forty years or more, lend maturity and credence to what might otherwise be seen as the latest hifi fad.

In fact, I doubt that they do. The historic situation concerns allegedly obvious effects arising from path differentials measured in feet; present day phase linear arguments are concerned with path lengths measured in inches (oops, millimetres) and effects which are, at most, extremely subtle. There is a huge difference in degree.

I am aware, of course, that in the April 1978 issue I recounted a demonstration set up Technics engineers in Osaka, which seemed to indicate that differences between high and low frequency drivers did produce an audible effect.

In conversation since then, quite a few audiophiles have re-echoed the reservations expressed in that article as, for example:

• In the test reported, a difference was observed using a square wave from a mono source in an anechoic chamber. It cannot be assumed that it would be apparent with program signal from a stereo pair in a normal room.

• Merely to note a difference does not mean that the respective sounds are right or wrong. Moving a microphone arbitrarily in a studio in relation to a sound source will also produce a difference!

• The phase relationship of audio signals suffers multiple arbitrary

The waveform at the top is a copy of one specifically referred to in "HiFi Topics" elsewhere in this issue. The lower waveform results from shifting the instantaneous phase of the same three components. To the eye, the resultants have obvious differences; the as yet unresolved argument concerns whether such a difference is apparent to the ear.

variations along the complex chain between the mic. diaphragm and the amplifier output terminals. Why seek to preserve in the loudspeaker a relationship which is arbitrary, elsewhere?

While prepared to concede these very practical objections, our own attitude was to accept the phase linear concept as a technically valid step in the right direction, even though it may not be subjectively very significant at this point in time.

We finished up with a warning that: "A manufacturer who spends more money on a stepped enclosure and then compensates by using cheaper drivers might well effect an "improvement" sideways or backwards!"

Incidentally, in seeking to illustrate "HiFi Topics", and the spillover into these columns, we went a step further than usual and opened up a line of thought which I can't remember having heard expressed before.

Most observations and articles to do with phase involve square waves or other contours formed from harmonically related sine waves. In either case, the contour can be plotted or viewed on an oscilloscope, and does

not vary with time.

Our own illustration was based on three waveform segments, with the centre one not harmonically related. When we asked our draftsman to fiddle the phases and produce another contour for purpose of illustration, he made the very valid observation that, with non-harmonically related waveforms, the contour would itself be constantly changing and would in fact, tend to be cyclic or repetitive. Any contour he might draw would be approximated naturally in due course.

And, when you think about it, the components in normal program material are never phase locked in the way they are from a square wave generator. Even in an ostensibly sustained chord, they will drift to form an ever-changing pattern. Can a listener really be expected to discern a specific change in a pattern that is, itself, subject to constant change?

Put like that, it would seem that, if phase is going to have any audible effect, it will be confined to transients, not of the "Fred Astaire" kind, but at the percussive leading edge of er . . . er ... er ...

Audio resultant waveforms

In the light of all this, it was intriguing to hear a spirited reply to a question on the subject by Vice President of AR (Teledyne Acoustic Research), Herb Horowitz.

As reported in our last issue, Herb Horowitz was in Sydney to explain and demonstrate his company's current line of loudspeaker systems, including the new AR-9 designed to be "the best speaker in the world". But the AR family is noticeably flat faced, as compared with the protruding chins of many of their phase-linear rivals.

How come?

According to Herb Horowitz, Teledyne engineers made a special study of papers on the subject and discovered a basic flaw in the maths. The engineers were keen to make a "big deal" of their discovery but were restrained by AR management on the grounds that prizes are not awarded for being negative! However, Herb Horowitz indicated that the word had got around and that we could expect to see some of the champions of phase linear loudspeakers backing off from their earlier attitudes.

It will be interesting to see whether this does, indeed, happen!

One other observation about phase relationships flows from the Topics" feature elsewhere in this issue. In constructing a resultant from three sine waves, and talking about preserving that resultant, I made the deliberate decision not to complicate the discussion by bringing in the subject of phase.

In fact, by simply shuffling the phase relationships of the components relative to one another, the original contour of Fig. 1d becomes something

quite different, as indicated.

Phase shifts of this kind will occur along the recording and amplifier chain, if only because frequency conscious networks and processes are involved. For this reason, if for no other, the groove tracing on a mono, lateral disc will be an audio resultant

# You won't want to miss this ...



# 27 DO-IT-YOURSELF PROJECTS FROM "ELECTRONICS AUSTRALIA"

If you like building electronic projects in your spare time, you can't afford to miss out on this exciting book of popular projects. There's a tacho, a dwell meter and a CDI unit for your car; a model train controller; a Doppler burglar alarm; a digital clock; a loudspeaker protector; a variable power supply; and a windscreen wiper control unit . . . plus much more. Order your copy now!

Many projects suitable for the beginner!

**ONLY \$3.00** plus 60c pack & post.

Available from "Electronics Australia". PO Box 163, Beaconsfield, NSW 2014. Also from 57-59 Regent St, Sydney.

# REAL POWER LINE UP

sanwa

# N-501

2μA suspension movement 0.05mA/1mV resolution

Double protection - fuse

Constant 1MΩ input impedance (ACV) - RF-diode rectified current direct to



# **U-60D**

44µA movement - quality



# **AX-303TR**

44 A meter movement -Si diode protection against pulse input. Measures hFE (0-1000) by using the extra connector.



# **BX-505**

Fast-response, 24µA movement - fuse & diode protected with high resolution factor. (0.4µA/scale division) Revised scale marking intermediate readings readily determined.



performance, diode protected.

of -30°C to +150°C with extra scale.



# PDM-500/C

Performs as low resistance ohmmeter besides insulation

Measurement, scale calibration and battery check are all operated by pushbutton

Has constant voltage impressed irrespective of the value of resistance checked.

# **CAM-250D**

Clamp meter

Economical and multi-function. Single motion core

Compact yet provides 4 ranges on ACA and 2 ranges on ACV.



# N-501

±DCV 0-60m 0-0.3-1.2-3-12-30 0-120-300-1.2k-30k (w/HV probe) ● ±DCA 0-2 µ 0-0.3-0.3-1.2-3-12-30m 0-0.12-0.3-1.2-12A

ACV 0-3-12-30-120-300-1.2k ±2.5% Freq. 20Hz to 50kHz • ACA 0-1.2-12 • Ω x 1-x10- x 100-x 1k-x 10k-x 100k(max. 200M)Batt. 1.5V x1&9Vx1 • dB -20 to +63

# **AX-303TR**

± DCV 0-0.3-3-12-30-120-300-1200 • ACV 0-6-30-120-300-1200 • ± DCV 0.60µ -3m-30m-0.3-12 •  $\Omega \times 1 - \times 10 - \times 1k - \times 10k$ (max. 20M)

## U-60D

• DCV 0-0.1-0.5-2.5-10-50-250 -1k-25k (w/HV probe) • DCA 0-50 u -2.550-500m • ACV 0-2.5-10- $50-250-1k \bullet \Omega \times 1-x \cdot 10-x$ 100-x 1k (max. 5M)

# **BX-505**

±DCV 0-0.12-3-12-30-120-300-1200-30k (w/HV probe) ● ± DCA 0-30µ -3m-30m-0.3-12 • ACV 0-6-30-120-300-1200 • ACA 0-12 • Ω x 1-x 10x 1k-x 10k (max. 20M)

## **CAM-250D**

● ACA 6-30-60-300 ● ACV 300-600 • kΩ 0-50k • Batt.

## PDM-500/C

V/Ω rated 500V/100M

 Scale range 0-0.1-100-200m (1st effective scale range underlined)  $\bullet \Omega$ 0-100Ω • Power source AM or UM-2 x 3



WARBURTON FRANKI

 ADELAIDE 356-7333 • BRISBANE 52-7255 • HOBART 23-1841 MELBOURNE 699-4999 • PERTH 277-7000 • SYDNEY 648-1711

AUCKLAND N.Z. 79-7781 • WELLINGTON N.Z. 698-272

# FORUM — continued

waveform but not necessarily of the same visual shape as at the amplifier in-

Ideally, I suppose, after all the fiddling in the recording and amplifier chain, the ultimate output waveform should be the same as the original input, with components, amplitudes and phases restored to the original relationship. But that's really what the argument is all about.

The traditional view, supported by a wealth of traditional research is that the ear is sensitive to frequencies and amplitudes but not to relative phase; that changes in contour, shown up by plotting, or as depicted on an oscilloscope are purely visual, with no auditory significance.

But the phase linear proponents think otherwise. And that just about brings us back to where we were in April last!

# "NOISE FREE" RADIO

To change the subject, we reproduce the letter below from a New South Wales reader, concerning car ignition hash and FM radio. The whole subject was raised by a correspondent J.R. in the September issue and, as noted above, mentioned further in December.

J.R. was concerned because his reception of FM/stereo, in an ostensibly reasonable location, was bedevilled by ignition interference from passing cars. We tended to blame his antenna or his tuner but left the matter open with the thought that other readers might have similar problems. If they have, they have been remarkably reticent, remarks being confined to FM interference problems in vehicles.

We'll leave that subject open, too, to see what comes out of it but, in the meantime, I note T.B's reference to antenna polarisation.

Early in the piece, the now defunct Australian Broadcasting Control Board adopted the guideline for FM that the transmitted signal should have the same polarisation as had already been set for television stations in the relevant areas. This meant horizontal for most places, but vertical in a few others, and notably in Canberra.

It seemed a fairly routine decision at

the time, with the conveniece that listeners could take a split from the TV antenna to feed the FM tuner.

More recently, it has become apparent that the majority of FM receivers in use will be portables and car radios, in every case with a vertical whip. About the worst signal you can provide for them is one that is horizontally polarised! Yet to standardise on vertical polarisation would be to disadvantage users of more elaborate equipment operating from a TV or TV-style antenna

The seemingly obvious course is to standardise on mixed polarisation for all FM stations in Australia, with signals having both a vertical and a horizontal component. Based largely on overseas experience, it would appear that circular polarisation is the best all round proposition, giving the listener the choice of either a vertical or horizontal antenna, or a more complex unit designed to take full advantage of the signal.

The problem seems to be that the present administration hasn't yet got around to confirming a standard based on local findings. In the meantime, we're likely to end up with a true mixture of polarisation, with some stations following the old guidelines and others, with departmental acquiescence, taking a punt on circular!

The way things look at present, the answer will be established by practice and confirmed officially mush later.

# More about ignition hash and FM

Dear Sir,

I read with interest, in your December edition, Mr William's article about "FM AND IGNITION HASH" and the letter from Mr N. H. about Melbourne problems in mobile FM reception.

As I have been involved for a long time in car radio and car interference

suppression development, I felt that I should add a few words.

It is true, that interference was almost an insurmountable problem when FM reception was first introduced into mobile applications. The car wiring and even the chassis and the body are very effective radiators and reradiators around 100MHz. Metal panels, which shield effectively on medium wave lengths become vicious interference sources and aerial cables if not terminated with the correct characteristic impedance can add to the difficulties.

Even so, with a lot of care and time, and fully understanding the sources, any car can be made interference free while it is alone on the highway. As soon as another car approaches the whole procedure is wasted!


This has been realised by quite a few FM radio manufacturers and several methods were developed which solve this problem by selecting out the offending pulses and cancelling them by phase reversion. The electronics is involved but still far more simple than the microprocessor controlled car radios, which soon will appear on the market, and it works very well.

These devices are sold either as additional suppressors or are built into better products. As with most devices these days, they exist as an integrated circuit (monolithic or thick film) and are modestly priced. The surprising fact is that Mr N. H. does not know of these suppressors, because for every practical reason they render the interference problem non existent.

Unfortunately the polarisation problem is still with us; most of the FM transmitters in Australia are horizontally polarized. The car radio manufacturers requested the ABC several times to change to mixed polarization but with no result. The polarization problem emphasizes the multipath problem (this is for some reason worse in Melbourne than in Sydney) which sometimes can mar good stereo reception in moving vehicles. Again special care in ratio detector design can help quite markedly, but in certain areas

the receiver has to be switched back to mono reception.

T. B. (St-Ives, NSW)

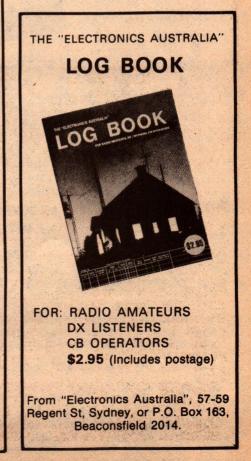

# with the ARRL 1979 Handbook. ARRL AMATEUR RADIO HANDBOOK -

**NEW 1979 EDITION** Brand new and up to date 'bible' for the person

interested in all aspects of Amateur Radio. The 1979 issue has been revised to bring it completely up to date. IMPORTANT - Dick Smith is the first retailer in Australia to be selling the prestigous 1979 ARRL


Cat. B-2218 .... \$14.95

ONLY \$14.95

# \*\*\*\*\*\*\* **OMRON MINI PC MOUNT RELAY - DPDT**

Miniature relay specifically designed for use on printed circuit boards. 12V DC/290 ohms coil. Precious metal contacts for optimum reliability and maximum life.

INCREDIBLE VALUE

 

# TOP PROJECTS FROM ETI

- VOL. 5.

Brand new and fantastic as always - the Electronics Today International Book of Top Projects (Vol. 5), Contains constructional details of many interesting and useful projects, e.g. Graphic Equalizer, Shutter Speed Timer, Dual Power Supply etc. Add this superb volume to your shelf and improve your knowledge of ele-

ctronics. Cat. B-3648 .. .. .. .. \$3.00

**ONLY \$3.00** 



# SMOKE DETECTOR

rotect your own life and others with this brand new smoke detector. Fire can happen at any time and any where be ready. Our detector has dual chambers for high sensitivity and reliability. A LED flashes every 40 seconds to indicate power on and the 9V alkaline battery supplied) lasts for over a year. The alarm norn delivers an ear shattering 85 dbA for warning of smoke. Remember that a smoke detector is far more effective than a heat detector. Easy installation with



**FANTASTIC** VALUE \$35.00

# Cat. L-5258 ..... \$35.00. **NEW RESISTOR PACK**

# **FANTASTIC BARGAIN**

Guaranteed over 200 resistors, all preferred values within range 1 ohm - 10 Megs, 1/4 watt - all brand new and fully guaranteed.

At our one off price would cost you over \$8.00.

NOW ONLY \$3.00 Cat. R-7015 THATS LESS THAN 1.5c EACH! LIMITED QUANTITY - HURRY! CALCULATOR BARGAIN

A handy calculator for business people, shoppers, students etc. An essential tool in today's modern technological society. Does all basic calculations plus more e.g. square root, pi, reciprocal, percentage and

# **UPGRADE YOUR 2650 MINI** COMPUTER

memory. Requires two penlight batteries Cat. S-3003 @ 15¢ ea. Has socket for external DC supply.

Expansion board (See EA Nov. 1978 p70) PC Board 78uP9 .. Cat. H-8358 .. \$5.60 8K RAM board (See EA Dec. 1978 p83) PC Board 78uP10 .. Cat. H-8359 .. \$5.50

# TAKYA WAS \$16.75 SAVE OVER 40%

# SCOOP PURCHASE

Dick has purchased a quantity of the MM5314 clock chip as used in the 6 digit clock (See EA Febuary 1979). This prime spec. device is from National Semiconductors and represents fantastic value.

ONLY .... \$5.90 each .. Cat. Z-6814

# SPECIAL NOTICE.

Check out the **Super Dick Inflation** Fighting Bargains in special insert (EA Feb. 1979).

# SAVE \$1525 on tantalum capacitors

You know how useful Tag Tantalum Pack of capacitors are - and usually how expensive they are — around 40 cents

So how much would a pack of 50 of the most used values cost? \$20.00? Here are 50 PRIME SPEC tantalum capacitors at less than 1/4 normal price! Buy now (in bulk) and save!

R-7060

# STOP PRESS!

Our new DUTY FREE STORE will be open in HONG KONG shortly. A new deal for Australian travellers: HONG KONG (duty free) prices with AUSTRALIAN guarantees! Build your own watch



A full function digital electronic watch in KIT form. So simple to put together in a couple of minutes. Showsday, date, hours, minutes, seconds. Comes complete with batteries and strap. Instructions included.

NOTE: Prices and stock availability could change between publication deadline and on-sale date due to circumstances beyond our control. Please check with our stores for latest availability and prices.

# **SAVE 20% FANTASTIC** SAVING....

# Famous 'Weller' cordless soldering iron

Yes! This top name Weller cordless iron is now reduced - we've ration-

alised the packaging and now supply only the bits you really need - so you save. In-built re-chargeable cells give hours of soldering away from a power source. A built-in light shows the way in dark corners. Mains charger and one spare tip included.



# INCREDIBLE SCOOP PURCHASE

(For Mail Order Customers Only)

A MUST for all Electronic Enthusiasts **TOP QUALITY UNIVERSAL TERMINALS** 





# BOTH AVAILABLE IN RED & BLACK

WE HAVE PURCHASED THE COMPLETE STOCK FROM PLESSEY EXCLUSIVELY FOR OUR MAIL ORDER CUSTOM-ERS - SO HURRY AS STOCKS WON'T LAST AT THESE PRICES!

ADD THEM TO YOUR NEXT MAIL ORDER!

# Paper Tape Reader Kit

Communicate with your computer! Easy to build with complete interface instructions - will interface with all microprocessors via an 8 bit parallel port. This kit has no moving parts.



# **WATCH THIS SPACE**

AND FIND OUT WHAT YOU MISSED

Each month all of our stores feature an outstanding special which is actually BELOW COST! N.B. Specials are strictly while store stocks last. Don't miss out!

# LAST MONTH:

HOW TO HEAR/SPEAK CB IN SHORT SHORT FOR ONLY \$1.69 - NORMALLY \$3.00.

# VING \$1.31

WHAT'S THIS MONTH'S SPECIAL? CALL IN AND FIND OUT FOR YOURSELF!

# **PARTS FOR** MAGAZINE **PROJECTS**

6 DIGIT CLOCK (See Feb. EA) Cat. K-3495 \$19.75 Complete kit, including instructions

Case with mounting bracket and bezel.

AC Mains adaptor Cat. H-3194 \$3.60 Cat. M-9514 \$5.25 PLAYMASTER AM/FM TUNER (See Nov/Dec EA)

Complete kit, including instructions SEPARATE PARTS Cat. K-3494 \$159.50 Cat. F-4610 \$59.00 Cat. H-8357 \$9.75 Cat. Q-2100 \$4.95 Cat. Q-2095 \$4.95

Signal strength meter Tuning meter - centre zero Most other electronic parts for this project in stock.

MODEL TRAIN CONTROLLER (See Oct EA)
Not produced as a kit - all parts available from stock:
PCB only.
Zippy box
2N3055 transistor
2N3055 transistor Cat. H-8355 \$3.75 Cat. H-2752 \$3.75 Cat. Z-2145 \$0.95 Cat. Z-2130 \$0.80

FET INPUT AC-DC VOLTMETER (See Sept EA) oduced as a kit - all parts available from stock: Cat. H-8353 \$2.75 Cat. Q-2060 \$12.50 Fabricate your own meter scale using the Scotchcal

8005 black Scotchcal photo-sensitive aluminium CA-3140 FET op-amp Cat. H-5694 \$6.00 Cat. Z-5417 \$2.50 VARI WIPER Mk 2 (See Sept EA) Not produced as a kit - most parts available from stock:

Cat. S-7125 \$4.80 Cat. Z-4315 \$1.00 Cat. Z-1786 \$1.20 2N2646 (DS2646) unijunction. UPGRADED 40/200MHz FREQ. COUNTER (See Aug EA)

Same style as previous kit, but new circuitry means it is easier to build, set up and is more sensitive. Basic counter is 40MHz - by adding a single 95H90 IC the range is extended to 200MHZ.

Complete kit for 40MHz, inc. instructions 96H90 IC to extend range to 200MHz.... SEPARATE PARTS: Cat. K-3437 \$99.50 Cat. Z-5360 \$12.50 Cat. H-8346 \$8.50 Cat. Z-5415 \$1.95 Cat. Z-5781 \$2.50 Cat. Z-5414 \$6.50 Cat. K-6031 \$3.00

PHOTO TACHOMETER (See Aug EA).
Although we do not produce a full kit for this project, all parts are normal stock lines at all of our stores.
PCB (only).

NEW 10 GAME TV GAME KIT (See July EA) Complete kit, including instructions SEPARATE PARTS Cat. K-3491 \$49.50

Fully built RF modulator Fully built audio modulator AY-3-8600 IC Cat. K-6040 \$3.95 Cat. K-6040 \$3.00 Cat. K-6042 \$4.50 Cat. Z-6852 \$15.00

Many other PC boards for current magazine projects in stock.

# **ELEC**

SYDNEY 125 York Street, SYDNEY. Ph. 290-3377 147 Hume Hwy, CHULLORA. Ph. 642 8922

162 Pacific Hwy, GORE HILL, Ph. 439-5311 30 Grose Street, PARRAMATTA. Ph. 683-1133 MELBOURNE 399 Lonsdale Street, MELBOURNE. Ph. 67-9834

656 Bridge Road, RICHMOND. Ph. 42-1614 BRISBANE 166 Logan Road, BURANDA. Ph. 391 6233 ADFL AIDE 203 Wright Street, ADELAIDE Ph. 212 1962

MAIL ORDERS P.O. Box 747, Crows Nest, N.S.W. 2065. Post and packing extra.

Dealers across Australia

SHOPS OPEN 9AM to 5 30PM (Saturday 9AM 12 noon) BRISBANE 1 2 Hour earlier

ANY TERMS OFFERED ARE TO APPROVED APPLICANTS ONLY

Many lines available from the Dick Smith Electronics Centres at

# GRACE BROS

MAJOR DICK SMITH DEALERS: Listed below are the names and addresses of dealers who stock a large range of our products - however we cannot guarantee that the dealers listed will have all items in stock and at the prices advertised

Brian Bambach Electronics Sound Components GM Electronics Trilogy Elec. Supplies Crystal TV Rentals Pty Ltd Langman's Sound Centre


ner Electronics

68 William St, Gosford NSW. Ph 24 7246 78 Brisbane St Tamworth NSW Ph 66 1363 76 Bissane 31 Aniworth Usaw Fri 60 1202 94 Brown Road, Newcastle NSW. Ph 591 222 99 Fitzmaurice St. Wagga NSW. Ph 21 3044 40 Princes Hwy Fairy Meadow NSW Ph 83 1219 66 Crystal St, Broken Hill NSW. Ph 6897 Magellan St & Bruxner Hwy Lismore NSW Ph 878-361 Shop 15, Treasure Island, Coffs Harbour Jetty NSW. Ph 521-570 95 Mitchell Street, Bendigo VIC. Ph 43-1977. Citcom Electronics **ADS Electronics** Advanced Electronics Aero Electronics Hutchesson's Comm Gawler CB Centre 11 Altronics Hocks TV Rentals

Hopkin's Arcade, West St, Mt Isa QLD. Ph 434-791 312 Oxley Ave, Margate QLD. Ph 204-1276
5a The Quadrant, Launceston TAS. Ph 31-7075
123a Bathurst St, Hobart TAS. Ph 34-8232
5 Elizabeth St, Mt Gambier SA. Ph 256-604
51 Hillier Road, Evanston SA. Ph 222-149
105 Stirling St, Perth WA. Ph 328-1599 87 Hannan St. Kalgoodie WA, Ph 211-906
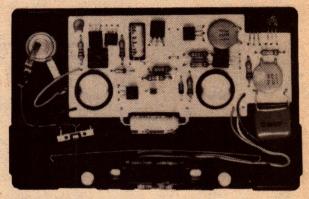
# TDK's Revolutionary New Product — The HD-01 Head Demagnetizer Built into a Cassette Shell.






# Simply load the HD-01 into any cassette recorder as you would a standard audio cassette and depress the 'play' button.

The HD-01 Head Demagnetizer was designed by TDK for easy, convenient head demagnetization of any cassette deck, insuring crystal-clear, perfect recordings every time.
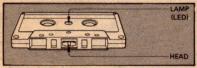
## The TDK HD-01 Head Demagnetizer features:

- A unique cassette format, designed to insure complete compatibility with any cassette deck.
- Powerful de-gaussing circuit instantly demagnetizes recorder heads the moment the play button is depressed. The above diagram depicts the oscillating waveform applied to the recorder heads, removing every trace of residual magnetism in only one second!
- A red LED (Light Emitting Diode) built into the HD-01 cassette shell will light up the moment your recorder heads have been completely demagnetized.





The TDK HD-01 Head Demagnetizer ends forever the fuss and mystique surrounding the demagnetization process and is much easier to use than conventional wand-type tools. Anyone can use the HD-01 and get perfect results every time.

The TDK HD-01 Head Demagnetizer is completely self-contained, battery operated and portable. It can be taken anywhere and stored with your present audio cassettes. The TDK HD-01 is ideal for all types of cassette decks especially those with heads located in hard to get at places such as:

- recorders with heads positioned in the front of the unit but which point to the rear.
- those with 'pop up' loading mechanisms which can not be detached, thus making the heads almost inaccessible.
- cassette decks with heads positioned laterally with respect to cassette loading (car decks are good example of this type).
- automatic loading machines.


## WHY IS DEMAGNETIZING SO IMPORTANT?


TDK, in conjunction with many cassette deck manufacturers, recommend that cassette decks be maintained on a regular basis. Cleaning the heads, capstan and pinch rollers is one important aspect of that maintenance program. — Periodic demagnetizing, about every thirty hours of use, is the other. Failure to do so will cause a build-up residual magnetism on the heads, which can seriously affect tape and machine performance in the following critical areas:

- The noise level in the low and midrange frequencies is increased by 5 to 7dB, thereby reducing the overall signal-to-noise ratio.
- Pre-recorded tapes can also be affected with midrange and high frequency distortion, as well as attenuation by as much as 2 to 6 dB, virtually eliminating any hopes for clear sound reproduction.

The interaction of these factors will not only prevent both the tape deck and tape from displaying their true performance capabilities, but will severely limit the Dynamic Range properties of both, rendering pure sound reproduction an impossibility.

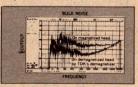The following comparison data clearly demonstrates the effect of residual magnetism on recorder heads in the areas of both Noise Level and Frequency Response.



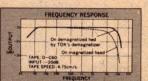

# TECHNICAL DATA

## **Major Components:**

Transistors (8)
Diodes (2)
LED (Light Emitting Diode)

Power Supply - Control Section - Oscillation Section - Head Section

## Specifications:


Maximum Magnetic Flux Density Oscillation Frequency

Shape

200 Gauss 630 Hz (External Dimensions) Conform to IEC Standards

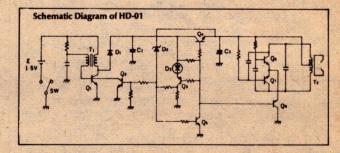**Battery for Power Supply** 

G-13 1.5 volt, Silver Oxide Battery (option)



For additional information, direct all inquiries to:

# **CONVOY INTERNATIONAL PTY. LTD.**

4 Dowling Street, Woolloomooloo, N.S.W. 2011 Telephone: (02) 358-2088. Telex: AA23111





# DIGITAL RECORDING: DIRECT CUT QUALITY WITHOUT THE HASSLE

Slowly but surely, pulse and digital technology is invading the audio-hifi area, traditionally an analog stronghold. This article explains something of the background and refers in particular to the application of digital techniques to the master recording chain.

Rather than launch straight into a discussion of the digital system, it may be helpful first to recall the kind of waveforms involved in a conventional audio signal; then to look at the pulse concept and finally the full digital approach. First, the audio signal:

Fig. 1a shows a basic audio sinewave. Looking at it, the average enthusiast will have no great difficulty in imagining a stylus, or a voltage, or a loudspeaker cone oscillating in this simple mode. For purposes of illustration, it is probably too simple!

Actual program material is far more complex and, in the ultimate, can be analysed into a very large number of sine waves, present simultaneously and making up the total sound. It is rather difficult to visualise a stylus, or an amplifier, or a loudspeaker cone responding to them all at the one time.

Fortunately, however, the situation can be illustrated graphically, using a practical number of signals.


Let's say that, to the simple sine wave of Fig. 1a, we add two others (b) and (c), variously related in terms of amplitude and frequency. Adding them together arithmetically produces the complex resultant (d).

Without getting too pedantic, if the three signals (a), (b) and (c) were present in the studio at a particular instant, the resultant pressure wave adjacent to the diaphragm of the microphone might look something like (d). So also would the movement of the diaphragm, plotted against time, and the variation in the microphone output voltage.

Nor is Fig. 1d the mere creation of a draftsman. The track on an ordinary lateral cut mono disc is virtually the graph of an audio resultant (like 1d) inscribed in vinyl!

Ultimately, a recording and amplifier system has to preserve and recreate just such a complex resultant pressure wave in the listening room, so that it causes a corresponding movement of the "drum" in the listeners' ears. Thereafter, the listeners' audio sensing faculties sort the complex wave (Fig. 1d) back into its original frequency components (a), (b) and (c).

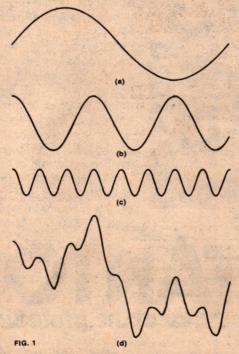Traditionally, audio equipment has operated on an analog basis. The tiny signal from a microphone is passed through amplifiers which deliver an output, larger in amplitude, but closely related to the original in contour. Each tiny variation in input is matched by a proportional variation in output.



Showing how the multiple components in a complex signal (a), (b) and (c) combine to produce a resultant (d), which is the kind of waveform which an audio reproducing system has to handle.

# by NEVILLE WILLIAMS

A prime requirement of a hifi recording and amplifier component (or system) is that it should exhibit a linear transfer characteristic, such that the output (although amplified) is a replica of the input. If it is not so, the component or system has introduced distortion of one kind or another.

No practical equipment is completely free from distortion, but the efforts of designers through the years have brought about a quite dramatic progressive reduction in its overall percentage level. However, sound engineers have to worry about more than just distortion.

In some ways a more urgent problem is the intrusion of system noise upon the wanted signal. Every segment of a reproducing system introduces some spurious noise, evident on otherwise pure musical tones. Under the most favourable conditions, noise may be so low as to be virtually indiscernable during ordinary listening; under poor conditions, it may be distractingly evident.

Because noise is most apparent during soft passages or breaks in music, it is one of the factors which determines the "dynamic range" of an audio module or system: the difference between the intrinsic noise level and the signal overload level.

By way of illustration, the dynamic range of a good/average quality prerecorded cassette is about 50dB; a good/average disc is usually somewhat better at about 60dB. To cope effectively with demanding program requirements, a figure approaching 80dB would be more appropriate, indicating an obvious present-day problem area.

In fact, the level of noise - and distortion — apparent in pre-recorded cassettes and discs is not necessarily inherent in the piece of tape or vinyl that the consumer actually buys. A

# PROFESSIONAL

Ohio Disco Packager, SWB Electronics, uses Stanton Exclusively.





Larry L. Decker, Designer/Owner, examines finished control table for Disco use.

The trend to Portable Disco continues strong. An ambitious Company in Canton, Ohio, SWB, is achieving excellent success with their units (their goal is a national franchising operation). James C. Fravel, General Manager/Promotions, writes to Stanton, "We use Stanton cartridges in each and every unit we sell. Two of our units have been running for about a year and a half without failure. We are proud of the track record of our units and the Stanton cartridges."

They use the 500AL because it's a durable cartridge and "gives SWB a 4 dB base boost that we like to have with the music we play. It has been, by far, the best cartridge we have used (and we have tried many)".

So, Stanton, world famous for its top-of-the-line calibrated cartridges, the 881S and the 681 series, also serves the professionals in the Disco Industry.

Whether your usage involves recording, broadcasting, archives, disco or home entertainment, your choice should be the overwhelming choice of the professionals in every field . . . Stanton Cartridges.



The choice of the professionals™

Sole Australian Distributors

# MULEROYA INDUSTRIES

Head Office: 156 Railway Pde, Leederville, Western Australia, 6007. Phone 81 2930 NSW Office: 100 Walker St, North Sydney 2060. Phone 922 4037

Victoria Office: 103 Pelham St, Carlton 3053. Phone 347 7620 Available at quality conscious Hi-Fi dealers throughout Australia!

# HIFI TOPICS — cont.

significant proportion is a heritage from the signal processing further back in the chain.

By the time the source signal has passed through the mixing console onto multi-track tape, been edited, compensated and mixed down to a stereo master, dubbed for distribution to licencees, dubbed again to produce factory masters and so on, quality has inevitably been compromised.

This is one of the reasons why "direct cut" discs have found so much recent popularity: discs where the signal has been fed direct to the disc cutter, without the intrusion of tapes and dubbings.

But direct cut discs pose many problems: the strain on the performers; the inability of engineers to "rehearse" the cut; the risk of repeated failures; the lack of variable pitch facility; the inability to cut at half speed; the limited production run and the resulting price disadvantage. And


Recording engineers have adopted many measures in an effort to contain the noise and distortion problem while still retaining the advantages of tape mastering, and it is probably true to say that, under the best conditions, many such measures yield gratifying results. The problem is that the margins for error are too small and companies are too frequently obliged, by commercial necessity, to release recordings which are merely average in quality.

Digital recording technology holds firm promise of a way around these difficulties, offering the conveniences of tape mastering, without a significant retreat from the potential quality of direct cut.

The digital approach is a combination of computer technology with audio pulse techniques. To gain an appreciation of the latter, we should go back to Fig. 1d — the kind of complex waveform which any audio system has to preserve and reproduce.

Whereas the analog approach is to respond directly and continuously to every tiny convolution of the complex waveform, pulse technology relies on "sampling". Special circuitry, gated at a very precise "clock" frequency, samples, and measures the amplitude of the audio wave at short intervals and produces a train of pulses, which vary in one way or another, according to the audio content.

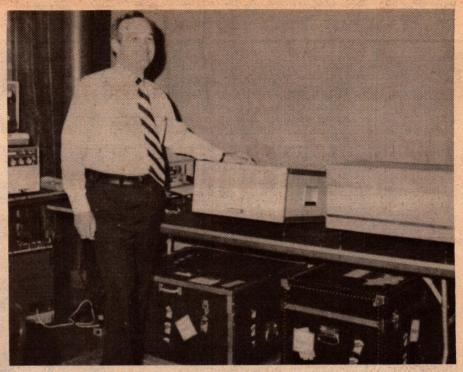Having been translated into pulses, the one-time audio signal is processed and/or recorded using modern pulse technology. At some later stage, the pulse information is translated back into analog form, suitable for recording on to present-day discs or tapes and for reproduction through conventional hifi systems.




Dr Stockham with the Soundstream digital recorder mentioned in this article.

Whatever the purpose and mode of such manipulation, it leads to an obvious objection: if the contour of the complex wave is so sacrosanct, how can it possibly survive being reduced to a sequence of tiny, isolated samples? Surely the recovered waveform must be a mere approximation of the original, lacking fine detail and therefore containing significant distortion?

This would, in fact, be the case, if certain basic requirements were not met.

The first relates to the sampling frequency, which must be at least twice the highest audio frequency component which it is desired to retain in the signal being processed. Thus, for a top audio frequency of 15kHz, the sampling frequency must be not less than 30kHz.

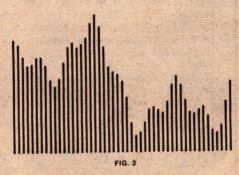In practice, a high quality system would more likely use a sampling



Using pulse technology, complex audio waveforms are translated into, and recovered from, a long train of pulses, which are encoded in some way to indicate the instantaneous signal voltage which each represents.

frequency nearer 50kHz. This provides a margin on potential bandwith and also ensures that the sampling frequency can be filtered out effectively from the analog signal, when the latter is finally reconstituted.

A further requirement is that the means of describing the height of each sample pulse must itself be accurate and not subject to significant cumulative error. If it were suspect, the recovered waveform would be subject to distortion and the whole exercise would be rendered futile. More about this later

A possible interference flowing from Fig. 2 is that the pulses are equally spaced and of equal width but of a height directly related to the waveform. In fact, such a train of pulses would be said to be amplitude modulated and described by the letters PAM (Pulse Amplitude Modulation). Indeed, because the pulses are amplitude modulated and still so obviously related to the original waveform, the method falls into what is sometimes referred to as a "quasi pulse system".

A different approach, which is more representative of true pulse technology is to so arrange the analog-to-pulse conversion that height and frequency remain constant but the pulse width varies in proportion to the signal amplitude. This is referred to as PWM (Pulse Width Modulation).

A still further method is to keep the pulse height and width constant but to vary the position of the pulse according to the analog waveform. This is called PPM (Pulse Position Modulation).

In fact, the method which holds so much promise for master recordings goes well beyond any of these into full digital techniques. As each individual

# HIFI TOPICS: Digital Recording — continued

sample of the complex waveform is taken, its amplitude is measured electronically and translated directly into a row of binary digits, which can be processed by computer style circuits and memories, and stored on tape as computer-style data.

In short, the system does not store and process audio waveforms at all, or even pulses modulated in one or other of the possible ways. It simply stores a series of numbers indicating the amplitude of successive samples. At a later point in time, the "measurements" of the complex waveform, encoded by an A-D (Analog

to Digital) converter can be utilised by its D-A (Digital to Analog) counterpart to reconstruct a closely equivalent waveform.

However, those familiar with digital technology will see one immediate objection. While in one sense capable of high accuracy, digital systems can deal only with discrete numbers. Therefore, in turning an analog waveform into data, there will inevitably be some approximation, with the last digit rounded off.

The answer to this problem lies simply in having a sufficient number of binary digits, or "bits" in the

measurement code. For example, a 16-bit code can specify 65,536 voltage levels in binary numbers, ranging from: 0000 0000 0000 0000 to 1111 1111 1111

One scarcely needs to be a genius, of course, to realise that a large number of "samples" each involving a large number of "bits" must add up to a very substantial "bit rate" or bit frequency. Thus 50,000 samples per second, each with 16 binary bits would work out at 800,000Hz, or just on 1MHz — all for one audio signal. However, with the bit rates involved in modern computer technology, and with even home video recorders handling a signal several MHz wide, the need for a 1MHz facility to handle an audio signal is of no great consequence to a recording engineer, if it confers other advantages.

# Digital recordings impress with quality, dynamic range

THE FIREBIRD SUITE (1919). Stravinsky. OVERTURE and POLOVETSIAN DANCES, Borodin. Robert Shaw and the Atlanta Symphony Orchestra. Telarc stereo, Digital, DG-10039. (From speciality record stores or direct from P.C. Stereo, PO Box 272, Mt Gravatt, Qld 4122. \$19.50 post paid.)





First reaction, in slipping this disc out of its cover, is that side one in particular is only half utilised, with plenty to spare outside the lable. Yet there are about 21 minutes of program on each side. The reason lies simply in the very wide dynamic range, which has allowed the recording engineers to record the lengthy softer passages at a very low level, with minimal spacing between the tracks.

But I was forewarned by the sight of other, narrower segments where the grooves are obviously very widely separated and very heavily modulated. Indeed, I sampled these first, set the amplifier gain for an acceptable maximum level, then started at the beginning, leaving the controls thereafter untouched.

And the dynamic range is every bit as wide as it looks, with a weight of bass that is nothing short of electrifying. Yet it is completely clean, although it may easily distress anything but a compliant cartridge and a good speaker system. It makes one wonder how much deliberate compression or accidental "crushing" operates in a normal studio analog tape system.

For the rest, the general quality is excellent and, in this respect fully comparable with other top-of-the-line discs, produced by whatever process. The whole point, however,

is that this remark can be made alongside an observation, about extremely wide dynamics and a massive sound from the drum department.

Recorded only in June 1978, the album is an import in a generous double-fold jacket, with notes on the digital recording system, the orchestra, the conductor, the music and the composers.

Concerning the performance, I think you'll find it well up to expectations and, provided the music appeals, it will let you enjoy and experience what modern digital recording is all about. (W.N.W.)

HOLST: Suite No. 1 in E-flat; Suite No. 2 in F. HANDEL: Music for the Royal Fireworks. BACH: Fantasia in G. Frederick Fennell conducting the Cleveland Symphonic winds. Telarc digital stereo No. 5038. (From specialty record stores or direct from P.C. Stereo, PO Box 272, Mt Gravatt, Qld 4122. Price \$19.50, post paid.)

The remarks made about the "Firebird" album apply equally to this one: 20 minutes or more on each side, with track spacing giving a clear visual clue to the wide dynamic range.

In fact, there is a statement in the specifications of this disc to the effect that absolutely no limiting,

filtering, compression or low frequency cross-over is used and that the effective dynamic range is at least 20dB greater than is found on normal commercial discs featuring the same works.

The manufacturers further warn that it is an "audiophile" recording, intended to be played on equipment with intrinsically low noise and capable of handling large groove amplitudes. And I can assure you that that's the way it sounds!

The 60 or so wind and percussion players — half of them drawn from the Cleveland orchestra — offer a superb performance, matching the quality of the engineering.

If your cheque book will stretch only to one of these records, buy the one which appeals in terms of program content. Technically they both illustrate well the potential of the digital mastering technique, with its clean sound, wide dynamic range and massive bass.

Like the "Firebird", this one carries the endorsement on the double fold jacket "Imported pressing". The notation is actually for the benefit of US audiophiles and confirms that it was manufactured overseas from American digital tapes. As before, the jacket contains complete notes on everything from the system to the composers. Another good one. W.N.W.)

# STOP PRESS

CONSUMER REPORT MAGAZINE RATE MARANTZ HIGHEST ACCURACY SCORE IN HIGH PRICED LOUDSPEAKERS!





# MARANTZ HD880

40% x 16 x 13% in. 62 lb. Bass half-loudness point: Very 40% x 16 x 13% in. 62 ib. Bass nair-loudness point: Very good (40 Hz). Freedom from bass distortion: Better than average. Power range required: 25-60 watts. Impedance: 4 ohms. Comments: Has very-high-frequency level control. 4 onms. Comments: Has very-high-frequency level control. Has removable bass-port plug to increase bass (see story). Had highest accuracy with tweeter control set at % of maximum, other controls set at maximum, and bass-port plug in.

y Rating 93 92 90 90 89
90 90
90
90
THE RESERVE AND ADDRESS.
89
89
89
88
87
86
86
85
83

The Report, which was prepared by the highly respected American organisation, Consumers Union, combined computer and laboratory measurements with expert listening tests to show that Marantz HD880 was the most accurate in a group of 14 highly regarded Hi Fi Loudspeakers.

"In CU's view, the most meaningful single standard for judging loudspeaker," a speaker's ability to reproduce sound energy smoothly.

performance is accuracy - a speaker's ability to reproduce sound energy smoothly and uniformly over the entire musical spectrum. The higher a speaker's accuracy, or fidelity, the more fully it can respond to the entire spectrum of musical sound, from the tinkling of a triangle to the deepest tones of an organ."

But the sad truth is that most speaker manufacturers have given up on the accurate loudspeaker. Instead, they produce models with booming bass, sizzling highs and great vocal presence, and call it "personality". Trouble is, that "personality". ality" doesn't come from the music at all, but from shortcomings in speaker design that actually distort sonic accuracy and create coloration.


Marantz chose instead, the more formidable task of working to 'ard a loud-speaker which is as accurate as theoretically possible. When you comuine accuracy with Marantz quality, YOU HAVE A WINNER.

# FULL COPIES OF REPORT AVAILABLE ON REQUEST

Superscope (A/Asia) Pty. Ltd. 32 Cross St. Brookvale. N.S.W. 2100 Tele: 939 1900

# REDPOINT

# **Heatsinks**

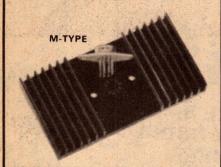


# M-Type

For applications including that of printed circuit boards and suitable for external mounting on equip-

Height 0.56"-14mm Width 3.69"-94mm

2M	2"—51mm
3M_	3"—76mm
4M_	4"—102mm
6M	6"—152mm

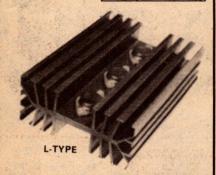

# L-Type

Height 1.97"-50mm Width 4.33"-110mm


2L	2"—51mm
3L	3"—76mm
4L	4"-102mm
6L	6"—152mm

All D.I.L. packs with 14 pins and most 16 pin packs.
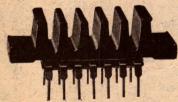
# **DIP 14/8**

Size 9 x 28 x 7mm high

Supplied complete with cyanoacrylate adhesive



Ex Stock



99 Alexander St, Crows Nest 439 2488

Adelaide 42 6655 Brisbane 277 4311 Canberra 82-3581 Newcastle 69 1625 Perth 325 5722 Melbourne 598 9207

# HIFI TOPICS: Digital Recording — continued

Using such a code, it is possible to record and reproduce a complex waveform audio waveform at least as accurately as by the best analog techniques, but with a much wider dynamic range — in excess of 90dB.

This means that a recording engineer can commit a performance to tape without the need for any signal compression or anit-noise processing, and recover it with virtually no more distortion or noise than was inherent in the original microphone and console

What is more, if he needs to dub or mix down from the multi-track digital master, he can do so with virtually no cumulative deterioration, as long as the signals remain in digital form. He is simply merging data in a computer style operation.

Provided the digital circuitry does not malfunction - and there is no special reason why it would - a long series of numbers describing a waveform will remain intact, no matter how many times it is copied. And that simply means that the waveform, as reconstructed, will remain intact, free from added noise or distortion.

Another important advantage is the opportunity to avoid wow and flutter during such processing.

During the original recording session, the timing of the samples is dependant entirely on a pulse generator or "clock", which can be as precise as the engineer cares to arrange for. During replay, he does not have to accept the samples as they flow from the tape, as with a normal analog system. The pulses can be fed into a memory buffer and subsequently gated out with the same timing precision as the original sampling.

Apart from the obvious advantage, elimination of wow and flutter confers another benefit by minimising "modulation noise" — that subtle muddying of tones when audio waveforms are subject to slight time

Print-through, too, ceases to be a problem - the tendency for the magnetic pattern to appear at low level on adjacent layers, when a tape is stored for a significant period of time. As indicated in these columns in the November issue, it prejudices the choice of tape for conventional analog master recordings, and the length of time and the conditions under which they can be stored.

Print-through does occur in digital tapes, of course, but not with the same dire results. Whereas a low-level printthrough signal will be reproduced directly by an analog system, the printthrough pattern on a digital tape is never likely to even approach the level of a true "bit" signal, equivalent to full particle magnetisation. The printthrough signal is therefore totally

ignored.

Last but not least, digital technology offers to the audio engineer certain unique facilities. For example, if the dynamics of a recording have to be modified for any reason, it is no longer necessary to rely on analog devices, such as for compression, Dolby processing, DBX processing, etc. A digital system can be programmed to modify the numbers, which define the audio waveform, in very specific ways. It becomes a highly predictable and routine exercise in "number crunching", computer style.

Another facility, inherited from professional video tape technology, is the ability to merge and edit by purely electronic means, without cutting tapes or even compromising the steady flow

of timing pulses.

The one obvious technical hazard to the digital system is the possibility of "dropouts" in the mastering tapes tiny areas where theere is a flaw in the magnetic coating. Such a flaw may effectively change a 1 to a 0 in a digial number, radically altering its value and what it says about the amplitude of the audio waveform at the relevant point.

However, the resources of the entire tape and computer industry have been ranged against the dropout problem and, apart from quality control of the tape itself, a variety of parity and redundancy techniques have been evolved to minimise the incidence of dropouts. This work is happily available to audio engineers.

Such then is the general theory behind digital recording. How does it stand up in practice?

Pictured on these pages are two

# AT LONG LAST, IT'S HAPPENED!

To Stanton Magnetics Inc, making magnetic phono cartridges is a serious business, particularly when they turn out one like their state-of-theart 881S.

It hurts them, therefore, when they see magnetic cartridge makers humiliated by dealers' "one cent" sales: the customer is offered a turntable for \$150 as is, or fitted with a "magnificent" magnetic phono cartridge for \$150.01.

But the HI FI FO FUM stores on Long Island N.Y went part of the way to make amends, recently, when they offered Stanton's 881S cartridge for its recommended retail price of \$150, with a FREE Lenco L60B turntable!

# Foster and Fostex?



HOLT AD108


Simply a beffer sound.

The Plessey Foster-Fostex range of hi fi speakers. If you've ever heard from them you'll know you've listened to the results of superb craftsmanship in the science of sound. Top performance can be yours through Plessey with the Foster-Fostex range of speakers.

Here they are, and we'd like to hear from you if you'd care to have the catalogue of their impressive technical features. Please write Plessey Australia, Components Division, PO Box 2, Villawood

NSW 2163 or phone 720133.

PLESSE

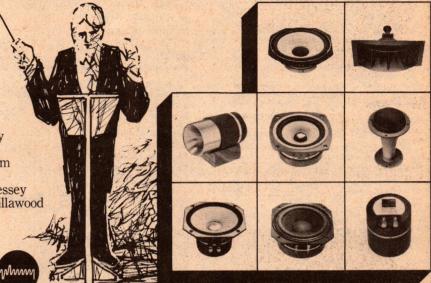





# GARRARD Model SL65B

RECORD CHANGER AT LESS THAN \$35.00 1/3 LIST PRICE -

> (RECOMMENDED RETAIL PRICE \$110.00) SUPPLIED WITH SHURE MAGNETIC CARTRIDGE AND DIAMOND STYLUS.

Also available with ceramic cartridge All changers new in original cartons Send S.A.E for full specifications

A precision automatic and manual record-playing unit fitted with Garrard Synchro-Lab4 pole shielded motor to provide constant speed conditions for the 10½ inch aluminium turntable. The low resonance tubular pickup arm is counter-balanced with a resiliently mounted weight to permit light sensitive tracking, and the slide-in cartridge carrier enables styles inspection and the interchange or replacement of cartridges to be carried out simply and quickly. Fine stylus force adjustment and bias compensation are both calibrated for accurately setting the arm to give optimum playing conditions for the chosen cartridge.

The fluid-damped level-type cue and pause control ensures gentle lowering of the pickup to the surface of the record. A short spindle is supplied for single record play records. Precision engineering is reflected in the styling of the SL65B, which is elegantly finished in black and silver.

> POST AND PACKING EXTRA Send SAE for details NSW \$3.75

Tas., WA & NT \$7.00

Vic., SA & Qld \$5.75 (Reg. post \$2.00 extra)

BASE & PERSPEX COVER FOR GARRARD OF B.S.R. UNITS \$29.50 EXTRA PLUS FREIGHT

## **NEW IMPORTED HOKUTONE 12" HI-FI SPEAKERS**

These 12" speakers have a frequency range power to 5000 cycles with a resonant frequency of 30 cycles. Max. power 30 watts. Post & packing NSW \$2:50. Interstate \$3.50.

**\$**16.50

## **NEW GOODMAN-FOSTER 3-WAY** 4 SPEAKER HI-FI SYSTEM

## \$39.00 PER KIT

Frequency Range 45 to 22,000 cycles. Power rating 25 watts. RMS Imp-8ohms. Supplied in kit form (less cabinet) each kit comprises two English Goodman 8" bass units. Foster 5" mid range. Foster 1" dome tweeter crossover components Ocodensers and inductance innabond, speaker fabric and plans of cabinet. Cabinet dimensions 23" x 13" x 10". CABINETS AVAILABLE.

Post & packing extra: NSW \$2.70; VIC, SA: QLD \$4.70; WA \$5.70. (REGISTERED POST \$2.00 EXTRA IF REQUIRED) cabinets available

## NEW MAGNAVOX — MV50 — 50 WATT SPEAKER SYSTEMS As featured in Feb. 1976 issue of Electronics Today

Complete kit of parts (less cabinet) comprising Magnavox 10-40 10" bass unit. 625 mid range 6" two XJ3 dome tweeters, crossover network, innabond, speaker silk and plans of cabinet.

> \$87.00 PER KIT

Freight extra per rail or air freight. Cabinet available. 830 System also available.

# NEW STANDARD B.S.R. C129 RECORD CHANGERS \$25.00

## LESS THAN 1/2 LIST PRICE

Fully automatic turntable plays up to six records fully automatically and single records automatically and single records automatically or manually as required. 11" turntable. Cue & pause control. Record speeds 33 1/3, 45 and 78 rev/min. Finished in black with silver trim. Player and changer spindles supplied. Fitted with ceramic cartridge. Post & packing extra. NSW \$2.70; Vic., Qld., SA \$3.70; WA \$4.70 (registered post \$2 extra it



Spare cartridge and stylus for above \$3.50 uist price \$10.00)

B.S.R. STEREO PLAYER MODEL LESS THAN 1/2 PRICE P128B \$39.00 WITH MAGNETIC CARTRIDGE

## PROFESSIONAL SERIES

Auto or manual operation 3 speed, 11½" diecast turntable 4 pole shielded motor. Slide-in cartridge carrier. Counter-balanced pick-up arm. Fine stylus force adjustment & bias compensation. Damped lever type cue & pause control. Diamond stylus.

Post and Packing extra

NSW \$3.75, VIC. SA & QLD \$5.75, Tas. WA & NT \$7.00 (reg post \$2.00 extra)

# **GARRARD CC10A** RECORD CHANGER

Fitted with a Sonatone Garrard Ceramic Cartridge Sapphire Stylus supplied with template and instructions. Post & packing NSW \$2.50. Int \$3.50.

\$15.75

245 PARRAMATTA RD, HABERFIELD 2045, PHONES 798-7145, 798-6507.

typical albums, which have been produced from digitally recorded masters, and which are being marketed in Australia through PC Stereo, of Brisbane.

According to the jacket notes, the source signals from a group of special transformerless microphones were fed to a Studer 169 console and thence direct to a Soundstream multi-channel digital recorder. This operates at a sampling rate of 50,000 per second and uses a 16-bit encoding system, with provision for error detection as a precaution against dropouts.

Harold A. Rogers of "High Fidelity" magainze, who wrote the jacket notes, makes the points previously mentioned about low noise, dynamic range, freedom from wow and flutter, programmed in-computer editing, etc. He ends up with the observation that the stereo master and the copies which emerge from the digital processing are still true masters. Because, for all practical purposes, the digital processing has preserved the full response and added no noise, wow, flutter or distortion.

And this is certainly borne out by the figures on the Soundstream digital recording system:

Frequency response: Flat from 0 to 21kHz; -3dB at 22kHz. Total harmonic distortion: at 0 VU, less than 0.004%. Total harmonic distortion: At peak levels 0.03%. Signal to noise ratio: 90dB RMS unweighted. Dynamic range: 90dB RMS unweighted. Wow and flutter: Unmeasurable.



Andrew Powell, 19, capped his first year as an engineering student at Melbourne University by winning an interstate competition which provided most effective promotion for the BASF Ferro Super LH1 cassette. Andrew is shown accepting a Mini Moke — his first car — from Nigel Price, National Sales Manager/Magnetic Products, BASF Australia Ltd.

Digital master recorders like the Daystream don't come cheaply, being currently much more expensive that even top of the line analog equipment. But, if they can offer immunity to distortion and noise build-up, the major recording companies won't argue for too long.

As one overseas expert put it recently: It is no longer a question of what recording system will be dominant; it's simply a matter of how soon.

And, by the look of the figures, the

sooner the better!

**NATIONAL PANASONIC** have released their TR5000A, a combination monochrome TV receiver, cassette recorder and AM/FM radio. Adding to its versatility is the fact that it can operate from an AC power point, from a 12V car or boat supply, of from its own internal batteries. The 13cm (diagonal) picture is bright enough to



view outdoors but a sunshield is provided for use where necessary. A three-way tuning/level meter is provided, plus separate bass and treble controls. All-up weight, without batteries is 4kg (9lb) and the construction is uch as to withstand "knockabout" use. The price: \$330. For information: G. A. Dawes, National Panasonic (Australia) Pty Ltd, 5759 Anzac Parade, Kensington

**STUDIO ELECTRONICS** are distributors in Australia for a line of tape splicers manufactured by Nagy Research Products, Box 289 McLean VA 22101, USA. According to the brochure supplied, there are six models available, two for cassette tape, three for standard 1/4-in tape and one for 1/2-in tape. All of them employ in-built self-sharpening shears which are claimed to cut the thinnest mylars cleanly and consistently, and without blunting of the cutting edge. For a brochure and price quotation: Studio Electronics, 3 Borwood Rd, Burwood, NSW 2134.

AMPEX AUSTRALIA PTY LTD has announced new appointments to its Sydney Head Office staff. Greg Martin is now Product Manager and David Williamson sales representative for professional tapes. Frank Kandelous has been appointed National Sales Manager, consumer tape products, and Barry Hume as NSW representative.

M.R. ACOUSTICS advise that they can now offer a stylus replacement service, by arrangement with the Garrott

**Up-dated recording** studios for Madrigal

Although established for only three years at 89 Berry Street, North Sydney, Madrigal has just completed its second re-build to provide it with up-to-the-minute facilities for sound mixing and recording. The main studio is "floated" free of the

building structure and can accommodate about 20 musicians, with isolation for vocalists and drums. A new control booth ensures optimum monitoring conditions with a "tight" stereo image. Maurie Wilmore, co-owner of the studios, is

pictured with the 3M model 79 16-track recorder, with 24-track up-date capability. Studios and booth were designed by Eclipse Audio Design Pty Ltd, of 89 Chandos St, St. Leonards,

Brothers of Melbourne. A new conical stylus, fitted to the existing cantilever, costs \$25, while a new elliptical can be fitted for \$35. M.R. Acoustics are very keen, however, on the German Weinz parabolic stylus, which costs \$45 to fit, or \$55 for a moving coil cartridge.

Where a completely new cartridge is required, M.R. Acoustics - and the Garrott Brothers - recommend their own P-77 cartridge, fitted with a parabolic stylus and retailing for \$89. For details: M.R. Acoustics, P.O. Box 110, Albion Qld 4010.

# **AUDIO ENGINEERING & PRODUCTION**



If you are serious about Audio Engineering and are willing to study hard, attend lectures and practical recording sessions, contact

John Burnett or Stephen Penning A.S.R.E.

# SCHOOL OF **ELECTRONICS**



Basic Electronics 12 weeks \$180 \$180 Phase 1 Audio 12 weeks \$180 Phase 2 Digital 12 weeks Phase 3 Radio & CB 12 weeks \$180

Courses designed to teach you the maximum knowledge in practical period of time.

Day & Night classes, weekend seminars.

Sydney 922 6301 Canberra 80 4446

**Adelaide 261 1383** Newcastle 69 4021 Melbourne 95 9510

# JVC SK-61 3-way loudspeaker

The JVC SK-61 is a bookshelf-sized three-way loudspeaker system housed in a sealed enclosure. It has a 25cm woofer and cone-type tweeter and midrange units. Power rating is quoted as 65 watts RMS.

In appearance, the bookshelf-sized JVC SK-61 is little different from other loudspeaker systems. Removing the grille does little to change that impression, although possibly the JVC is less flashy in the finish on the three drivers than some other brands.

Dimensions of the SK-61 are 545 x 300 x 231mm (W x H x D) and mass is 9.5kg. The enclosure is made of 12mm particle board finished in simulated walnut veneer. The removeable grille is covered with a charcoal coloured fabric

At the rear of the enclosure is a recessed panel which has two knurled screw terminals for the cable from the amplifier.

The enclosure is partially filled with fibreglass batts in special synthetic fibre bags. Presumably the bags are to prevent allergy problems with the assembly workers and curious people such as audio reviewers!

The woofer is a nominal 25cm unit with a large ceramic magnet and a 40mm diameter voice coil. It has a fairly heavy curvilinear cone, generous roll surround and a pressed steel chassis. The effective cone diameter is about 18cm.

Both the midrange and tweeter and cone type units with ceramic magnets and sealed backs. The crossover network employs three iron-cored inductors and two non-polarised electrolytic capacitors to provide crossover frequencies of 2kHz and 8kHz. There is also a tweeter attenuator which can be adjusted when the front grille is removed.

Nominal impedance of the system is 8 ohms. Measurements indicate that the impedance peak is 27 ohms at about 77Hz which corresponds to the bass resonance. There is another impedance peak at 1kHz of 18 ohms, which probably corresponds to the resonance of the midrange driver.

Minimum impedance of the system was about 6.2 ohms (below 40Hz) so that the SK-61 is unlikely to present any loading problems with amplifiers designed for nominal 8 ohm loads.

During our initial listening tests we were most impressed with the overall balance of the SK-61. With the tweeter

level control set at its midpoint the overall sound quality was surprisingly similar to our large reference loudspeakers. Further listening indicated that the frequency response was not quite as smooth in the midrange and the SK-61 lacked the more fundamental bass response of the bigger reference unit.

more drive power.

JVC quote the power handling capability of the SK-61 as 65 watts RMS and we would take this to mean that the speakers could handle the output of amplifiers up this power rating on normal program material. We would add the proviso that for heavy rock and organ material, the bass should not be boosted otherwise distortion will become objectionable.

For similar reasons, we do not recommend that the cabinet be placed on the floor or close to the corners of the room. In any case, the enclosure is really too small to be placed on the foor—



As with most sealed enclosures, the bass response is well maintained down to the system resonance and tapers gradually below it. There is a tendency for the woofer to distort (frequency double) with strong sine wave drive at frequencies of 50Hz and below.

Transient response of the SK-61 is quite good and even though the panels of the enclosure are relatively thin, they do not seem to add significant colouration. Efficiency of the system is slightly lower than average for this class of loudspeaker, so that it needs a little

you would have to lie prone to hear the treble.

Our overall reaction to the JVC SK-61 is very favourable. It is a good-sized bookshelf loudspeaker system which most people will find easy to live with. Recommended retail price of the JVC SK-61 is \$270 per pair.

Further information on JVC equipment may be obtained from high fidelity retailers or from the Australian distributors Hagemeyer (Australasia) B.V., 25 Paul Street, North Ryde NSW 2113. (L.D.S.)

# An omnidirectional microphone for conferences, &c.

A new microphone, announced recently by the Astatic Corporation of Ohio USA, will be of special interest to anyone who needs to amplify or record proceedings in a conference situation where, for example, the participants are grouped around a table.


For such an occasion, conventional microphones can pose a number of problems. A prominent central microphone can prejudice discussion, deterring the timid and motivating the outspoken.

Small multiple microphones can have a similar effect, besides which they require multiple connection facilities.

Either way, the sound pickup patterns can be lumpy, and the set-up sensitive to noise transmitted via the table top.

The new Astatic "Model 1070 Spectrum" microphone has been designed with these things in mind. Described as a "vertically orientated cardioid dynamic" unit, it is intended to rest face-up on the table, being little more noticeable than a decorative ash tray. The diameter is 127mm and height 82.6mm, and the finish black with a black grille and woodgrain trim.

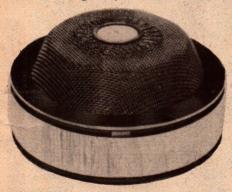In this position it offers a 360-degree coverage, with a top response to at least 12kHz, a slight "presence" rise just




above 3kHz, and a bass response deliberately tapered below about 200Hz. Impedance is 250 (approx.) ohms and output a nominal —54dB.

It has in-built hum-bucking to counter stray fields and employs internal shock mounting to give it almost complete isolation from external vibration.

A single 1070 Spectrum microphone in the centre of a 5ft table is typically adequate for 6 participants. For a longer table, two units would be used in parallel. According to the distributors, one unit on the altar can usefully supplement a church P.A. system.

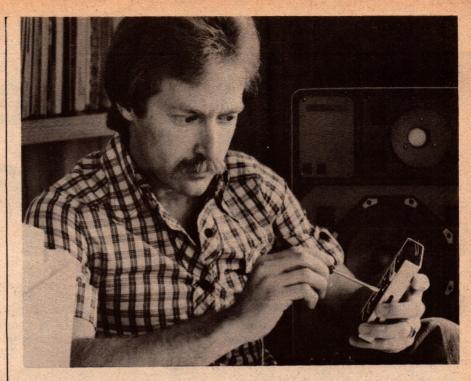For further details: Nomis Electronics Pty Ltd, 689 South Road, Black Forest, S.A. 5035. Phone: (08) 293 4896.




# "HOW TO TURN ELECTRONIC THEORY INTO PRACTICE AND MAKE IT PAY."..

"If you understand and enjoy radio and electronics and want to extend your knowledge and experience, then we at Stott's can help you.

Stott's have home-study courses for complete beginners in Radio theory and basic Electronics through to the standards needed to maintain and service Colour Television.

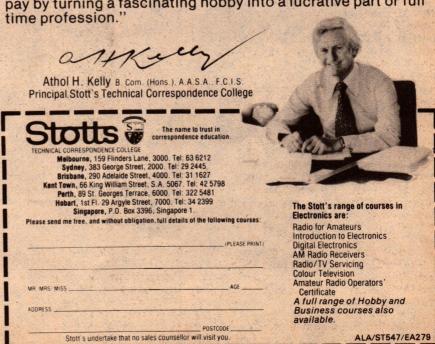Anyone who has these skills at their fingertips can make it pay by turning a fascinating hobby into a lucrative part or full



# Features bi-directional control without a reversing switch:

# Bipolar model train controller

This simple train controller is ideal for both N gauge and 00/H0 gauge model railways. It is fully overload protected, and features smooth speed and direction control with a single knob. Estimated cost of all components, including the case is only about \$25.

by DAVID EDWARDS

As you have probably guessed from the name we have given this project, it is based on the use of complementary transistors, in this case BD262 and BD263 power Darlingtons. The circuit is essentially a bipolar emitter follower.

essentially a bipolar emitter follower.
As you can see from the circuit diagram, the only active devices used are the Darlingtons themselves.

Overload protection and indication is provided by two light emitting diodes (LEDs). The unit can supply positive and negative voltages variable from 0V to about 20V, with the output current limited to a maximum of 1A.

The output voltage is determined by the setting of the 1k potentiometer, which forms the loco speed and direction control. When the control is centred, there is no output voltage, and the loco remains stationary. When it is rotated clockwise, the output voltage increases, driving the train in one direction, while anti-clockwise rotation produces movement in the opposite direction.

Operation of the circuit is as follows: the voltage at the wiper of the potentiometer is passed to the bases of the transistors by the 470 ohm resistor. This will forward bias one Darlington transistor, and cut off the other one.

The forward biased Darlington transistor operates as an emitter follower, and supplies current to the load (in this case the loco) via the 0.47 ohm emitter resistor. The emitter follower action applies local negative feedback, and tends to keep the voltage applied to the train constant, irrespective of the load current. So the loco tends to have improved "pulling power", even at low speeds.


In normal operation, the combined base-emitter drop of the conducting Darlington (1.2V), and the voltage produced across the 0.47 ohm resistor is less than 1.7V, and so the LED does not emit. (The LEDs are connected in inverse parallel, so that one or the other will tend to be forward biased whatever the output polarity.)

In an overload situation, however, the voltage drop produced in the 0.47 ohm resistor will increase as the load current increases. When the output current reaches 1A, the combined voltage across the LEDs will rise to 1.7V, and the forward biased LED will start to

As the LED starts to conduct, it will emit, giving a visible indication of the



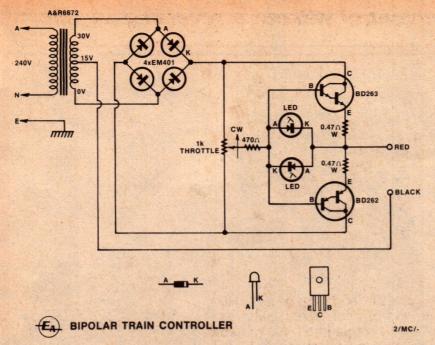The neat appearance of the prototype can be seen in this photograph. One or other of the LEDs will light in an overload condition.



ABOVE: As you can see from the diagram, the circuit of the controller is very simple.

overload condition. But more importantly, it will bleed some of the base current away from the Darlington, and hence it will limit the output current. The purpose of the 470 ohm resistor is to limit the current to the LEDs and the transistors to a safe value, particularly at either extreme of the potentiometer.

The required positive and negative power supplies are derived from a 30V centre tapped transformer with a 1A rating, via a bridge rectifier. No filter capacitors are required, as ripple on the output is actually beneficial to the operation of the train — the AC components help to overcome "stiction".

We constructed the prototype in an extruded aluminium case, measuring 152 x 101 x 76mm. This was a Horwood case, code number 34/6/DS, and is available from a number of suppliers. The prototype case came from Radio Despatch Service, of 869 George Street, Sydney, NSW 2000. The extruded aluminium tube, which forms the major part of the box, is fitted with two removable end plates, and is also split in two lengthwise.

This latter feature is most important, as it greatly facilitates assembly of the components into the case. The transformer we used was an A & R type 6672; an equivalent transformer is also available from Dick Smith stores. All other components should be readily available from your local electronic store. The LEDs can be any red type, and are not critical. The types supplied with the plastic mounting clips are the most suitable from a constructional point of view, as well as being cheaper.

The 0.47 ohm resistors should be 5W ceramic-cement types. The 470 ohm resistor can be a standard ½W part.


BELOW: Even inexperienced constructors should be able to build the controller, by following this wiring diagram explicitly.

### PARTS LIST

- 1 Horwood case, 34/6/DS, 152 x 101 x 76mm
- 1 1k linear potentiometer
- 1 knob
- 2 red light emitting diodes, with
- mounting hardware

  1 BD262 PNP power Darlington transistor, with mounting hardware
- 1 BD263 NPN power Darlington transistor, with mounting hardware
- 4 EM401 silicon diodes
- 2 0.47 ohm 5W resistors
- 1 470 ohm 1/2W resistor
- 2 terminals, 1 red, 1 black
- 1 mains transformer, 30VCT @ 1A
- 4 rubber feet
- 1 mains flex, plug, grommet, cord clamp and terminal block
- 3 6-way tagstrips
- Solder, hookup wire, solder lugs, insulated sleeving, machine screws and nuts.

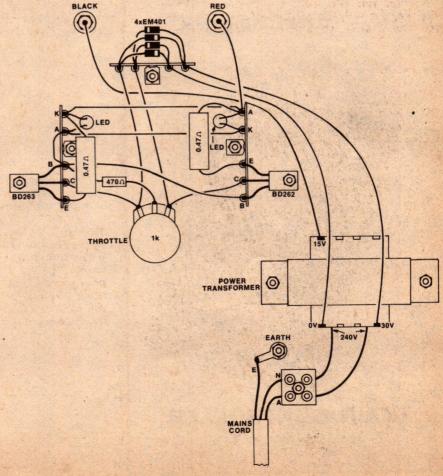NOTE: Resistor wattage ratings and capacitor voltage ratings are those used for our prototype. Components with higher ratings may generally be used provided they are physically compatible.




### Bipolar train controller


RIGHT: In this photograph, you can see how the case splits into two sections, with only three wires between them.

Make sure that you obtain insulated mounting kits with the transistors, as these must be insulated from the case. Three lengths of 6-way tagstip are also required, to form a mechanical support for the wiring and small components.

We made a front panel for the prototype from photosensitive aluminium. The artwork we used is reproduced full size with this article, and may be used directly, or copied. Use it as a guide to mark the positions of the three holes required in the front panel.

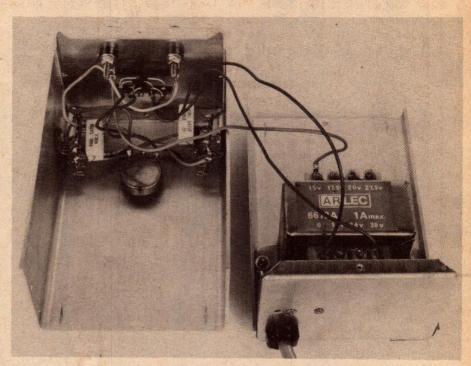Construction of the unit should not prove difficult. Use the exploded wiring diagram as a guide, and complete all the mechanical assembly first. The mains cord must be securely grommetted and clamped at the entry point to the case, and the earth lead connected directly to a solder lug bolted securely to the case chassis.



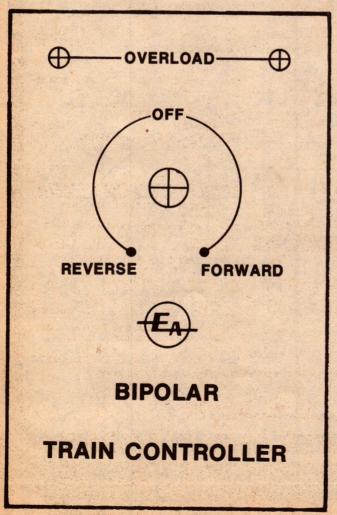

LEFT: This actual sized reproduction of the front panel can be used directly if required. Commercial panels should be available in due course.

The active and neutral leads are terminated in a two-way terminal block, and then are routed directly to the primary of the transformer. The rectifying diodes are mounted on a small tagstip positioned between the two output terminals. The remaining two output terminals. The remaining two tagstips are used as shown to mount the LEDs, power transistors and emitter resistors. The 470 ohm resistor is wired directly between the pot wiper and the base of one transistor. You will need to insulate the leads with plastic sleeving.

Care will be required to mount the appropriate transistor in the correct location (the BD263 goes on the left, as in the diagram), and to wire the LEDs into circuit correctly. Follow the diagram explicitly.

Once you have completed the unit, double check all wiring, and then switch on. Use a voltmeter to check that the output voltage can be controlled by the knob, and that both positive and negative output voltages can be obtained.

If all is OK, connect up to a train, and give the unit a practical test. The LEDs should illuminate (only one at a time) when an overload is applied. If you have a suitable ammeter, connect it directly across the output, and check that the maximum output current is about 1A, in both directions.

If you wish to increase the output current capability, insert a 1N914 silicon diode in series with each LED and use diodes with a higher current rating for the bridge rectifier. 1N5408 types are suitable.

WONDERING WHAT TO BUILD NEXT?

# BUILD A PROJECT.

from a Dick Smith kit

SAVE TIME - SAVE MONEY and the finished article will look so good your friends will never believe you built it!



CAR STEREO BOOSTER (E.A. January 1979) Boosts power output of your car cassette or FM stereo radio to 12 watts per channel - gives you home-quality sound while you drive.

This project is extremely easy to build. The Dick Smith kit contains everything you need - even a special anodised heat

sink/bracket and front panel decal - plus a specially written step-by-step construction manual, Cat K-3493



### **AUDIO AND AMPLIFIERS**

PLAYMASTER AM/FM TUNER (E.A. November/December '78) Matches Playmaster amplifiers. Full digital tuning, inbuilt digital clock, superb performance. Kit includes exclusive 32 page construction

manual. Cat. K-3494 .. .. .. .. .. .. \$159.50 PLAYMASTER 40/40 STEREO AMP. (E.A. December '76)

Our most popular kit ever. Thousands sold. Cat. K-3411 .. .. .. .. .. .. .. \$129.50

PLAYMASTER TWIN 25 AMPLIFIER (E.A. May '76)

Similar to above, but less power. Also a great kit.

Cat. K-3410 .. .. .. .. .. .. \$105.00 ET1480 100W POWER AMP MODULE

(E.T.I. December '76) 100 watts for \$25.00? Unreal, man! (mono

module) \$25.00 Cat. K-3442 ET1480 50W POWER AMP MODULE

(E.T.I. December '76) As above, but 50W. Easily extendable to 100W version.

Cat. K-3440 ... ETI480PS POWER SUPPLY MODULE (E.T.I. December '76)

To run either 1 x 100W or 2 x 50W modules. Cat. K-3438 .. .. .. .. .. .. \$19.50 MUSICOLOR MK 111 COLOR ORGAN

(E.A. September '76) Turns your music into light! Just add the

Cat. K-3140 .. .. .. .. .. .. \$65.00 ETI601 MINI ORGAN (E.T.I. August '76)

YOU can play your favourite tune in style Cat. K-3430 .. .. .. ..

LOUDSPEAKER PROTECTOR

Eliminates turn-on and turn-off surges from most amps.

\*\*MAIL ORDERS? Certainly! \*\*

\*\*Postage & packing extra.\*\*

Cat. K-3425 ... .. .. .. .. .. \$13.50

COMPUTERS, ETC.

2650 MINI COMPUTER (E.A. May '78) ALL parts, case, front panel, power supply, etc. - not a 'part' kit. Ik of memory - a powerful mini system.

Cat. K-3447 .. .. .. .. .. .. .. \$125.00

LOW COST VIDEO DISPLAY UNIT (E.A. February '78)

Mates with above. Communicate with a computer! .. .. .. \$97.50

VIDEO MODULATOR for use with VDU (E.A. April '78) Allows above VDU to be used with any TV

set. Cat K-3462 ASCII KEYBOARD ENCODER

(E.A. April '78) Uses our standard keyboard (Cat. X-1180) Cat. K-3464 .. .. .. .. .. .. .. \$39.50

CASSETTE INTERFACE (E.A. April '77) Use any cassette player to communicate with computer. Cat. K-3465 .. ..

MINI SCAMP COMPUTER (E.A. May '77) Still the best way to get started in the field of computer technology. Cat. K-3486

WAS \$105.00 SAVE \$16.00 NOW \$89.00

### TV GAMES

10-GAME VIDEO GAME (L.A. July '78)

Features 4-way bat control, many combinations of bat sizes, ball speeds, angles, etc. Cat. K-3491 .. STUNT MOTORCYCLE GAME KIT (E.T.I. June '78)

Play 4 different games, motorcross, enduro, drag and stunt, easy to build! Cat. K-3474 .. .. .. .. .. .. \$32.50



(E.A. August/September '78) Versatile piece of test gear. Easily upgraded to 200MHz by adding 95H90 Pre-scaler IC (Cat. Z-5360 . . . \$12.50) Cat. K-3437 .. .. .. .. .. .. .. .. .. .. \$99.50

40MHz DIGITAL FREQUENCY COUNTER

TEST EQUIPMENT

NEW MODEL TRANSISTOR TESTER

(E.A. July '78) Checks most transistors and FETs quickly and easily

Cat. K-3052 .. .. .. .. .. .. \$19.75

R-L-C BRIDGE (E.A. March '78) Ideal project for the beginner. Handy to have around! Cat. K-3468 .. .. .. .. .. .. .. \$34.50

AUDIO OSCILLATOR (E.A. June '78) Outstanding value for a valuable service aid. Cat. K-3469 .. .. .. .. .. .. \$32.00

### AMATEUR CB, ETC.

MORSE KEYER (E.A. April '78) Perfect Morse code - electronically generated. Inc. paddle. .. \$39.50 Cat. K-3470 .. .. .. .. .. VK POWERMATE (E.A. May '78) Short form kit - no metalwork, mains .. .. .. .. \$32.00 Cat. K-3449 .. CB POWER SUPPLY 13.8 volts at 2A continuous (4A peak) complete kit. Cat. K-3448 .. .. .. .. .. .. .. \$29.50 45 WATT VHF AMPLIFIER F'glass PCB, 13.8V operation. Req. 8 -12W of drive. Cat. K-3132 .. 30 WATT 80 METRE AMPLIFIER

Cat. K-3133 .. .. .. .. .. .. \$35.75 **MISCELLANEOUS** 

Ideal for the novice. 13.8V. Adaptable to

50W output.

CAPACITOR DISCHARGE IGNITION (F.A. July '75)

Save on petrol; end ignition troubles. Prewound coil.

Cat. K-3280 .. .. .. .. .. .. \$27.50 DRILL SPEED CONTROL Mk2

(E.A. July '76) Suits 240V 'universal' motors (not electronically switched or controlled types). A must for the home handyman.

Cat. K-3080 .. .. .. .. HIGH POWER STROBE (E.T.I. August '71) A real blast - ideal for parties, discos, etc. Dazzler

Cat. K-3150 .. .. .. .. .. .. .. \$29.50

TV MASTHEAD AMPLIFIER

(E.T.I. August '71) Can turn an unwatchable mess into a brilliant picture.

Cat. K-3230 .. .. .. .. .. .. .. \$32.00

NOTE: Prices & stock availability could change between publication deadline & on-sale date due to circumstances beyond our control. Please check with our stores for latest availability & prices.

SEE OUR DOUBLE PAGE AD FOR FULL LIST OF STORES AND DEALERS DICK SMITH ELECTRONIC



# 12-230V inverter with overload protection

This article describes the operation and construction of a 300VA inverter capable of supplying 230 volts at 50Hz from a 12 volt DC source. The output is voltage regulated, and has current limiting with ultimate thermal shutdown.

by I. M. WOODHEAD\*

It is often necessary to operate 230V AC equipment in an area where the mains supply is unavailable. This may include, for example, electric hand tools, measurements in the field with laboratory equipment, or perhaps domestic appliances.

There are two alternatives: either an engine-driven alternator, or an inverter operating from a storage battery. If a large power output is required, or if it is necessary to operate the supply for an extended period of time, an engine-driven alternator is the obvious choice.

But if energy requirements are relatively low, an inverter has the advantages of quietness, efficiency, and the possibility of exact frequency control.

A transistor inverter can be either self-oscillating or driven. However, the low-cost and relative compactness of a self-excited inverter are outweighed by two disadvantages: frequency and output voltage are notoriously variable with changes in supply voltage and load. In addition, the transformer used in a self-excited inverter has to meet tight specifications on leakage inductance, mutual inductance, and winding resistance if the operating frequency is to stay within the design limits.

In a driven inverter on the other

hand, these problems are eliminated. The output voltage can be controlled by pulse width modulation and if it is necessary to control the frequency precisely (to drive chart recorders, turntables, or tape recorders for example), then this can be done using a crystal oscillator. It is the drive circuitry which determines the characteristics of the driven inverter; the transformer is merely used for voltage conversion so its specifications are not critical.


For all these reasons, a driven inverter is considered the most versatile and so forms the basis of the design described here.

Referring now to the circuit diagram, a conventional crystal oscillator using a CMOS NAND gate drives four seriesconnected CD4017 decade dividers. The crystal frequency is 1MHz so the resultant frequency is 100Hz. This is then fed to a CD4018 presettable counter wired in the divide-by-two mode to give two antiphase outputs.

These outputs are fed via NAND gates to drivers consisting of two seriesconnected Darlington pairs, and thence to the primary windings of the transformer. The NAND gates are capacitively coupled to the drivers to prevent one driver conducting should the oscillator fail.

Two output transistors are used for each phase. These ensure adequate gain, the typical gain of a 2N3771 being 20 at 15A, and 10 at 30A. The use of a transistor pair also reduces the saturation voltage since the current in each transistor is halved. In the prototype, with a 250W load, the saturation voltage when using one transistor was 2.0V. When the second was connected, the saturation voltage dropped to 1.1V.

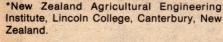The ideal way of ensuring that two paralleled transistors take on equal current is to use emitter resistors chosen so that the voltage across each resistor is of the order of 0.5V. This applies negative current feedback





Above is the prototype. A PC board accommodates most of the components, and is mounted on top of the chassis with the heatsink and power transformer.

which reduces gain and saturation voltage variations between the two transistors. However, this is rather wasteful of energy when large currents are involved. To avoid this, base resistors R14 and R15 along with R16 and R17 were used to equalise transistor collector currents. Current sharing using this method has proved to be quite satisfactory.

Diodes D1 and D2 conduct the reactive current after their opposite transistor pairs have ceased conduction. The current pulse they have to pass is of the order of 30A when the power factor is 0.2. However the conduction period is short and diode specifications indicate that a 2.5A rating

is sufficient.

The 100Hz square wave is picked off the input of the CD4018 and differentiated by C1 and C2 with R3 and R5 before being fed to the inputs of each phase driver. This slows the switching times of the drivers and therefore reduces the maximum possible pulse width of each phase to slightly less than 180°, ensuring that under conditions of maximum power transfer, the current in one transistor pair has decayed to zero before the other pair begin to conduct. It also slows the switching time from 10us to 60us. At full power this results in a switching loss at only 0.6W which is negligible.

The power output of the inverter is determined by the pulse width of the signal fed to the driver stages. This is controlled by error voltages derived from both the output voltage and current. A sample of the output voltage is obtained from secondary winding S1. This voltage is rectified by the full wave bridge D3, filtered, and applied to the inverting input of operational amplifier IC7(a) via the output voltage control potentiometer VR1. The resulting DC voltage is compared in the amplifier with a 5.6V reference from D5 to yield a

voltage error signal.


To obtain a current error signal, the supply current to the output transistors is passed through R18 to develop a voltage proportional to current. This is averaged and compared with a reference derived from diode D4, which is pre-regulated by D5.

Operational amplifier IC7(b), which amplifies the current error signal, has a large feedback capacitor to ensure stability when the inverter is in the current limited mode. The amplifier has, in this configuration, a large DC gain equal to the open loop gain of the amplifier — about 100dB — and an AC gain of almost unity.

The outputs of IC7(a) and IC7(b) are

The outputs of IC7(a) and IC7(b) are fed via a diode OR gate to the inverting

At right is the complete circuit diagram of the 12-230V inverter. Main features of the circuit include crystal-controlled output frequency, voltage regulation, and overload protection.

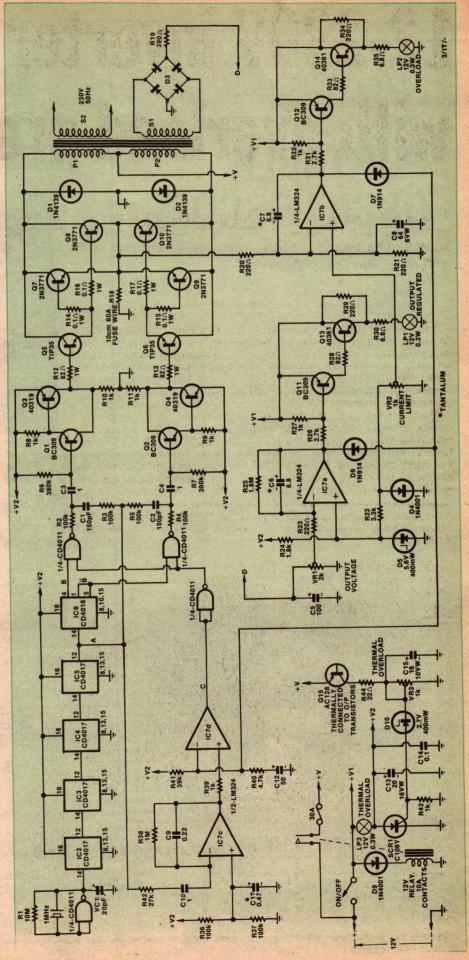



MODEL 303

## PORTABLE OSCILLOSCOPE

15 MHz Dual Trace Portable Oscilloscope with three-way power supply

15 MHz/5 mV

Offers high sensitivity of 5 mV/DIV in DC to 15 MHz bandwidth. 3 inch CRT with 1.5 kV regulated accelerating voltage gives you a clear bright display.

### **FULLY AUTOMATIC TRIGGERING**

In the automatic position the time base is free running (in the absence of a signal) for quick zero line references at all sweep ranges. The time base is linked to the chopped/alternate modes and TV line/frame displays and change-over is completely automatic. Fastest sweep rate of 200nsec/DIV makes the display of fast transition time signals possible.

### THREE POWER SOURCE

Operates with standard line voltage (90 to 260 V) or from the internal rechargeable Ni-Cad battery, that provides 2 hours operation before recharging is required. It also operates from any external DC voltages of 11 to 30 V, eg car batteries, standard "C" size or UM-1 battery cells, etc.

### **SMALL and LIGHT**

Measures 113 mm high by 223 mm wide by 298 mm deep and weights only 4.5 kgs (5.5 kgs including battery). A robustly built handle is provided for carrying in the field and for the best viewing of the display on the work bench.

\$650 excluding tax.



# You have your own calculator.



Why not a DMM

Fluke 8020A DMM for Field Service:



Finally, a digital multimeter that's yours, just like your pocket calculator, and more useful.

You pack only 13 ozs. in your pocket or service kit, but size is deceptive. The 8020A has more useful features than any other multimeter available—at any price! Features like 26 ranges and seven functions, including conductance. 2000-count resolution. Hi/lo power ohms.

And it's rugged. The high-impact case protects a minimum number of component parts (47 in all), and they're all readily available from any of the worldwide Fluke service centers. Your 8020A is factory calibrated by NBS traceable equipment. And we guarantee it'll live up to published specs for a full year.

The 8020A is a true field instrument, designed with a highly readable LCD display, and inexpensive 9V transistor battery power for continuous use up to 200 hours. Reliability, quality and value: that's Fluke tradition.

\$188 excluding tax.

Available soon will be a more sensitive version of the TTM303 oscilloscope. It will also feature an add slash subtract mode. Data sheets and prices available now.


### ELMEASCO Instruments Pty. Ltd.


SYDNEY
PO Box 30, Concord,
NSW. 2137. 13-15
McDonald St, Mortlake,
NSW. Phone (02) 7362888. Telex 25887.

MELBOURNE PO Box 107, Mt. Waverley, Vic. 3149. 21-23 Anthony Drive, Mt. Waverley, Vic. Phone (03) 233-4044 ADELAIDE Phone (08) 51-3521.

PERTH Phone (09) 325-3144 bankcard bankcard

BRISBANE Phone (07) 229-3161

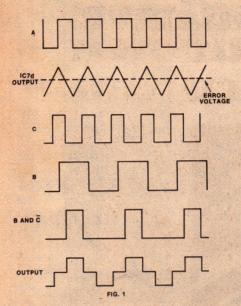

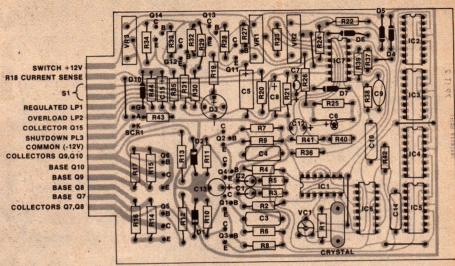

This component overlay diagram shows the PC board as viewed from the component side. Make sure that polarised components are correctly oriented.

input of IC7(d). A delay circuit, consisting of R41, R40, and C12, controls the rate of change of voltage on this input. This is necessary because the long time constant of the voltage sensing circuit would otherwise cause the output voltage to overshoot when the unit was switched on. R40 is included to allow a small rapid change to be made to the output voltage. IC7(d) is wired as a comparator.

The DC error signal applied to the inverting input is compared with a 100Hz triangular wave fed to the non-inverting input. The triangular wave is generated by IC7(c), which integrates the 100Hz square wave obtained from

the 4018 input.

The result of the comparison in IC7(d) is a pulse-width modulated 100Hz square wave. This signal is fed via an inverter to the NAND gates of each phase of the 50Hz drive, the phasing being such that the off-time of each phase is proportional to the error signal. Reference to Fig. 1 will clarify the formation of the various waveforms.

A National LM324 (or RCA CA324) quad op-amp is specified for IC7. This was chosen because, for the current error amplifier, the inputs are almost at zero volts. The 324 can be kept in the linear mode, even when the inputs are

at ground potential.

The outputs of the error amplifiers are fed to discrete lamp drivers to indicate the running mode. Lamps were chosen because LEDs are difficult to see outdoors or under strong lights. The lamp driver transistors Q13 and Q14 each have a parallel resistor to keep a small current flowing through the lamp. This keeps the filament just less than red and its resistance somewhat


greater than its value when cold. In addition, series resistors, R30 and R35, are used to ease the load on the 40361 drivers, thus enhancing their reliability.

As can be seen from the overlay diagram, the PC board has been designed to plug into a socket. If the socket is not going to be used, holes should be drilled through the contacts in order to properly secure the connec-

ting wires before soldering.

Although the layout is not critical, the wires connecting the output transistors, transformer primary, fuse, relay contacts and battery leads should be capable of handling 30A. Attention should be paid to solder joints and to cleaning the enamel insulation from the transformer primary wires. Poor joints can cause considerable voltage drops at 30A. The supply fuse should have a rating of 30A-35A.

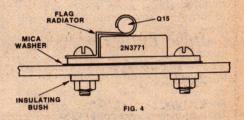The current sensing resistor consists of about 100mm of 60A fuse wire



mounted on either a component board or between two tag-strips. This wire has a diameter of 1.3mm but any copper wire with a diameter between 1mm and 2mm would be satisfactory.

Thermal overload sensing and protection is provided by Q15 and

SCR1

Since the prototype is to be used in arduous conditions, quality Canon sockets were used for the input and output. For general use however, flying leads for the battery supply and a conventional mains socket for the output

### Performance of prototype . . .

### 12-230V inverter

are suitable.

The output transistors are mounted on 20cm of extruded aluminium heatsink. Although the heatsinking reguirements are guite small in the normal operating mode, all the power is dissipated in the output transistors when the output is shorted, so an appropriate heatsink is required. Q15 is thermally connected to one of the output transistors with a flag type heatsink. Mounting details are shown in Fig. 4.


The transformer may have a specification similar to a mains transformer and can be specified by the VA rating and the turns ratio.

Suggested windings are:

Primary 10.5 - 0 - 10.5V Secondaries 12V, 0.1A 230V, 1.5A Rating 300VA

The reverse polarity protection relay must have contacts which are capable of passing, but not necessarily switching, 30A. A relay with a 12V coil and having a contact rating of 10A will suffice. Ten-turn trimming poten-tiometers are used as they allow easier setting of the voltage and current limits.

The setting up procedure should be adhered to because, until it is set up, the inverter has no protection and failure of the output transistors could result. Before connecting the power, set the voltage and current potentiometers fully anticlockwise and the thermal overload fully clockwise. Apply the power and, if the unit has been correctly wired, it will operate with either the regulated lamp or the overload

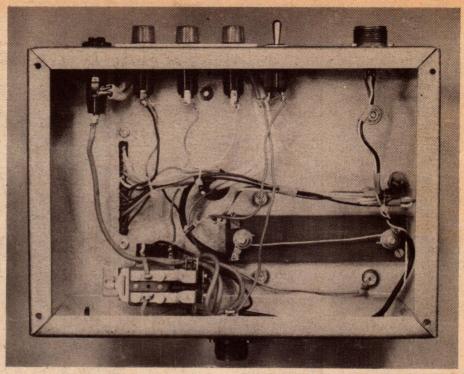

An "under-the-chassis" view. R18 (10cm 60A fuse wire) is located on the tagboard at right, while below left is the relay. Leads to heatsink transistors and transformer pass through grommetted holes.

lamp illuminated.

To set the output voltage, either a true RMS voltmeter will be required, or the adjustment will have to be carried out using an approximate comparison method. If an RMS meter is available, lightly load the inverter (using a 100W lamp for example) and advance the voltage control potentiometer until the meter, connected to the output, reads

To adjust the output using the com-

parison method, put a 100W lamp on the inverter output beside another 100W lamp connected to the mains. Advance the voltage control until the light output of each lamp appears the same. If during this procedure the overload lamp is illuminated, advance the current control one turn.

Note that because the waveshape of the output is non-sinusoidal, a normal voltmeter will give an erroneous

reading.

### PARTS LIST FOR 12-230V DC-AC INVERTER

**SEMICONDUCTORS** 

1 CD4011 quad 2-input NAND gate

4 CD4017 decade dividers

CD4018 presettable counter

LM324 quad op-amp BC309 or BC212 PNP transistors 40319 or BC640 PNP transistors

TIP35 NPN transistors

2N3771 NPN transistors

40361 or BC337 NPN transistors

AC128 PNP transistor

IN4139 silicon diodes

2 IN4001 silicon diodes

IN914 silicon diodes

1 2.7V 400mW zener diode 1 5.6V 400mW zener diode

1 B60 C800 bridge rectifier

1 C106Y-SCR

RESISTORS (1/2W unless stated)

4 x 0.1 ohms 1W, 2 x 6.8 ohms, 1 x 22 ohms, 2 x 82 ohms, 2 x 82 ohms 1W, 5 x 220 ohms, 1 x 390 ohms, 8 x 1k, 1 x 1.8k, 2 x 2.7k, 1 x 3.3k, 1 x 4.7k, 1 x 27k, 1 x 39k, 6 x 100k, 2 x 390k, 1 x 1M, 1 x 1.8M, 1 x 10M, 2 x 1k trimpots (Bourns Model 3069), 1 x 2k trimpot (Bourns)

CAPACITORS

2 150pF ceramic or polystyrene

1 0.1uF polyester

1 0.22uF polyester 1 0.47uF 16V tantalum

3 1uF 16V tantalum

2 6.8uF 16V tantalum

1 16uF 10V electrolytic

20uF 16V tantalum

50uF 16V tantalum

64uF 6V electrolytic

1 100uF 16V electrolytic

1 20pF trimmer (optional)

MISCELLANEOUS

1 Transformer (see text)

1 PC board, 100 x 147mm, Code 79it2

3 12V 0.3W lamps and holders

1 1MHz crystal

1 15-way Amphenol PC socket, 0.156in connector spacing

1 12V SPST relay, 10A contacts

1 SPST toggle switch

1 240V ouput socket

20cm extruded aluminium heatsink

1 Flag-type heatsink

1 30A fuse and fuseholder

1 chassis with vented cover

4 rubber feet

NOTE: Resistor wattage ratings and capacitor voltage ratings are those used for the prototype. Components with higher ratings may generally be used, provided they are physically compatible.

After the output voltage has been set, put a 300W load on the inverter (three 100W lamps) and adjust the current control potentiometer until the inverter is just at the point of going into the overload state. Alternatively, if a true RMS ammeter is available, set the current limit to 30A.

The next step is to check and adjust the thermal overload protection. To ensure that it is operative, turn the overload control fully anticlockwise and then put a large load, for example a 1kW heater, on the output and switch on. The protection circuit should shut down the inverter within about 30 seconds, lighting all the lamps. However as a precaution, keep a finger on one of the output transistors. If the thermal overload circuit hasn't shut the unit down by the time the transistor is too hot to touch, switch off and recheck wiring.

Assuming that everything functions correctly, all that remains is to set the shutdown temperature. Allow the unit to cool and set the control fully clockwise. Switch on again and, when the transistors are almost too hot to touch, remove the load and turn the control back until the unit goes into the overload mode. Alternatively if a contact thermometer is available, set the temperature limit when the transistor case reaches 65-70°C.

The design of this inverter incorporates some features which may not be required and could therefore be omitted to reduce the cost.


Crystal frequency control is only required when the load is particularly frequency sensitive. If this is not the case, the 4011 may be replaced with a 4093 quad two-input NAND Schmitt trigger. Then by replacing VC1 with a fixed capacitor and removing the crystal, a free running oscillator is formed (see Fig. 2). All the 4017 dividers are thereby eliminated and a wire link is taken from pin 4 of the 4093 to pin 14 of the 4018.

With this oscillator, the frequency depends somewhat on supply voltage but will suffice for most applications; it will still remain independent of load.


The reverse polarity protection relay may be eliminated. Reverse supply polarity will then blow the fuse. However diodes D1 and D2 may be destroyed by the heavy current surge so they should be replaced with diodes rated at more than 10A. Also, a diode should be wired across C14 with its anode to the negative rail so that the control circuits won't "see" the reverse voltage.

The lamp drivers can also be eliminated if desired. R26 and R31 should then both be changed to 1k and the rest of each driver circuit replaced by a LED, the anode of which is connected to the positive supply (see Fig. 3)

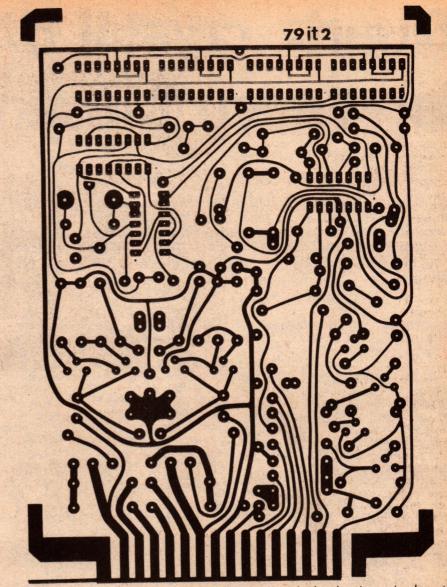The prototype has an idling current of 1.2A with an efficiency of 85% at



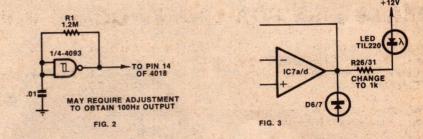Here is an actual size reproduction of the PC board. The shorting strip along the bottom is to allow the edge connectors to be gold plated.



250W. The inverter can handle power factors from zero to unity, lagging or leading. The output voltage is within 5% of 230V except for zero load and

power factors deviating too far from unity. This is due to the voltage sensing circuit which reads the average output voltage rather than the RMS value.

### Notes on components . . .

The transformer specified for this project is not a normal stock item. We understand that if there is sufficient interest, the transformer will be manufactured by Transcap Pty Ltd (Brookvale, Sydney) and distributed through Watkin Wynne Pty Ltd, 32 Falcon St, Crows Nest, NSW 2065. Alternatively, readers may be able to take advantage of the specifications given in the text by modifying an existing mains transformer. 2N3771 NPN power transistors are available from Radio Despatch Service, 869 George St, Sydney, NSW 2000.

# Quartz crystal driver for Yaesu Musen clock

Following on from our article in October last, describing how a Yaesu Musen clock could be synchronised with the 50Hz mains frequency, here is how the same clock may be synchronised from a low cost American colour TV crystal. The short term accuracy should be better than before but with some overall drift over a long period.

by IAN POGSON

In October 1978, I described how a Yaesu Musen Model QTR-24 clock could be synchronised to the 50Hz mains. At that time I suggested that it should be possible to synchronise the same clock by using a quite cheap American colour TV crystal, in association with a CMOS IC (type MM5369) which divides to 60Hz. This idea worked extremely well in practical terms, and the reader should have no difficulty in duplicating our prototype.

ty in duplicating our prototype.
The crystal frequency is 3579.545kHz and the MM5369 IC includes a crystal oscillator section. The crystal oscillator output is available via a buffer, so that measurements may be taken. The IC also divides it by 59659, which gives a

nominal output of 60Hz.

We say "nominal" because if we divide 3,579,545Hz by 59659, we get 60.000084Hz. If we used this odd frequency we would expect the clock to gain a little over one second in 10 days. Fortunately, by simply trimming the crystal frequency a little lower, to 3,579,540Hz, we get precisely 60Hz.

At this point we needed to consider whether this 60Hz could be used to drive the clock directly, or whether it would need dividing to 30Hz. In the earlier project we changed the 50Hz mains frequency to 30Hz so that it would be a multiple of the six beats of the clock to be driven. Happily, the 60Hz available from the 5369 is also divisible by six. However, we had to establish whether the pulses of the clock movement to be driven were wider than the positive going pulse of the 60Hz component. A check showed that all was well and that we could synchronise directly from the 60Hz.

So much for the figures. Let us look at the circuit and see how it is done. The crystal is connected between pins 5 and 6 of the 5369. It is shunted by a network of capacitors to trim the crystal to the exact frequency. There is a 33pF capacitor in series with a 7-36pF trimmer, the latter as a coarse frequency adjustment, and a 3.5-13pF trimmer in series with fixed 3.3pF as a fine frequency adjustment. These latter are

shunted across the larger trimmer.

The crystal is an AT cut. This has a very good temperature coefficient which is usually (but not always) negative, ie, decreases in frequency with increasing temperature. We sought to introduce further temperature compensation in the form an N750 type for the 33pF series capacitor. With the particular crystal shown on the board, the compensation is a little more than required. This will vary from crystal to crystal, and the compromise should be a fairly good one.

The 60Hz emerges from pin 1 of the 5369. Before it can be used to synchronise the clock movement, it must be processed. The output level is reduced by the 4.7k and 560 ohm resistors forming a voltage divider. The reduced signal is fed to an emitter follower Darlington pair, via a 1uf blocking capacitor. The required DC level across the 220 ohm output resistor is set with the 220k trimpot, giving a DC component on which is superimposed the correct level of 60Hz component.


The switch between the emitter follower output and the clock movement is used for setting the time and more will be said about this under set-


ting up and adjustments.

For a convenient power supply, I used a "plug pack". These are available in a number of brands and they consist basically of a small transformer, with rectifier and filter, built onto two pins of the standard three-pin plug. The device is double insulated.

The circuit needs about 9V DC, and this voltage should be as stable as possible, since voltage changes can change the oscillator frequency. The voltage regulation from the plug packs is quite poor and the nominal 9V output can be as high as 12V when unloaded or lightly loaded. The logical approach is to regulate this higher voltage down to 9V or so with a zener diode.

As zener diodes vary their voltage

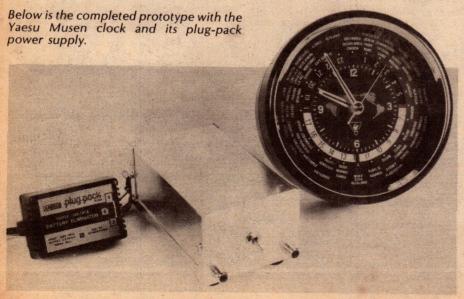

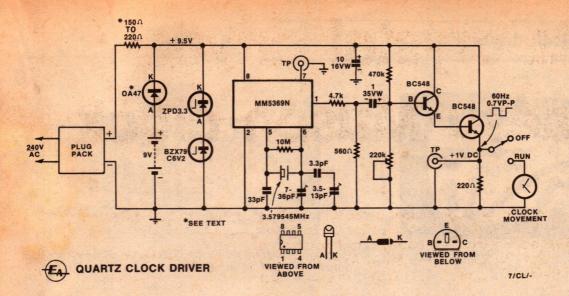

At left is the complete diagram of the crystal drive unit. The crystal is a low-cost type as used in American colour TV sets

output with changes in temperature, we have taken steps to combat this as well. Without going into a lot of details, suffice it to say that different nominal zener voltages have different temperature coefficients. By combining two diodes with opposing temperature coefficients, we can more or less cancel the temperature effect. Combining a 6.2V zener diode with one at 3.3V gives us a nominal 9.5V regulated, with very little variation due to temperature change.

The usual dropping resistor is required between the unregulated source and the zener diodes. The value will vary according to the brand of plug pack. With the Arlec brand, the unregulated voltage was 11.2 and, on the basis of 12mA drain, the resistor works out to be 150 ohms. We also tried a Ferguson pack and the unregulated voltage from this was 12.2, which requires 220 ohms. If you use a pack which delivers a voltage other than those quoted, then the series resistor should be changed accordingly.

It may be asked why the dropping resistor needs to be changed at all, provided that the zener diode dissipation is not exceeded. The answer is that, due to the rather broad knee on the zener diode curve, the output voltage rises significantly if the input voltage is increased by the amount which we have just quoted. This may not matter in itself but we have also provided for a battery backup in the event of a mains failure. In the worst case, the difference between the normal supply voltage and that from the battery would be too great, leading to a significant change in oscillator frequency.

The standby battery is isolated from the main supply by a diode. Of the diodes available, the OA47 gold bonded type appears to offer the least voltage drop (about 0.3V) at the current drain involved. However, this could be too low in some circumstances. It is possible for a new battery to be as high as 9.6V, while the zener network could

be as low as 9V. If so, it would be better to use either an OA91 or a silicon EM401, or similar.

It must be realised that operation from the battery involves some drop in voltage and, therefore, some change in frequency. On a short term basis, such as is usually involved with power failures, the error will be minimal and, in any case, is far preferable to a complete clock failure.

Some comments on components may be helpful. The two-piece sheet aluminium box used for the prototype accommodates all the components without overcrowding. However, if you wish to use another box there is no reason not to do so. At the same time, I would recommend an all-metal box, in that it shields the crystal against the proximity effects of other objects.

By the time this appears in print, the printed board should be available from the usual sources. There should also be no problems in obtaining the IC and the transistors. Any transistor similar to the BC548 should be satisfactory. We used a tantalum 1uF capacitor to couple into the Darlington pair but an ordinary electrolytic of similar ratings may be substituted. The 33pF N750 ceramic

should be used if possible. Alternatively, an NPO ceramic may be substituted with some slight deterioration of time keeping due to temperature changes.


The two trimmers in the prototype are made by Cermet and these should be used where possible. However, the Philips series of plastic trimmers will fit the board and should be a satisfactory substitute. Some variation in capacitance value may have to be tolerated here but maximum values of 40pF and 10pF should be OK.

The crystal is one of the most important components of all but no problems should be experienced in getting a suitable one. The one shown in the prototype came originally from Dick Smith. This crystal is one of the larger packages and may not be currently available from this source.


However, there is a smaller package available from Dick Smith and these should be readily available. The pin spacings are different for the two packages but the printed board has been made to take either type.

Construction is only a small job and should require only a short time. Take care not to overheat components while soldering but, at the same time, make

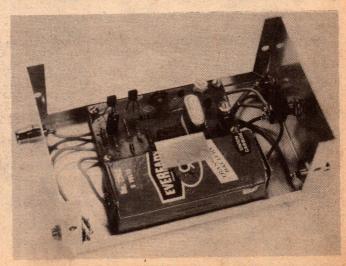
A single printed circuit board accommodates most of the components. Socket at top left is the clock drive output, while the DC supply input is at lower left. Sockets on right are: one to pin 7 of the IC, and one in parallel with the output socket.



### Quartz crystal clock driver

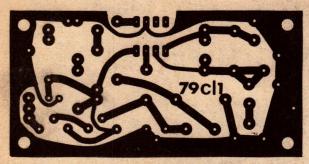

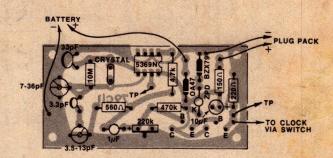For those readers who make their own boards, here is an actual size reproduction of the PC pattern.



This overlay diagram shows the PC board as viewed from the component side. Pay attention to polarised components.

sure that good joints are made. Leave the 1uF tantalum capacitor off the board until final setting up.

The 5369 IC should be left until last. If you do not use a socket, the 5369 should be soldered in place with the barrel of the soldering iron connected to the earthy copper on the board.

With the board completed, check to make sure that all components are in the right places and that all polarities have been observed. On the prototype box we fitted two sockets at one end, one to suit the DC supply input and the other for the clock drive output. At the other end we fitted the output switch and two more sockets, one across the output and the other to the crystal oscillator output from pin 7.

A small bracket is needed to hold the battery and we made one from a scrap of aluminium. It, and the battery, are best fitted before mounting the board. The board sits alongside it, supported by four brass spacers, as shown in the photograph. Before fitting the board, check that all leads for external con-

nections have been fitted. Do not connect the battery at this time.

The unit is now ready for adjustments. Set the two trimmers and the 220k trimpot to their mid points. Plug in the plug pack and switch on. Measure the voltage delivered by the plug pack, and select the dropping resistor as already explained. The regulated supply should be 9.5V, plus or minus 5%.

Check the DC voltage across the 220 ohm resistor at the output of the Darlington pair. It should be set to 1.0V by means of the 220k trimpot. At this stage switch off and fit the 1uF tantalum coupling capacitor.

Before attempting to run the clock from the driver unit, fit a normal dry cell and run it for a few days. If necessary, regulate it until it keeps within 10 seconds per day.

To connect the clock movement to the driver use a length of audio type coax cable fitted with an RCA plug at one end and crocodile clips at the other. Plug it into the driver and connect to the movement in place of the 1.5V dry cell. Make sure that correct polarity is observed.

Switch on the power supply and switch on the movement start switch. The movement should start after a delay of one to two seconds. When the movement is switched off it may take up to 30 seconds to stop. These points must be taken into account when setting up the clock for correct time.

Set the second hand about two seconds past the 60 and, with the movement start switch off, wait for an appropriate time signal and switch on. An ideal time signal is provided by VNG on 7.5MHz and 12MHz (day) or 4.5MHz (night). If this is not available, use a time signal on the hour from one of the broadcast stations, or the Telecom telephone time service.

When the clock is running, I suggest that you check its time daily to see that it is regulated correctly. If you have already adjusted the crystal frequency against a good counter, the clock should run well within one second per day. If not, the drift should be no more than one second per day and this error should be adjusted very carefully with the 7-36pF trimmer.

With the clock regulated thus far, which may take several days, its performance should be checked over several more days to see which way it is going. Any small drift should then be corrected with the 3.5-13pF trimmer. From here on it is up to the individual to decide just how far he will pursue the adjustment procedure.

If, after initially starting the clock it is found that after the first day it has gained or lost several seconds, it means that the movement is not synchronised and it should be regulated by means of the screw adjustment at the back of the movement.

Having set up your clock it should keep time within the limits of the crystal oscillator and the degree to which it has been adjusted. Suffice it to say, it should be reasonable to expect no more than one second drift over a period of about 11 days, which is equal to about one part in one million.

### PARTS LIST

- 1 Aluminium box 133mm x 76mm x 54mm
- 1 Printed board 76mm x 38mm code 79cl1
- 4 Rubber feet
- 3 RCA sockets, single hole mounting
- 1 Miniature toggle switch SPDT
- 1 Plug-pack with nominal 9V DC output
- 1 Socket to suit DC plug on plug-pack
- 1 9V battery No 2362
- 4 Brass spacers, %in long tapped %in Whitworth
- 1 MM5369 oscillator/divider 8-pin DIL
- 1 Socket 8-pin DIL
- 1 Crystal 3579.545kHz
- 1 OA47 diode (see text)
- 1 ZP3.3 zener diode
- 1 BZX79C6V2 zener diode
- 2 BC548, or similar transistors
- 1 220k Philips miniature trimpot

### RESISTORS (1/2W)

1 x 150 ohms or 220 ohms (see text), 1 x 220 ohms, 1 x 560 ohms, 1 x 4.7k, 1 x 470k, 1 x 10M

#### CAPACITORS

- 1 3.3pF NPO ceramic
- 1 33pF N750 ceramic (see text)
- 1 3.5-13pF Cermet trimmer
- 1 7-36pF Cermet trimmer
- 1 1uF 35VW tantalum
- 1 10uF 16VW electrolytic

### MISCELLANEOUS

Hookup wire, solder, screws, bracket for battery, battery connector clips. Note: Resistor wattage ratings and capacitor voltage ratings ar those used in the prototype. Components with higher ratings may generally be used provided they are physically compatible. Components with lower ratings may also be used in some cases, provided the ratings are not exceeded.

### **Central Data**

# Get into computing the economical, expandable way

### **FEATURES:**

- \* Signetics 2650 microprocessor based -
- \* All processor signals buffered for TTL fan out of 10
- \* Supervisor programme in 1k of PROM
- \* 730 bytes of RAM available to the user
- \* Provision for 3k of additional PROM on the board
- \* Cassette Interface on the board using 1200/2400 Hz
  Kansas City standard
- \* Composite Video output with 16 lines of 80 characters display format

\* Two parallel input ports, and one bit selectable output port


The Central Data System Board CDYSBDA facilitates the writing

The System Board can be expanded by connecting the S-100 Board CDS100BDA. This allows you to plug in any S-100 static memory board with an access time of less than 500ns or the Central Data

of programmes in Hexademical with only the addition of a TV

monitor, ASCII Keyboard and power supply.

dynamic RAM boards CDXXKBDA.

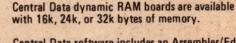

Central Data software includes an Assembler/Editor and an 8k BASIC tape. A Debugger, 12k BASIC and Assembly Language Package is coming soon.

Other hardware now available and on the way includes Central Data Computer Mainframe with Power Supply, ASCII keyboard with solid-state-low-profile keyswitches and +5 volt operation and Floppy Disc controller with one, two or three drives.

For general and specific information:

TECNICO ELECTRONICS



Premier Street, Marrickville, N.S.W. 2204. Tel. 55 0411.

2 High Street, Northcote, Vic. 3070. Tel. 489 9322.

## Special offer + nine simple projects

# 20 transistors for \$2.50!

Here's an offer that's simply too good to refuse — 20 small signal silicon transistors for just \$2.50, or a little over 12 cents each! To help you take advantage of this special price, we describe here a number of simple projects which use the offer transistors extensively.

This special transistor offer comes from — you've guessed it — Dick Smith Electronics Pty Ltd. The transistors are available only in packs of 20, each pack containing five BC237s, five BC238s, five BC307s and five BC558s. As far as the projects described here are concerned, these may be considered equivalent to types BC107, BC108, BC157 and BC158 respectively (see data table).

At \$2.50 for the pack, Dick's price is particularly good value, especially when one considers that the normal price for 20 transistors of this type

would be around \$5.80!

Dick Smith emphasises that the devices are in no sense factory rejects or "seconds". The transistors are all made by Siemens, and are standard quality items which meet all the

manufacturer's specifications. The offer is simply because Dick has been able to purchase 200,000 of the devices at a rock-bottom price. It will remain open until stocks are exhausted.

To take advantage of the offer, all you have to do is fill out the coupon which appears at the end of this article and take it — with your money — to Dick Smith Electronics. Note that the price quoted in the introduction applies only to over-the-counter customers. Mail order customers can still take advantage of the offer, but should add another 50 cents to cover postage and packing.

As you can see from the data the BC237 and BC238 transistors are NPN types and, in the circuits presented here, may be freely interchanged. The

same comment on interchangeability applies to the BC307 and BC558 PNP types.

It is also worth remembering that you can substitute PNP transistors in those circuits using only NPN types, provided you reverse the polarity of the power supply rails and reverse other polarised components (diodes and electrolytic capacitors etc). The circuits which lend themselves most easily to this approach are the amplifier and the fuzz box.

Whatever you do, make sure you connect the transistors into the circuit with the correct lead configuration. An incorrectly wired transistor will not only refuse to function, but may be damaged as well! Follow the lead wiring diagram shown next to the data table.

### Simple Moisture Alarm

This device will not stop the rain, but at least it will help the lady of the house to get the washing dry — by sounding a strident alarm when the rain starts. Besides acting as a rain alarm, the device could be used as a bed-wetting alarm, an excessive condensation indicator, a pool splash alarm, a novel form of doorbell system or as an indicator that the bath water is at its correct level. The applications for a reliable moisture detector are many and varied.


Basically, the unit consists of a moisture sensing element, an NPN silicon transistor which conducts in proportion to the amount of moisture on the sensor element, and an SCR which is triggered when the current through the transistor rises above a set value. When the SCR conducts, it applies power to a two-transistor multivibrator which has a loudspeaker as part of the collector load of one of the transistors.

sistors.

Once the SCR has triggered, the alarm will continue to sound until it is turned off.

Our sensor was made from Veroboard. For those not familiar with the product, it is a phenolic composition board with parallel copper strips bonded to one side, small holes being punched at regular intervals along the copper strips.

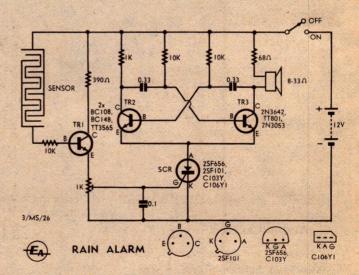What we have done is to connect alternate copper strips to form interlocking grids. There are actually three grids on



the board, with no connection between. One grid is connected to the positive supply, one grid connected via a resistor to the base of the transistor, and the third is left "floating".


By having three "grids" on the sensor, the unit becomes more reliable as a rain indicator. With a simple sensor one raindrop could reduce the open-circuit resistance and allow

### Here are the transistor specifications:

Туре	Case	Polarity	Vce	Vcb	lc (mA)	Hfe	Ft (MHz)	Power (mW)	Equivalent
BC237	TO-92	NPN	45	45	100	120-220	250	220	BC107
BC238	TO-92	NPN	20	20	100	120-220	250	220	BC108
BC307	TO-92	PNP	45	50	100	75 min	150	300	BC157
BC558	TO-92	PNP	25	30	100	180 min	150	500	BC158

the alarm to be triggered. This would mean that on overcast days when there is sometimes light intermittent "sprinkling" the unit could be triggered by just one drop, constituting a "false alarm". By having three grids, a minimum of two raindrops is required to trigger the unit — the two raindrops have to "bridge" appropriate copper strips for triggering to occur. This feature, in combination with the sensitivity control, allows the unit's sensitivity to be set for reliable triggering on anything from a light shower to quite a heavy downpour.
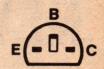
## Follow this diagram when wiring transistors into circuit




Make sure that you solder the transistors into circuit with the correct lead configuration. An incorrectly wired transistor will not only refuse to function, but may be damaged as well. The above diagram shows the lead configuration of the offer transistors as viewed from below.
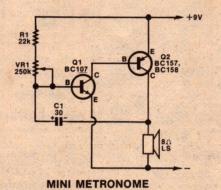
### Mini Metronome

Here is a really simple project — a unit that simulates beautifully the sound of a time bomb ticking away! For those more attracted to gentler pastimes it may also serve as a metronome, that is it gives a loud click at regular intervals, the actual interval being varied by a potentiometer in the circuit. It's very simplicity also makes it highly suitable for use as an audio warning device with the alarm switch inserted in the supply line.

The actual working of the circuit is fairly simple; on applying a voltage across R1, VR1, C1 and the loudspeaker, capacitor C1 charges up till a point is reached when Q1 switches on. This in turn switches Q2 to a conducting state — meaning that a voltage



is applied across the loudspeaker causing it to "plop".

The base current of Q1 reduces the charge on C1 to the stage where the transistor turns off; thus the cycle starts all over again. The rate at which C1

charges depends upon VR1 and by altering this the interval between the cycle can be varied.

A wide variety of transistors may be used for Q1 and Q2. Q1 is an NPN transistor and may be either a BC237 or a BC238. Q2 is a PNP type and can be either a BC307 or a BC558.


The components are mounted on a small piece of Veroboard. One end is drilled to take the potentiometer and the other components are mounted and soldered at the other end. The project is so simple that very little can go wrong and immediately you switch on regular "plops" will be heard. By altering VR1 a wide range of intervals should be covered but if you want slower ones — that is with several of C1. If you want faster ones, lower its value.

### Model Train Signaller

One of the most useful devices for the model railway enthusiast is the reed switch, a simple and extremely reliable unit which can be located between the rails of a track and used to sense the passing of a train. A small magnet mounted under the loco will trip these switches. One very obvious application is to operate an automatic signalling system.

A suitable system is shown in the accompanying circuit. It is based on a two-transistor configuration called a "flip-flop", one being needed for each signal

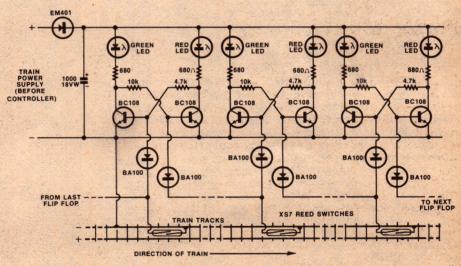It uses a basic signalling system employing two light emitting diodes (LEDs) — red for stop and green for go — and any signal remains on green until a train passes it, whereupon it changes to red. The signal remains on red until the train has cleared the next section of track, that is, up to the next signal. When the next signal changes to



MODEL TRAIN SIGNALLING SYSTEM

red the first signal reverts to green.

Each reed switch is connected to two flip-flops, isolated from each other by silicon diodes. These diodes stop unwanted interaction between signals behind the train. When the train passes over the reed switch, the contacts close, connecting together the base and emitter of the associated transistors. The forward bias is removed, cutting each transistor off and forward biasing its partner.

Coming Soon!

# FW BOOKS from NEWNES-BUTTERWORTHS for the ELECTRONICS ENTHUSIA

### RADIO CIRCUITS EXPLAINED, G. J. King

Circuits used in modern radio receivers are examined in detail ranging from the simple transistor radio to the specialised hi-fi receiver. The book will provide a clear understanding of principles and operation and design parameters of contemporary sets. Invaluable to radio and audio service technicians, to the student and to anyone interested in radio.

1977 160 Pages Illustrated Cloth

#### BEGINNER'S GUIDE TO TAPE RECORDING, I. R. Sinclair

An easy to understand introduction to the principles and techniques of tape recording. Covers choice and use of machines, transcription from radio, disc or tape, mixing, editing, sound and picture synchronisation and nature recording. Will help lead to rapid mastery of the skills of making good recordings.

1978 176 Pages Illustrated Paper
Reviewed ELECTRONICS AUSTRALIA December 1978

#### 110 WAVEFORM GENERATOR PROJECTS FOR THE HOME E CONSTRUCTOR, R. M. Marston

Many electronic devices, from simple alarm generators to complex test equipment, are based on waveform generators. This addition to the popular series for projects builders shows 110 wave-generator circuits with a variety of applications of interest to the electronics amateur, student and engineer the circuits have been designed, built and fully evaluated by the author. book includes design charts for readers wishing to design or modify waveform generators to their own specifications.

1978 144 Pages Illustrated Paper

BEGINNER'S GUIDE TO COMPUTERS, T. F. Fry No technological development over the past 30 years has had as great an impact on society as the computer. This book examines what computers can do, and how they do it. Computer number systems, logic and logic gates, as well as the central processing unit and the memory, are all examined, together with input and output devices, and programming. The book concludes with a brief survey of the effect of the computer on society.

1978 192 Pages Illustrated Paper

#### NEWNES RADIO AND ELECTRONICS ENGINEER'S POCKET BOOK 15/Ed., H. Moorshead

An invaluable compendium of facts, figures and formulae, indispensable to the designer, student, service engineer, and all interested in radio and elec-

This edition has been completely revised. The omission of obsolete and unnecessary information has made room for a considerable amount of new material relating to recent developments in radio and electronics. New tables include information on TTL, CMOS and logic.

1978 176 Pages Illustrated Cloth

### **NEWNES CONSTRUCTORS PROJECTS SERIES:**

Newnes Constructors Projects books have been specially written for the electronics enthusiast. Each book contains a collection of projects, each giving details of how the circuit works, how it may be assembled and how setting-up and trouble-shooting problems may be solved. The skilful use of colour in the text helps to clarify circuit operation, circuit board layouts are suggested and shopping lists of components drawn up for each project.

### ELECTRONIC PROJECTS IN THE HOME, O. Bishop

Useful, instructive and entertaining projects with domestic applications are described in this book, which will be invaluable to the electronics enthusiast. 1978 96 Pages Illustrated Limp

### ELECTRONIC PROJECTS IN AUDIO, R. A. Penfold

This book described a selection of projects which can be used in conjunction with audio and hi-fi equipment to increase its versatility and performance. The projects will prove useful, instructive and entertaining to the electronics 96 Pages Illustrated

### PROJECTS IN RADIO AND ELECTRONICS, I. R. Sinclair

This book contains a variety of Radio and Electronic projects which will prove useful, instructive and entertaining to the enthusiast.

1979 96 Pages Illustrated Limp

### ADDED FARM

Please send me the following books:	
36909H ( ) RADIO CIRCUITS EXPLAINED	\$12.50
33190L ( ) BEGINNERS GUIDE TO TAPE RECORDING	\$ 8.00
49165L ( ) 110 WAVEFORM GENERATOR PROJECTS	\$ 8.00
48914L ( ) BEGINNERS GUIDE TO COMPUTERS	\$ 8.50
35508H ( ) NEWNES RADIO & ELECTRONICS ENGINEERS	
POCKET BOOK — 15TH EDITION	\$ 6.50
34171L ( ) ELECTRONICS PROJECTS IN THE HOME	\$ 6.50
33662L ( ) ELECTRONICS PROJECTS IN AUDIO	\$ 6.50
34297L ( ) PROJECTS IN RADIO & ELECTRONICS	\$ 6.50
( ) Cash Enclosed ( ) Please Bill Me	
NAME:	
ADDRESS: Postcode	1.216-0.27.
SIGNATURE: DATE:	CHARLES ALL
(Recommended Domestic Retail Prices include postage and are subject to change without notice. Thi ject to acceptance by the Head Office of Butterworths.)	s order is sub-

BUTTERWORTHS PTY. LTD., 586 Pacific Highway, Chatswood, N.S.W. MAIL TO: 2067.


### Simple Intercom

Many readers could, no doubt, find a use for an intercom, but doubt whether the expenditure on a commercial unit would be justified. The unit described here is a relatively low-cost project. It can easily be used as a baby alarm — it is certainly sensitive enough — merely by switching one of the units on permanently.

The unit is not fitted with a buzzer as calling over the unit is usually enough to draw the attention of the distant party. It cannot be used for eavesdropping (an undesirable, "Big Brother" type feature) and thus its installation can cause no offence.

The basis of the intercom is a simple amplifier which boosts the "microphone" output to feed a speaker.

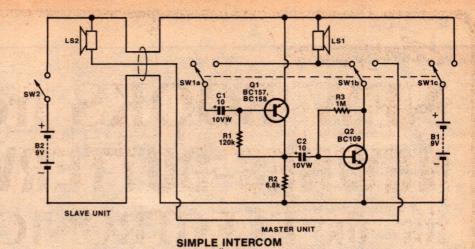The amplifier is slightly unusual and is very simple. It uses a PNP and an NPN transistor and is RC coupled. The switching is straightforward; two batteries are used, one each in the



master and slave section.

• In the normal position (as shown in the circuit diagram) no currrent is drawn and the switch on the master is set to receive calls from the slave. The only thing the slave has to do is apply battery voltage to the master by making SW2 When the master makes a call the output from the amplifier is fed to the slave loudspeaker, its own loudspeaker is switched to the input, becoming the microphone, and the slave's microphone becomes the loudspeaker. The master unit will, of course, override the slave.

### Hee-Haw Siren

This hee-haw siren can be installed in a toy fire engine or police car in order to provide a more interesting and realistic toy. Although many siren circuits have been described, this one has the advantage that it also provides one or two flashing beacons.

Transistors Q1 and Q2 form a multivibrator with a period of about 0.6 second, flashing the LED beacons and "frequency modulating" and multivibrator formed by Q3 and Q4. Q5 amplifies the output and drives the speaker.

A small speaker from a scrapped transistor radio can be used for the output transducer. If a speaker with an im-

Q1-Q5: BC107, BC108

LED A)

R2

S.6k

S.6k

120k

0.12

0.12

0.12

0.12

0.12

0.12

0.12

HEE-HAW SIREN FOR TOYS


pedance greater than 22 ohms is used, the series resistor may be omitted. If only one beacon is required, the LED in the collector circuit of Q1 may be omitted and the 220 ohm resistor in creased to 560 ohms.

### Microphone Preamplifier

This handy microphone preamplifier circuit can be built on a printed board (no. 72/p2) measuring 64 x 54mm. It has a voltage gain of 100 and draws only 0.45mA at 9V, which can be supplied from a small battery. Alternatively, supply can be obtained from a convenient positive point in the associated amplifier, through a dropping resistor.

If supplied through a dropping resistor, the 0.1uF capacitor should be replaced by an electrolytic bypass of 50uF or more at a working voltage of 12VW or more.

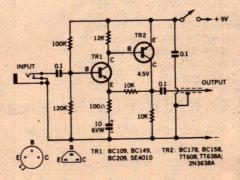A conventional circuit configuration is used. An NPN and a PNP silicon transistor are connected together in a direct coupled feedback-pair arrangement with both transistors operating as



common-emitter amplifiers. Negative feedback is applied from the collector of the PNP transistor, TR2, to the emitter of the NPN transistor, TR1, via a 10k resistor. The ratio of the 10k resistor to the 100 ohm resistor in the emitter circuit of TR1 sets the voltage gain of the circuit to 100.

Input impedance of the circuit is close to 50k, set by the parallel com-

bination (to the input signal) of the bias resistors for TR1. As such, it is suitable for dynamic microphones requiring a load of 50k. It can also be used to follow low output impedance FET preamplifiers for condenser microphones

Note that although BC237 and BC238 transistors can be used for TR1, individual transistors may prove somewhat noisy in this application. Try substituting for best results. If this proves unsatisfactory, then you will have to use a branded low noise transistor such as a BC109 or BC549. Transistor TR2 may be either a BC307 or a BC558.

Physically, the preamplifier should be mounted inside a metal box connected to the negative supply line to combat hum and penetration of radio and TV signals. The microphone input lead should be a shielded type, as also the connection to the main amplifier.

### **Fuzz Box**


For the guitar enthusiast, this simple device will have a lot of appeal. Using two BC108s (or BC238s) and a few resistors and capactiors, it can be built for a modest cost. It is designed to be interposed between the guitar and the main amplifier, thus confining the "fuzz" effect to the guitar signals only. A foot switch allows selection of "fuzz" or "normal" as required; the level remains much the same in both modes, the degree of "fuzz" is variable, and the unit provides a small amount of gain.

The unit can provide a wide range of wave shapes, from


The unit can provide a wide range of wave shapes, from simple half wave clipping to complex peaks. As well as the unit's own control, the guitar's volume control can be used

to vary certain aspects of the waveform.

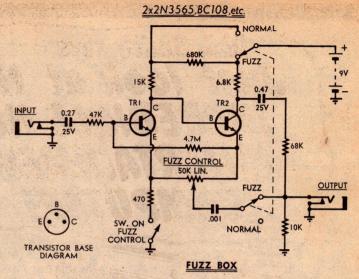The unit is battery powered, thus making it completely self-contained. The prototype was built into a small metal box with a sloping front on which the foot switch was mounted, the whole unit being designed to sit on the floor near the player's foot. Most of the circuit can be built on a short length of tag board, or strung between it and the input and output sockets, controls, etc.



## Two Stage Amplifier & RF Probe

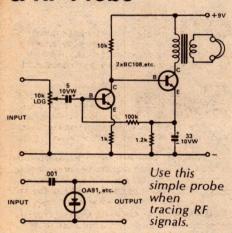


This simple two-stage audio amplifier with volume control has several applications. It can be used as a general purpose amplifier to amplify the output of such things as crystal sets; it can be used for tracing signals in audio circuits; and, when coupled to a suitable probe, can be used for tracing modulated RF signals.

The circuit employs just two NPN transistors, and can be built on a small piece of Veroboard. Layout is non-critical. The output transformer is a type commonly employed as a speaker transformer in valve equipment, and should have a primary impedance of 5000-7000 ohms and a secondary of 8-16 ohms.

When the amplifier is to be used for signal tracing an isolating capacitor of about 0.1uF, 400V, should be connected in series with the active input terminal (top of the 10k pot).

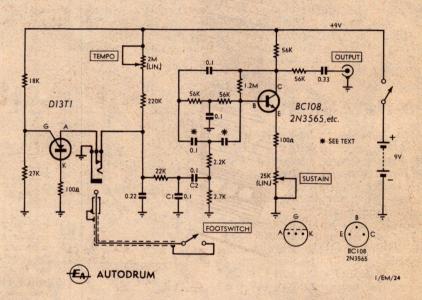In order to trace modulated RF signals it is necessary to precede the amplifier with a detector or RF probe. Such a device is simplicity itself, and consists of only two components, as shown above.



### **Autodrum**

This simple unit generates a drumlike damped oscillation which sounds most impressive when fed into a higher power amplifier. It uses only two solid state devices, one of which is a BC108 (or BC238) and the other a programmable unijunction transistor (D13T1).

The beat rate may be determined in

two ways; directly by the musician operating a foot pedal in much the same manner as for a real drum, or by means of the tempo control.

The whole unit can be accommodated in a small plastic box and powered from an internal battery. The tone of the drum can be varied over a wide range, from a bass drum to a kettle drum, or even imitate a set of tomtoms.

			-		-		-	-	-		-	-			W. 36	No.	500		
•		E	_	124 CO				7		AND NA		the same of	220	200	100		2223		
				<b>FRE</b>	~	-		4 1							1000				•
				STREET	-	88	_	4 I		TO SECURE					12.00				
				15 (20)	-						10000				12 500	753		_	

Enclosed is my cheque/postal order for \$.....

Please forward ...... pkt(s) of 20 transistors at \$2.50 per pkt + 50c pack and post per transistor order.

NAME

**ADDRESS** 

..... POSTCODE.....

Complete and forward this coupon, together with your remittance, in an envelope marked "TRANSISTOR OFFER" to Dick Smith Electronics, PO Box 747, Crows Nest, NSW 2065.

\*Coupon not required in states where this requirement is illegal.

Dick Smith says: Just look at this INCREDIBLE HOME ENTERTAINMENT COMPUTER!



BE ONE OF THE FIRST TO ENJOY THIS AMAZING COLOUR COMPUTER - CONNECTS TO ANY TV SET.

Your children can actually learn or improve mathematics:

addition, subtraction, multiplication and division right there on the TV screen. It even tells you when you're wrong or right!

You can play incredibly complex games like BLACKJACK!

Imagine: it actually draws your cards, raises the bet, 'pays' you for a win . . . you won't believe it!

Over twenty thousand sold in the USA since its release a short time

ago - now available in limited quantity here in Australia. Don't miss out!

Imagine! For only \$259 you get a real computer - the heart of this unit is an incredibly powerful Fairchild microcomputer containing thousands of transistors. No, this is not just another TV game this incredible machine has a mind of its own, giving versatility and performance not even thought possible just a few months ago!

Basic price includes the computer console with two inbuilt games (tennis and football), the two 8-way hand control units, an AC power supply plus a BONUS 'noughts & crosses' game cartridge.

SPECIAL 7 DAY TRIAL OFFER Purchase this Fairchild Video Home Entertainment Computer with two or more cartridges and try it in your own home for 7 days. If you're not completely satisfied, return it to us in the condition you received it and we'll refund your money in full!

A pleasure. To approved personal shoppers, terms are available from \$29.00 deposit and \$2.90 p.w.

#### MAIL ORDERS:

Yes. We'll send this unit anywhere in Australia for \$5.00 extra - game cartridges post FREE with unit. (If purchased separately p&p \$2.00)

ADD MORE EXCITEMENT! ALL OF THESE **FULL COLOUR** CARTRIDGES **ARE NOW** AVAILABLE!

Cat X-1200

ONLY \$2450

EACH.

BLACKJACK Cat X-1201
You can play the TV (the bank) by yourself or with a partner.
Try to break the bank at your home without losing a cent!

Easy terms available!

DESERT FOX Cat X-1203
Try and destroy the desert fox without being blown up yourself (tank game) — or try the shooting gallery game on this cartridge

NAZE Cat X-1204
Four great games: Maze, Jailbreak, Blind-man's-bluff and Trail-blazer. Games that will test your skill and give you feal fun.

BASEBALL Cat X-1205
All the skills and thrills of the real game — played in the comfort of your own home. For two players.

SPITFIRE Cat X-1206
Two games: Solo the red baron is hot on your tail, or for two players you try to shoot each other out of the sky.

SPACE WAR Cat X-1207 Can you escape the piercing laser beams? The aliens from outer

spaec are out to get you. Just how good are you? MATH QUIZ 1 Cat X-1208

Teach the kids addition and subtraction — or brush up on your own basic arithmetic skills.

MATH QUIZ 2 Cat X-1209

Multiplication and division on this cartridge. It poses the problems – it's up to you to come up with the answers

PINBALL CHALLENGE Cat X-1217

ove different coloured walls of bricks to become the pinball

BACKGAMMON Cat X-1213

All the rules of this exciting game are programmed on the cartridge No cheating! Also has Acey Ducey (a variation of Backgammon)

TORPEDO ALLEY Cat X-1211
Sink as many ships as possible. Or play Robot War — try and escape the robots by destroying them in a force field.

SONAR SEARCH Cat X-1214
Use your ears to try to sink the enemy's hidden fleet. Hours of fun for everyone.

DODGE IT Cat X-1216
Dodge a varying number of hidden balls to win this game. Tests your endurance!

Number come and go. But can you remember where they were? A modern version of Kim's game.

MAGIC NUMBERS Cat X-1210
Guess the right digits in the right places to win. You can play the clock or play for points.

DRAG RACE Cat X-1212

Don't eat dust: stomp on your accelerator and beat your opponent in an exciting drag race.

DICK SMITH ELECTRONICS



147 Hume Hwy, CHULLORA. Ph. 642-8922 162 Pacific Hwy, GORE HILL. Ph. 439-5311

30 Grose Street, PARRAMATTA. Ph. 683-1133

MELBOURNE 399 Lonsdale Street, MELBOURNE. Ph. 67-9834 656 Bridge Road, RICHMOND. Ph. 42 1614 BRISBANE 166 Logan Road, BURANDA. Ph. 391-6233

ADEL AIDE 203 Wright Street, ADELAIDE. Ph. 212-1962

SHOPS OPEN 9AM to 5 30PM (Saturday 9AM 12 noon) BRISBANE 1/2 Hour earlier

ANY TERMS OFFERED ARE TO APPROVED APPLICANTS ONLY

GRACE BROS

MAIL ORDERS P.O. Box 747, Crows Nest, N.S.W. 2065. Post and packing extra.

Dealers across Australia.

# Intersil ICL 7106 **DVM** evaluation kit

Using a new Intersil evaluation kit, you can now build a single chip 31/2 digit liquid crystal display digital panel meter. In this article, we review the kit, and give details of how to use it to construct a simple 10 megohm input impedance voltmeter.

by DAVID EDWARDS

At the heart of this project is the Intersil 7106 LSI chip. This 40-pin device contains a precision dual slope analog to digital converter, BCD to seven segment decoders, liquid crystal display drivers, a clock generator and a reference voltage. To build a high performance digital meter it is only necessary to add a display and a handful of passive components.

Features of the 7106 chip, which is a single CMOS device, include a guaranteed zero reading for a 0V input, automatic polarity indication, 1pA typical input current, true differential test and reference inputs, and low power dissipation — typically less than 10mW. In fact, operation from a single

9V battery is quite feasible.


The evaluation kit, coded ICL7106EV/KIT, has a recommended retail price of \$39.10, and enables a 0 to 200mV DC meter to be built in less than half an hour. All parts are included apart from a 216 type 9V battery. A single sided, screen printed circuit

board is provided, measuring 89mm x 126mm. All components mount on this, including the battery (a clamp is supplied). A 40-pin socket is provided for the 7106, and Molex connectors for the display.

The display is a liquid crystal type with 31/2 digits 12.5mm high, polarity indication, and decimal points. These latter are not used in the basic kit. The display has 40 connection points, arranged in a wider than normal dual in line arrangement.

..... INTERSIL Single Chip Panel Evaluation Kit ICL 7106 EV/Kit 

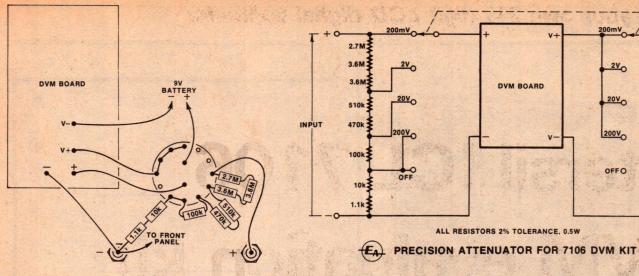This photograph shows an assembled kit, and the components required to construct a second kit. Note the battery clamp.



ABOVE: This diagram shows how the additional components for the attenuator are mounted on the switch.

BELOW: This photograph shows the completed DVM. The batteris mounted underneath the printed circuit board.

ABOVE: The circuit diagram of the attenuator, and of the power supply switching, is shown above.

7/M/-

A 10-turn trimpot is provided to trim the reference voltage, and is adjusted to give a full scale reading of 200mV. To change the full scale reading to 2V, several passive components are required to be altered. Details of the changes required are given in the

literature accompanying the kit. Construction of the kit is quite simple, and should present no problem. Care is required when fitting the display, as there is no pin 1 indication. If you view the display in reflected light, you will be able to see the individual segments. The half digit (+1) goes on the left hand side, when the PCB is viewed from the component side with the terminals at the bottom.

To test the completed board, connect up a battery (watch the polarity), and check that the display becomes ac

### PARTS LIST

- 1 Intersil ICL7106EV/KIT DVM evaluation kit
- Zippy box, 159 x 96 x 53mm
- 1 2-pole 6 position rotary switch
- 2 20-pin SIL wire wrap sockets

RESISTORS (1/2W, 2%)

23.6M, 12.7M, 1510k, 1470k, 1100k,

1 10k, 1 1.1k

MISCELLANEOUS

1 knob

1 216 type 9V battery

Solder, hookup wire, machine screws and nuts, spacers

NOTE: Resistor wattage ratings and capacitor voltage ratings are those used for our prototype. Com-ponents with higher ratings may generally be used provided they are physically compatible.

tive. With the inputs shorted, the reading should zero, with the minus sign coming on about half the time.

In order to produce a more useful instrument, we built the kit into a small plastic and aluminium box, and fitted a precision attenuator to extend the measuring range up to 200V full scale. In order to do this it was necessary to raise the display up from the PCB, so as to provide clearance for the switch.

We did this by using single in-line wire wrapping sockets, which have tails approximately 15mm long. This gives sufficient clearance for the switch, provided that the switch lugs are bent over as much as possible. The PCB is mounted on spacers so that the top of the display is just below the front panel of the box.

The terminals provided with the kit are transferred from the PCB to the front panel. Connect the front panel to the negative terminal using a piece of tinned copper wire fastened underneath the switch bush.

We used photosensitive aluminium to make a front panel for the unit. The artwork we used to reproduced elsewhere in this article. It would also be possible to letter the panel using pressure sensitive lettering, protected with a coat of clear lacquer.

Drill a clearance hole in the side of



The completed DVM is shown above, while the artwork for the front panel is reproduced actual size at the right. This can be useddirectly if required. An alternative to this panel would be to use pressure sensitive lettering.

31/2 DIGIT LCD DVM 20 V 200V OFF. 200mV 0 0

0

the case so that the calibration trimpot can be easily adjusted. It may also be necessary to remove the internal ribs from the box (use a sharp chisel), to allow clearance for the PCB.

The resistors we used for the attenuator are all 2% tolerance types, and are available from Radio Despatch Service, of 869 George Street, Sydney NSW. This firm also has stocks of the basic DVM kit and the wire wrap sockets.

Mount the resistors around the switch, keeping them close to the front panel, so that there will be adequate clearance for the PCB. Complete the connections to the PCB using light gauge hookup wire. It may be necessary to extend one of the leads from the battery clip. Remember to insulate the joint, to prevent short circuits.

To calibrate the complete DVM, you attractive in can use a new mercury cell, of the type cial DVMs.

used in cameras and hearing aids. When these are new and fresh, they have an open circuit terminal voltage of 1.355V. Adjust the trimpot till this reading is obtained on the 2V scale.

No provision for decimal point

0

No provision for decimal point switching has been provided, as this would require an extra pole, and hence a larger switch. In addition, an extra IC is required if the display is not to be damaged. (See the literature accompanying the basic kit for more details on this point.)


We have not provided extra functions for the unit, as this adds considerably to the complexity and the cost, and makes the complete unit unattractive in comparison with commercial DVMs.

## BASIC ELECTRONICS

Basic Electronics begins with the electron, introduces and explains components and circuit concepts, and progresses through radio, audio techniques, servicing, test instruments, etc.

\$3.50 plus 60c p & p Electronics Australia, Box 163, Beaconsfield, NSW 2014.

### Hurry! limited stock accessories

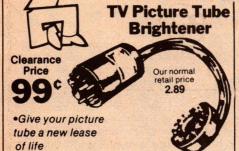

Black and white set/duodecal base. Parallel or series. Standard 12-pin tube renews brilliance, contrast, sharpness and detail. Just plug in!

**Battery Clips** 



Heavy duty, tight fitting, with screw terminals. 4.76cm long. Jaws open to 1.27cm.

**Subminiature Offset Lamp Assemblies** 

Clearance Price



Set of 3 includes 2 red, 1 green jewel-type. Requires T-13/4 threaded bulbs. Mount in 5/16" holes.

### **Miniature Electrolytic Capacitors**



Manufactured with welds at all critical terminations. 500 uF 16 WVDC axial type. Pack of 2. 272-1007

### **Miniature Dual Jack** Coupler



Allows two cables terminating with miniature phone plugs to connected together. Shielded type.

### Flexible "Y" **Adaptor**



Two phone jacks connected in parallel to a standard 1/4" 53/4" long. 'plug. 274-306

### **Dual Stereo Head**phone "Y" Adaptor



One end has two 1/4" phone jacks, connected in parallel to 1/4" phone plug. 10" long. 274-319

### **Adaptor Set**



For 1/4" phone plug to phono 3/32" subminiature jack, phone jack and 1/8" miniature phone jack.

### Stereo-to-Mono headphone Adaptor



Stereo jack to 3/32" ultra-mini phone plug.

### **Phone Jack**

Clearance



Accepts standard 1/4" phone plugs. Versatile, panel or printed circuit mounting. 3conductor. Closed circuit type.

### Component/Console


Clearance Price

retail price 1.49



Gold-colour aluminium-alloy with black base, concave top, faceted grip. 2.69cm dia. 1.9cm deep. Double set screw. 274-422

### **4-Pole DT Miniature** Slide Switch

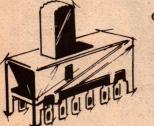

Clearance Price

Our Normal

Contacts 0.3 amps at 12VAC. Size 3.17x

### **Mini Audio Amplifier**



350mW output, 5 transistors

Dual inputs: 5,000/10,000 ohms. For 8-12 ohm load. 10.16x5.08x1.9cm. 15,000 Hz.

### **Mini Test Clips**



Miniature test clip on both ends for rapid interconnection of test points.

278-1158 Black. 5.08cm long ..... 

MINIMUM MAIL ORDER ACCEPTED 2.50 — AVAILABLE FROM ANY TANDY STORE OR PARTICIPATING DEALER

# 9kHz Whistle Filter

Since AM broadcast stations in Australia are now spaced at 9kHz intervals, the problem of heterodyne whistles is more severe than before. The whistle filter featured here was originally designed to suit the new Playmaster Digital AM/FM Tuner, but will suit virtually any tuner with a 9kHz whistle problem.

### by LEO SIMPSON

Previously, with the 10kHz AM station spacing, whistles were not a problem unless the listener had a tuner of reasonable bandwidth, loudspeakers of fair quality and ears of equally fair acuity. Now, however, with 9kHz AM station spacing, tuners of only modest bandwidth can present even less sensitive ears with a whistle problem.

sitive ears with a whistle problem.

Whistles will normally be more noticeable at night, when reception conditions are improved. This allows distant stations to be picked up with sufficient strength to cause interference with local stations. If you listen to the radio only during the daytime, it is unlikely that you will notice any whistle problem.

How does the 9kHz whistle become audible? This is best understood by a brief consideration of the superheterodyne principle which is used in most radios. After passing through a tuned input circuit (which may involve a ferrite rod aerial) and perhaps an RF stage, the incoming radio frequency is mixed with the local oscillator of the radio to produce an intermediate frequency of 455kHz.

The 455kHz signal is amplified in one or more IF stages and then passed to a detector, which is usually a diode, to recover the amplitude modulation. A simple RC filter removes most of the rectified 455kHz signal to leave the audio modulation.

When two stations separated by 9kHz are received and fed together to the mixer, any sum and difference products other than those close to 455kHz are removed by the following IF stages. But if the tuner has a bandwidth of say, 10kHz at the —3dB point, the IF stages will pass frequencies between 445kHz and 465kHz.


So if the desired incoming station beats with the local oscillator to produce 455kHz, the interfering station 9kHz away will produce 464kHz (or 446kHz) as the beat product. These two frequencies, 455kHz and 464kHz are each amplified to the same extent in

the IF strip and then rectified in the detector.


Since the detector is a non-linear device, the two frequencies are not only rectified but they are mixed to produce sum and difference frequencies. The sum frequency is removed by the RF filter following the detector, but the difference frequency is 9kHz! Thus it is amplified and fed to the loudspeaker in the normal way.


This problem is solved by inserting a notch filter in series with the output of the detector. The idea is to remove as little of the wanted audio signal as possible, but introduce very high attenuation at the undesired frequency, namely 9kHz.

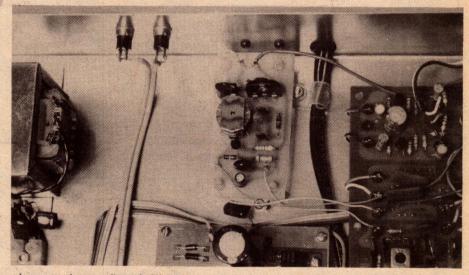The whistle filter described here uses a high-gain, low-noise transistor connected as an emitter-follower driving a bridged-T network. As used here, the bridged-T network is essentially a parallel-tuned circuit. At resonance, the parallel-tuned circuit is a very high



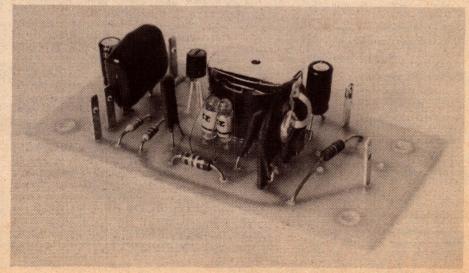Above is shown the whistle filter installed in the recently described Playmaster AM/FM tuner. Below is a 19kHz version of the filter.



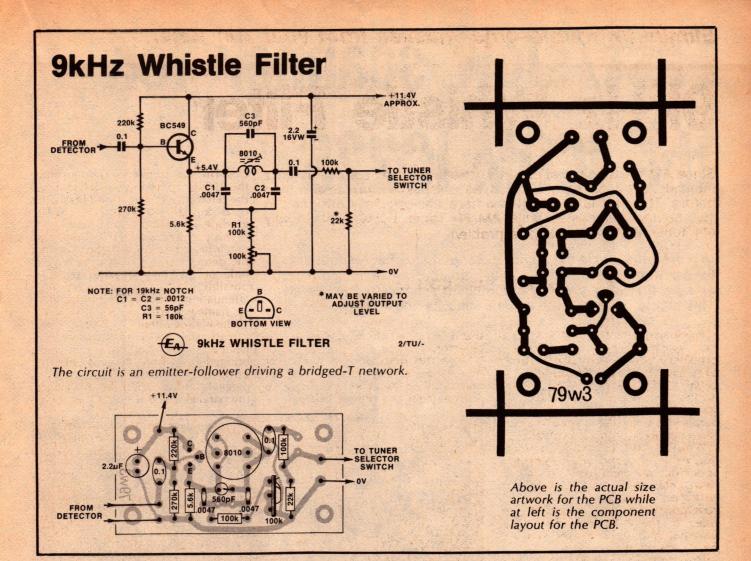

### **PARTS LIST**

- 1 PC board, 79w3, 40 x 78mm
- 1 BC549 low noise NPN transistor
- 1 Jabel 8010 whistle filter coil
- 1 2.2uF/16VW PC electrolytic
- 2 0.1uF metallised polyester (greencap)
- 2 .0047uF metallised polyester
- (greencap)
  1 560pF polystyrene capacitor
- Resistors (¼W, 10% tolerance):
- 1 x 270k, 1 x 220k, 2 x 100k, 1 x 22k, 1 x 5.6k, 1 x 100k preset potentiometer
- 5 PC pins or stakes

impedance. The adjustable resistor centre-tapped into the capacitive arm of the circuit produces a small phase correction to compensate for the losses in the inductive arm.

The inductor is adjusted to give resonance at precisely 9kHz and the adjustable resistor optimises the null.

As noted above, the whistle filter may be installed in any AM tuner and can be run from positive supplies up to 30 volts DC with no modifications, apart from changing the voltage rating on the

2.2uF electrolytic capacitor.

The circuit is accommodated on a PC board measuring 40 x 78mm, and coded 79w3. Assembly is a straightforward matter requiring little comment.

The whistle filter coil has a nominal inductance of 107 millihenries and is wound on a Neosid ferrite potcore. Made by Transcap Pty Ltd, it is distributed by Watkin Wynne Pty Ltd, 32 Falcon Street, Crows Nest, NSW 2065 under the "Jabel" brand, type 8010. As it has a current retail price of more than \$8, we are delighted to report that only one is required!

When the PCB is complete and installed in the tuner, the inductor is adjusted for maximum null by rotating the top section. This has the effect of varying the air gap between the core sections, and thus adjusts the inductance. Since the null obtainable is very sharp, the adjustment is quite critical. Nevertheless, it is possible to obtain a null of more than 50dB using your ears.

Accurately tune to a station which has a 9kHz whistle (at night), boost the treble and volume controls on the amplifier if necessary and adjust the inductor and 100k preset pot for the best

The alternative method, using instruments, is actually more difficult. A low distortion oscillator which can be set accurately to 9kHz within ±10Hz is required. If the null is to be better than 50dB down, the oscillator distortion must be less than 0.3%. This is because, when the null is measured, with an oscilloscope or millivoltmeter, the reading is actually the harmonic distortion of the oscillator and buffer stage.

If you have access to an accurate, very low distortion oscillator it is possible to adjust the circuit for 9kHz rejection of 75dB or more.

The circuit may also be used as a 19kHz filter for FM tuners. Two PCBs will be required in this case, one for each channel. The three capacitors and fixed resistor in the bridged-T network need to be changed as follows: C1 = C2 = .0012uF; C3 = 56pF and R1 = 180k.

Order your copy now of the
"ELECTRONICS AUSTRALIA"
PROJECTS & CIRCUITS NO. 2
\$3.00 plus 60c p & p
Electronics Australia,
Box 163. Beaconsfield, NSW 2014

# Fast/slow scanner for the ICOM IC22S

In a previous article the author described a digital readout display for use with the ICOM-22S as either an attachment in its own right. or as a first step towards a combined scanner/readout system. This article describes the scanner and its construction.

by MARK HOPKINS\* VK2BME

Hopefully by now the readout system will be operational, and you will be ready to build the scanner. Dividing the project into two steps, in this way, should simplify the approach for most

When the scanner was envisaged a number of performance requirements were set:

(1) Ability to scan in 25kHz steps.

(2) Cover the full 2MHz from 146MHz to 148MHz, the range over which the IC22S is guaranteed to operate.

(3) Ability to traverse the band very quickly so as not to miss short CQ calls.

(4) Stop upon encountering a signal, but scan on after a few seconds.

(5) Provision to prolong or override the stop mode in (4) above.

(6) Ability to stop and operate the transceiver on any of the 80 25kHz channels in the 2MHz it covers.

(7) Protection against transmitting while in the scan mode.

(8) Means to avoid stopping on the two spurious responses, 147.075MHz and 147.200MHz, which are inherent in the IC22S.

(9) Still allow normal operation of the set, using the 22 channel selector switch.

(10) Use cheap, readily available components, and consume a minimum of additional power.

(11) Require no alterations to the standard operation and performance of the set.

The final version of the scanner has achieved most of these aims, with few compromises, as a result of much experiment and some hard thinking. It scans in 25kHz steps and, in the fast mode, covers the entire 2MHZ from 146MHz to 148MHz in less than two seconds.

(In order to achieve this fast scan, the mute circuit had to be duplicated but



with less delay than the mute in the receiver. This in no way affects the receiver operation, nor does it require any modifications to the radio; simply the addition of one wire to pick up the mute audio signal.)

The scanner will stop when it encounters a signal capable of opening the mute. Once the device has stopped on a channel it remains there for five seconds. (This can be adjusted by varying R2 and C2) Then it begins to scan once again. This was found to be a good compromise. The operator can hear call signs and repeater "Ident" and have time to move the control switch into the "hold" mode if he so desires before it begins to scan again.

The system will immediately begin to scan again as soon as the signal disappears, ie, if the device stops on a signal and that signal is removed two seconds later the device begins to scan immediately. It will not wait the full five seconds before moving off, as this would be a pointless waste of scan-

A slow scan facility has been provided and this enables one to step the device to any desired frequency. This completely obviates any need for a programmer type device. The slow scan dwells for 0.5 second on each channel. This time was found to be adequate to enable stopping if and when desired on any channel.

Special circuitry prevents the scanner from stopping on the two spurious frequencies, so that signals on these channels will not be recognized either. This was found to be far preferable to turning the mute hard on to prevent the scanner from stopping on these frequencies every time around, which also prevents it stopping on weak signals. Normal operation on these frequencies is not inhibited, ie, they can still be manually selected and used.

Unless the control switch is in the "hold" mode the transmit circuit in the 225 is inhibited, preventing any transmission while scanning. This switch is overridden under normal transceiver operation, ie., when the scanner is switched off.

CMOS ICs have been used throughout and all are readily available. 'garden variety", devices. As with the digital readout, any of the ICs for this project are "off-the-shelf" devices at Radio Despatch Service.

The only modifications to the IC22S

<sup>\*17</sup> Meadow Rd. New Lambton, NSW 2305

are the addition of 21 wires soldered to various points as detailed in the photos. The scanner was mounted inside the unit, as this saves connections from the outside world, and it fits easily into the available space. The only external leads are to the "fast-slow-hold" switch which is mounted on the digital-readout box.


The operation of the scanner is best described by reference to the block diagram in Fig. 8. The interested reader may also refer to the circuit diagram

Fig. 9 for greater detail.

Audio from the transceiver is tapped off before the volume control and fed to point A. Transistor Q1 amplifies this signal which is then rectified by the OA95 Diode. Q2 and Q3 provide a DC amplifier so that when the mute opens Q3 is turned hard-on. Two gates of a 74C14 shape the signal which is fed to the B input of a 4528 monostable multivibrator. This signal is now in a form suitable to control the scanner.

What is needed to scan the band is a system of connecting all the diode combinations in sequence to the matrix board. This is achieved by connecting one end of a set of diodes to the matrix and the other end of the diodes to the outputs of a 7-stage binary counter (4024). When the outputs Q1 to Q7 go high the diodes are effectively in circuit and when low the diodes are out of circuit. Hence all frequencies can be achieved by incrementing the counter.

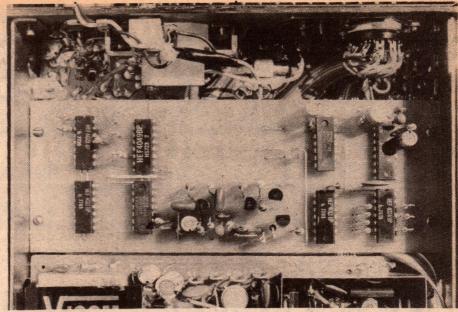
A 74C14 gate forms the clock oscillator, along with C1 and R1, which increments the 4024 counter. As the clock



Close-up of the scanner board showing its component layout and its position in the set. The set's 9-pin socket is at top right and the speaker socket, with modified wiring, at top left. The set's synthesizer board is at the bottom.

pulses are generated the frequency is incremented in 25kHz steps until 148MHz is reached, whereupon the reset circuitry returns the system to 146MHz where it starts counting again.

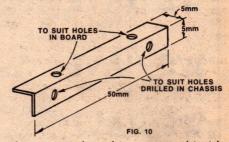The clock pulses from the 74C14 are controlled or gated on their way to the 4024 counter so that, by stopping the pulses, the counter is stopped on a particular frequency. Four gating circuits are provided to inhibit these pulses.



The scanner board is supported inside the set on two small aluminium brackets made to the dimensions shown.

One gate is controlled manually, by the "hold" switch, so that the device can be stopped at will. A further gate inhibits clock pulses to produce the slow scan mode. Another gate is controlled by the mute signal which inhibits pulses when the mute opens, ie, when a signal is encountered the device stops on that channel. There is also a special spurious response gate which inhibits the counter from stopping on the spurious signals in the IC22S (147.075MHz and 147.200MHz).

The "hold" switch also controls a transmit inhibit circuit. This prevents transmission while in the fast or slow scan modes, as a safety precaution.

When it is desired to use the radio in a conventional manner, ie, use the ordinary 22 selectable channels, it is simply a matter of turning the channel knob to the required channel. The scanner is turned off and completely overridden on any channel except the one to which it is connected. In my case I connected the scanner to the 23rd position on the diode matrix. This corresponds to one of the two dots on the two blank positions, but the constructor can put it on any channel he desires.

The scanner is built on a single-sided board 54mm x 143mm. All components

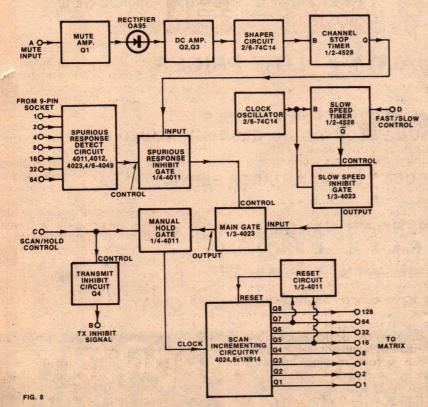


Fig. 8. This block diagram should give the reader a good idea of the various sections of the scanner, and their function. The specific form of each section is shown in greater detail in the circuit diagram on the next page.

# FOR THE PAST 20 YEARS WE HAVE CATERED FOR TOMORROW'S ELECTRONICS ENGINEERS.

E.D. & E. (SALES) PTY LTD

Now trading as

### KALL ELECTRONIC COMPONENTS K

COME TO THE PEOPLE WHO SPECIALISE IN KIT SETS

TS

# YOU NAME IT WE'VE PROBABLY GOT IT!

WE HAVE . . . ONE OF THE BIGGEST RANGES OF KITS, PARTS & P.C.B.'S IN AUSTRALIA.

WE HAVE . . . OVER 300 DIFFERENT TYPES OF I.C.'S

WE HAVE . . . OVER 250 DIFFERENT TYPES OF TRANSISTORS ONLY "RECOGNISED BRANDS" STOCKED.

### TOP QUALITY — LOW PRICES

SPECIAL SERVICE FOR SCHOOLS —
EVERYTHING THE YOUNG ELECTRONIC STUDENT WOULD NEED

INQUIRE ABOUT OUR MAIL ORDER SERVICE.

WE STOCK A COMPREHENSIVE RANGE OF TOP QUALITY P.C.B.'S FOR E.A. & E.T.I. PROJECTS.

(For full list refer to E.A. November 1978)

FOR FULL LIST OF KIT SETS REFER TO E.A. JANUARY 1979

### ALL ELECTRONIC COMPONENTS

TELEPHONE 662-3506 THE FAMILY BUSINESS
118 LONSDALE STREET, MELBOURNE 3000

TELEPHONE 662-3506

### **ICOM 22S SCANNER**

except the switch are mounted on the board. Construction should be quite straightforward if the component overlay is followed. Observe capacitor polarities and IC orientation. (The 4049 is reversed with respect to the other seven ICs.)

The four transistors should preferably be plastic types, as metal cans may touch. There are 20 links and these should be put on first. NOTE: One link running between the 4049 and the 4012, needs to be insulated as it crosses two others running under those chips.

There are 21 connections to be made to this board. A group of eight run from the diodes associated with the 4024 to their respective locations on Ch 23 of the diode matrix board. Connect them to the points where the diode cathodes would normally go and leave the anode holes vacant. Rainbow cable makes this job easy. While dealing with the matrix a lead from switch position 23 needs to be run back to the +9V on the scanner board. This then supplies power to the scanner only in that switch position.

Seven leads need to be run from the 9-pin socket on the back (where the leads go out to the digital readout) to the seven 150k resistors associated with the 4023 and 4012 (spurious response detect circuit) on the scanner board. The lead from 64 (ie, from pin 7 of IC1) which was left floating and unused by the digital readout, is connected to the corresponding lead from the scanner. The other six leads solder onto pins 1 to

6 of the socket.


Three leads need to be connected to main IC22S board. One is from the ground connection of the scanner board to the same point on the main board. The second is from point "A" on the scanner board to the junction of Q14 collector, L12, and C61 on the IC22S main board. The third is from point "B" on the scanner board to the junction of Q33 collector, Q32 base, R143, and D22. The terminations of leads "A" and "B" on the main board are marked on the photograph.

Leads from points C and D on the scanner go to pins 8 and 9 on the 9-pin socket. (These pins should have been unused until now.) The 9-pin plug is wired correspondingly, its leads going to the switch inside the readout. The common of the switch is wired to chassis inside the readout. The schematic in Fig. 11 should make this


wiring clear.

The scanner board is mounted behind the synthesizer board in the transceiver, with a 2mm gap between


Fig. 9. The general concept of the scanner, shown in Fig. 8, is shown in greater detail in this circuit. The main connections to the set are shown.

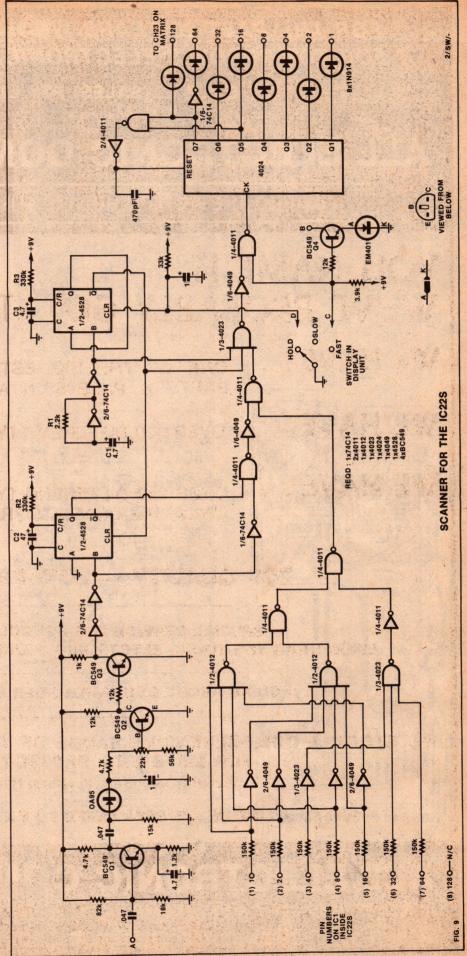

### **ICOM 22S SCANNER**

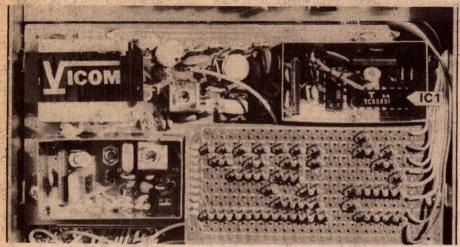

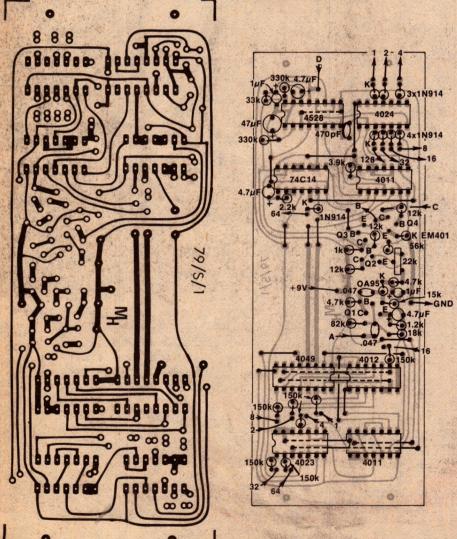This picture shows the front section of the set, including the synthesizer board, the matrix board, and the lower edge of the scanner board at the top of the picture. The ICOM IC1, TC5080P, is indicated in the shielded enclosure at top right.



The diagram on the left is of the printed board, actual size, as seen from the copper side. On the right is shown the component positions, from the component side, superimposed on the copper pattern. Note IC orientation carefully.

### PARTS LIST

### **SEMICONDUCTORS**

- 4011 Quad 2 input gates.
- 4023 Triple 3 input gate.
- 4012 Dual 4 input gate. 4049 Hex buffer inverter.
- 74C14 (40106) Hex Schmitt Trigger.
- 4528 Dual monostable.
- 1 4024 7 stage ripple counter.
- 4 BC109, BC549, etc. (Plastic preferable)
- 1N914 or diodes supplied with IC22s matrix.
- 1 OA95 Germanium diode or similar.
- 1 EM401 Silicon rectifier or similar.

### CAPACITORS

- 1 470 pf Ceramic disk
- 2 0.047uF Polyester or plastic film.
- 3 4.7uF 10VW Electrolytic single ended.
- 1 47uF 10VW Electrolytic single ended.
- 2 1uF 35VW Tag tantalum.

### RESISTORS

(All resistors miniature 1/4 Watt unless otherwise specified.)

		k
1	1	.2k

			STATE OF THE PARTY
1 1.2k		1 x	18k
1 2.2k		1 x	33k
1 3.9k		1 x	56k
2 4.7k		1 x	82k
3 12k		7 X	150k
1 15k	<b>国际企业的基础</b>	) v	330k

1 22k Skeleton preset pot (miniature)

### MISCELLANEOUS

- 1 Single pole, 3 position switch.
- 2 L-shaped mounting brackets. (See text.)
- Scanner printed board. (79/S/1)
- 4 Self tapping screws for bracket.
- 4 Self tapping screws for PC board. Rainbow cable and hook-up wire. Solder,

them, and at the same level as the synthesizer board. It should not be mounted any lower, as it will be too close to the main board, and it should not be any higher as it may foul the speaker. In any case, it would be wise to put some insulating tape on the dome of the speaker, in case it touches the links on the board. (If you intend to mount it any lower a shield similar to the one used on the synthesizer board is recommended.)

Two angle brackets support the scanner board at either side of the case. They were fashioned from 22 gauge steel and Fig. 10 shows their construction. Self-tapping screws hold the bracket and the PC board. The photos give a good idea of what has to be done.

Having completed construction check all wiring carefully. If it is correct the scanner should be ready to turn on. The preset pot needs to be adjusted to make the scanner of equivalent sensitivity to the transceiver mute.

# MODEL 100A LOGIC ANALYZER Features: DLOW COST: USE WITH VIRTUALLY ANY SCOPE OR XY DISPLAY □ 128-BIT TRUTH TABLE (8 BITS WIDE BY 16 WORDS DEEP) "POSITIVE TIME" AND "NEGATIVE TIME" DISPLAY MODES ☐ STATIC OR DYNAMIC DISPLAY OF TRUTH TABLES HEXADECIMAL AND OCTAL DISPLAY FORMATS ☐ FULL COMPATIBILITY WITH POPULAR LOGIC FAMILIES LOGIC ANALYZER PARATRONICS, INC.

The Model 100A Logic Analyzer converts an ordinary oscilloscope into one of the most useful digital testing, analysis, and development tools available. It is ideal for applications requiring an in-depth exploration of hardware and software performance. Use it to trace computer program flow, examine the contents of ROMs and other memories, check counter and register operations, and monitor I/O sequences. An input data rate in excess of 8 Megabytes/second assures compatibility with most microprocessors and general purpose digital systems.

The Model 100A provides data domain analysis features not possible using an oscilloscope alone. It will capture data before or after a trigger word, and display the associated truth tables statically or dynamically in your choice of hexadecimal or octal formats.

The low cost of the Model 100A permits engineering companies, educational institutions, and hobbyists to take advantage of data domain analysis to support a variety of advanced development, training, and trouble-shooting applications.

The Model 100A is easy to operate and will interface directly with most common logic families including TTL, Schottky, CMOS, MOS, and DTL. Connection to the system-under-test is accomplished using a color-coded flat ribbon cable terminated in gold-plated "universal" pin connectors.

A 100-page owner's manual provides extensive information on theory of operation as well as educational, production testing, field service, and general digital applications. The analysis procedures for seven popular microprocessors are also included.

### KENELEC (AUST.) PTY. LTD.,

142 HIGHBURY ROAD, BURWOOD, VICTORIA 3125. (03) 288 7100 N.S.W. (02) 439 3954, S.A. (08) 223 2420. QLD (07) 358 3549, W.A. (09) 444 5826.

### **ICOM 22S SCANNER**

If it is too sensitive the scanner will stop on signals which do not open the mute. If it is not sensitive enough it may not stop on weak signals.

To set this pot correctly proceed as follows. Connect the digital readout and turn the rig on. Remove the aerial lead and turn the present pot fully anticlockwise (ie. mute fully open). Now


set the scanner switch to fast scan. The readout should now increment quickly


and unimpeded.

Advance the panel mute control until it is almost closed, ie, just barely "chattering". Ignore the "crash" that occurs when the device resets from 148 to 146MHz. Advance the preset pot on the scanner board slowly, while watching the digital readout. Keep advancing it until the display begins to falter and momentarily stop on random channels. This is the most sensitive setting, but suffers from the disadvantage that it produces a crashing sound each time the PLL goes out of lock on resetting.

For normal operation the mute control can be advanced somewhat from this threshold position. With a small advance the crashing sound will disappear and the device will scan silently. At this setting a signal which barely moves the S meter will stop the scanner. Even with the mute hard-on, an S1 signal will still stop the scanner. The individual can ex-

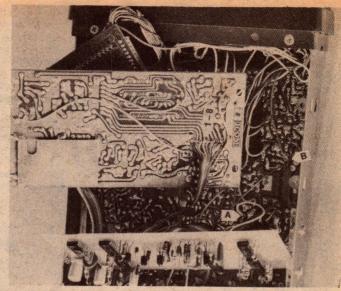Shown here is the underside of the synthesizer board showing the eight leads from the IC1 (IC5080P). The leads "A" and "B" from the scanner board are also indicated. The scanner board shown is an earlier version.



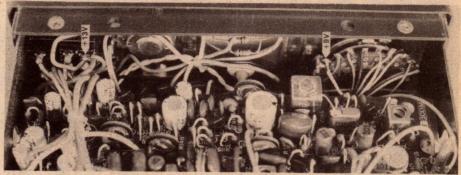

Looking towards the front of the unit, the channel selector switch is on the right, with position 23 marked (+9V) The power switch is on the left with the extra lead from it also marked (+13V).

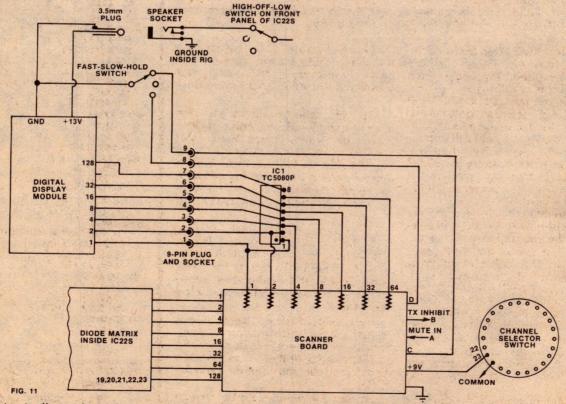


Fig. 11. Getting it all together! This interconnection diagram should help the constructor to follow the connections between the various units and sections. Cross check it against the photographs and main circuit diagram.

### **ICOM 22S SCANNER**

periment with the control, for personal preference, but it must be emphasised that if it is not accurately set, the device will not perform as well as it should.

The fact that the scanner has but a single control switch on the front panel may suggest limited facilities. But this is not the case. This single pole, 3-position toggle switch performs the equivalent function of two double throw switches and a pushbutton switch.


Consider such a system with a "scanhold" switch, a "fast-slow" switch, and

conditions for him to become completely familiar with its operation. While the written explanation may sound complex, it is really quite easy to

use in practice.

Perhaps this is a good time to mention a few limitations of the system. Firstly repeater operation needs a little practice because, unlike more conventional rigs, the IC22S moves either the transmit or receive up 600kHz, not the transmit up or down 600kHz. Hence, to work a repeater when the scanner is being used the offset must be on before it stops on the repeater output frequency.

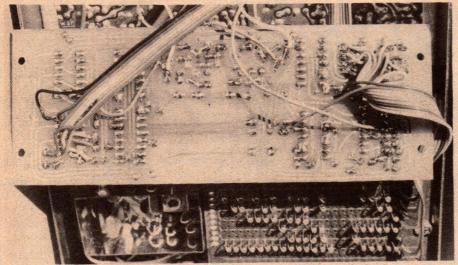Also, the mute characteristics change with temperature. This results in a



The scanner board turned over from its normal mounting position. On the right can be seen the rainbow cable running to the matrix board. Portion of the scanner board brackets are just visible at the top of the picture.

device to scan on before the five seconds has expired). The single switch achieves all this as follows -

In the upper position it will "fastscan", stopping for five seconds on encountering a signal. In the middle posi-tion it will "slow-scan" and will stop for 0.5 seconds on every channel, regardless of whether there is a signal on it or not. In the lower position the switch will cause the scanner to "hold"

or stop on a channel.

If the system is fast-scanning and the operator wishes to override a five second stop he should move the switch from "fast" to "slow" and back again fairly quickly. This will reset the timer and the device will immediately "scanon". If, alternatively he wishes to stop the device indefinitely on that channel he should move the switch from "fast" through "slow" to "hold". NOTE: With either of the above operations if the switch is left in the slow position for more than 0.5 seconds the scanner will begin to increment channels at the slow rate.

No amount of explanation can give the user a "hands-on" feel for the switch operation, but it requires only a few minutes practical use under typical

an "override" pushbutton (to force the tracking problem between the transceiver mute and the scanner mute gains. In practice this is not a real problem if the mute is not set too fine-

> The only other hassle is the one already mentioned; the noise created when the system jumps back from 148MHz to 146MHz, causing the PLL to momentarily go out of lock. This is more annoying than anything else and, as already explained, may be overcome by setting the mute a little harder on than usual.

> (Editorial note: As this article went to press the author had indicated that he was working on a modification to the system, aimed at eliminating this noise burst. Should the modification prove successful, we will probably cover it in a later issue.)

> Even considering these minor limitations, the system performs exceptionally well considering its simplicity. So that's about all there is to putting a digital readout and scanner on your

> One last comment might be in order here. If we all just scan the band and don't call, then nobody will know that anyone else is listening!

# **SEMICONDUCTORS** DISPOSAL **PRICES**

limite	d au	antiti	es o	nlv
HILLICE	u uu	anteres	60 0	

Tuesdatava						10.00	
Transistors							\$0.18
BC 107					••	**	\$0.18
BC 108		••	**	**		*	
BC 109			••	••	**	••	\$0.18
BC 177					**	*	\$0.20
BC 178	••						\$0.20
BC 179							\$0.20
BC 547							\$0.14
BC 548	7						\$0.14
BC 549							\$0.14
BC 557							\$0.15
BC 558							\$0.15
	300			**			\$0.15
BC 559		**	••	**			
BD 139	2.00		••	••			\$0.40
BD 140	1						\$0.40
BFY 50	-	300					\$0.26
BU 126	10						\$2.65
BU 208A						2.	\$2.65
MJ 2955							\$1.20
PN 3568							\$0.10
				**			\$0.25
TIP 31A	**	19.00		••	••		\$0.26
TIP 32A				2.4	••	•••	
TIP 2955		-					\$0.72
TIP 3055		-				2	\$0.68
2N 3055		.0	-				\$0.45
2N 3642						•	\$0.14
2N 3772			1			**	\$2.35
2N 3773	••						\$3 40
2N 3819		••					\$0.25
			300		**		\$0.12
2N 4250			**	1			Φ0.12
Diodes/Bride	ges	_					40.74
BYX 2IL	.20	0				••	\$0.74
BYX 21L	20	OR				-	\$0.74
OA 91				100			\$0.07
IN 914		13.					\$0.05
IN 400A							\$0.08
IN 5060		¥	-				\$0.10
VK 1048				127			\$2.20
SCRS/Triacs							\$0.68
C 106D		••		••	••		
SC 141D							\$0.77
V 413 D		С					\$0.13
Linear I.C.S	- 25						
LM 555	CN	b					\$0.35
LM 723							\$0.56
LM 741							¢0 22
114 700							¢1 00
UA 706 UA 790	6 0	11/1	14	320	T.G	4	01 EE
UA /90	0 C	U/L	_101	320	1-0		W1.00
Opto Device	es				-		40 00
TIL 306	Di	spla	ay v	vith	100		\$8.00
RED LE	D	5	mm				\$0.14
YELLO	WI	EE	) 5	mn	1 .		\$0.28
GREEN	LE	ED	5	mn	1 .	•	\$0.18
Mos I.C.S.							
MM 170	12 1	40	THE REAL PROPERTY.	1			. \$4.50
MM 210				E CONTRACTOR			Ø1 25
IVIIVI ZIC		40	UIIS	10	CD		41 00
NANA FOR	7	D					
MM 501	17 -	Du	ial 5	12	311		
I.C. Socket	17 - s	Du					¢0.21
I.C. Socket 8 PIN .	17 - s						. \$0.21
I.C. Socket 8 PIN . 14 PIN	17 - s						\$0.21 \$0.23
I.C. Socket 8 PIN .	17 - <b>s</b>						\$0.21 \$0.23

QUANTITY DISCOUNTS AVAILABLE All Prices Plus Tax If Applicable

ELECTRONIC and SEMICONDUCTOR DISPOSALS Post Office Box 72, Parkville, Vic. 3052

### BRASS SHIPS CLOCKS SMITHS 8 DAY 7 INCH DIAMETER \$110

Post A \$1.75; B \$3.00; C \$3.60.

GENUINE EX ARMY WRIST WATCHES

Complete with nylon band \$19.50 Post \$1.10

### P.M.G. TYPE TELEPHONES

Standard desk type with magneto bell calling device. Range 30 miles. Uses standard batteries at each phone. Any number can be connected together on single line. \$39.50

(2 TELEPHONE SETS)

\$2 Cartage to Rail. Freight payable at nearest attended Railway Station

### RECEIVER No. 210

2-16 M/cs \$65

Transmitter No. 11 suits 210 \$35. 24 volt Power supply to suit above \$15. Or complete station with Headphones, Mic. Morse Key, Antenna \$110.

#### EX ABC MAGNETIC RECORDING TAPES 1/4"

PROFESSIONAL QUALITY	
5" x 600"	\$1.50
7" x 1200'	\$2.75
P + P \$1.30	
1016" × 2400' \$7.95	

P + P A.\$1.65 B.\$2.75 C.\$3.10

### COLLINS INDEPENDENT SIDEBAND TRANSCEIVER TRC/75

Fully synthesised transceiver with am. upper, lower and independent sideband operation, 1KHz steps from 2MHz to 29.999MHz 1 microvolt sensitivity, 2.5KHz bandwidth ssb, 6KHz bandwidth AM 1 RW. PEP max output. Fully automatic tuning of both transmitter and receiver from remote control unit. Complete with automatic aerial coupling unit, mic, headset, etc, 400Hz supply Ideal for amateur use.

PRICE \$750

#### COLLINS SYNTHESISED 1 SB RECEIVER

TRC/75 receiver section of transceiver specification as above. PRICE \$400

#### **TELEPHONE WIRE**

mile twin (2 miles) genuine ex-Army Don, 8 perfection condition \$35 per drum, \$2.00 cartage to rail freight payable at destination.

### RCA 44BX MICROPHONES

PROFESSIONAL QUALITY \$75 P&P A. \$1.80, B. \$3.50, C. \$4.55 D. \$4.55

### 20X to 60X **ZOOM TELESCOPE**

With Tripod, \$115.50. Post A\$2.25, B\$4.10, C\$6.10.

AERIAL CAMERAS
WITH 8" FL 3" DIAM. LENS F24 MARK
IV 2.9 LENS STOPS 11. 8, 5,6,4,2.9 - \$65
\$2 CARTAGE TO RAIL FREIGHT
PAYABLE TO NEAREST ATTENDED
RAILWAY STATION

PENTAC LENSES
3" DIAM. 8" FL WITH DIAPHRAGM
STOPS 11, 8, 5.6, 4, 2.9. MOUNTED IN METAL HOUSING — \$65 POST: A. \$1.85, B. \$3.25, C. \$4.10

### PRISMS

4" SQUARE FACED RIGHT ANGLE PRISMS TOP QUALITY EX AIR FORCE - \$65; OR LENS & PRISM FOR \$120. POST: A. \$1.75, B. \$3.00, C. \$3.60

#### SOLENOIDS

200 MA 24 volt, ½in push movement, \$2.50 P+P 80c

#### NIFE CELLS

1.2 volt, fully charged, 4in x 3in x 1in 4

\$1.50 each P&P 80c

**CENTRE DRILLS 15"/64 x 5/64** Carbon Steel, \$3 dozen Post 60c

### ARTILLERY DIAL SIGHTS MK2

Can also be adapted as a Dumpy Level or as base for a telescope has full 360? 51/2" diam. gunmetal rotating circle. Adjustable elevation and depression. Has top grade ¾" diam. object lens. F.L. 10" with cross hairs, eyepiece, ½" right angle prism — height 10" — weight 3½kgs. With leather carrying case. Original cost

Our Special only \$27.50 P&P A.\$2.25 B.\$4.00 C.\$6.00

### POSTAGE KEY:

A: NSW B: Vic, Qld, SA C: NT, Tas. D. WA

#### VALVES

BRAND	NEW		
6SN7	\$1.95	6BN8	\$1.95
5U4	. \$1.95	6GV8	\$1.95
EF50	\$1.50	6AK5	\$1.95
5Y3	. \$2.95	1H6	\$1.50
2x2	\$1.50	832	\$5.00
	P+F	80c	
6x4			. \$1.95
VR65			

### ROLA 66 MK 2 TAPE RECORDERS

Good condition \$275.00



#### SPY TELESCOPES

8 x 17 mag size of a rifle cartridge extends to 8". Only \$7.95 each, post 60c.

#### BINOCULARS

PRISMATIC Coated Lenses. Brand new Complete with case

8	x	30	\$36.50	20 x	60 \$102.00
7	x	50	\$48.95	P&P	
10	X	50	51.00	A	\$1.75
12	X	50	53.00	В	\$3.00
20		50	\$56.00	0	6210

### SMALL CLIP-ON POCKET TELESCOPE

15X \$6.50, P+P 80c

### 3" ASTRONOMICAL REFLECTOR TELESCOPE

117X magnification FL 700mm with 5x24mm finder scope and two section hardwood tripod. \$169.25.
Post A\$2.25, B\$4.10, C\$6.10.

#### 3000 TYPE RELAYS

P.M.G. 200 ohms — 1,500 ohm Coils **\$2.50** each P+P 80c

### AIRCRAFT INSTRUMENTS

**Directional Gyros** AN5735-1 Air Operated \$35 Sperry Artificial Horizon. AN5736-1 Air Operated.

\$45. Slip and Turn Indicators \$17.50.

P&P A. \$1.65, B. \$2.75, C. \$3.10

### SIEMENS **Typing Perforator**

240 Volt Type with Keyboard \$57.50

P.M.G. TYPE KEY SWITCHES. 75c P+P 80c

### CONDENSER LENS

1%" diam 4%" F1 75c 2%" diam 2" \$1.50 each or \$2.50 per pair. P&P 80c

### **IMPELLER PUMPS**

New gunmetal body, Stainless Steel Shaft, Neoprene Impeller. Up to 15ft. Lift, suitable for almost any type of liquid Self priming. Ideal boat bilge pump, sullage drains, etc. Approx. size 8" x 5" %" \$30.35, ½" \$43.30, ¾" \$47.60 P+P: A. \$1.95, B. \$3.50, C. \$4.60

Liquid filled compass



With magnified lens sight and degree

Only \$7.95 each. Post \$1.30

### POLARITY & CURRENT CHECKER

3 volt to 400 volt. Simple leads and prods quickly determines positive or negative with illuminated indicators, also checks AC current and intensity, fully insulated only \$4.95, pp \$1.30.

#### MAGNESIUM DRY CELL BATTERIES

Suits PRC 25 and dozens of other uses 15 volts long life only \$1.50 ea. P+P: A. \$1.35, B. \$2.75, C. \$3.60

### WRIST WATCHES SWISS JAEGER

Le Coultre ex RAAF rated one of the world's best in smart chrome case with black dial. Original cost \$250.

> SPECIAL \$49.50 Post \$1.30

#### THEODOLITES

Made by Wilds Microptic, with tripod Model T1, reads down to one minute of ARC \$750. (Usual Price \$1750).

Model T2 reads down to one second of ARC \$1000 (Usual Price \$3200). Freight payable at nearest attended R'way Stn.

### 200Z FOCUSING MICROSCOPES

200m focusing microscopes, 750X battery and mirror illuminated \$31.75. 200m 1200X similar to above \$47.95 P&P A \$1.65, B \$2.75, C \$3.10.

### TRANSCEIVERS Ex Army

No. C45 set. 23 to 38MHz with headphones, mic. 24V power supply, etc. \$95.00

\$2.00 cartage to rail, freight payable at nearest railway station.



### EX-ARMY TWO-WAY FM RADIOS

1.2 WATTS OUTPUT SUPERHET
PRC9 AND 9A 27 to 39M/HZ
PRC10 AND 10A 38 to 55M/HZ WITH HANDSET ANTENNA \$25 EA. UNTESTED

Battery \$3.95 extra. Harnes \$4.50 extra \$2 Cartage to Rail. Freight payable nearest attended Railway Station.

#### 16MM SOUND PROJECTORS IN GOOD WORKING ORDER

240 volts operated complete with Speaker and Amplifier.

RCA \$275
BELL & HOWELL \$195.
\$1 Cartage to Rail. Freight payable at nearest attended Railway Station.

### SELSYN MOTORS MAGSLIP RECEIVERS 2" MK2 \$5.50 TRANSMITTER 3" MK2

\$15.00 Post Packing A. \$1.75, B. \$2.75, C. \$2.75, D. \$3.65. P+P: A. \$1.75, B. \$3.00, C. \$3.10

### COMMUNICATIONS RECEIVER

COLLINS R — 391/URR Continuous tuning of range 500 Kills -32MHz in 32 bands. Receive frequency indicated directly on digital counter type readout to within 300Hz. Selectivity adjustable in six steps. From 100Hz to 16KHz bandwidth. Sensitivity 1 microvolt or better 240 VAC operation — 10 inch rack mount — autotone on eight preset channels available complete with instructions and service manual and tested

### Deitch Bros.

PRICE \$500.

70 OXFORD STREET, SYDNEY 2010

SORRY NOCOD

# Circuit & Design Ideas

Conducted by Ian Pogson

Interesting circuit ideas and design notes selected from technical literature, reader contributions and staff jottings. As they have not necessarily been tested in our laboratory, responsibility cannot be accepted. Your contributions are welcome, and will be paid for if used.

### Modification lets PIPBUG work at 300baud

The following are details of a hardware modification to the PIPBUG monitor program for the Signetics 2650. This modification allows the program to run at either 110 baud or 300 baud. Programs can be entered at 100 baud and run at 300 baud, and vice versa.

Standard TTL was used in a 2650 Mini Computer as described in May 1978, to which address and data buffering had been added. It should be possible to use LS TTL in an unbuffered version. The conventional approach in changing the delays is to reduce the number of loops and to change the number loaded into RO. However, I decided to attempt to modify the instructions. The modifications are as follows:


300baud modification ADDR B1 B2 02A8 20 F8 02A9 7F A4 7E (A4 — SUBI) 02AB F8 7E (88 - ADDR) F8 7E 02AD 02AF 04 E5 02B1 F8 7E

Note that "88" may be used instead of "A4".

02B3

17

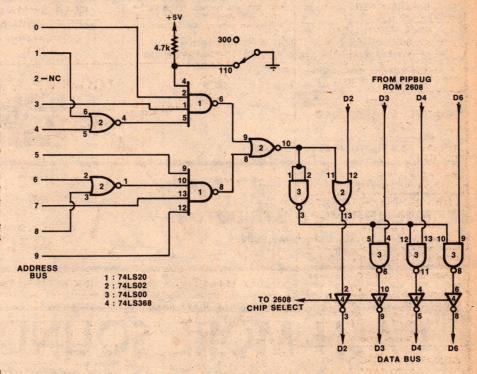I leave the reader to work out the fine details but the principle is as follows: The "A4" at 02A9 destroys one loop and loads RO with 00 — 7E, ie, 82. The "A4" at 02AD destroys the loop and makes a redundant instructions, as the next instruction (04E5) overrides it. If "88" is used instead of "A4", RO is loaded with "88".



As you can see, only two instruction bytes have to be changed, and both need to become the same code. As these cannot be changed inside the PIPBUG ROM itself, the logic circuit shown is used to detect when either of the two addresses concerned is called by the processor. When this occurs it simply disables the relevant ROM data outputs, and presents the substitute


code instead.

The design as shown uses four simple LS TTL gates. No board design is given. Pin connections are those used in my particular design. It should be noted that the data output lines from the 2608 ROM must be cut and that AD2 is not decoded.

(By Mr R. W. Brown, VK7ZRO, 215 Carella Street, Howrah, Tasmania 7018.)
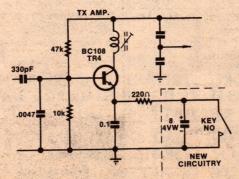
### Simple change allows CW operation on 3.5MHz Transverter

Here is a modification for amateurs who have built the 27/3.5MHz Transverter as described in April, 1976. It enables the operator to send CW (Morse code) with few changes in the transverter. The modifications are as shown in the diagram. Further modification may be either, (a) set the transceiver to AM mode and use an elastic band or similar to hold the microphone button down, (b) use PA/transceiver switch to lock transmitter on, (c) use DPDT switch on transverter to switch transceiver as well. The method to be adopted may vary according to the peculiarities of each



individual arrangement.

According to the power output of

the transceiver, it just may be necessary to change the two 100 ohm terminating resistors to cope with a higher rating. It should also be noted that for normal phone use, the CW key must be locked down.

To receive CW, switch the transceiver to LSB and adjust clarifier for a suitable beat note. I find no need for a sidetone oscillator, although one could be added if required. I have had many enjoyable CW QSOs with the above modifications.

(By Mr K. Madden, VK4AKM, 19 Allawah Street, Albahy Creek, Qld 4035.)

### Good DJs won't tolerate drop-outs

That's why they insist on the British Goldring G 820 DJ Cartridge specially designed for disco and professional use.



Its reinforced stylus, with a naked point encapsulated in a steel sleeve, just won't drop out when you least want it to.

Its built in durability will withstand endless punishment, backtracking and cueing without you getting frayed round the edges.

But for all that, the British Goldring 820 DJ cartridge tracks with a featherlight touch to give you the authentic British Goldring sound. Real sound, faithful sound.

The British Goldring 820 DJ — it's like music to the ears.



FOR FURTHER DETAILS RING:

AUSTRALIAN DISTRIBUTORS FOR GOLDRING PRODUCTS LTD. U.K.

### SOUNDRING DISTRIBUTORS


1/514 Miller St., Cammeray 2062. Tel. (02) 92 1990

#### AGENTS:

VIC.: Jasper Coote Pty Ltd, 304 Coventry St., Sth Melbourne, 3205. Tel. (03) 699 4455.

QLD: Green Brothges Pty Ltd, 83 West St., Rockhamptom. Tel. 27 3047 467 Flinders St., Townsville, Tel. 72 1544.

## CASH-MORE SOUND SYDNEY

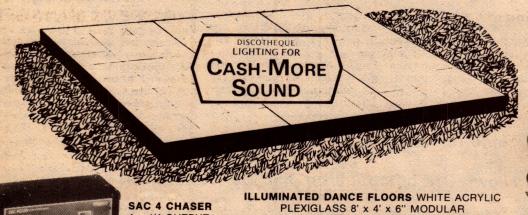



4 x 1K OUTPUT WILL RUN 8-8' x 4' x 6" MODULES

ALL SIZES MANUFACTURED TO REQUIREMENTS



SL6 SPACE BEACON With 6 revolving lights 24" dia 18" high 4018S

CASH-MORE SOUND IMPORTERS, RETAILERS, HIRERS, MANUFACTURERS OF QUALITY SOUND. DISCOTHEQUE + EFFECTS LIGHTING. MIRROR BALLS, STROBES, PROJECTORS. SOUND TO LIGHT CHASERS — AMPLIFIERS — SPEAKERS MICS, ETC.

149-151 GEORGES RIVER ROAD, CROYDON PARK, NSW 2133. TEL: SYD 798 6782, 298 5647

> OPEN SUNDAYS BY APPOINTMMENT, BROCHURES - PRICE LIST BY REQUEST

#### Crystal oscillator suits 2650 Minicomputer

This is a simple crystal oscillator, suitable for use with microprocessor systems requiring a 1MHz clock frequency. It can be used to replace the RC oscillator of the 2650 Minicomputer, and uses only a single CMOS IC. Either a 74C00 or a 74C02 can be pressed into service.

All of the gates are used as inverters, three as the oscillator proper, and one as a buffer. An RC delay circuit is included in the oscillator loop, to prevent oscillations at the third harmonic of the crystal. The 1M resistor biases the loop into the linear region.

There are no special requirements

1MHz 74C00,74C02 13 011 4.7k 100pF

for the crystal. Output drive capability is two low power TTL loads. Refer to the 74C series data sheets for more information on this point

(by David Edwards, Electronics Australia staff).

#### Non-destructive backspace, space and line feed for VDU

Simple modifications to the VDU described in February and March 1978 add the facility to specifically alter any character on any line of the display while in the typewriter mode. Only 512 of an available 1024 display locations are used in the original design.

are used in the original design.

The "extra page" can be displayed by cutting the track, on the upper side of the board, betweeen pins 10 and 14 of IC43, soldering a 330 ohm resistor across the cut and shorting pin 14 of IC 43 to earth with a toggle switch. When text is entered on this second page, only the position of the cursor is altered on page 1. Thus one can select page 2, position the cursor in the equivalent position of page 1 which requires alteration, select page 1 and perform the alteration. In particular, 15 line feeds when in this mode, are equivalent to a reverse line feed. A further line feed restores the display to its original (apparent wrap around of the 16 lines occurs).

These operations are combined to provide a single-key facility by using the low frequency clock output of IC5 to operate a double pole relay via an unused keyboard switch. One set of contacts alternately selects pages 1 and

PIN 1 OF IC3\*
PIN 3 OF MM5740AAF\*

\*NORMALLY LINKED

SELECT O1

SELECT O1

IN914

RELAY

PAGE
SELECT O1

IC43

MM21L02

CUT 330A

10

2, while the other set disables the keyboard encoder whenever page 1 is selected. If the contents of page 2 are cleared, depressing the switch causes the display to flash and the cursor can be moved normally to the location required without altering page 1.

Layout is not critical. The relay may

Layout is not critical. The relay may be attached to the case in any convenient position and the transistor and diode may be soldered directly to it. (By Mr D. W. Johnson, 2/13a Aberfeldy Avenue, Edwardstown, SA 5039.)

# MARKETING SERVICES MANAGER

The Dick Smith Group of Companies, which operates very successfully as a Retailer and Wholesaler of electronics equipment and components, is seeking a dedicated executive to be responsible for its inhouse Advertising Department and Marketing facilities. Nine persons are currently employed in this area and the annual budget runs at \$600,000.

A good basic knowledge of Electronics would be a distinct advantage. Practical experience in Advertising and Marketing is a basic requirement.


The company is dynamic and aggressive and an opportunity exists for future personal advancement. As a result, the successful applicant will be a young, well-motivated person capable of contributing effectively to the management team.

This is a senior position reporting directly to the Managing Director and an appropriate salary will be paid to a suitable applicant.

Please submit detailed letters of application in the first instance to:

Alan Walker,
Dick Smith Electronics Pty Ltd.
24 Carlotta St, ARTARMON, NSW 2064.
Enquiries: (02) 439 5311

#### Try this simple diode tester

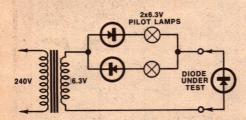

In this very simple diode tester, if one lamp lights the diode is OK. If no lamp lights the diode is open circuited. If both lamps light the diode is short circuited.

(From "Dragnet".)

Editorial note: The idea seems to be a good one. However, care should be taken with small signal diodes to ensure that ratings are not exceeded, with the possible demise of the diode. An improvement which comes to mind is to replace both of the circuit lamps and diodes with two LEDs and suitable current limiting resistors. This should avoid any danger to small diodes under test.

#### THE "ELECTRONICS AUSTRALIA"


#### LOG BOOK

FOR: RADIO AMATEURS DX LISTENERS CB OPERATORS

From "Electronics Australia", 57-59 Regent St, Sydney OR by mail order from PO Box 163, Beaconsfield 2014. Price includes postage.

\$2.95



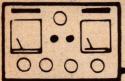

# The Serviceman

### When the data sheets are wrong — try mathematics

I have two stories this month, both from fellow servicemen. I make no apology for this, since both are more interesting than the rather routine jobs which have come my way lately. One emphasises the tricky nature of direct coupled circuits, and the other describes a problem caused by incorrect manufacturer's data.

These items come from various sources; readers' letters, brief snippets from colleagues, and even comments in overseas magazines. So long as they touch on the servicing scene, I feel that

they are worth passing on.

My first story comes from a reader—and fellow serviceman—who confesses to having read these notes regularly for the past 22 years! Such dedication is surely deserving of some reward; even if it is only the satisfaction of seeing one's own story in print. (This doesn't mean that any other reader who has been around this long will automatically qualify to have his story published!)

Anyway, to get on with the story. The contributor is Mr P. T., of Altona, Victoria, and he writes as follows:

I would like to tell you about a most unusual intermittent fault I encountered recently. It concerned a 12in portable monochrome TV set, HMV model 1184, which arrived with the complaint, "... the picture collapses to one inch high after a few hours".

Well, that sounded easy enough. Probably some component packing up when it became hot. But it wasn't as simple as that. After pulling the chassis

out of the case I switched it on and let it run. Sure enough, after about 20 minutes the picture suddenly collapsed to about one inch high, as stated.

Referring to the circuit revealed that the vertical section used five transistors in all, and all direct coupled. There were two transistors in a Miller integrator/oscillator combination, a third as a driver, and two more in a complementary-symmetry type output stage driving the deflection coils.

DC measurements compared with the circuit showed that all was not well with any of the transistors, though some were further from the mark than others. Suspecting a faulty transistor, I changed each one in turn, only to draw a blank. But I learned one thing from the exercise; the periodicity of the fault could be anything from five minutes to four days!

Next I tried freezing each component in the vertical section when the fault occurred, but again drew a blank. The fault remained even with the whole of the vertical section covered in frost from the instant freeze spray.

Another unusual aspect of the fault was that it would just correct itself and then run merrily for hours without


recurring. Nothing could persuade the fault to re-appear until it was ready. I tried cooking the board, flexing it, thumping it — you name it, I did it, but all to no avail.

Subsequent testing eliminated the yoke, the diodes, and the thermistor. I then tried a trick I have used with much success with direct coupled audio amplifiers under similar conditions. I use a 10k pot which I connect between the positive supply rail and chassis, with the moving arm going to an "Ezi-hook" via a 1k resistor. This can be clipped to the base of any transistor.

Making sure that the moving arm was at the earthy end of the pot I connected the hook to the base of the driver stage, TR503. Then, by advancing the arm of the pot it was possible to restore all the DC voltages around the output pair, suggesting that the fault was back towards the oscillator/integrator section, TR501/502. I repeated the procedure from the collector of TR501, with the same results.

Earlier DC voltage checks had indicated that the oscillator self-bias on TR501 was falling under fault conditions, but the cause was not clear; was it lack of feedback from the output stage caused by the change in DC potentials on all stages? Or was it the TR501 stage itself going faulty and not sending enough amplitude towards the output stage?

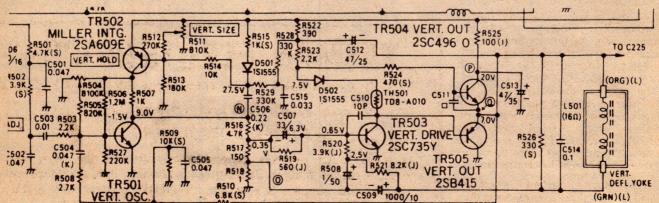The test with the pot suggested the latter, so I began checking every com-



Relevant portion of the HMV 1184 circuit, showing the vertical oscillator and output stage. As well as being intermittent, the fault was made more difficult by reason of the direct coupling used throughout.

ponent around TR501/502, while the fault was in evidence. Nothing showed up until I measured the value of resistor R503. Supposedly a 2.2k, it read 3M—Ah, at last!

I removed the resistor from the board and measured it again. I read 2.2k! What was going on? I replaced it on the board and measured it again, getting a reading of 7M. Then it suddenly hit me; I had been making these measurements with the set running, which seemed permissible because the resistor was isolated, in the DC sense, by its associated capacitor, C503. But now I was convinced that DC was flowing through the resistor and this upsetting the ohmmeter readings.

I removed the resistor again and then measured from C503 to chassis on the 1mA range. Sure enough, I found a current of 0.1mA, a sure indication that C503 was faulty. I replaced it, then checked it more closely. It was a.01uF greencap and I hooked it across the ohms range of a digital multimeter. It read infinity initially and no amount of heating or freezing would vary this reading, so I just left it connected.

After about half an hour it started — the meter went beserk. First 10M, then 7M, then 1M, then back to 10M. This went on for about half an hour, then it came good. It is the most unusual fault I have ever encountered, especially as the capacitor was not sensitive to temperature variations.

Well, I suppose you can't win 'em all — not straight away, anyhow.

Well, that's Mr P. T.'s story and I can only agree that it is a most unusual fault, considering the component involved and its behaviour. Also, I like the idea of the 10k pot for dealing with direct coupled circuits; it's a tip worth remembering.


Next comes a story from a New Zealand serviceman, Mr R. C., of Paraparaumu. (I'm glad I don't have to pronounce that!) He asks:

What should you do when a manufacturer gives incorrect data? Perhaps what I did and revert to that ancient stuff called math-ahem-matics.

It all began with a call to repair a Hammond Piper electronic organ. The symptom was no percussion. Inspection of the circuit showed that a direct-coupled amplifier applied amplification only to the percussion section. I checked the voltages and found them way out. Two replaced transistors later and all was well, with the percussion section percussing boldly. So was I two nights later, when I received a call saying the percussion had failed once more — only this time it was intermittent.

On my return I checked the voltages around the amplifier and decided that, since they were still wildly out, I would take the organ back to the shop to "soak" for a day or so.

Initially, it appeared to function only

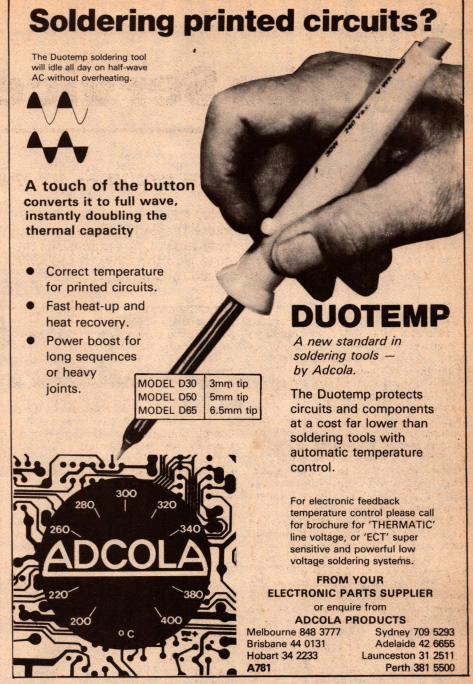

# TASMAN ELECTRONICS

12 Victoria Street, Coburg 3058. Phone (03) 354 5062

FOR TOP QUALITY COMPONENTS
AT ROCK BOTTOM PRICES

Transistors & ICs, resistors, capacitors, transformers, switches, wire and cable, diodes, bridges, SCRs, triacs, audio and TV leads, plugs and sockets, power supplies & adaptors, stylii, DMMs, calculators, instrument cases and boxes, knobs, heat sinks, fuses, cassettes, batteries, TV antennas, musical instruments and accessories, etc.

We are also dealers for "AIWA" quality hi-fi products.

164-166 REDFERN ST., REDFERN P.O BOX 156 REDFERN. N.S.W. 2016. TEL. 699 5922 OR 699 6912

#### TRADING HOURS

MON-TUES-WED & FRI: 9am-5.30pm. THUR: 9am-7pm. SAT: 9am-12 noon. COD's Please add \$2.40 to posting fee. NO ORDERS UNDER \$5.00 ACCEPTED (exclusive of P&P) For replies please send SAE. Post and packing 50c where not included in price PLEASE . . . PLEASE PRINT YOUR NAME AND ADDRESS ON ALL ORDERS AND CORRESPONDENCE. BANKCARD ACCEPTED.

#### DON'T LET THIS HAPPEN TO YOU!!

**Buy from** US!



#### SAVE NOW ON OUR BARGAIN PAC OFFERS

CAT. NO: CP.16
ELECTROLYTIC CAPACITOR. Can type with mounting clip. Made by Ducon. 100mfd 160V. 5 for \$1 P&P \$1

CAT. NO: CP.20.

POLYESTER CAPACITOR. Philips tubular foil type 315. 0.01mfd 160V. Axial leads. 20 for 75c P&P 50c CAT. NO: CP. 23.

FERRITE BEADS. 6 holes. Size 10mm x

7mm dia. Ready wired. Anywhere else 45c each. From us only 10 for \$1 P&P 30c. CAT. NO: CP.24 FERRITE BEADS. 2 holes. Size 5mm x 6mm

dia. Ready wired. Another great buy. 10 for 90c P&P 30c.

CAT. NO: CP.28.
MINIATURE TRIMMING CAPACITORS Rotary Vane type. In 12-75pf & 9-60pf. Only 10mm x 15mm deep. 5 of each for only \$2.25 P&P 40c.

\$2.25 P&P 40c. **CAT. NO: CP.29.**MINIATURE TRIMPOTS. Made by PIHER. PCB & Horizontal mounting. 2 of each of  $50 \Omega_{\star}$ ,  $100 \Omega_{\star}$  &  $100 K \Omega_{\star}$ . 6 for 75c P&P 30c.

CAT. NO: CP. 30.

AIR SPACED VARIABLE CAPACITOR. Made by JACKSON BROS. (U.K). Top quality. Silver plated vanes & ceramic end-plates. 150pf. \$1.50 each or 4 for \$5.00 P&P single 30c or 4 for \$1.

CAT. NO: CP.36.
FERRITE POT-CORE ASSEMBLIES. Non-FERRITE POT-CORE ASSEMBLIES. Nonadjustable. Supplied complete with Formers & Clamps. Ready wound, but no data available. Demensions: 40mm x 40mm x 25mm. 
Type H74-MB. \$1 each. P&P 50c. 
CAT. NO: CP. 37. 
As above (CP. 36) but size is 30mm x 30mm x 16mm. Type A75-MB. 75c each P&P 40c. 
CAT. NO: CP. 40. 
CMOS I.C TYPE 4001. Once in a lifetime offer. ONLY 18c each YES. Only 18c each or 10 for \$1.50 . . . where else but at 'SHERIDANS' can you get this kind of 'Giveaway'? 
P&P 30c.

DANS' can you get this kind of 'Giveaway'? P&P 30c.
CAT. NO: CP. 49.
EDGE CONNECTORS. Top quality brand. 2 types available in 0.15" pitch. For 1/16" board. 18 way \$1, 12 way 75c. In 0.1" pitch 32 way double sided for 1/16" board \$1.50 each. P&P each item 30c.

CAT. NO: CP.58.
MINIATURE 12V MODEL MOTORS. Made
by LENCO. Precision made with inbuilt speed regulation. Length: 70mm x 35mm dia. Spindle length 20mm. Also 0.K. for 6VDC. \$1.75 each or 2 for \$3.25 P&P 40c

CAT. NO: CP. 92 CLARE MERCURY-WETTED RELAYS. Coil resistance: 1.1K ohm x 1.1K ohm. Operating Voltage 48V. Switches 2amp 500V. Change-over contacts. Cost over \$13. Our price only \$1 each or 5 for \$4.50. ALL NEW. P&P 30c ea or 5 for \$1.

# FIRST TIME OFFER of SPRAGUE COMPUTER GRADE 'POWERLYTIC' ELECTROLYTIC CAN CAPACITORS

**Type 360** 

\$15

Type 'A'. 160,000 mfd, 10VDC. 150mm high, 75mm dia. ONLY \$15 ea. P&P \$2.50.

100 000mfd 10VDC. 115mm high, dia. 75mm. ONLY \$10 ea. P&P


\$10


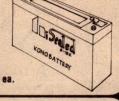
#### HI-SEALED 'GEL' **RECHARGEABLE BATTERY**

Manufactured by the reputable KONO Co. of Japan 6V 1.2 A.H. Superbly made, and suitable for Alarm Systems or Stand-by applications. Enclosed in High Impact moulded case. Size: length 100mm x Height 50mm x Width 25mm. (These cells require







IR STUD MOUNTING **RECTIFIER.** Type 70U60, Rating: 600V, 250 amps. \$15.00 ea. post paid. (worth \$45 ea. LIMITED QUANTITY ONLY).



#### **OUT SHORTLY** . . . a monthly bulletin and mini-catalogue

Bringing you all the up-to-date stocklisting of all our components. Will be automatically forwarded with all mail orders or on receipt of SAE.





20A Electronic Organ .....\$5.60







CAT No CP 11 3 for only \$6 P&P 75c.

CAT No CP 7

P&P 40c, 10-\$1.25

5 for \$4.95

RELAYS Minature PC mounting type by FIRE. 8 amp contacts, single & double pole changeover. Values 750 ohm, 2.1K & 7K. All new, unused.

2SB337 PNP germanium PNP Power trans-

istor in TO-3 case. Similar to OC28. Vcb 40 12W 7 amp.



CAT No. CP 41 20 for \$3 P&P 75c

2N3055 Power Transistors. Unmarked but all guaranteed useable. Below specs. We have sold 1000's with very little returns.



CAT No. CP 56 Only from us at \$6 ea. P&P \$2.50 all states.

C' CORE TRANSFORMER by General Electric. Type MSC225. Pri: 240 & 254 VAC. Sec: 36V & 5.3V at 1 amp. Worth treble.



CAT No. CP 88 Only from us at \$10 ea. P&P \$1.00

SONY 9 BAND SELECT ROTARY SWITCH. 9 position, 12 pole. Used on Sony SW AM Radio mod. CRF 5090. Normally \$27. Fantastic multi-purpose - see to believe.




CAT No. CP 94 Only \$1.50 ea. or 4 for \$5.50.

P&P 40c ea. or 4 for \$1.

PYE PLUG-IN RELAYS, minature 2C/202A. Twin 1K ohm colls. Normally operate on 18 VDC. Connect coils in parallel and operate on 12 VDC. 2 pole change-over, 2 amp contacts. Complete with base.

initial charging) P&P \$1.00.

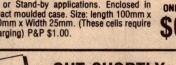









### NEW! NEW! NEW! . . . 1 in 1 EDUCATIONAL KITS FOR KIDS & ADULTS OF ALL AGES. Completely safe, battery operated, no mains connections. 20 kits to give you hours of 20K Morse Code Practise Set ......\$4.90

208 Electronic Flasher ... \$4.50 200 Electronic Touch Switch ... \$4.50 20D Electronic Touch Switch ... \$4.50 20L Electronic Siren.....\$4.50 20M Electronic Water Purity Tester..\$4.50 .....\$4.50 20N Transistor Radio .....\$4.50 200 Electronic Metronome ......\$4.50 20F Electronic Sleeping Bell \$4.50 20G Electronic Magic Touch \$4.50 20H Electronic Rain Alarm \$4.50 20P Ammeter/Voltmeter .....\$4.50 20Q Electronic Timer.....\$4.50 20R Electronic Mosquito Repeller ... \$4.50 20S Electronic Police Car Siren .... \$4.90 201 Photo Electric Switch ......\$4.50

20J Electronic Singing Bird ......\$4.50 20T Electronic Fan & Colour Wheel .\$4.50 Post and packing on all kits 50c.

# THUMBWHEEL SWITCHES



\$2.50 ea. Type TW1. 1 to 0. Size: 53mm x 45mm x 10mm. BCD & Complimentary BCD. P&P



\$2.75 ea.

Type TW2. 1 to 0. Size: 42mm x 27mm x 13mm. P&P 30c.



Type PB3. HARTMAN pushbutton. Forward & reverse. 1 to 0. BCD. Size: 62mm x 40mm x 12mm. P&P 30c.

OUTSTANDING METER BARGAINS: DUAL VU METER. In clear plastic case Left & Right meters read 0-100 plus/minus. Size: 80mm x 40mm. ONLY

\$5.50 ea. P&P 50c. TUNING METER Red & White scale on Black background. Fantastic value at only \$1.50 ea. P&P 40c.



Robustly and superbly manufactured in Canada. Flying leads and supplied with 2 keys, which are removeable from either the on or off position. ONLY FROM US at \$2.25 ea. EASILY WORTH DOUBLE. P&P 50c.

#### DIGITAL CLOCK MECHANISM



All new & unused. Fully imported. Complete with Time-setting control, denoting HOURS, MINUTES & SECONDS. Clearly visible figures of 5/16" Ht. Also incorporated are 2 remote micro-switches for setting Alarms, Radio or T.V. etc. With 240VAC 50 cycle Motor. SPECIAL CLEARANCE at \$10.25 ea.

#### SPEAKER CAT No. CP 111

RE-ENTRANT HORN SPEAKERS.

HOKITONE

Type RH-4. Suitable for Type Intel. State of the Cartesian of th

#### Philips SPEAKER KITS

do-it-yourself . . . all 40 watts World-famous brand known for quality & effi-ciency. The best tone around. All kits rated at 40 watts RMS.

KIT AD8K40	\$139
2-way, 8" system. KIT AD8K30	
3-way, 8" system. KIT AD12K12	
3-way, 12" system.	9243

All kits include cabinets. All kits despatched freight forward by 'Comet'.

#### THE SERVICEMAN

after a warm-up period which accounted for its intermittent operation. When I finally did get to look closely into its malady the first thing I found was an open circuit 15 volt zener in the power supply. This caused 30 volts to be supplied to some of the circuitry, including the percussion amplifier.

With the new zener firmly in place I switched on and struck a chord. The Qflat minor that reverberated off the walls sapped away my self-esteem. Distortion — piles of it — was pouring out of the speaker. This I traced to a corroded spring contact in a multi-way connector on the power amplifier board and it just happened to be in the 15 volt line. With this changed all was now working. Even the burble some black accompaniment keys were emitting was gone. (The owner had said nothing of this fault.) I switched off and left it overnight. That night I dreamed of melodious music accompanied by piano, sitar and harpsichord.

But the next morning I wished I had changed jobs. During the night my percussion had crept away and was probably hiding under a diode or the like. This time I returned to the little pre-amp, as I was now sure that all factors external to it were normal.

The manufacturer's circuit (reproduced herewith) gives various voltage values, and these I tried to duplicate, but to no avail. My first suspicions were aroused when I looked at the AC gain of 100 suggested by the manufacturer. (5mV in - 500mV out.) On the basis of R1 divided by R2 the maximum gain for stage one would be 4.5 and for stage two (R5/R6) about 3; a maximum overall gain of 13.5, not allowing for the feedback via R3.

Equally confusing were the manufacturer's suggested voltages for V1 and V2. If the V2 value (0.4V) was to be believed then Ic was 120uA, but if the V1 value (1.8V) was correct, then Ic was closer to 800uA. Even allowing for a reasonable Q2 base current flowing through R1, it was hard to reconcile the two figures.

The voltages actually measured in the circuit were as follows:

> V1 = 3VV2 = 2.2VV3 = 6.5VV4 = 2.7V

Was Q2 drawing too much current thus forcing the issue? Its collector voltage certainly indicated so. I checked Q2 and found it was up to its original specification, so back to the maths. A quick check proved that all resistors measured correctly. Now I looked more closely at V3 and V4. Two milliamps through 5.5k (4.7k plus 820 ohms) should have produced an 11 volt


drop. It showed 18.5 volts! It was the voltage drop across R5 and R4 that highlighted the problem.

R4 = 8.5VR5 = 10V

From these figures I calculated that 2mA was flowing through R5 but 10 milliamps were flowing through R4. C2 provided the answer to that riddle. It was busily sinking 8mA all by its clever little self. With that replaced V3 rose to 13.6 volts and all voltages then adjusted

> V1 = 3.4VV2 = 2.3VV3 = 13.6VV4 = 2.9V

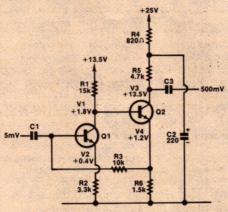Now Q1 was drawing 0.7mA and Q2 two milliamps with the circuit stable and with an AC gain of 10 - about what one would expect. But what about those voltages? Only by changing resistor values (eg R2 to 390 ohms)



Circuit of the percussion amplifier as taken from the manual, showing the voltage and gain figures which were suspect. The input and output signal voltages imply a gain of 100, which was unlikely, while the V1 and V2 voltages (Q1) are incompatible, in that they imply quite different collector currents.

would the voltages reach the values given but, as I am not one to redesign manufacturers' circuits, I decided it was best left functioning the way it was. It has been three months now ...

One last word on the gain. The measured input signal was 75mV and the output 750mV. As well as confirming the calculated gain figure, it suggests that the 5mV shown on the circuit was intended to be 50mV; which would at least explain that anomaly.

Mathematics or intuition, whichever you use it certainly pays to have it honed and ready. You just never know when

Well, that's Mr R. C.'s story and, while I may not be as adept at pushing figures around the slate as he is, I have always believed that ordinary everyday ohms law-type maths can play a vital part in servicing. This is particularly so where the manufacturer's data is not available or, as in this case, suspect.

So keep those calculator batteries in good nick.

#### METAL CHASSIS

#### BOXES

#### CASES

#### **PANELS**

Big range of sizes in painted steel and aluminium

See June Issue Electronics Aust.

## WARDROPE & CARROLL Eng. Pty Ltd

82 OAK ROAD, KIRRAWEE, NSW 2232

Phone 521 5833

PO Box 330, Caringbah, NSW 2229

# LANTHUR ELECTRONICS

69 Buchanan Ave. or PO Box 162 North Balwyn, Vic. 3104. Phone: 859 4061.

CONTROLLER KITS

Controls down to stop without loss of torque. Consists of triac mounted on heat sink, diodes, resistor, pot & knob, 3 pin bass & plug and circuit. Use with hand tools, lathes, potters wheels, etc. Suitable for ac/dc brush type motors only. 10 amp 2400 watt capacity.

Price including post, \$10.95.

LAMP DIMMER KITS

Controls from full to out incandescent lamps up to 2400 watt. Consists of triac mounted on heat sink, diac, pot. & knob, resistors, caps, ferrite rod & wire, circuit. Use for spots, stage, projector etc. 10 amp. 2400 watt capacity. Price including post, \$8.95. Rotary or slider control available. Please say which preferred.
Cabinets to suit above speed controller and lamp

dimmer kits.
Plastic with alum. lid ...... All aluminium \$2.95
NEON INDICATORS — 240 volt, red ... 3 for \$1.00

DPDT 3 for \$1 10 for \$3 post free. SWITCHES — Toggle. DPDT. 2 amp

3 for \$2.70 Sub-min. toggle. SPDT. 2 amp 3 for \$3.50 250 volt

RESISTORS — Half watt. Pack of 50 \$1.00 4mm Red or black . . . . . Five pairs for \$2.00 All above items — POST FREE.

# Classical Recordings



### Cilia — Adrienne Lecouvreur: "a set you shouldn't miss"

CILIA — Adrienne Lecouvreur.
Complete Opera. Renata Scotto
(Adrienne); Placido Domingo
(Miaurizio); Sherrill Milnes
(Michonnet); Elena Obraztsova
(Princess of Bouillon); Giancarlo Luccardi (Prince of Bouillon) and others
with the Philharmonia Orchestra and
the Ambrosian Opera Chorus conducted by James Levine. CBS Stereo
79310. (Three discs with libretto in
English, French, German and Italian.)

My relationship to this opera has been a strange one. As a small boy back in the first decade of this century I found a libretto of it at home in London in an old box-type piano stool. My parents must have attended an early performance of it at Covent Garden though, as far as I can recall, they never mentioned the work in my hearing.

At that time the only opera I had heard was Aida — not a bad start — when my father took me as a birthday treat. I read the libretto of Adrienne and woundered what sort of music it would be set to. I even tried to write some myself and did about six or seven bars. I came across them later. They were awful. Since then, despite its fairly frequent revivals, I had never heard a note of it until this set arrived for review.

I knew that to be cast in its title role was the ambition of the greatest sopranos of their day. Apart from that nothing. It still remains in the repertoire of Italian operas, is fairly often presented in Italy and occasionally at Covent Garden and the Met.

So it was with more than usual curiosity that I put the first side on my turntable. Its story tells in true operatic style of the usual tragic love affair. By the way, Adrienne Lecouvreur actually lived, was one of the greatest actresses of her period, had countless love affairs including a very serious one with, of all people, Voltaire, and the story sticks, as nearly as is possible in opera, to the facts of her life.

I was immediately enchanted by the first act with its backstage bustle and occasional soaring melody rather in the style of Puccini during his Manon Lescaut period. But as much as there was to be praised in the singing my special delight was in the orchestration,

always original and sensitive, the harmonies sometimes unexpectedly subtle. By this I do not intend to disparage Puccini's scoring which also has its own particular merits, but Cilia's was entirely different.

In the first act there is a concerted vocal number that speeds along at a terrific pace not unlike the smugglers' quintet in the second act of Carmen. And there is a theme associated with Adrienne that will hang about in your head for hours after you've heard it. But during the second and third acts my interest started to wane ever so little. This was not because of the lack of drama in the action — there's plenty of that - but because the drama seemed to be confined mostly to the stage and the vocal parts and was not forcibly enough expressed in the exquisite scoring. The wooing tunes continued in plenty but the general format was too much like so many other Italian operas of the period — Cilia outlived Puccini by 26 years — that its novelty started to wear off.

But I must again try to impress that despite my continued mentioning of Puccini, Cilia made no effort to copy that composer who at that time was enjoying huge success with his works. However, I must point out that Puccini's orchestra was never at a loss to express all the drama that was going on on the stage and his sense of the theatre was outstanding. And that is my explanation of why Puccini's operas continue their attraction for present day audiences and Cilia's are starting to fade.

But whatever the reason Cilia's work remains an elegant example of that school. Everything about it is highly civilised, the work of a most ingenious and sometimes inspired composer, but its effect is rather like meeting a close relative several times a year. Mostly it's intensely pleasurable but hardly ever blood-stirringly exciting.

Dominating the cast is Renata Scotto in the title role. Her performance taken vocally alone conveys to perfection her changing mood of love and jealousy and her hopeless despair in the last act when she thinks her love has deserted her, turning to joy when she buries her face in the poisoned bouquet which

her rival has sent her to make her think she has been reconciled with her lover. In her role as an actress she also has to declaim in speech some lines from the Racine play she is appearing in with the same fine effect.

The rival, Elena Obraztsova, gives you as unpleasant a woman character ever provided for a female "villain". The viciousness she projects both in her singing and vocal acting is quite astonishing. Both she and Scotto tend at times to harden a little on top fortissimo notes. The rest of the cast is on the whole excellent with special mention of Placido Domingo and Sherrill Milnes. All work together in perfect harmony (no pun intended) under the baton of James Levine who makes sure the balance between voices and orchestra is such that Cilia's wonderfully transparent scoring is always audible but never intrusive. The Philharmonia (no longer the New Philharmonia?) is in top form, evidenced by their obvious pleasure in their work. If you are a lover of Italian opera this is a set you shouldn't miss.

BEETHOVEN — The Five Piano Concertos. Arthur Rubinstein (piano) and the London Philharmonic Orchestra conducted by Daniel Barenboim. RCA Stereo CRLS-1415. (Five boxed discs with a most comprehensive brochure included.)

Arthur Rubinstein must have been just on 90 years old when he recorded this new set of the Beethoven Concertos with young Barenboim. Issued separately from time to time, they are now offered in a handsome box together with an interesting brochure.

It would not be reasonable to expect an artist to perform with the same freshness and accuracy at such an age as he previously did during a long and distinguished career. (All right, I know Titian did.) But his playing in this new set is still that of a master albeit, not unexpectedly, with some blemishes that he would never have passed in earlier days. These consist for the most part of a slight lack of control of changes of sonorities and absence here and there

of the old time panache.

But he has retained his authority and his almost miraculous stamina. You soon realise that your are hearing some fine piano playing and that the player could be no one else but Rubinstein. I have never known a Chopin player of Rubinstein's genius who shone equally well in the works of Beethoven - or vice versa. These composers demand different temperaments from their executants and this fact must also be borne in mind when assessing the performances.

There are many, many passages when the old Rubinstein skill and freshness shines as it always did, and in the matter of interpretation there is always Barenboim to nudge him along the right path. Indeed I cannot remember when I heard better orchestral parts better

Technically, the piano usually sounds so far in front of the orchestra that, despite Barenboim's superb accompaniments, the piano sometimes momentarily disturbs the balance between soloist and orchestra, though on the whole the sound is fine. In the usual run of recording, blemished passages can be replayed and the correct version spliced in. This calls for an exhausting bar to bar series of repetitions until everyone is satisfied.

At a guess, this would have been just that too much to demand of the old gentleman who is now totally blind but, by all reports, retains his reputation of being one of the wittiest men in the world.

This is a most interesting issue. Barenboim's contribution is superb, and not to be missed because of the minor faults mentioned above.

**DEBUSSY** — Orchestral excerpts from The Martyrdom of St Sebastian. Three Images for Orchestra. London Symphony Orchestra conducted by Pierre Monteux. Philips Universe Series Stereo 658-0266.

Little is heard of The Martyrdom of St Sebastian nowadays, and what there is, is mostly disparaging. It never has been really popular, even among Debussy's greatest admirers. In full, it is a mixture of stage and the incidental music Debussy provided. This is persuasive to some, even those who perhaps sub-consciously distrust a religious subject treated by an avowed atheist.

This, of course, is absurd and I could quote many examples to prove it, among them the Faure Requiem, composed by the free-thinking organist at the Madaleine, one of Paris' greatest churches. And what about Wagner's Parsifal and, to some extent, Lohengrin? Or Beethoven's Masses?

For those without a complete knowledge of the score and Debussy's oblique approach to the drama, Le Martyr is no easier to follow than Pelleas and Melisande, a point picked

# Rachmaninov: superbly played music

RACHMANINOV — Symphony No. 3 in A Minor. Der Fels (The Rock). Fantasie for Orchestra. Rotterdam Philharmonic Orchestra conducted by Edo de Waart. Philips Stereo Disc 9500 302.

While listening to this splendid orchestra, one is puzzled by the fact that it is used so little for recording purposes. It makes a grand sound, is perfectly disciplined, has excellent first desk soloists and an overall lustre that puts it right up among the world's best. At any rate that is how it sounds in the work under review.

Only in the first movement does de Waart seem to hesitate to bring the whole thing together — not technically but interpretatively. Elsewhere everything goes splendidly. The symphony belongs, of course, to the romantic school, but in it Rachmaninov

has toned down some of the more luscious aspects of the more popular piano concertos.

Yet this symphony, too, has its soaring melodies, its many changes of rhythms and its scholarly formal construction. It is not a long work but its beautiful proportions give it true

symphonic stature.

The fill is a "symphonic fantasie" — the composer's description of a work entitled Der Fels (The Rock). But since the sleeve notes are in untranslated German, and way beyond my elementary knowledge of that tongue, I cannot tell you anything about its program. But I can say it is typical Rachmaninov in form and content and no knowledge of a story is necessary to appreciate its many beauties. And this, too, is superbly played by the Rotterdam Orchestra.

out with a keen sense of perception by the writer of the sleeve notes, Derek Jole. Both have much the same air of spot on characterisation.

Debussy might have been an atheist but he was still artist enough to appreciate the beauty of the Christ legend. All the excerpts recorded on this disc are orchestral, a fact that doesn't help those unfamiliar with the complete work which consists of vocal and spoken sections and dance sequences. The pieces played here are the prelude to the first act: The Court of Lilies, Sebastian's dance on live coals, his Passion, and his vision of The Good Shepherd which occurs in the final scene.

The first has a strangely tonal atmosphere for late Debussy. The second, the Dance on the Burning Coals, shows no hysteria, no suggestion of the agony of burnt flesh - was there any? - though there is agony of the most exquisite kind in the Passion but which, by some miracle, never shows a hint of hopelessness. And how else could one describe a dying vision of Christ than by Debussy's music in the last excerpt?

Mostly, Debussy's approach to the work is nearly always oblique but he still manages to inject into it an occasional radiance that grows on the

listener with acquaintance.

The Three Images for orchestra take up most of the disc. The first, Gigues, is based on the popular north-of-England tune, The Keel Row, which, even if unknown to you by name, you will recognise if you are of British origin.

Great conductor of Debussy's music though he was, the late Pierre Monteux doesn't seem, to me, to quite capture the cheeky gaiety of the original, though he comes close to it. But this might be explained by the fact that though Monteux frequently visited England he retained the average Frenchman's view of that country as a grey, dour place. This, mind you, is only a guess and wide open to contradic-

The second Image, Iberia, is regarded by many as Debussy's finest orchestral work. I shall never forget the effect the slow movement had on me when I heard it for the first time in the late 1920s on an old 78 conducted by, I think, Lenau. To say that I nearly swooned with ecstacy is no exaggeration. Monteux' playing of it is faultless. Rightly did Debussy entitle it Perfumes of the Night. The Morning of a Festival is exactly what the title suggests: bustle, happiness, and a springlike freshness that captures one completely with its melodious buoyancy.

By the way, throughout the whole suite Debussy never uses one Spanish folk song or any tune resembling one. And I might add the curious fact that not one of the three most important composers to use Spain as a subject for their music - Tchaikovsky, Rimsky-Korsakov and Debussy - ever set foot in that country.

From memory, the original version was not notable for the quality of its engineering. In fact it was downright ordinary. The sound of the disc under review, played by the same artists as the original (many of whom have since died) is absolutely first class.

About the time you read this **OUR LATEST EDITION OF** BASIC ELECTRONICS will be coming off the presses.

Order your copy now! Available from "Electronics Australia," 57 Regent St, Sydney. PRICE \$3.50. OR by mail order from "Electronics Australia", PO Box 163, Beaconsfield

2014. PRICE \$4.10.

**SCOOP PURCHASE** OF WORLD FAMOUS FANTASTIC RANK ARENA SPEAKERS.

FANTASTIC 2 WAY HI FI SPEAKERS -Ideal as extension speakers in any room of your home.

- \* Huge 10 watts RMS (20 watts peak).
- 8 ohm input.
- ★ Two way system 8" woofer with ferrite magnet for ultra smooth bass and mid tones -quality tweeter for brilliant high notes.
- \* Wood grain finish with attractive brown grille.
- Perfect for main speakers or extension speakers in every
- Complete with leads and plugs for fast no fuss connection.

WERE SELLING FOR \$75 per

most fantastic special EVER 2,000 pairs of top name hi fi speakers

HS

TOP PERFORMANCE ONLY \$49.50 per pair

(Can be purchased separately) Cat. A-2465

P&P \$5

HO

☆SCOOP☆SCOOP☆SCOOP☆SCOOP☆SCOOP☆SCOOP☆

# **GARRARD SP125 SCOOP**

Deluxe stereo belt drive turntable

**BSR SCOOP** Deluxe stereo belt drive turntable

A superb belt drive turn—table with features normally found only on more expensive units! Ready wired for your hi fi, it comes complete with deluxe base and cover and a ready fitted magnetic cartridge. This unit will auto replay a record for you, so if you like a certain record, it will play it all night for you! Buy your new turntable today before inflation forces inflation forces the price up...... Not available from Grace Bros.

Terms available to approved applicants from 10% deposit



A sensational bargain from Dick Smith. The BSR turntable has belt drive for excellent reproduction and comes complete with a very modern base and cover. The magnetic cartridge fitted is one of the renowned ADC units.

The price on this unit is only possible to the price on the price of t unit is only possible through Dick Smith and his superb buy-

ing powers. Be the first in your street with a BSR turntable for less than \$100! Not available from Grace Bros

Prices and availability correct at time of going to press

# **ELECTRO**



SYDNEY 125 York Street, SYDNEY. Ph. 290-3377 147 Hume Hwy, CHULLORA. Ph. 642-8922 162 Pacific Hwy, GORE HILL. Ph. 439-5311

30 Grose Street, PARRAMATTA. Ph. 683-1133

MELBOURNE 399 Lonsdale Street, MELBOURNE, Ph. 67-9834 656 Bridge Road, RICHMOND. Ph. 42 1614 BRISBANE 166 Logan Road, BURANDA. Ph. 391-6233 ADEL AIDE 203 Wright Street, ADELAIDE Ph. 212-1962

Many lines available from the Dick Smith Electronics Centres at

SHOPS OPEN 9AM to 5.30PM (Saturday 9AM - 12 noon) BRISBANE 1/2 Hour earlier.

ANY TERMS OFFERED ARE TO APPROVED APPLICANTS ONLY

GRACE BROS

483EA279

MAIL ORDERS P.O. Box 747, Crows Nest, N.S.W. 2065. Post and packing extra.

Dealers across Australia



#### **Devotional Records**

THE BILLY GRAHAM LOS ANGELES CRUSADE CHOIR. Directed by Cliff Barrows Stereo, RCA VAL1-0177.

With the next Australian Billy Graham crusade in the offing, it is not surprising that RCA has resurrected one of the many crusade albums in its possession. The one chosen — Los Angeles 1963 — features the 5000-voice choir assembled at the huge City Coliseum, rounding off with a total of 153,000 people singing "The Lord's Prayer". The album carries the original 1963 pictures of Billy Graham, Cliff Barrows, Bev Shea, Tedd Smith (piano) and Don Hustad (organ), just as many will remember them from that era.

Track titles include: He's Got The Whole World In His Hands — \*He's The Christ Of Every Crisis —Wonderful Grace Of Jesus — To God Be The Glory — \*I Would Be Like Jesus — Hallelujah Chorus — Onward Christian Soldiers — \*Until Then — Glorious Is Thy Name — Brother James' Air — \*How Great Thou Art — The Lord's Prayer. (\*Featuring Bev Shea.)

It's a very typical crusade album, notable for the fact that the sound is completely "dry". In the open air, there is nothing to sustain and reflect even the sound of 5000 voices. Not surprisingly, however, with 135,000 performers, the last track scarcely needs it! (W.N.W.)

4 4 4

PRAISE SONGS. Orchestra and Chorus conducted by Don Wyrtzen. Stereo, Singcord ZLP-3031-S. (From S. John Bacon Pty Ltd, 12-13 Windsor Ave, Mt Waverley, Vic 3149.)

The compositions, the arrangements and the supervision of orchestra and chorus are all credited to Don Wyrtzen, a young man prominent amongst today's Gospel musicians.

The title and a conservatively dressed Don Wyrtzen, featured on the jacket, give a prior hint that the album has been created for middle-of-the-road family Gospel listening. This proves to be the case, with a mixture of tracks ranging from gentle melody to modestly up-tempo. The titles:



Our Sacrifice Of Praise — I Found It — Unbounded Grace — Psalm Of My Life — Hallelujah, Yes Praise The Lord — Love Is Now — Yesterday, Today And Tomorrow — Celebrate — I'll Never Be The Same Again — Love Was When.

The performance is smooth and well disciplined and the quality of the imported pressing is excellent. Couple this with the content and you have an album that should find ready acceptance for family listening. Recommended. (W.N.W.)

# Instrumental, Vocal and Humour

THE GREAT DISCO BOUZOUKI BAND. Astor Records Pty Ltd. Stereo FBSA071, Also on cassette (4BSAO71).

Greek music combined with a driving disco beat adds up to an enjoyable listening session on this rather unusual album. Featured are the traditional and infectious sounds of the Greek bouzouki and, with backing from guitar and percussion, the result is a record that you'll want to play "flat out".

that you'll want to play "flat out".

According to the jacket notes, the Great Disco Bouzouki Band is based in Paris and its members come from families with a strong tradition in Greek music. The group first came to prominence with the single "Disco Bouzouki".

Here are the track titles: Giogio — Greek Magic (instrumental medley featuring Never On Sunday, Zorba The

Greek, Pireas) — Ouzo & Retsina — Disco Bouzouki — Greek Girls — Do Re Mi Fa Soul.

Recording quality of the review album was impressive, with good stereo definition and negligible surface noise. Guaranteed to get the feet tapping. (G.S.)

4 4

ANDRE PREVIN IN CONCERT With The London Symphony Orchestra. Stereo, World Record Club WRC 04979.

Here is an excellent classical sampler with music from eight composers, ranging from Albinoni through Beethoven to Walton.

The titles are: Prometheous Overture (Beethoven) — Adagio in G minor (Albinoni) — Marche Slave (Tchaikovsky) — Jupiter, from The Planets (Holst) — Fantasia On Greensleeves (Vaughn Williams) — Roumanian Rhapsody (Enescu) — Romeo & Juliet Ballet (Prokofiev) — Portsmouth Point Overture (Walton).

The overall quality is good, except for a little surface noise intruding in the quieter passages. The sleeve notes give a short note on each composer and the work recorded and the disc would make an excellent gift for someone starting a classical collection. (N.J.M.)

GRAND GALA WALTZES. Benedict Silberman and his Orchestra, Stereo, Fable (Astor) FBAB-5322. Also available on cassette.

4 4

The 45-piece orchestra of Benedict Silberman sets out, on this album, to recreate the lush, fashionable atmosphere of a traditional ballroom. A chorus and instrumental solos serve to add variety but the sound never strays far from the traditional formula for the 12 waltzes:

Belle Of The Ball — The Perfumed Waltz — La Petite Waltz — Lovers Of Paris — After The Ball — El Patito — Grand Gala Valses — Monte Carlo Melody — The Chipmunk Song — Silhouettes In The Sand — Lover — Cocktails On The Champs.

The program will have its inevitable appeal but don't expect scintillating quality. The recording has a dated sound, with even the best tracks no more than medium-fi. (W.N.W.)

4 4

#### CLARINET JAZZ GIANTS. Astor Golden Hour series GH-649. Also available on cassette.

If you're partial to jazz, in particular jazz featuring the clarinet, this "Golden Hour" album from Astor will give you your money's worth. Featured on the eighteen tracks are Acker Bilk, Sandy Brown, Tony Coe, Wally Fawkes, Terry Lightfoot, Archie Semple and Monty Sunshine.

Eighteen tracks would take a lot of listing but here's a 50% sampling: Boodle Am Shake — Satin Doll — That Old

major independent research company proved that the ADC XLM MKII incurred no perceivable record wear over the life of your records!

Since then ADC's massive research programme has created a new state-of-the art, top of the line model-the ZLM Aliptic-designed for ultimate stereo performance combined with the concept of zero record wear.

Greatly reduced tip mass

The ZLM has a tiny nude diamond with a .004" x .008" rectangular shank.

This achieves more lateral strength than the fashionable ·006" square shank, plus a 10% reduction in mass.


The diamond is mounted on a new tapered stylus, which again reduces mass.

In fact, the ZLM has only half the tip mass of the famous ADC XLM MkII.

Less mass by patent
The patented ADC Induced Magnet system, where the magnet is suspended over the moving stylus arm instead of being attached to it, inherently means less mass for the record groove to move. This, coupled with major innovations in the pivot block stylus suspension (which have solved deficiencies in the old system), has resulted in greatly improved frequency response characteristics.

New low-wear ALIPTIC shape

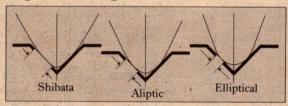The ZLM has a new tip shape that combines the advantages of the elliptical and Shibata shapes, while eliminating their disadvantages.



It is basically elliptical ( 0003" x 0007"), but its bottom radius has been modified to extend the vertical bearing surface on the groove wall by 100%.

Large enough to greatly reduce record wear, while still small enough to prevent dirt particles being reproduced. This new shape is called ALIPTIC.TM

The best polish available

We decided it was worth the extra cost to get the ultimate polish for the ZLM

The method involves a cam action to shape and polish evenly while forming the elliptical surfaces simul-taneously with the other radii. This Pathe-Marconi method is expensive, but the result makes another important contribution towards reducing record wear. Spatial sound

You'll notice a distinct difference in sound quality. Words such as 'open,' 'spatial,' 'uncoloured' and 'true' spring to mind. Individual instruments are easily identified, and there's no hint of listening fatigue.

That's strictly for the competition with its peakier response.

The new ZLM Aliptic

The culmination of all ADC's research has resulted in the new ZLM Aliptic.

Its specifications below are some of the most impressive around, and with each cartridge you receive an individual, signed, frequency response testimonial.

Certain ZLM's fall within a range of ±1/2 db 10Hz to 20kHz and ±1dB out to 26kHz.

These rare cartridges are called ZLM Select and are only available on special order.

The best cartridge we've ever made

The ZLM is without doubt the best cartridge we've ever made, but it's well worth taking a closer look at the new ADC XLM III which incorporates all of the reduced mass accomplishments of the ZLM, but with a tiny elliptical diamond. This also includes an individual specification.

Complementing the range, we have the new fourcartridge QLM Mk III series, incorporating our new design criteria and exciting innovations like the Diasa (diamond + sapphire) elliptical tip.

<b>ZLM Aliptic specif</b>	ications
Diamond tip	Nude Aliptic
Tracking force	½ to 1¼ gram
Frequency response	10Hz to 20kHz±1dB
	20kHz to 26kHz ±1½dB
Output	1.0mV per cm/sec
Output balance	1dB max. diff.
Channel separation	30dB at 1kHz/20dB at 10kHz
Inductance	580mH
Resistance	820 Ohms
Load resistance	47,000 Ohms
Load capacitance	275pF
Cartridge weight	5.75 grams
Accessories	Stylus brush, screwdriver, all
	mounting hardware and signed
	frequency response curve.



The new ZLM Aliptic Cartridge.
The difference between playing your records and wearing your records.

A BSR Company

Distributed by: EXPO International Trading Pty Ltd 27 Buckley St., Marrickville NSW 2204

#### THE LIGHTER SIDE — continued

Feeling — Wild Cat Blues — Hiawatha - Sweet Georgia Brown — Louise -Elephant Stomp — Slab's Blues, etc.

Depending on their source and their age the tracks are a mixture of stereo and mono, but the latter have apparently been spiced with a touch of reverb to enliven the sound. If the program appeals, the pressing itself will certainly not compromise your enjoyment. (W.N.W.)

BUNKY GREEN, VISIONS. Vanguard VSD 79413. Astor release.

Alto sax player Bunky Green gives us some very relaxed jazz on this record from Vanguard with seven fairly lengthy tracks: Alone Again Naturally What I Did For Love — The Greatest Love Of All — Never Can Say Goodbye - Ali Theme — I Write The Songs -The Entertainer — Visions. This last title track runs for seven minutes and 48 seconds.

The backing group consists of Wilbur Bascomb, Angrl Allende, Mark Gray, Jeff Bova, Hiram Bullock, Steve Jordan, Michael Carvin and Bob Cranshaw.

It is interesting to see how synthesizer music of various types has come of age, in so many musical styles. It was not so long ago that "Switched On Bach" was such a sensation; now a big proportion of records have at least one kind of electronic instrument in the credits. (N.J.M.)

LOS HERMANOS MALAGUENOS. Stereo, WRC S/5254. World Record Club Release.

If you're in the mood for some quiet Flamenco guitar music, this record could well satisfy you. Originally released by Harmonia Mundi, the record sleeve has little information about the artists, except that their names are Antonio and Marino. The eight tracks are: Bulieria — Solea — Rondena — Allegria — Taranta — Sigueriya — Milonga —

The quality is excellent, with a close, almost intimate sound, making an ideal record for quieter moments' listening. (N.J.M.)

公

SONGS OF JOY. Werner Muller & His Orchestra. Stereo, World Record Club WRC R-02409.

Turning aside from the ordinary middle-of-the-road standards, Werner Muller has built this album around titles and themes borrowed from the classics, but played in highly theatrical style. The titles:

Song Of Joy (Beethoven) - Theme, Piano Concerto No. 1 (Mozart) from "Elvira Madigan" — Forbidden Games (Trad.) — Aranjuez, Mon Amour

**AKKORDEON HITS 5. Die Fidelen Lim**burger. Stereo, Europa (Astor) 111-

To judge by the jacket, this is the fifth album of "Akkordeon Hits" by a group comprising two accordianists, a bassoon player to provide the rhythm bass and a young blond lass on drums.

From the very first bars, the sound is unmistakeably central European and it whisked me back in time and place to a particular folk concert in Austria. Ah

The jacket lists a profusion of titles in English and German (?) but, with music like this, I doubt that titles really matter. There's an obvious sameness, yet an infectious sameness, nevertheless. But,

(Rodrigo; Bontempelli) - Air On The G-String (Bach) - Theme From "2001" (Strauss) - Adagio (Albinoni) - Gymnopedie Nr 2 (Satie) — Bachianas Brasilieras Nr 5 (Villa Lobos) — Symphony No. 40 (Mozart).


As I said, it's all very theatrical, with strands of synthesiser and vocal effects threaded in with traditional orchestral sound. You may find it ingenious, interesting, entertaining - or you may see it as tedious tampering with traditional tunes that deserve temperate treatment!

The sound quality is okay, although not quite up to what one tends to expect from an album originally released under the Decca Phase-4 label. (W.N.W.)

WINNIE. Winifred Atwell In Concert. Stereo, RCA VAL1 0170.

On January 30, 1976, Winifred Atwell made this live recording at the Revesby Workers' Club in Sydney - her first such recording in years. And it was obviously a happy occasion for both performer and audience.

Side 1 was recorded using a full grand

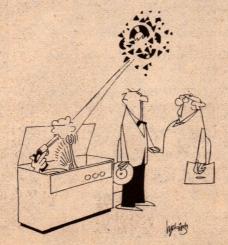

"We've set it to reject rock and roll!" ("Radio-Electronics")



for the record:

Rivers Of Babylon - Mull Of Kintyre - Lazy Bumblebee - Love Is In The Air - Singing In The Rain - Bye Bye My Love — Heidi — Isabelle — etc.

The recording quality is well up to standard and, if you're at all partial to the happy European "compah" style, you'll enjoy it. (W.N.W.)

piano and, backed by a small instrumental group is devoted to tracks like: Choo Choo Samba - Zorba's Dance - Burt Bacharach Medley -"Airport" Theme — Bumble Boogie — Macarthur Park — Hava Nagila — Medley including "When The Saints", "Alexander's Ragtime Band" etc.

On side 2, she resurrects "that other piano", for a honky tonk "Black And White Rag", followed by a singalong medley. Then comes "Tiger Rag" and four other medleys, with the audience having a ball and Winnie at her brilliant best, doing her own thing.

It's the hectic, happy sound of a workers' concert, very cleanly recorded and of generous length: just short of the label on both sides! If you like Winifred Atwell, you'll certainly enjoy this album. (W.N.W.)

A COLLECTION OF GOLDEN PERFORMANCES. Liberace. ABC

Records (RCA) ABCA-30020. By reason of his television appearances, we have come to expect a Liberace that is flamboyant, talkative, and involved in a constant two-way interchange with his audience.

For this record there is no repartee, no audience and no applause. Liberace is basically the fluent cocktail pianist/entertainer, playing a highly ornamented lead to an instrumental backing group, in some dead quiet studio.

It is a generous program, however, with a total of 18 tracks on the two sides. To mention just a few: Lara's Theme — Spanish Eyes — East To Love — Yesterday — It Was A Very Good Year - Love Is A Many Splendoured Thing - Sunrise, Sunset - Try To Remember — Strangers In The Night —

The sentimental nature of the program, its presentation and the tightly controlled dynamics rather belie its title "Golden Performances". My tip is that most will treat it as a soft lights and

#### LIGHTER SIDE — continued

#### Sounds in stereo from the West Australian countryside

AUSTRALIAN BIRD CALLS. Series 2 by John N. Hutchinson. Stereo cassette. From John N. Hutchinson, Balingup 6253, WA; price \$8.00 incl. postage. Also available on disc for the same price.

If you're anything like me, you've probably determined on more than one occasion to make your own recording of bird sounds — but you've never quite got around to it! Well, John Hutchinson of Wildlife Sound Studios Grampian and Sennheiser microphones, mixers, switchers and a Nagra and a Uher tape recorder.

There's one factor for east coast dwellers in that the sounds featured on this recording are from forest and farmland birds of Western Australia, rather than the species found at the bottom of your garden. Even with those you know, you'll have to be prepared for a different (common) name and



perhaps a noticeably different song.

As against series 1, this recording comes in stereo, with bird, bush or frog sounds blended by way of background. There are no announcements on the tape but the species and situations are explained in jacket notes, in the case of the disc, or in a physically much reduced copy with the cassette.

Quality is good and you won't be disappointed if you share John Hutchinson's interest in our feathered friends

and their habitats. (W.N.W.)

sweet music sound; music for dining and relaxing with none other than Liberace to help set the mood! The quality is okay. (W.N.W.)

> \* 4 4

#### STAGE. David Bowie. RCA CPL2 2913. RCA release.

This double-live album set contains 17 of David Bowie's great album tracks. The tracks on the album are: Hang On To Yourself — Ziggy Stardust — Five Years — Soul Love — Star — Station To Station — Fame — TVC 15 — Warszawa - Speed Of Life - Art Decade Sense Of Doubt — Breaking Glass — Heroes — What In The World — Breakout - Beauty And The Beast.

The two record set involves some excellent live recording, for which credit must go to the RCA Mobile Recording

Anyone who attended the David Bowie concerts in Australia late last year, could revive the experience by purchasing this "live" set. (D.H.)

> \* 3

#### SEA CRUISE. Jay & Germain. Celsius MLF 235. 7 Records release.

"Sea Cruise" is a disco album featuring great performances of the Beach

Boys' hits.

The first track on side 1 is a medley extending for 11.51 minutes: Dance, Dance, Dance — Do You Wanna Dance - Surfin' USA - I Get Around - Wendy — Help Me Rhonda — Little Surfer Girl — Fun, Fun, Fun — Good Vibrations — Little Honda — Shut Down - Little Deuce Coupe - California Girls - Summer Finale.

The remaining track on side 1 is "Keep Doin' It"

Side 2 consists of three tracks: Dancer — Crazy Motion — Barbara

In many cases the vocals are similar to the original Beach Boys' sound. However, the up-tempo disco beat adds to the virility of this performance.



#### CRUISIN. Village People. RCA VPL1 4101. RCA release.

With two highly successful albums under their belt, Village People have come up with a third smash hit album entitled "Cruisin".

The opening track on the album "Y.M.C.A." is their latest single. Other tracks on the album are: The Women - I'm A Cruisin — Hot Cop — My Roomate - Ups And Downs.

Every track is characterised by a heavy disco sound — every bit as heavy as the masculine image they seek to project on the jacket. Pictorially, Village People consist of a policeman, a cowboy, a construction worker, an Indian, a leather man and a GI! (D.H.)

#### RENEE GEYER WINNER. Renee Geyer. RCA Victor VPL10164.

Personally, I think that you'd have to be a real Renee Geyer fan to fully appreciate this album. To my ear, the tracks have a sameness of sound, typical of the "low-key" jazz style encountered in a night club. The only really distinctive track is "Baby Be Mine", which has also been released as a single.

Other track titles include: Money (That's What I Want) - I Miss You -Save Me — Baby I'm The One — Sweet Kisses — The Magic Is Still There — Bad Side Of The Blues — Apartment C & D - I Don't Wanna Lose A Good Thing.

The album was recorded at Crystal Studios in Los Angeles, USA, and mixed in RCA's Sydney studios. The result is an album of excellent technical quality, if of somewhat unvarying content. (G.S.)

#### BURGERS AND FRIES — WHEN I STOP LEAVING (I'LL BE GONE). Charley Pride. RCA Victor APLI 2983.

Charley Pride is in top form on this album, his deep smooth voice wending its way through 10 ballads and love songs. As usual, the backing musicians are kept in place, and never overshadow Charley's voice.

In order, the tracks are: Burgers And Fries - The Best In The World -Whose Arms Are You In Tonight — Nothing's Prettier Than Rose Is — Mem'ries - When I Stop Leaving (I'll Be Gone) - One On One - Where Do I Put Her Memory — You Snap Your Fingers (And I'm Back In Your Hands).

The two title tracks are the pick of the bunch, although the remaining tracks are also of a high standard. Recording quality is excellent, with a good stereo balance. (D.W.E.)

#### VICTIM OF ROMANCE. Michelle Phillips. A & M Records L36541. Festival release.

This is Michelle Phillips' first solo album, although her pleasant voice should be known to many from her work with the Mamas and Papas. On this record she covers quite a wide range of styles, from country rock to romantic ballads. Best track is undoubtedly the title track "Victim Of Romance", which has overtones of the Beach Boys and a slight touch of the Phil Spector sound.

Other tracks, which are all quite pleasant, include Aching Kind - Let The Music Begin — Trashy Rumours — There She Goes — Paid The Price — Baby As Your Turn Away — Lady Of Fantasy — Just One Look — Where's Mine? (D.W.E.)

World Record Club recordings reviewed in these columns can be obtained only through the World Record Club Pty Ltd, 605 Camberwell Road, Hartwell 3124. Tel. (03) 29 3636

# fact: you can choose your microphone to enhance your individuality.

Shure makes microphones for every imaginable use. Like musical instruments, each different type of Shure microphone has a distinctive "sound," or physical characteristic that optimizes it for particular applications, voices, or effects.

Take, for example, the Shure SM58 and SM59 microphones:


# SM59 Mellow, smooth,

silent...

The SM59 is a relatively new, dynamic cardioid microphone. Yet it is already widely accepted as a standard for distinguished studio productions. In fact, you'll often see it on TV... especially on musical shows where perfection of sound quality is a major consideration. This revolutionary cardioid microphone has an exceptionally flat frequency response and neu-

tral sound that reproduces exactly what it hears. It's designed to give good bass response when miking at a distance. Remarkably rugged — it's built to shrug off rough handling. And, it is superb in rejecting mechanical stand noise such as floor and desk vibrations because of a unique, patented built-in shock mount. It also features a special hum-bucking coil for superior noise reduction!

#### Some like it essentially flat...

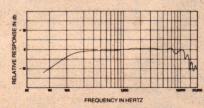


# **SM58**

# Crisp, bright "abuse proof"

Probably the most widely used on-stage, hand-held cardioid dynamic microphone. The SM58 dynamic microphone is preferred for its punch in live vocal applications especially where close-up miking is important. It is THE worldstandard professional stage microphone with the distinctive Shure upper mid-range presence peak for an intelligible, lively sound. Worldrenowned for its ability to withstand the kind of abuse that would destroy many other microphones. Designed to minimize the boominess you'd expect from close miking. Rugged, efficient spherical windscreen eliminates pops. Lightweight (15 ounces!) hand-sized. The first choice among rock, pop, R & B, country, gospel, and jazz vocalists.

#### ...some like a "presence" peak.

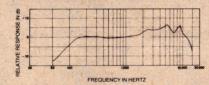

# professional microphones...by



AUDIO ENGINEERS P/L

342 Kent Street. SYDNEY 2000 N.S.W. AUDIO ENGINEERS (Vic.)

2A Hill Street. THORNBURY 3071 Vic. AUDIO ENGINEERS (QId.)

5IA Castlemaine Street. MILTON 4064 Qld AE130/FP
ATHOL M. HILL P/L

33 Wittenoom Street. EAST PERTH 6000 W A

# Simple EPROM burner suits SC/MP and 2650

Using only four low cost ICs, this single board design will allow any static microprocessor, such as the SC/MP or 2650, to program 2704 and 2708 type EPROMS. Programming time for 1K bytes is just under five minutes, and no special interface circuits are required.

by DAVID EDWARDS

The basic circuit configuration and idea used in this project came originally from one of our readers, Mr M.J. Ogden of Hope Valley, South Australia. As soon as we saw it, we decided that it was too good an idea to publish purely in basic circuit form. So with Mr Ogden's approval we have expanded the original concept into a full construction project.

Like all good ideas, Mr Ogden's is delightfully simple. PROM programming interfaces normally have to provide address and data latches, as this information must be held static during the relatively long periods taken to program PROM locations. But some microprocessors, like the 2650 and SC/MP, are static devices, and are capable of being forced into a "hold" or "wait" state without loss of data. This is to allow them to be used with slow memory or peripheral devices. Why not take advantage of this facility, and use the processor itself as the address and data latches for the PROM programmer?

With static processors like the 2650

and the SC/MP the idea turns out to be very easy and straightforward. All that is necessary is to arrange simple logic so that to program each PROM location the processor is made to begin a normal instruction cycle storing the required data to the appropriate address, then "held" or frozen with the data and address information present on the bus lines until the programming circuitry has done its job.


Before discussing the operation of the circuit in detail, an explanation of the operation and programming requirements of an EPROM is in order.


quirements of an EPROM is in order.
The popular 2708 EPROM uses floating-gate avalanche mode MOS transistors as the storage cells. Stored charges on the floating gates are used to control the conduction of the MOS transistors, to determine whether they effectively store a "I" or a "O".

The floating gate's charge is produced by inducing a non-damaging avalanche breakdown in the drainchannel junction of the cell. High energy electrons from the avalanche breakdown are then injected into the floating gate, charging it negatively. Since the floating gate is surrounded by an extremely effective insulator, this charge will remain practically indefinitely, and hence the stored pattern will also remain.

To erase a programmed EPROM, the chip is irradiated with ultra-violet light. The resulting photons impart enough energy to the trapped electrons to allow them to escape from the floating

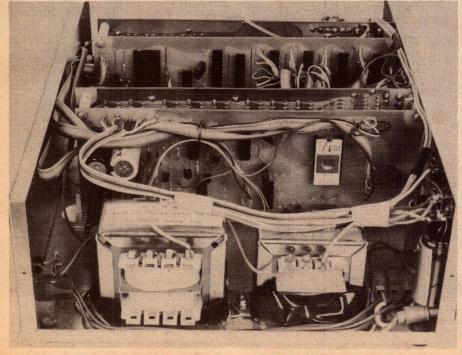In this photograph, you can see how the new board fits into the 2650 Minicomputer case.



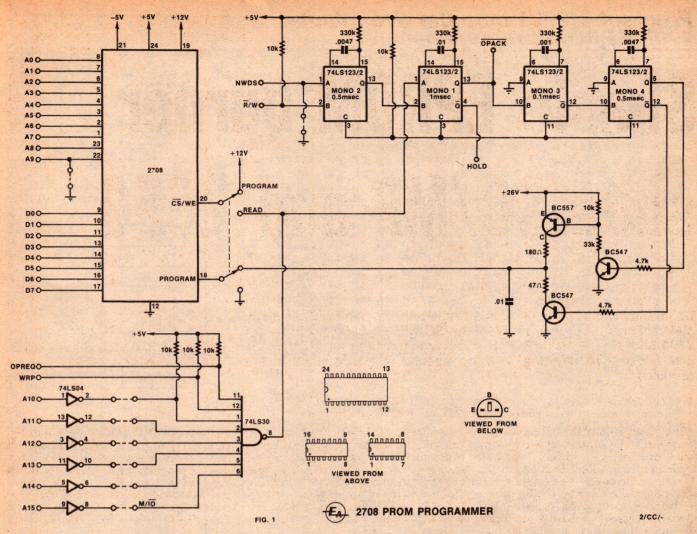

gate, leaving it uncharged.

An erased EPROM has all memory cells effectively containing 1's, so programming consists of inducing avalanche mode breakdowns in the appropriate cells to produce the required zeros. In principle one programming pulse is required for each memory location. The appropriate address and data information must be applied to the address and data pins of the EPROM.

In practice, due to power dissipation limits, it is necessary to apply relatively short programming pulses, and to cycle repetitively through all memory locations until a sufficient number of programming pulses have been applied

to each location.

Turning now to Fig. 1, we can see how the basic idea can be used to implement a simple EPROM programmer. The microcomputer's address and data lines are connected directly to the EPROM. In the read mode, a chip select signal is derived from the high order address lines by a decoder implemented with a hex inverter and an eight input NAND gate.

This decoder allows the EPROM to be patched into any available area of memory. To use the top 1K section of memory, it is not necessary to use the inverter; the address lines can simply be connected directly to the NAND gate.


In the program mode, the chip select input is connected to the +12V line. The output of the address decoder is now used to enable a monostable (mono 1) with a period of 1ms. This monostable is triggered from the output of a second monostable (mono 2), which itself is triggered from the write select signal.

Thus the first monostable is only triggered when a write instruction occurs to a valid EPROM address. The output of this monstable is used to drive the hold line of the processor, halting the write operation in midstream, and leaving the appropriate address and data information on the processor buslines. Fig. 4 shows the timing relationships schematically.

At the same time, a third and delaying monostable (mono 3) is triggered, with a pulse width of 0.1ms. The trailing edge of this pulse is used to trigger a fourth monostable (mono 4) which has a pulse width of 0.5ms. The outputs of this monostable are used to drive the programming pulse generation circuitry.

The programming pulse has an

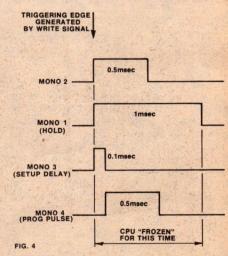
Above is the complete circuit diagram of the programmer, while below is a diagram illustrating the timing relationships between the monostable multivibrators.



amplitude of 26V, and lasts for 0.5ms. Approximately 0.4ms after the end of the programming pulse, the output from the first monostable returns to the quiescent state, and the hold is removed from the processor.


Thus to program the EPROM, all that

#### 2708 EPROM programmer

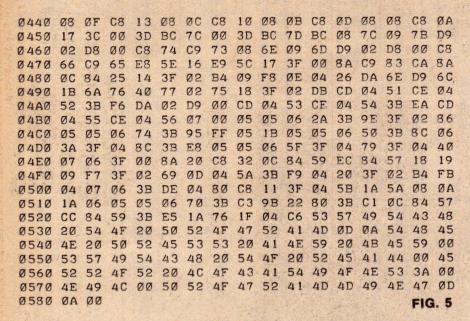

This hex listing is a 2650 version of the program required to control the EPROM programming operation.

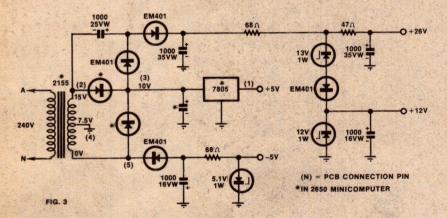Shown below is the power supply circuit. The components marked with an asterisk (\*) are already present in the 2650 Minicomputer.



is required is to switch to the program mode, and then to program the processor to write the appropriate data to each location in turn, repeating this writing sequence until the required number of programming pulses have been applied to each location.

All of the timing requirements are provided by the four monostables, all that the program has to do is provide a repeated "block move" function. A block diagram of a simplified routine to do this is shown in Fig. 2.


Power supply requirements for the 2708 are quite complicated. —5V, +5V and +12V supplies are required for normal operation, while +26V is required during programming. Fig. 3 shows how these voltages can be derived from a standard transformer, using zener diode regulators. The +5V supply can be obtained from the existing circuitry.

We have designed a suitable printed circuit board for mounting the EPROM, address decoder, monostables and power supply components. It is coded 79upl, and measures 218 x 81mm.

Provision has been made so that this board can be used with any suitable processor. Positive and negative going hold signals are available, and the write monostable can be triggered from either positive or negative going signals. Any starting address for the EPROM can be decoded, up to H'7C00.

Construction of the board should be well within the capabilities of most enthusiasts. We recommend that a good quality socket, preferably a zero-insertion force type, be used for the 2708. The remaining ICs can be soldered directly in place.

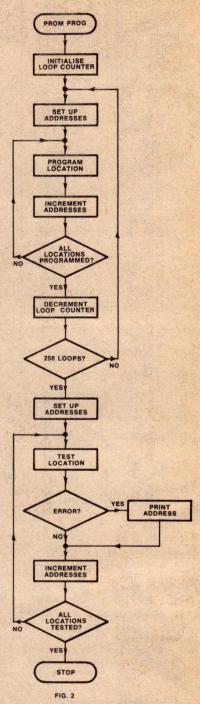The programming switch can be mounted directly on the board, using tinned copper wire, or it can be ex-



This is the flowchart for the controlling program. Use it to write the routines required by your processor.

tended with a cable if desired. It should be placed in a position where accidental operation is unlikely, to ensure that no accidental programming occurs.

As the board has to be wired directly to the address and data busses, we recommend that it be mounted in the main computer case. Make sure, however, that access can be gained relatively easily to the EPROM socket and the read/program switch.

Why haven't we been advertising for 12 months? Well, we have been spending all that lovely advertising money on R and D. Available March - the most incredible Z80 S100 bus micro computer you have seen. We are showing the Yanks how to do it!

CHARACTER ASC II OUTPUT 18- WAY CONNECTOR Supplied

CUSTOMISED ENCODER

FULLY ENCUDED 128-

ANYMHERE **AUSTRALIA** 

MRSOR 201790 2 USER - DEFINED RELEGENDABLE SKENS

Ø

0

%50

REPT

SHIFT

Z

 $\mathbf{\omega}$ 

SHIFT

I

ш

S

2

Ш

S CURSOR KEYS SPACE FOR LOCKABLE UPPER CASE

of keyboard comes from a fine family. Get the full story on the wiping action for long life and reliability, and plungproducts to the data terminal industry, and MAX new MAX keyboard for personal computing. Maxi-Switch is a leading supplier er action that is smooth and precise. NO MORE FIDDLING WIRING UP A KEYBOARD AND THEN HUNTING FOR A SUITABLE ENCODER for user assignment. Everything you need to start A low-cost MAX option kit (Part No. 620002) lets you add four CURSOR keys and a HOME key if you need those functions. Coding is already provided.

MAX low-profile switches have gold contacts with Individual keys for CARRIAGE RETURN, LINE FEED and ESCAPE are provided to give you these important functions without multiple key closures.

entering data immediately.

Now you can buy a complete operational key-board with full ASC11 code capabilities, built to commercial standards, yet priced for the personal user who needs only one. This is not a surplus unit or a manufacturer's overrun, it's a new board designed specifically for the personal computer user. MAX is MOS/LS1 encoded, and includes all 128 ASC11 characters, two-key rollover protection and two non-encoded keys with relegendable keytops

Full service backup and spares available. And by time of publication a case will be available. Phone or write for details.

ARTS

95 Latrobe Terrace PADDINGTON 4064 Woolworths Arcade PADDINGTON 4064 P O. Box 118.

Phone Brisbane (07) 36 1474

ELECTRONICS Australia, February, 1979

## 2708 EPROM programmer

In order to illustrate the use of the Prom Programmer board, we have used it with the 2650 Mini Computer. In this case, the M/IO-bar signal is connected to the address decoder instead of AD15. The OPREQ and WRP signals are also connected to the decoder, using the spare inputs to the

NAND gate.
The A input of monostable 2 is grounded, and the Rbar/W signal applied to the B input. The Q output of monostable 1 is used to drive the OPACK-bar line. We elected to make the EPROM occupy locations from H'3C00 to H'3F00, the last 1k of page 1. To do this, it is necessary to apply AD10, AD11, AD12, AD13, and AD14-bar to the NAND gate.

We chose this area so that it would be relatively easy to provide a small amount of RAM in the same page. This is required because of the limitations of the 2650 absolute addressed memory reference instructions. We used the spare RAM sockets on the main CPU board, wired up as the first

4K of page 0.

The 2650 program we developed to control the Prom Programmer is given as a hex listing in Fig. 5. It occupies locations H'0440 to H'0581 inclusive, and is not easily relocatable. To call the program, which uses Pipbug routines CRLF, COUT, GNUM, CHIN and BOUT, type G492 XXXX YYYY ZZZZ cr, where XXXX and YYYY are four digit hex numbers represneing the start and end addresses of the area of RAM to be copies into the EPROM, and ZZZZ is a similar number representing the address of the first EPROM loca-

The program will respond with the message "SWITCH TO PROGRAM THEN PRESS ANY KEY". The read/program switch (it should normally be in the read mode) is now moved to the program position, and any keyboard key of the

terminal pressed.

The program will then respond with the message "PROGRAMMING", and then appear to do nothing while it actually programs the EPROM. A 1K "burn" will take nearly five minutes, shorter burns proportionately less.

When the programming is complete, the program will print out "SWITCH TO READ THEN PRESS ANY KEY". When this command has been carried out, the program begins to verify that the data has been stored correctly in the EPROM. First it responds with "ERROR LOCATIONS:" and then gives a list of any locations not correctly programmed. If there are no errors, the message "NIL" will be displayed.

If you obtain a small number of errors, this indicates that there was insufficient programming at these locations. To remedy this, simply repeat the programming process for all

of the block you are attempting to program.

To use the programmer board with a SC/MP system, connect the address and data lines to the appropriate points on the board. Insert the two 10k pullup resistors on the OPREQ and WRP lines, but leave these lines unconnected. The Qbar output of mono 1 is used to drive the SC/MP HOLD line, while the SC/MP's NWDS signal is used to drive the A input of mono 2. The B input of this monostable is pulled permanently high by the 10k pullup resistor provided.


That is all the hardware alterations required, apart from

providing the appropriate power supplies. Of course, you will need to write an appropriate controlling program, to output the required data to the EPROM. Use the flow chart

provided as a guide.

Do not attempt to program a block of memory smaller than about 256 bytes, as otherwise the power dissipation limits of the 2708 may be exceeded. If you have to program a small block, reduce the number of program loops (specified in location H'04B6), by a proportionate amount, and then program the PROM repeatedly until a correct burn-in is achieved.

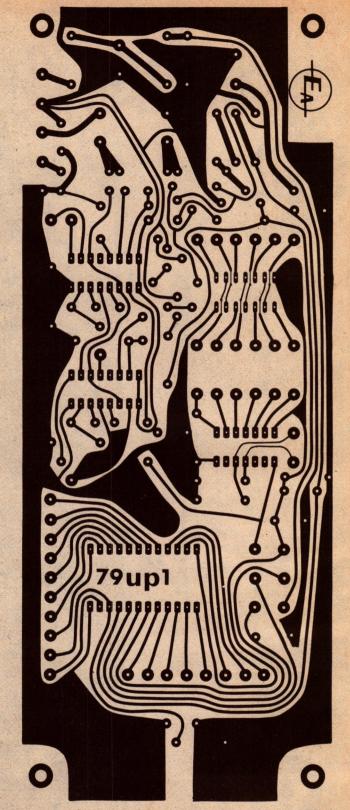Once an EPROM has been programmed, it is recommended that the transparent quartz window above





You can either copy this actual sized reproduction of the PCB artwork, or trace it directly. Alternatively, commercial boards should be available in due course.

the chip be covered with an opaque layer, to prevent possible leakage currents generated by ambient light from causing malfunctions.

If you wish to erase a programmed 2708 EPROM, you will need a source of ultra-violet light with a wavelength of 2537 Angstroms. A suitable source is the TUV 15W lamp (cat. no. 57415P/40), available from Philips. It fits in a standard 20W fluorescent holder, and should be ordered from an elecUse the overlay diagram at the right when you are assembling the PCB. Note that address decoding is achieved by the address wire connections, using the hex inverter as required.

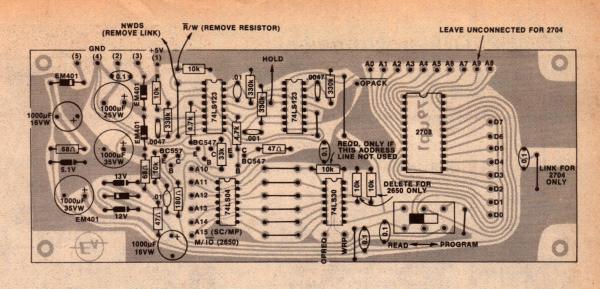The photograph below is of the completed prototype. Note in particular the way in which the address wiring has been completed for addresses 3C00-3FFF.



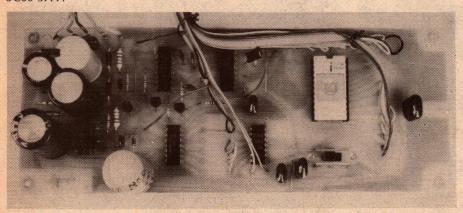

trical or lighting store.

With the window of the 2708 about 25mm from the tube, an exposure time of approximately 30 minutes will be required. This will erase all sections of the device. Note that lamps of this type must be used with caution, as eyes and skin may be affected by long exposures.

In the next issue, we plan to publish details of suitable 2650 utility routines for programming into a 2708. These will include a hex input routine, a hex listing routine, a block move routine, a search routine and a tape verify routine, and possibly other useful subroutines.

# ASP?

ASP is the superb ASP SYSTEM ONE Computer for business, scientific or educational use. Problem solving at a very reasonable price.

ASP is a professional quality conversion of the IBM SELECTRIC typewriter to a word processing quality printer with either \$100 or R\$232 interfaces.

ASP is the magnificent MALIBU DESIGN GROUP printer. 160 cps bi-directional and graphics capability with the looks of a high quality piece of furniture.

ASP is the new ASP Computer Portrait System - a profitable small business that can be transported in your vehicle.

DEAR ALI
please
rush me
brochures on:

EVERYTHING!
ASP SYSTEM ONE
SELECTRICS
MALIBU
COMPUTER PORTRAITS
DEALERSHIPS!

SELECTRIC is a Trademark of IBM

NOTE OUR NEW ADDRESS:

799 DANDENONG ROAD EAST MALVERN 3145

& OUR NEW TELEPHONE NUMBERS:

211 8855 211 8344



# Microcomputer **News & Products**



#### Melbourne's computer show





Despite its suburban venue, Melbourne's first Home Computer Show was voted an outstanding success by exhibitors and organisers alike. Held in the Box Hill Town Hall over the weekend December 9-10, the show attracted capacity crowds; at times the front doors had to be shut, to allow those inside to thin out before more were admitted.


When the doors finally shut on the Sunday night, just on 5700 people had paid to see and use the latest in home and small business computers. Although most had come from the Melbourne area, a significant number had travelled much further distances. Some had even flown in from inABOVE LEFT: Near the Futuretronics stand — it was hard to get any closer! ABOVE: Young enthusiasts at the Computerland stand.

terstate.

For virtually all of the weekend crowds were many rows deep around most of the stands. Almost every exhibitor provided visitors with the opportunity to try out equipment for themselves, and young and old alike accepted the challenge. At times the only problem was to prise young enthusiasts away from the terminals, to let others have a try!

A number of the exhibitors were selling direct to the public, and reported healthy sales of items such as video games and instructional books. Others reported many orders and preliminary inquiries.

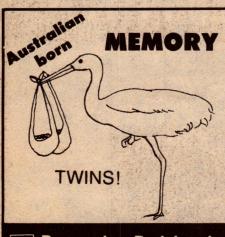
Many of the names on the stands will be well-known to EA readers: SM Electronics; Pennywise Peripherals; AJF Systems and Components; Sontron Instruments/The Byte Shop; ASP Microcomputers; Futuretronics; Abacus Computer Store; Rod Irving Electronics; Strand Electric; Dick Smith Electronics; Electronics Today International; Delta Scientific Electronics; RML Computers; Computerland



### PP Pennywise Peripherals

19 SUEMAR STREET, MULGRAVE, VIC. 3170 PH. (03) 546 0308

#### **16K STATIC RAM**

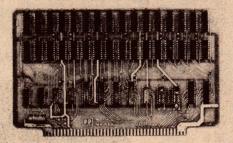


- Uses 2114 1K x 4 STATIC RAMS. Only 1.2 @ 5 V typical for 16K. Motorola Exorciser Bus as on D2.

- 8K blocks switch addressable. PCB plated through with solder resist.

PCB + support ICs Kit \$97.20° \$257.20° 8K (450 nS) ass & tested 16K (450 nS) ass & tested \$392.40 P&P \$3.00 (add 15% if sales tax applicable)

DEALER ENQUIRIES WELCOME

#### 16K PROM + PROGRAMMER

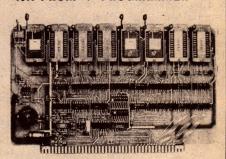

- For INTEL 2716/TEXAS 2516 2K x 8. Single +5 V supply, 25 V generated. Read PROMs and execute programs as for a normal PROM Card.
- Program any location with a single store Same Bus, address selection etc as for 16K STATIC RAM CARD.

Ass & tested with ZIF sockets Ass & tested with Low IF skts 2716 PROMs & 2114L RAMs also available.

\$197.30 \$236.20



Outside the Tandy TRS-80 stand - again it was hard to get closer!

Australia; South West Electronics; Box Hill Technical College; Honeywell; The Dindema Group; AJ & JW Dicker; Tandy International; Warburton Franki Industries; and Informative Systems.

All told, the show was such a success that the organisers are now giving serious thought to running a similar show in Sydney, early this year.

#### Low cost terminal



E & M Electronics has added a new model to its range of VDU products: a low cost interactive teletypewriter replacement which connects to a standard video monitor or TV receiver. Designated the EME-20, the new terminal incorporates the EME-2 module announced in the August 1978 issue. It also features a Hall-effect keyboard for improved reliability.

The EME-20 provides three serial communications options: TTL, 20mA current loop or RS232C, available via a standard 25-way D connector at the rear. Also at the rear are two switches, one selecting baud rate and the other half or full duplex. Baud rates available are 110, 300, 1200 and 9600, although other speeds are also available. A solid state alarm is mounted at the rear of the unit, providing an audible signal in response to the BEL control character.

The terminal is available in both a fully wired and tested version and a kit version. The fully assembled version sells for \$540, with optional RF modulator extra; the kit version (EME-20K) sells for \$450 and includes the modulator components.

Further information is available from E & M Electronics Pty Ltd, 136 Marrickville Road, Marrickville, NSW 2204. Telephone (02) 51 5880.

# Verbatiim

MD 525\* TRS80 COMPATABLE

\*SPECIFY SECTORING OR SYSTEM

1-9 \$4.25 10up \$4

P&P Incl - add 15% sales tax

THE BUTE SHOP

PO BOX 118., MAWSON ACT 2607



# An introduction to Digital Electronics

You don't need any previous knowledge of digital electronics — the book starts you right from scratch, and covers all of the basic concepts you need.

Available from "Electronics Australia", PO Box 163 Beaconsfield, NSW 2014. Price \$3.50 plus 60c pack and post. Also from 57-59 Regent St, Sydney.

# MICHOCOMPUTER

#### FLOPPY DISK

- \* VERSATILE
- \* SMALL BUSINESS APPLICATIONS
- \* BASIC WITH FILE HANDLING CAPABILITIES. FLEX® IS COMPOSED OF THREE PARTS.



IN KIT FORM.

SWILE

FOR FURTHER INFORMATION PLEASE PHONE (02) 31 3273 OR WRITE TO:

P.O. Box 380, Darlinghurst NSW 2010

# COMPUTER COMPONENTS

#### **S100 BOARDS**

#### 2708/2716 EPROM BOARD EP16K

- 16 2708 or 2716 PROM Up TO32K storage
- Selectable addressing allows ram overlay
- Plated thru P.C.B. solder masked with parts legend
- Full documentation supplied

#### BARE BOARD W/-

#### DOCUMENTATION \$36.50

#### VIDEO DISPLAY BOARD VDB-1

- 16 lines of 64 characters
- Full upper and lower case ASC11 plus symbols
- 7 x 9 dot matrix Normal or reverse video and blinking cursor
- Addressable to any 1K 'hole' Plated thru P.C.B. solder masked with gold connector and parts
- legend Full documentation supplied

#### PROTOTYPE BOARD WW1

- Bare Boards W/
- documentation \$32.00
- Prototype Board WW1
  For solder or wire wrap
  Plated thru P.C.B. with gold edge
- Provision for 3 regulators
- Accepts sockets for 6-64 pins

#### BARE BOARD W/-DOCUMENTATION \$32.00

#### Z-80 C.P.U. CPZ-80

- Runs up to 4MHz On board 2708
- Power on jump No front panel needed
- Selectable wait states 8080 or Z-80 style 1-0
- Plated thru P.C.B. solder masked with gold connector & parts
- software available

#### Bare board W/- documentation \$44.50 coming soon

- Floppy disc controllers and drives
   Phi-deck tape transports
- New software for 8080/Z80 and 6800
  - KEEP YOUR EYE ON THIS SPACE

#### S100-8080A PROCESSOR BOARD

- 8 level vector interrupt (8214) 8224 clock generator
- Double solder mask
- Silk screen parts layout
- Complete documentation re P.C.B. W/- documentation \$39 50

Intel. 8080A 1C \$8.95

#### S100 8K x 8 STATIC RAM BOARD Uses 2102 type RAMS

- Fully buffered
- Memory protect
- Dip switch addressing
- Double solder mask
- Silk screen parts layout
- Full documentation re PCP W/- Documentation

\$39 50

- 1mH XTAL oscillator 2 independent interrupts
- seconds Both software programmable

- Complete documentation in-cludes software to display time
- of day Double sided solder mask
- Silk screen parts layout

Bare Board W/- Documentation \$39.00

- Complete documentation

#### REAL TIME CLOCK FOR S100 BUS

- Pre-interrupt uses 16 bit counter
- in 10*u* sec steps Other Interrupt is in decade steps from 100*u* sec to 10
- Board can be selected by 128 device code pairs

#### S100 16K STATIC MEMORY BOARD

- Uses 2114 RAMS Wait state generation Addressed on 4K boundaries
- Silk screen parts layout

#### Bare b \$39.50 board W/- documentation

2114 250ms \$7.50 10 or more \$6.50

#### STEWART ELECTRONICS

# 9 SLOT BACKPLANE FOR M6800 Double sided board Solid shield on back

- Active or passive termination Provision for 10 bypass caps

#### Exorciser and D2 compatible \$39.00

#### COOLING FANS

- Popular Muffin' fan Standard 4.68" sq. size
- High air flow Grilles and filters available

\$25 50

#### POWER TRANSFORMERS

- FOR MICROCOMPUTERS Compact
- Good regulation
   Electrostatic shield provided

JDT-003 8V @ 5A 2x15V @ 1A \$14.00 JDT-00

8V @ 10 JDT-002 10A 2x15V @ 1A \$19.00

8V @ 24A 2x15V @ 1.5A \$28.00 \*Companion 10 or 24A regulator board available soon

# 8803

- MOTHER BOARD FOR \$100 BUS MICRO-

Fits in Vector-pak enclosures

Price: \$39.50

Vector



Universal Microcomputer/processor plugboard, use with S-100 bus Complete with heat sink & hardware 5.3" x

\$29.50

#### Please add sufficient freight. Any excess will be refunded

All prices good until March 1, 1979


#### DIP SOCKETS

Low profile tin plated 100+10-99 8 PIN 20 14 PIN 16 PIN 37 31 34 28 33 39 44 20 PIN 30 37 22 PIN 24 PIN 28 PIN 40 PIN 50 60 56 63 55 60 PIN 95 1-10 1-35

#### WIDE WDAR

WINE W			
	100+1	0-99	1-9
8 PIN	36	39	42
14 PIN	57	62	66
16 PIN	65	70	74
18 PIN	74	83	90
20 PIN	1-16	1-18	1-20
22 PIN	1-06	1-10	1-20
24-PIN	97	1-05	1-30
28 PIN	1-47	1-67	1-82
40 PIN	1-65	1-76	1-96

#### BRIDGE RECTIFIER

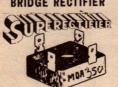

Motorola 35 AMP 100V P1V

CONNECTORS RS-232 DR25P

\$2.95

\*\*\*\*\*\*

male plug \$3.97 Hood \$1.90



DB25S female \$5.86

13.75

#### PROTO CLIPS 14 PIN \$4.50 16 PIN 24 PIN

40 PIN



CENTRES

Altair soldertail \$4.98 3/\$13.00

3 Level Wire 250 row \$4.98
3/\$13.00

Hexadecimal Keypad



19-key pad includes 1-10 keys, ABCDEF and 2 optional pad includes 1-10 keys and a shift key

Phone (03) 277 0622

#### HOBBY-WRAP TOOL-BW-630



 Battery Operated (size C) Weighs ONLY 11oz Wraps 30 AWG Wire onto (Standard DIP Sockets (.025inch)

(Complete with built-in bit and sleeve \$47.75


#### WIRE-WRAP KIT - WK-2-W WRAP . STRIP . UNWRAP

- Tool for 30 AWG Wire Roll of 50 Ft. White or Blue 30 AWG Wire

\$16.69

not

included)

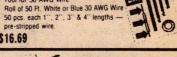

WIRE WRAP TOOL WSU-30

WRAP . STRIP . UNWRAP \$7.80

#### WIRE WRAP WIRE - 30 AWG

1000 ft, \$15.00 SPECIFY COLOR - White-Yellow-Red-Green-Blue-Black

#### WIRE DISPENSER - WD-30

- 50 ft roll 30 AWG KYNAR


\$4.80 ea. wire wrap wire

Cuts wire to desired length Strips 1" of insulation Specify - Blue-Yellow-White-Red

REPLACEMENT DISPENSER SPOOLS FOR WD-

Specify blue, yellow, white or red

\$2.60 spool

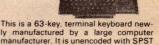

keys, unattached to any kind of PC board. A very solid molded plastic 13x4" \$39.50 base suits most applications. IN STOCK /each

## MOLEX CONNECTOR PINS

#### COMPUTER GRADE CAPACITORS



\$17.00 \$17.23 100,000 MF 10 Volt Mounting clamps to suit above 80 cents per set

LOGIC PROBE LP1 \$52.00

Compact, circuit powered. Detects pulses as short as 50nSec. Multi-Family Compatibility — DTL, TTL, HTL, CMOS.

STEWART ELECTRONIC COMPONENTS PTY LTD 33 SUNHILL RD, MT WAVERLY, VICTORIA

> Mon.-Fri. 9am-6pm Sat. 9am-12noon



All prices plus 15% sales tax. Plus freight

# The Apple-II system

The Apple-II is one of the latest generation of compact desk-top computers. Offering high resolution colour graphics and a variety of other features, it has become very popular in the USA and is collecting quite a following here as well. Here is a review of the Apple-II written by an experienced user.

#### by IAN P. PHILLIPS

Villanova College, PO Box 231, Coorparoo 4151.

There I was with several thousand dollars burning a hole in my pocket. I knew I had to buy three small computers, but what kind should I buy?

Much of the money was provided by a grant under the Special Projects Program of the Schools Commission for me to do development work in CAI (Computer-Assisted Instruction). The fact that I was using taxpayers' money was itself a heavy responsibility. I could not afford to be wrong.

I had another reason for not wanting to be wrong. For several years I had been sure that computers could be used as great instructional media. I didn't really want to teach students about computers, but rather to use computers to help students learn about English, chemistry, etc.

The machines had to be reliable, easy to operate, easy to expand. They had to be disarmingly simple in appearance and rugged enough to withstand the press of young, excited fingers. Repair facilities has to be readily available.

It was after I had actually ordered the Apples that I began to get the jitters. How could I have been so silly as not to order an S-100 machine? But I calmed my fears with soothing philosophical reveries about the precariousness of human existence, about the nature of judgement itself and about Apples.

The Apple-II Computer is, as it turns out, a very simple machine. It is a single-board computer based on the 6502 microprocessor. On that board is the 6502 and supporting circuits, 8k of ROM and sockets for 4k more, sockets for up to 48k RAM, complete video circuitry including two kinds of colour graphics, audiocassette interface, a two-inch speaker, a socket to accept the keyboard cable and a "Game I/O"

Here is the Apple-II together with optional colour TV receiver, floppy disc drive and video game controls. (Pictured by courtesy Computerland Australia).

socket. Also on the board is a "motherboard" section for the 50-line Applebus with eight connectors soldered in.

The case includes this main board together with a keyboard and a power supply. In Australia, the machine comes with a 240V power supply and with an extra board which converts NTSC colour to PAL colour. I bought our machines with 16k of RAM installed, and I could not recommend less.

The video output is uppercase only in 24 lines of 40 characters. In graphics mode you can have a grid of 40 x 40 little squares, each one being able to be set to any of 16 colours. Below this grid remain four lines of ordinary text display. In high resolution graphics mode

you can have a grid of 280 x 160 points

with four lines of ordinary text display.
I have been disappointed with the RF output and must recommend that video monitor be used. I believe that the colour is of no great value for anything except games, but that the high resolution graphics does have great potential. Apple Computer Inc is certainly doing a great deal to help simplify the difficult task of programming in graphics. Their latest version of BASIC allows such a statement as HPLOT 1,49 to 200,142 which plots a

line joining the two points.


The keyboard is sturdy and wellconstructed. However, the RESET switch is a key on the keyboard and it is adjacent to the RETURN key. Things have a habit of coming to a grinding halt at precisely the wrong moment because the student pressed RESET when he meant to press RETURN. It is such a poor design feature that I have at last decided to "do a hack" and shift

the RESET key.

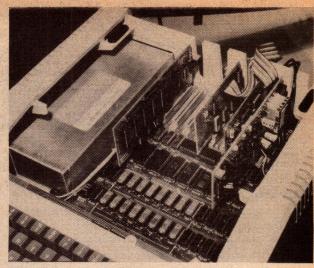The audio-cassette interface at 1500 bits per second is surprisingly fast and surprisingly reliable. If you are very







In the picture at left, the attractive young lady is the only item not available in an Apple system! Above is a view inside the Apple itself. (Courtesy Computerland).

careful about using the digital counter on the recorder, there should be no problems. I have students as young as 10 years old using the machines, and they can handle the cassette interface well. It is certainly the least convenient part of the system — but that is true for all computers of this class. We are waiting for the good fairy to provide discs.

The Game I/O connector is a 16-pin IC socket which provides four TTL lines out, three TTL lines in, a strobe, +5V supply and lines for four pots. It is one of the best features of the Apple. It is therefore a shame that it is so poorly located. It is virtually inaccessible if you have boards plugged into nearby connectors on the motherboard.

There are a number of plug-in peripheral boards already available for the Apple. The NTSC-PAL board comes as standard in Australia. There is a wirewrap prototyping or "hobby" board available from Apple for less than \$30. It looks like good value for anyone able to deal with hardware innovation.

There are two other boards available from Apple — a parallel printer interface and a 300 baud serial interface. They are particularly flexible and well designed boards, and very easy to interface to your software. But to my mind they are ridiculously overpriced at more than \$200 each. Happily there are independent manufacturers offering parallel and serial boards at very much cheaper prices. These do not offer quite the same ease of use as the boards manufactured by Apple, but the savings are considerable.

Another board available from an independent manufacturer is one that enables remote control of electrical devices by sending signals along the AC power line. Still another board enables the programming of 2716 EPROMs. These EPROMs can then, with an adapter, be plugged into the empty ROM sockets on the main board or into the sockets of Apple's own ROM/PROM board.

The Apple-II has considerable and useful software. The on-board ROM contains a cut-down BASIC, and a powerful monitor. Integer-BASIC is a very convenient piece of software, although limited to 16-bit integer arithmetic. In many other respects it is an improvement on standard BASIC. It allows variable names up to 100 characters long. It allows multistatement lines, it has strings and it has good debugging facilities. Its most convenient feature is that it is there when you power-up, and no glitch can overwrite even one bit of it.

Another version of BASIC, called APPLESOFT, comes on cassette. It occupies 10k of RAM and is the 6502 version of Microsoft BASIC, also known as Altair BASIC. Apple have added extensions, particularly in the area of graphics. It is a very good extended version of the language, with 9-digit precision. It is now available on a plug-in ROM board for \$120 (not bad for 10k!). We now have just one of these boards. It is great — when we get rich, we'll buy two more.

The on-board ROM includes a 2k monitor, plus a "mini-assembler". The monitor allows for examining and changing any memory location. You can move a block in memory, verify a block, read and write cassettes, trace and single step any program. You can set input/output ports, set normal or inverse video, and do hex arithmetic. The mini-assembler and dis-assembler are limited in scope, but very adequate for a surprisingly large number of purposes.

The Apple-II is, then, a very im-

pressive machine, one well-suited to being used in a CAI project. Our progress here is very slow, but that has more to do with the nature of the institutional process than with the Apple. My principal task is to persuade teachers with no knowledge of or interest in computers that such machines can be very useful tools. To this end, I have just completed a software package for the Apple which will enable the most inexperienced person to write quite powerful tutorials.

While the Apple-II is a great machine, life is never without its upsets. Our first one developed a puzzling intermittent fault. Our Sydney supplier, Electronic Concepts (otherwise known as Computerland) returned it to us early in June, unable to find the fault. Meanwhile we procured two more Apples from them, one of which never operated owing to a faulty IC. This machine was instantly replaced. The first computer was still causing problems and Electronic Concepts replaced it at the end of July.

I would be surprised if other purchasers of the Apple-II had as much bad luck as we had. But our experience would make me very wary of buying from anyone but a thoroughly reputable dealer with good repair facilities and plenty of stock.

What about those early jitters I had? Well, the Apple-II is still not S-100. Not only do I not have the jitters about that, but I now cannot remember what was supposed to be so great about S-100.

The best feature of the Apple-II is that it is a single-board machine and thus has greater inherent reliability. I love the BASIC-in-ROM, and the graphics facilities are superb. The Apple-II is not without flaws and it is not as cheap as the PET, but it is available off the shelf now and it is a very good computer. I wish we had a dozen, maybe if that good fairy.

# **Discount Components**

**SPECIALS** 

10 RED LEDS			ED LEDS			10 uA301		
7805			16			4N28		
7812			TAG STRIPS					\$1.10
LM317K						10 7490		
TIL209			REEN LEDS			10 74123		
10 BC547			LLOW LEDS .					\$2.90
IN4003			11			LED CLIPS .		
IN4002		10 74	LS00		\$2.00	10 723		\$4.50
						<b>医</b> "表演工作。		
301	40 1N4002		7437			30		1.40
307	65 1N4003	8	7440	30		45	4008	1.25
308	25 1N4004	9	7441			45		1.25
311		50	7442					
317K	DECICTOR		7448	95	74LS47	1.40		
318	25 1/2 Watt I.R.H. M	etal	7450		74LS48	1.50		1.30
3254	60 Glaze 1 ohm to 1		7453				4016	50
339	00		7454				4017	1.30
349	25 TRANSISTO		7460				4019	75
356			7472	45	74LS74	50	4020	
377	95 BD139		7473					1.35
380 14 Pin 1.	30 BD140	55	7475	65	74LS78	50	4023	25
381	95 2N3055	85	7476	45	74LS83		4024	90
387		25	7480			1.50		2.10
3861	.90 BC338	25	7485	. 1.45	74LS90		4027	80
555			7486			1.20		1.25
5651	.90 PN3643	25	7490	50		1.10	4030	40
566			7491	1.00				1.30
567		5	7492					1.25
723 (VR)	.50 100V	4.10	7494				4043	1.59
741	30 MDA3502 35A		7495	95		55		
3900		4.20	74100					
3909	.20 400V	4.50	74121	50	74LS125	1.90	4050	60
CA3028	.90 WO4 1.5A 400V .10 SCR	80	74123			1.50		1.20
CA31301	.95 C103YY .8A 60V		74150			79		1.20
CA3140 1			74151	1.10	74LS138	1.20	4060	2.60
RL41362	.90 C106D1 4A 400' C122D1 8A 400'		74153			1.90		
78051	01005 01 50011		74157	1.10	74LS153		4069	
7806	.20 I.C. SOCK		74160			1.60		40
7808		33	74164			1.90		40
7815	20 16 PIN	35	74165			2.20	4073	40
78181	.20 .18 PIN	50	74173			2.20		
7824 1 7905 1		75	74180	1.35	74LS163	1.20	4077	40
7906	.50 24 PIN	80	74192			1.30		40
7908	.50 28 PIN	1.00	74193			3.30		40
7912	.50 TTL		74221		74LS170		4510	
7915	.50 7400	25	74251	1.50				
78L05	40 7401	25	74368		74LS175	1.00	4519	95
78HGKC8	50 7403	25	74LS		74LS190		4520	1.45
78H05 7	.90 7404		74LS00	25		1.20		7.30
78H12	.50 7406	50	74LS02	25	74LS193	1.20	14584	
309K1	.90 7407			30		1.20		40
317K	7408		74LS04			1.20	74004	40
ОРТО	7410	25	74LS08	30		1.90		40
FND357 C.C 1 FND500 C.C 1	.30 7411		74LS09			1.90		
FND507 C.A 1	.40 7414		74LS11	30	74LS279	65	74C48	2.40
FND800 C.C 3	7416	60	74LS12		74LS365			1.20
RED LEDS			74LS14	35				1.35
100 for13	.00 7421	50	74LS20	30	74LS368		74090	
YELLOW	.30 7422		74LS21		74LS386	CMOS		
GREEN	30 7426	45	74LS22		4000	CMOS40	74C192	2.20
DIODES	7430	30	74LS27	30	4001	25		2.20
1N4148	5 7432	40	74LS28	40	4002	25	740221	
THE RESIDENCE OF THE PERSONS ASSESSMENT								

Minimum pack and post \$1.00 please stipulate if any items are out of stock that a credit be issued or the items to be backordered or an immediate refund be issued.

Send 40c stamp for copy of free condensed catalogue.

Open from — MON-THURS 8.00am—5.30pm;
FRI 8.00am—7.00pm; SAT 8.30am—12.30pm.

ALL GOODS ARE PRIME SPEC. FROM LEADING
MANUFACTURERS

MAIL ORDERS TO: P.O. BOX 135 NORTHCOTE, VIC. 3070 PERSONAL SHOPPING AT THE SHOP AT 499 HIGH ST NORTHCOTE. VIC. 3070.

Ideal for expanding D2 kits:

# Backplane, card cage & supply for 6800's

Looking for an elegant way to expand a Motorola MEK6800D2 evaluation kit, without spending too much money? If so, Stewart Electronic Components have some products which should interest you: a nine-slot backplane PCB with provision for active termination, a matching card cage, and heavy duty power supply components.

Probably the main item of interest is the model JBP680 backplane, a solidly-made double-sided PCB "mother board" with provision for up to nine of the 43/86 way edge connector sockets used by both the D2 kit PCB and those made by Motorola and others for Exorciser systems.

The backplane is a little unusual, in that the earthed groundplane is on the top or connector side of the PCB. This provides better shielding of the active bus lines and hence minimises radiation.

The PCB used for the backplane is of 2.4mm thick fibreglass, providing adequate mechanical strength. It also establishes a suitable characteristic impedance for the buslines, which act as microstrip lines in conjunction with the

earthed ground plane.

A further unusual feature of the backplane is that provision is made for active termination of the buslines. While this may seem to be "gilding the lily" where a relatively small system is concerned, the designer argues that the benefits are well worthwhile. In some notes sent to us with the sample backplane reviewed, he points out that even in small systems some form of busline termination is desirable in order to prevent subtle troubles caused by ringing.

If the only termination on the buslines is provided by device inputs, ringing tends to be produced because of the high input impedance. With TTL type devices the input impedance is


also non-linear.


Using a ground plane on the. backplane tends to further accentuate the problem, as this lowers the busline impedance.

The simplest way of providing some form of termination is to use pull-up resistors to the 5V line. This can give some improvement, but the resistors cannot really be made low enough for correct termination without absorbing most of the IOL current capability of the busline drivers.

Currently an alternative method is to use resistive voltage divider ter-minations, with each busline connected via a 360ohm resistor to the 5V line and a 390ohm to ground. This provides reasonable termination, but as each divider draws 6.7mA from the supply the total supply drain is significant

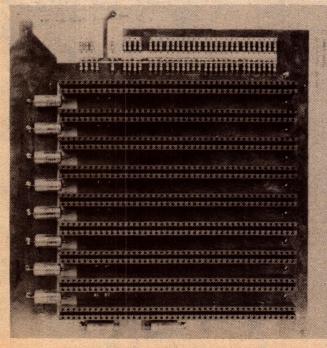A third and more attractive approach is to use active termination. This involves the use of a small auxiliary power supply to generate 2.6V at a very low source impedance. The buslines are then each connected to the 2.6V supply via a suitable series resistor, typically 2700hms, which forms the actual ter-



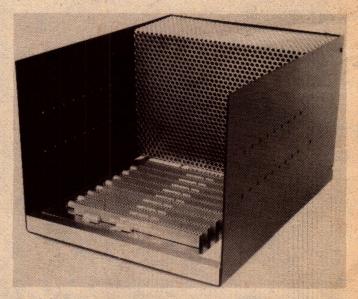

At left is the JBP680 backplane, with all edge connectors and other components fitted — including the series resistors in the active termination circuitry. Above is a view of the JCG680 card cage, with the backplane in position.

A Review of New Products and Literature from

National Semiconductor • Volume 5 No. 3

V to F!

F to V!

Standard

is Born

### One Part for Many Needs: Adjustable Voltage Regulators

3-terminal adjustable voltage regulators to provide you greater flexibility and the convenience of stocking only a minimum number of parts

LM117/217/317 1.2V to 37V LM150/250/350

1.2V to 33V 1.2V to 33V

1.5A In stock In stock 3A Available soor

Negative

LM137/237/337



In addition, these adjustable voltage regulators offer much higher performance than fixed voltage regulators, with internal current limiting, thermal shutdown and safe area compensation to make them virtually blowout-proof against overloads.

They also feature

- 100% electrical burn-in
- Line regulation .01%/V
- Load regulation .1%
- Ripple rejection 80 db

Send for the data sheets and find out how our adjustable voltage regulators can make life easier for you.

#### Silicon Software

How's that again? Silicon software? Yes, that's right. Our family of Maxi-ROMs -32K- and 64K-bit read-only memories - are the base upon which we're building a family of readily available software...canned soft-ware, if you will. Until now, the programs that we're loading into these large ROMs have been available to you and your system only by loading them from disk into RAM. So far, we've got two high-level languages canned and available

The first canned language, INS8295, is aimed at the control area, as typified by SC/MP-based (INS8060) systems. The INS8295 has loaded into it the 4K-byte, Na-tional Industrial Basic Language, which you already know as NIBL

The second canned and available language is the INS8298E Basic Interpreter for 8080-based systems. This 8K-byte language is perhaps better known to you as LLL—the Lawrence Livermore Labs Basic, a very general Basic package.

We're looking into other software packages, as well — Micro-Soft Basic, for example — because canned software is a powerful concept: anything heretofore loaded from disk into RAM can now be made available in the system, and immediately so. Besides saving valuable RAM space, canned silicon software greatly speeds program development. With it, you can communicate with a CPU in English, and with very simple statements. You need not know the CPU's architecture, nor need you be a sophisticated programmer. With canned software, if you can say, "When X happens, then do Y," you've got it made. 2

#### Stay on TOP of It

To insure that all your people have all the instruction they need for full use of your microprocessors, send them to NSC's regular courses offered on both the East

"Microprocessor Fundamentals" - for engineers/managers/technicians with little or no experience on computers. This 5-day course provides instruction on microprocessors and their applications, as well as extensive practical lab sessions on development systems and micropro-cessor programming. It costs \$495.

"Complex Peripheral Chips" engineers who already have system design experience but who need further information on application of the complex peripherals such as floppy disk, CRT and SDLC controllers. The course covers about 20 complex support chips and their use. It runs 3 days, has no lab sessions, and

"8060 SC/MP Applications" - for the design engineer who wants to know how to design a system with SC/MP or the 8060 microprocessor. Both hardware and software design techniques are discussed, in-cluding the NIBL language and the LCDS and USDI systems. This 5-day course in-cludes extensive hands-on time and costs

For details on specific dates, phone: (408) 737-6453 (West Coast) (617) 275-8530 (East Coast)

#### Need a Low-Cost Pressure Sensor?

Our LX0603GB and LX0603D - the first in a series of new monolithic pressure transducers — feature single-chip reliability at one-third the cost of previous semiconductor pressure sensors. The devices can provide differen-tial output voltage for full-scale pressure to ± 30 psi with the LX0603GB propor tional to gage pressures and th LX0603D proportional to differential.

In addition, these devices can boast a low supply voltage operation, higher signal-to-noise ratio, a separate temperature-sensitive output terminal, and easier interface circuit flexibility.

All of this comes in a small, light package with the same excellent linearity and hysteresis, temperature-compensated span voltage, high natural frequency, and low volumetric displacement. A special feature of the LX0603GB is that it can be used with most working fluids, including water

Of course, National, the leader in semiconductor pressure transducers, provides extensive environmental testing to assure lifetime stability while operating at 85% relative humidity and We can also provide a data sheet with complete specs and com-prehensive applications information. Ask about our new LX0603GB and LX0603D

#### We've E-x-p-a-n-d-e-d **Our Data Acquisition Line**

We now have FOUR single-chip data ac quisition systems, all available in military as well as commercial specs, all at low, low

Our latest entry is the ADC0808/0809 8-Bit A to D Converter, similar to our recent ADC0816/17 8-Bit A/D Converter, but

Fach of the 0808/09, 0816/17 devices con solidates an entire data acquisition system on a single chip — an industry "first." This allows direct access to 8 or 16 single-ended analog signals, eliminates the need for external zero and full-scale adjustments, and pro-

All four chips offer very high accuracy (1/2 minimal power consumption. And all four chips are now also available in military temperature ranges (-55° + 125°C) and specs. Check the data sheet for details.

Because these devices consolidate many

featuring 8-channel input (rather than 16) and a 28-pin package (rather than 40) for lesser requirements and a smaller package.

vides easy interface to microprocessors

bit for the 0808 and 0816) with high speeds. minimal temperature dependence and

functions on one chip, you save money. Because they come from NSC, a high volume producer, the price is right.

We have a new versatile building block — the LM131/231/331 Voltage to Frequency Converter — which gives you fantastic performance at a low cost. First, our LM131/231/331 acts as a V to F converter replacing a 14-bit A/D converter and sending data down long lines. But then it also acts as a F to V converter, transforming frequency to voltage at unbelievable linearity and precision.

**An Industry** 

This new industry-standard device operates over a 4-40V power supply with super-superior performance guaranteeing linearity to 0.01% max with temperature coeffi-cient ±50 ppm/°C ("A" version). In fact, you'll get eye strain trying to spot just how good the linearity and drift really are.

#### The TOTAL Approach

You can replace up to 50 ICs with one device, our INS8250 Programmable Asynchronous Communication Element, and save yourself a lot of board space and

Our INS8250 Programmable ACE provides total serial data input/output interface with your microcomputer in just one chip and in-corporates all those line control functions that previously needed hard-wired logic.

It includes a programmable crystalcontrolled Baud rate generator which works at any asynchronous speed from DC to 56K and requires only a single +5V power

It has complete MODEM-control capability and a prioritized processor-interrupt system that can be programmed to your requirements to save time

Our INS8250 can be used with virtually any processor in virtually any application because it's MICROBUS<sup>TM</sup> compatible. It's in stock now.

#### Whoosh! There We Go Again

We've just introduced a one bit-slice microprocessor that's so fast no one in the world can catch up with it. With speeds below 100 nanoseconds at regular power levels, it's half again as fast as our competition's functional equivalent.

What is it? - the new super-speed version of our fast 2901A - the IDM2901A-1.

Why is it so fast? — because it uses a new proprietary process called SCLIM which combines ECL and Schottky.

Look at the specs:

	Typical	Commercial	Military
Our Data:	25%	0°-70°C	55° + 125℃
	(5V)	(4.75-5.75V)	(4.5-5.5V)
A.B Inputs   Y Output	37ns	50ns	60ns
Cn Y Output	18	25	32
D Input   Y Output	20	32	40
Clock   Y Output	35	50	60
Minimum Clock Period	45	60	75
Read-Modify-Write Cycle	45	60	75
Then get there fa	est an	d first with	h our IDM
2001 4 1			2

## Static RAMs Run Rampant

Our Salt Lake City facility is now on-line and spewing out RAMs by the millions. We are now delivering huge quantities of our

MM2102A/MM2102AL 1K x 1 16 pin MM2114/MM2114L 1K x 4 18 pin MM5257/MM5257L 4K x 1 18 pin (a pin-for-pin replacement for the

All are available in standard or low power and in selected speeds from 200 to 450ns.
All feature single 5V supply (TTL compatible), TriState\* outputs for bus interface, and static operation. No clocks or refresh

National's high-volume production guarantees you competitive prices, so whether yours is a large order or a small one, check us



A Review of New Products and Literature from National Semiconductor

### We've Got It ALL TOGETHER

Integrated is the key word for NSC's new Development System - STARPLEXIN Starting with the single purpose of making life easy for the user, we specifically planned the software to meet the needs of the design engineer, programmer, or first-time user. Then we designed the hardware around the

By utilizing three built-in microprocessors, communication with STARPLEX 11 has been simplified. For instance, a"what-to do-now" manual has been built right into the ogramming. A single keystroke on the "Help" button gives the user instructions, in plain English, on the CRT terminal. This alone saves your design engineers hours of hunting through instruction manuals.

Another example — errors are immediately displayed on the CRT in easy-to-understand English, eliminating cross reference to a



#### Low Cost — Full Featured



Our new MA1020/MA1022/MA1023 series of LED clock modules offers a full spectrum of functions and features at a price that gives you more function-per-dollar than any other existing clock module.

Available in 0.84", 0.5" and 0.7" display heights, the MA1020/1022/1023 also features PM, Colon and Alarm indicators, Power Loss indicator, multiple 9-minute Snooze, "one-finger" Sleep setting, and easy-to-use "Fast" and "Slow" controls.


Your End Product or Application

Have Salesman Call YES

Also, there's 12 or 24-hour operation, direct display drive, battery back-up, 50 or 60 Hz operation...and the list goes on and on.

Applications for these very compact clock modules include clock radios, timers, alarm clocks, instrument panels, controllers, etc

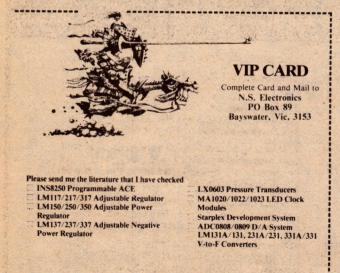Data sheets for our MA1020/1022/1023 series are available from National Semiconductor Corp. or your local sales rep, and the product is in stock now.



manual for decoding. Also, a debug program is already built in and can be activated by a single keystroke.

Need to make a few changes? A single stroke of the Edit key displays the text on the CRT Four arrow keys 11 -- help you locate the cursor blip on the problem area. Then one, plainly marked key instructs STARPLEXIM to insert a line or character, or delete, or scroll the page, etc.

We've planned for high-level computer languages too. The software includes FOR-TRAN, BASIC and Microassembly languages. One key stroke starts up any of the language processors.

Compact, modular, flexible, STAR-PLEXIMalso includes a thermal printer (50 characters per second), a main keyboard of 58 alpha-numeric ASCII keys, 38 additional keys, two 256K byte floppy disks, 64K RAM, and an optional PROM program-

Both the hardware and software are expandable to allow you to plug in your own previously designed programs or functions and to give you space for future needs

All of this at a price you wouldn't believe (\$13,800). STARPLEX<sup>TM</sup>— saves money and saves time.

#### High-Current, **Full Temperature** Range, Precision **Programmable Voltage** Regulators

National's LH0075 (positive) and LH0076 (negative) voltage regulators eliminate most or all external components usually associated with precision programmable sources

For example: Appropriate connection of its external pins makes available + 5, 6, 10, 12, or 15 V from the LH0075; and - 3, 5, 6, 8, 9, 12, 15, or 18 V from the L H0076. And these outputs are accurate to 0.1%

But if you insist on some other voltage, then one external resistor is all you need to set these regulators' outputs between zero and

The output current capability of both units is high – 200 mA. And if you'd like current-limited operation, simply add two more resistors to set the limit at any desired level between zero and 200 mA

Featured specifications include (for the LH0075 and LH0076, respectively): line regulations (typ.) of .008%/V and 0.005%/V; load regulations, 0.075% and 0.02%; ripple rejection, 80 dB and 70 dB.

Remote voltage sensing and programming are not only possible, but eminently prac-tical. And both regulators are specified over the full military temperature range of -55 to + 125°C; the LH0075 is also available in a 0° to +70°C version, and the LH0076 in a - 25° to + 85°C version. All are packaged in 12-pin, TO-8 metal cans.

# What's That, Neighbor?

You say you need a six-digit display about half an inch in size, and it's gotta be common cathode multiplex, and you need two mounholes, and you've been buying the DL6500 but thought you were sole sourced?

Well, you're not. NSC makes a direct replacement, a pin-for-pin equivalent, a "Yank-theirs-out-and-plug-ours-in." It's called the NSB5931 and it's available today. Contact your local Rep or Distributor.

#### There's More to LEDs Than Red



NSC has a full line of red lamps - but that's not all. We also make green and yellow ones. The following T13/4 size, high-efficiency lamps are now available in a new "A" version with higher light intensity, lower prices:

NSI 5252A Green Transparent Lens NSI 5253A Green Diffused Lens NSL 5352A Yellow Transparent Lens NSL5353A Yellow Diffused Lens

Featuring low power consumption and a doubled light intensity, these yellows and greens are a perfect complement to our NSL 5050 family red LEDs.

#### Recent Literature of Special Note:

AN203: Bit Slice Microprocessor Design Takes a Giant Step Forward with Schottky-Coupled-Logic Circuits

Linear A+, B+ Brochure BIFET IN and BIFET IN II Op Amp Brochure

Audio Radio Products Brochure

Voltage Reference Guide A Spectrum of IC Components for Minicomputers (Brochure)

Reliability of Schottky PROMs

Reliability of NMOS ICs (Brochure) Mil M-38510 Brochure

New or Newly Updated Catalogs

Available at a Small Fee: Memory Applications Handbook IDM2900 Family Databook Linear Databook

Data Acquisition Databook Memory Databook Discrete Databook

Interface Databook

#### We Know a Good Driver When We See One

National's DS3245 is a quad, bipolar-to-MOS clock driver with DTL/TTL-compatible inputs. Pin- and function-equivalent to Intel's 3245, our DS3245 is designed expressly to provide the high output current and voltage capabilities necessary to drive into the high capacitance of large, N-channel MOS memory systems. And it drives such loads at high speeds, using Schottky-clamped transistors. In addition, PNP transistors are used to minimize input

Even though the DS3245 requires only two A Review of New Products and Literature from National Semiconductor

power supplies - 5 Vdc and 12 Vdc - our design does not compromise the high VOH spec common to other, three-supply circuit

Further, the design offers memory system protection via an internal fail-safe circuit, which forces all outputs to their low state should the 5-Vdc supply be lost.

Other features of the DS3245 include two common enable inputs, a refresh input, and a clock control input for simplified system designs

NAME

COMPANY

NO

PE

Please print clearly; this information will be used for our mailing list.

#### BACKPLANE, ETC FOR 6800 SYSTEMS

mination impedance.

The idea of the 2.6V supply is that this voltage is just above the minimum "logic high" level for TTL type devices. As a result the current drain from the termination supply is very low in the logic high and Tristate (high impedance) conditions, and only significant in the low condition. Average current is therefore quite small.

In addition to the provision for active termination, the JBP680 backplane also provides for up to 8 bypass capacitors on the main 5V supply line, and a bypass capacitor on the + and —12V lines. These features should make it very suitable for expanding D2 kits or similar small Motorola 6800 systems, while retaining maximum performance and reliability.

You can buy the backplane in either bare-PCB or fully wired up versions, the latter with all nine sockets fitted.

latter with all nine sockets fitted.
To go with the backplane Stewart Electronic Components has available a matching card cage, model JCG680. This measures 356 x 269 x 210mm, and is made from 2.4mm thick aluminium sheet finished in black anodising. It comes with support rails for the backplane, and a perforated steel cover for the power supply compartment at the rear.

The sides of the cage are provided



Steward Electronics' type JDt2 power transformer, which provides 8V at 24A and 2 x 15V at 1.5A.

with holes for card guides, which are available separately in pairs.

Also available are a variety of power supplies and supply components. There are four complete power supplies, each of which is available either in free-standing form or in modular form suitable for mounting in the JCG680 cage.

Smallest supply is the JPS001/JPS011, which provides 5V at 5A and +12V at

1A. Then comes the JPS002/JPS012, providing 5V at 10A and +12V at 1A. For bigger systems there is the JPS003A/JPS013A, rated at 5V/24A, +12V/1.5A, -12V/1A and -5V/500mA, or the JPS004/JPS014 rated at 5V/24A, +12V/1.5A and -12V/1.5A. In each case the second type number applies to the bolt-in module version.

Features of all supplies include over voltage crowbar protection, adjustable current limiting, soft-start on the 2.6V termination bias supply rail, and remote sensing capability.


Components available separately include power transformers, reservoir capacitors and power supply PCBs, etc.


Price of the JBP680 backplane in PCBonly form is \$39.00, or \$103.00 for the fully built-up version. The card cage metalwork is \$33.95, plus 50c per pair of card guides.

Prices for the built-up power supplies are \$106.07 for the JPS001/011, \$176.00 for the JPS002/012, \$225.50 for the JPS003A/013A and \$220.38 for the JPS004/014. The power transformers range from \$7.50 to \$28.60, the latter for the JDt2 offering 8V/24A and 2 x 15V/1.5A.

All of the above prices are plus tax, if applicable.

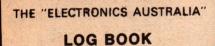Further information on all of these products is available from Stewart Electronic Components, 33 Sunhill Road, Mt Waverley, Victoria 3149. Telephone (03) 277 0600.



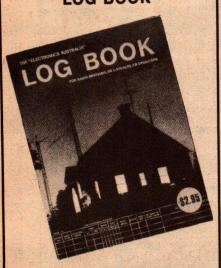

FOR: RADIO AMATEURS
DX LISTENERS
CB OPERATORS
\$2.95 (Includes postage)

From "Electronics Australia", 57-59 Regent St, Sydney, or P.O. Box 163, Beaconsfield 2014.

# BYTE SHOP

Melbourne: 17 Arawatta St., Carnegie 3163. Phone: (03) 569 7867, 568 0642 Canberra: Cnr. Colbee Crt. & Townshend St., Phillip, 2606. Phone (062) 82-2523

SYSTEMS MEMORY Z80, 8080 and 6800 based.

RAM - 8, 16 & 32K

ROM - 4, 8, 16 & 32 utilizing 2708 or 2716.

INPUT/ OUTPUT 5" mini floppy, 8" Persci dual floppy, 8" IBM compatible floppy; cassette; VDUs; Keyboards; paper tape readers: printers; monitor.

SPECIAL PURPOSE

Prototyping boards; digital to analog converters, data acquisition, PROM programmer, speech recognition, speech synthesizer, music synthesizer, interfaces built to your requirement.

HARDWARE

Transformers (suited to S100 bus supply), bridge rectifiers. low profile IC sockets, special components, S100 sockets and guides.

SOFTWARE


BASICS, FORTRAN IV and COBOL, Macro Assembler, Assembler/Disassembler, Disc operating systems, Word processors, Inventory, Data Base Management.

KILOBAUD

U.S. magazine — understandable for beginners, interesting for experts. New readers only send \$3.00 for a copy now.

Send \$1.00 for quarterly newsletter per annum charge, and \$5.00 for quarterly product and price updates.

BYTE, P.O. Box 156, Carnegie, Vic. 3163

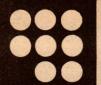

# abacus

# MELBOURNE'S FIRST TRUE COMPUTER STORE



#### Soroc IQ 120

- Cursor Control Kevs
- Numeric Key Pad
- Line and Page Erase
- Addressable Cursor
- Switch Selectable Transmission from 75 to 19.200 bps
- Communication Mode: HDX/FDX/Block
- Interfaces: Printer Interface/RS232 Extension
- RS232C Interface
- Non-Glare Read Out Screen
- Protect Mode
- Tab

#### Soroc IQ 140 ILLUSTRATED

a price/performance breakthrough in professional terminals All the capabilities of the IQ 120, plus a

score of user-oriented features. Screen edit, status/mode conversion, wrap-around insert/delete. reverse video are just a few. Controllable from 16 function keys on the detachable keyboard. Limited availability so

- order now. status/mode indicator line on screen
- printer port & block mode
- switch-selectable baud
- rates, 110-19200
   field protect, dual intensity
- polling capability optional



#### 4 MODELS TO SUIT ALL REQUIREMENTS

M110A MODEL \$985.00

- CPU: Z80
- Memory: 4K ROM (max 8K) 16K RAM (max 32K)
- Full ASCII Keyboard & 20 BASIC command keys.
- Audio Cassette controller 2 channel.
- CRT moniter controller.
- RS232C interface.
- 8 bit digital I/O
- Journal printer interface.
- 2 octave output speaker.
- Digital clock.
- 8 bit 2 channel A/D converter & joystick.
- S100 bus signal edge connector

M110B model \$1281.00 Same as above plus an additional 16K of RAM.

M170A \$1527.00

- Includes all of M110A model
- black and white TV monitor (24 lines x 64 characters)
- one cassette unit
- power supply box M170B \$1822.00 Same as M170A model plus an additional 16K of RAM.

OPTIONS

- S100 BUS extention cabinet
- Colour Graphic (256 x 192 dots) display monitor
- Colour TV monitor

#### DIGITAL



**BRAND NEW** LA36

IQ 120

\$1245

IQ 140

\$1850

Decwriter II keyboard printer terminal

LA36

- \$1625.00

LS120 - \$2825.00 LA180 - \$2325.00

VT100 - \$1865.00

#### WE NOW HAVE THE OHIO SCIENTIFIC COMPARE AND BUY

#### CHALLENGER 1

Superboard	\$335
Complete 16KB	
and Mini Floppy	\$1 428

#### CHALLENGER 2

 20kB and Mini Floppy
 32kB % December 1 \$1.840 32kB & Dual 8" \$3.116 CHALLENGER 3

#### • 48kB dual 8" floppy \$6,108 With 74M byte disk \$13,680

#### SOFTWARE

**BUSINESS APPLICATIONS** AND MANY OTHERS

WE HAVE SYSTEMS FOR THE BUSINESS MAN UP AND RUNNING. A DEMONSTRATION IS JUST A PHONE CALL AWAY.

WE WILL ALSO BE OPENING IN SYDNEY SOON. WATCH OUR ADS FOR MORE DETAILS.

#### CONSUMABLES

PAPER & CASSETTES FLOPPY DISCS (5") \$4.60 ea. FLOPPY DISCS (8") \$4.80 ea. DIGITAL CASSETTES TAPES ALSO COMPUTER PAPER, DISC PACKS. MAG CARDS, TAPE CARTRIDGES, ETC.



#### **BOOKS & MAGAZINES**

Obviously we've run out of room to list all our titles but we do carry all the current magazines and many, many books.

Plus: LOTS LOTS MORE

# **ABACUS COMPUTER STOR**

TEL (03) 429 5844

512 BRIDGE ROAD, RICHMOND 3121 **TELEX: 35621** 

TEL (03) 429 5844

ALL QUOTED PRICES ARE EXCLUSIVE OF 15% SALES TAX.

# A low-cost EPROM eraser

Erasing an EPROM is basically quite simple, but some problems can occur. In this article we present details of a simple, economical eraser, as well as some hints on how to use it.

by DAVID EDWARDS

2708 EPROMs are the most commonly available user-programmable and erasable "read-only" memory devices used by hobbyists and small industrial users. Erasure is achieved by irradiating the chip itself, through the window provided, with intense ultra-violet radiation.

The radiation must have a wavelength of 2537 Angstroms, and the required dosage is 15 watt-seconds per square cm. Commercial erasing devices

are available which include suitable light sources and exposure timers, but these are rather expensive, and beyond the financial reach of most enthusiasts.

Fortunately, suitable UV lamps can be purchased locally, and allow a quite practical eraser to be constructed for about \$30.00.


The lamp in question is a Philips type, from their range of germicidal tubular lamps. The model number is TUV 15W (catalogue number 57415 P/40). This is a

low pressure mercury vapour lamp, similar to a standard fluorescent lamp, but without a phosphor coating, and using a special glass which transmits the ultra-violet light with low attenuation.

Almost all of the energy from this

Almost all of the energy from this lamp is concentrated about the requied 2537 Angstrom line. Incidentally extreme caution must be used with this type of lamp, as the light can cause eye and skin diseases.


Order the tubes, along with a

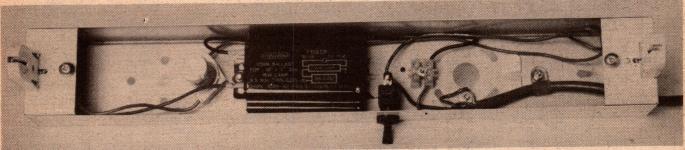

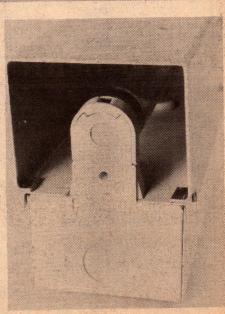TOP & BELOW: These three views show the UV light source at various stages of assembly. Devices to be erased are placed under the tube for 30 minutes.







The ends of the top cover are bent so that it sits naturally on the batten.

HANDS OFF THE T.V. SET

# Video Games

# A Major breakthrough in portable electronic fun

It's only natural. Television affects our lives in an extraordinary number of ways. It is today's major communication vehicle with the world. Innovative scientific efforts have expanded the possibilities of the television receiver console. Teletext, home computers, and programmable video games are just some of the more recent examples.

#### THE VIDEO TRAUMA

Perhaps most obvious has been the use of television receivers for the playing of video or television games. These games which utilised dedicated chips, often caused family frictions during prime time viewing hours as siblings fought to secure the use of the monitor either as a VDU (visual display unit) for game use, or to watch a desired programme on the favourite channel.

#### THE DISCOVERY

MATTEL Scientists realised the possibilities. Using a combination of available microprocessor technology and special miniature circuits, they were able to develop a sophisticated, challenging, portable video game that did not even need a television set.

#### THE CHALLENGE

These little microprocessor marvels are technological lightweight you can carry them in your hand, take them out with you to picnics, long car rides, or just sit in the corner while others are watching their favourite television programme.



#### THE EXCITEMENT

Beat the Clock!

Shift into first gear and you're off. Dodge the oncoming cars or watch out. You've got just ninety-nine seconds to complete four laps of the electronic track. Hear the roar of the crowd — GO!!

# ELECTRONIC VIDEO EXPERIENCE

These Electronic Games are the latest in a series of space age non video, video games, and are backed by the world wide Mattel organisation, so that you may have confidence in the high quality of the product.

In those rare cases where service may be required, simply mail the Electronic Game in its original packaging to our service by mail centre, at the address shown below.

To order your Electronic Car Race or Missile Attack simply send your cheque for \$27.95 plus \$1.50 postage and \$34.95 for Basket Ball, plus \$1.50 for postage, handling and insurance to the address shown below.


Send order to: Offer 75/78, Mall Order Dept., G.P.O. Box 4000, Sydney 2001.

Mattel Video Game Offer 75/78	8
Name	
Address	Control of the Contro
	CONTRACTOR OF THE PARTY OF
P/codeState	
Please send	
I have enclosed \$	w 4 weeks
for delivery.	EA 1.79

suitable 460mm batten and 15W ballast and starter, from your local electrical retailer. At the time of writing, Circuit Components (A/Asia) Pty Ltd, of 383 Forest Road, Bexley, NSW 2207, have stocks of lamps and suitable

As you can see in the photographs, we were able to use the batten direct, with only minor modifications. We
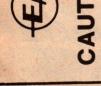
> CAUTION: UV LIGHT IS HARMFUL TO EYES AND SKIN 2537 °A ULTRA-VIOLET LIGHT SOURCE KEEP COVER ON WHILE IN



PROTECT YOUR EYES: Make two copies of this warning panel and attach them to the batten and to the top cover.

fitted rubber feet to the bottom, and a three-pin mains plug and suitable flex.

In order to minimise the radiation hazard, we fashioned a U-shaped aluminium lid. If desired, this could be hinged to the batten, and a microswitch fitted so that the tube is only energised

when the lid is in place.

We made up a suitable warning label, which we fixed to both the batten and the lid. A copy of this label is reproduced with this article, and should be used with any erasor. It can be either copied, or cut out and used directly.

In use, the EPROMs are simply placed on the top of the batten, underneath the tube, and the cover placed over both the tube and the chips. At

least 15 devices can be erased at once.
The energy output of the TUV 15W tube is specified as 3.5W and, assuming that the chips are placed 25mm from the centre of the tube, we have calculated the energy intensity at the chip surface as between 1.6 and 5 mW/cm<sup>2</sup>, depending on the efficiency of the reflector.

This translates to an exposure time of between 15 and 50 minutes, so a good compromise would be to expose for half an hour. Under-erasing should be avoided, as this may cause problems in programming. Over-erasing is not advisable, but should not cause any problems.

Timing of the exposure is not very critical. You can use either a wristwatch or clock, or a mechanical kitchen timer

can be pressed into service.

Finally, we would like to point out that although the TUV 15W tube cannot be used to expose Scotchal lightsensitive aluminium and similar products (the wavelength is too short), suitable 15W actinic tubes to fit the batten can be obtained. This may permit expansion of the uses to which the eraser can be put, and hence offset some of the cost.

Electronics is going ditital. This book can help YOU go right along with it.

#### AN INTRODUCTION TO DIGITAL ELECTRONICS

You don't need any previous knowledge of digital electronics the book starts you right from scratch, and covers all of the basic concepts you need.

Available from "Electronics Australia" 57 Regent St, Sydney. PRICE \$3.50 OR by mail order from "Electronics Australia", PO Box 163, Beaconsfield, 2014. PRICE \$4.10.

# **Economic Digital Control** Pty Ltd

# announce their PRE-OPENING SALE

Compu			Price off basis
compo	nents	A	UII Dasis
2102	RAMS		\$ 1.50
2114	RAMS		\$14.60
2513	U/Case,	dual suppl	y\$10.00
2708	<b>EPROM</b>		\$13.00
6502	CPU		\$13.25
63 key	unencod	ed keyboar	d\$45.00
19 key	y keypad	unencoded	\$15.00
	- 9 + AE		

- Prices do not include Sales Tax.
- Minimum order \$30.00, include your full address and telephone number.
- Money with order basis only.
- Bankcard Number may be sent.
- Discounts available on Quantity basis.
- Send us a shopping list and we will send you our prices.

FOR ORDERS AND ENQUIRIES WRITE TO:

> **Economic Digital** Control Pty Ltd PO Box 817, Crows Nest, NSW 2065. Telex aa20149.

# INCREDIBLE BUT TRUE Near half price! WASP CB reduced to SAVE \$60 THE CB BARGAIN OF THE YEAR! Thousands of these advanced Wasp CB's from Dick Smith sold for \$129.50 - now look at the price. Hurry - this

# Huge savings on SIDEBAND sets



#### HORNET MOBILE

The set with a sting reduced to a price that won't hurt!

LED readout, maximum legal power. Save an incredible \$100!

Cat D-1720 HURRY!

#### SCORPION BASE

HURRY IN FOR YOUR WASP NOW!

Designed and built as a base station: 240 & 12 volt operation, large 'S' & power/SWR meters, LED readout: Save \$50.00 NOW!



Cat D-1520

# PRICES SLASHED ON CB ACCESSORIES T

RUSH THESE - AT SUCH LOW, LOW PRICES THEY WON'T LAST LONG.

#### DELUXE ALTERNATOR FILTER

Ferrite core - for really tenacious alternator whines. Cat. A-7926 WAS \$9.50 SAVE \$3.00 NOW \$6:50

#### WHITE FLASH HELICAL ANTENNA

The famous 'top adjust' helical allteling \$29.00 \$ 19:50 Now \$19:50

Simply clips on the rain gutter of any vehicle. Complete with lead & plug. Cat. D-4411

#### MAGNETIC BASE ANTENNA

Centre-loaded, stainless steel construction with strong magnetic base. Lead & plug included. Cat D-4412

### WAS \$22.50 GAVE \$6.00 NOW \$ 19:50

#### CB/FM/BC ANTENNA

Three antennas in one! Locks down when not in use. All Three antennas in one! Locks down when the connecting cables and fittings supplied. Cat. D-4418

WAS \$32.50 SAVE \$3.00 NOW \$29:50

**ELECTRIC CB/FM/BC ANTENNA** Similar to D-4418 above with the added convenience of

electrical operation controlled from dashboard switch. Cat. D-4419 WAS \$65.00 SAVE \$15.55 \$49:50 WHITE NIGHT TOP LOADED ANTENNA

roof mount base, trunk tip mount, cable & plug. Cat. D-4452
WAS \$29.50 SAVE \$11.00 NOW\$18:50

#### MAGNETIC BASE

Uses a powerful base so no need to drill holes in car roof. Nylon gasket prevents scratching. Cat D-4622
WAS \$25.00 SAVE \$9.50 NOW \$15:50

is your last chance to buy at this incredible bargain price. Next shipment must at least double (even treble) in price as a result of import duty and deteriorating exchange rate.

#### **ANTENNA MATCHBOX**

Connect into antenna lead. By adjusting four knobs virtually all mismatch between antenna and rig can be eliminated. Cat..D-5512 WAS \$15.00 SAVE \$2.50 NOW \$12:50

#### **CB ANTENNA ELIMINATOR**

Enables you to use your car radio airial for your CB and car radio. Cat. D-5516 WAS \$29.50 SAVE \$5.00 \$24:50

#### SWR/POWER/FIELD STRENGTH METER

Get the best out of your rig by ensuring antenna is SWR'ed properly & transmitter is putting out maximum legal power. Cat Q-1352 WAS \$21.50 SAVE \$6.00 NOW \$15:50

#### 27MHz TESTER

A must for CB servicemen & serious CBers. Measures SWR, power, modulation, field strength, checks crystals too.

Cat. Q-1380 WAS \$59.50 SAVE \$10.00 NOW \$49.50

Mail Orders? Certainly! Add the following amounts for delivery: Order value \$5.00 -\$9.99 P & P \$1 \$10 - \$24.99 P&P\$2: \$25 - \$49.99 P&P\$3; \$50 - \$99.99 P&P\$4; \$100 or more P&P\$5.50



125 York Street, SYDNEY. Ph. 290-3377

147 Hume Hwy, CHULLORA. Ph. 642-8922 162 Pacific Hwy, GORE HILL. Ph. 439-5311 30 Grose Street, PARRAMATTA. Ph. 683-1133

MELBOURNE 399 Lonsdale Street, MELBOURNE. Ph. 67-9834 BRISBANE 166 Logan Road, BURANDA. Ph. 391-6233

656 Bridge Road, RICHMOND. Ph. 42-1614 ADELAIDE 203 Wright Street, ADELAIDE, Ph. 212-1962 SHOPS OPEN 9AM to 5 30PM (Saturday 9AM - 12 noon) BRISBANE 1/2 Hour earlier

ANY TERMS OFFERED ARE TO APPROVED APPLICANTS ONLY

Many lines available from the lick Smith Electronics Centre



MAIL ORDERS P.O. Box 747, Crows Nest, N.S.W. 2065. Post and packing extra.

Dealers across Australia.

# the Australian CB SCENE



#### AT THE CROSSROADS: WHAT'S AHEAD FOR UHF CB?

All the indications are that UHF CB is at the crossroads. Right now, nobody can be quite certain whether it will plod along in a minority role "down under" or head off to a large scale success both here and overseas.

by NEVILLE WILLIAMS

When Philips-TMC took up the challenge of UHF CB a couple of years back, the portents for success were most favourable.

Philips had a development and manufacturing facility dedicated to 2-way radio communication, and considerable experience with professional UHF equipment. It would not be too large a step to divert some of that expertise to the design and production of a mobile UHF transceiver for the proposed 470MHz CB band.

Indeed as the project actually began to take shape, Philips-TMC management saw in it an opportunity to rethink their overall production approach, taking advantage of the potentially greater factory through-put. Automation and other techniques, invoked for a new CB venture, could ultimately find their way into established

production lines.

And the Federal Government certainly liked the idea. Largely through neglect in the preceding decade, they had been pressured into legalising CB on 27MHz, thereby inheriting the consequent problems already familiar on the American scene. They were nothing, if not willing, to add the 470MHz option and to spell out regulations which would make it the only legal CB band after June 1982.

Twelve months ago, the planning became a reality, with the Philips-TMC FM320 transceiver on sale at just over \$300 per unit, backed by guarantees and a provisional national network of service facilities.

To those inclined to be cynical about local production efforts, release of the FM320, more or less on schedule, was notable in itself. Even more so was the fact that the selling price was not too far removed from the original prediction of: "around \$300, complete with antenna". This, at a time when most other prices were tending to skyrocket!

It led quite a few to speculate as to how Philips-TMC could produce a completely new and unique transceiver, with up-to-the-minute facilities and sell it for that kind of money. Having in mind the development costs, they surely could not be making any money on it!

I have every reason to believe that they weren't, nor did they expect to in the short term. The price had to be low enough to attract the up-market buyers who would inevitably become disillusioned with conditions on 27MHz, even assuming the best available SSB equipment. The ultimate reward would come from economies of scale as production built up.

Over and above that, Philips worldwide had a stake in the venture. If their team in Melbourne — design leaders in this field — could demonstrate a production-proven UHF CB transceiver, it would give the whole organisation an advantage in pioneering UHF CB in other countries.

Unfortunately, as we said at the out-

set, just when UHF and the FM320 should be on the high road to success, it is hesitating at the crossroads.

Why?

The most significant factor is what has happened in the meantime to 27MHz CB, which the FM320 was designed to

supersede.

At the time when the FM320 was under development, enthusiasm in Australia for CB-style communication was unbounded. It was the "in" thing, particularly at a youth and young family level. Illegal or not, suppliers couldn't get stocks fast enough to meet the demand.

One did not need a crystal ball to foresee that the channels would become hopelessly choked; that those who wanted deliberate, rather than casual, communication would look around for an alternative that offered predictable performance, even if it meant a modest increase in cost over then current up-market 27MHz equipment.

In the December '77 issue, carrying



Designed expressly to meet specifications laid down by the Australian P&T Department, this Midland prototype model 13-405 passed readily through local acceptance tests. Whether it is ever launched on the market depends on Dick Smith Electronics — or somebody else — signing a quantity order that will get production under way.

# RADIO PARTS GROUP

### AND NATIONAL SEMICONDUCTOR COMBINE TO OFFER THE BEST PRICED DIGITAL WATCHES IN AUSTRALIA

QUARTZ LCD DIGITAL WATCHES FROM NATIONAL SEMICONDUCTOR



STANDARD MODELS D.A.D. WS \$23.88 Chrome with strap YS \$30.23 Gold with strap WB \$30.23 Chrome with bracelet YB \$32.51 Gold with bracelet



DELUXE 6 DIGIT MODELS DRK WB Chrome with bracelet \$46.52 YB Gold with bracelet



CHRONOGRAPH DBSWB-98 Chrome with bracelet \$44.48 with lapsplit timer, day/date indicator



MEN'S ALARM DBSWB-14 Chrome with bracelet **\$57.57** 



STANDARD LADIES KEKWS

Chrome with strap \$27.95 YS Gold with strap \$30.23 WB Chrome with bracelet \$30.23 YB Gold with bracelet \$34.27



DELUXE LADIES Kel WB Chrome with bracelet \$46.51

PLEASE SEND ME THE FOLLOWING .....

I AM ENCLOSING CHEQUE . MONEY ORDER . OR PLEASE DEBIT MY BANKCARD NUMBER..... SIGNATURE

......

NAME (BLOCK LETTERS) ADDRESS .....

DISTRIBUTED BY:

# Radio Parts Group

562 SPENCER STREET, WEST MELBOURNE (03) 329-7888 1103 DANDENONG ROAD, EAST MALVERN (03) 211-8122

# The Australian CB SCENE

pictures of the first production batch of FM320s, Dick Smith Electronics was offering their "Australianised" 27MHz "Scorpian" SSB unit for \$299.50 and their "Hornet" SSB for \$259.50. EMI had just announced their "Roadhound" AM/SSB for \$239, while the "Electrophone" from the Radio Parts Group was listed at \$249.63.

Against these figures, \$300-plus was indeed a modest increase.

But, shortly afterwards, the bottom fell right out of 27MHz CB, due in part to the overcrowding that had been predicted. But the position was aggravated by bad publicity, both local and overseas, which discredited CB and alienated many of the potential upmarket buyers. Instead of turning from 27MHz to UHF, they simply rejected CB altogether!

The nett effect on the CB market was disastrous, importers found themselves with tens of thousands of 27MHz transceivers in stock, in bond or on the water, which they had no hope of clearing in the normal way. So, during 1978, prices began progressively to

collapse.

Profit margins were cut drastically, then eliminated altogether as marketers sought merely a recovery of capital. They even began to sell below cost rather than be completely ruined by dead stock and by interest and other changes. In the extreme, CB gear changed hands for as little as half the logical selling price and the message around the industry was: "CB has had it!"

In the event, Philips-TMC found themselves with an industry and a marketplace that was thoroughly "browned off", and trying to sell against a product that was in gross oversupply both here and overseas. Against the ruling clearance prices, the FM320 CB now looked "too expensive".

Faced with a drastic slow-down in sales, Philips appear to have switched their selling emphasis right away from the once magic letters "CB". Indeed, at the most recent Bathurst 1000 car races, the array of FM320 advertising signs had a quite different emphasis: "Per-

sonalised 2-way Radio".

In a way, instead of feeding a product into a capacious CB pipeline, the company now faces the task of establishing a new market, still nominally CB, but in reality "personalised 2-way radio". They have the lonely job of reenthusing all those buyers who thought it would be nice to have 2-way radio but who could not justify the expense and hassle of a formal commercial

Because it is a lonely job, Philips would obviously welcome some com-

## The Australian CB SCENE

petition and additional promotion for the 470MHz band. In fact, their wish seemed to have been met when Dick Smith Electronics received a prototype of a 40-channel Midland transceiver, developed expressly for the Australian UHF CB band. Provisional pricing indicated that, allowing for duty, etc, it could be marketed at about the same recommended retail figure as the FM320.

It arrived, complete with specifications and test data and, when submitted to the North Sydney Testing Laboratory of the P&T Department, it apparently met all type approval requirements without difficulty.

Dick Smith claims that, in important respects, it betters the performance and specifications, of the FM320 and, certainly, when we opened it up in our own workshop, there was little to suggest that it was a prototype. Presumably, Midland could put it into production with a minimum of delay.

However, the word seemed to be that Dick Smith is unwilling to place an order for what would have to be a substantial production batch. He still has a lot of capital tied up in unsold 27MHz equipment and is naturally hesitant to make a further substantial investment in what may turn out to be a rather slow moving line.

"After all," says Dick, "we do sell the FM320, and it's there for anyone who wants the relative privacy of UHF CB.

"I just don't accept that splitting the market at this stage would improve matters for anybody."

In the meantime, what do Philips say? Officially, very little but, from "unofficial" conversations I gained firm assurance on two points:


There was no foundation whatever for the rumour that Philips-TMC intend to abandon the FM320 and UHF CB. Production will continue at whatever rate is necessary to meet the market demand.

 There is no present intention to increase the recommended retail price for the FM320. Philips will simply spread recovery of development costs over a longer period.

In fact, the emphasis was on the longterm view. Philips are certain that the UHF band will experience increasing usage as citizens realise its very real advantages, and as they - and the industry - get over the mental and financial blocks created by 27MHz CB during 1978. And, of course, interesting developments on UHF still lie ahead in America and on the continent.

But the hiatus will exacerbate the Federal Government's problem with the existing 27MHz CB band. Their stated and still official policy is to

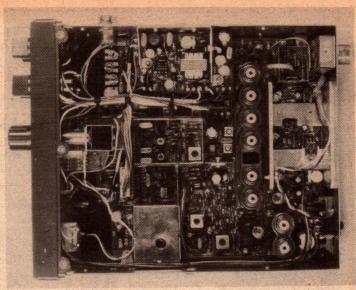The Midland 13-405 UHF CB transceiver gives the impression that, with a minimum of further development, it could go straight into production. Perhaps Midland also have an eye on UHF CB in countries other than Australia!



withdraw all licences for 27MHz-CB on July 1, 1982. It always would have been a tough decision to implement but, by setting the cut-off date five years ahead, there was the hope that imports of 27MHz equipment would have dried up spontaneously and that the UHF alternative would have become entrenched and popular.


But we enter 1979 with importers still holding large unsold stocks of 27MHz gear and with UHF CB in the doldrums. The Government may not find too many supporters as the critical date approaches — rather a quarter million 27-meggers screaming "leave us alone".

Other complications for the Government include whatever may emerge from WARC '79 and their undertaking to amateurs that their access to the 27MHz band would be restored on July 1, 1982

Significantly, it was a member of Parliament, Mr David Jull, who advised amateurs at the WIA Queensland Division convention to keep pressure on the Government, in case it should feel tempted to back off from the earlier decision.

One would feel really sorry for the parliamentarians if they weren't so well

## NOTICE Ham Radio Dealers

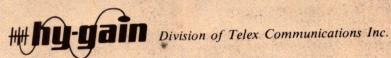

**nu-uain** the world's finest range of amateur antennas, will shortly be available from Audio Telex Communications Pty Ltd.

We will provide:

- Advertising support
- Parts back-up
- Direct delivery
- Point of sale information, displays, etc.
- Audio Telex Service and stock holding in Sydney, Melbourne and Brisbane.

**114-4311** is a profit earner because it performs, and with Audio Telex support will continue to be the first choice for amateur users throughout Australia.

We are seeking additional trade outlets to market hu-main in 1979. Please write:

## AUDIO TELEX COMMUNICATIONS PTY. LTD.

54 ALFRED STREET, MILSONS POINT, 2061 Telephone: 929 9848



## SUPERB KITS from DENMARK



Additional high quality kits coming soon!

JOSTYKIT is Europe's leading manufacturer of electronic kits featuring attractively styled boxes of Scandinavian design and high quality electronic components which will satisfy the most demanding kit builder.

JOSTYKIT's staff of qualified electronic engineers and educationalists supply up-to-the-minute, reliable electronic kits, designed around space-age solid state technology, but capable of construction without any great technical know-how or practical experience.

The JOSTYKIT instruction booklets supplied with each kit give clear, precise directions for assembly and testing. For those with special technical interests, each instruction booklet ends up by describing how the kit works. You'll always learn something when you construct a kit from JOSTYKIT.

	You'll always learn something when you construct a kit from JOSTYKIT.
Audio	Light Shows
A Fool work bases this privated name and be said as a first factor.	AT465 LIGHT SHOW
A real work-horse, this universal power amp has a wide range of applications such as car radio, record players and small receivers. Due to its well designed electronic circuit, the AF300 can be used over wide voltage ranges without deterioration of the specification parameters.	Turn your music into light. Simply connect this 3 channel light show to the audio terminals of your amplifier and this quality kit does the rest for you!
Kit AF300	Kit AT465
AF340 40 WATT AUDIO AMPLIFIER MODULE	AT468 4 CHANNEL LIGHT SHOW
High quality 20-20,000 Hz, 37w RMS with low distortion.	This superb kit drives 4 lights (400w per channel) from the audio amplifier
Kit AF340	output.
	Kit AT468
FM Tuners	AT365 LIGHT SHOW
HF325-2 QUALITY FM TUNER MODULE	
The HF325 is a complete high quality FM tuner of professional standing.	This quality kit uses microphone input instead of connection to the audio output. 1500w max.
The tuner unit is ready-made and pretrimmed, making it child's play to	Kit AT365 \$69.00
assemble. Tuning range 88-108 MHz, operating voltage 12-55v ac.	Box and knobs B3265
Kit HF325       \$79.00         Stereo decoder HF310       \$24.00	
HF310 FM RECEIVER	FM Transmitter
The HF310 is a very reasonably priced HF FM tuner. Fully trimmed, the	HF65 FM TRANSMITTER 60-148 MHz Will run 5w output with heat sink. Ideal for signal testing or for a minia-
sensitivity according to IHF standards is better than 10uV. Features 60 dB	ture transmitter which could be received on a standard FM receiver.
S/N radio and low harmonic distortion.	Kit HF65
Kit HF310	Ham Converter
HF330 STEREO DECODER Gives 40-45 dB channel separation, just add to a good quality FM receiver.	HF305 AMÁTEUR BAND 2m CONVERTER
Kit HF330	Converts 2m FM down to the FM band 88-108 MHz.
\$24.00°	Kit HF305
Pre-amps (RF)	· 是是 图 文 图 4 图 4 图 4 图 4 图 4 图 4 图 4 图 4 图 4
HF395 RF PREAMPLIFIER	AM Receiver
Gain 30 dB to 20 MHz, 10 dB to 100 MHz and 5 dB to 225 MHz. Ideal to	HF61 MEDIUM WAVE RECEIVER
boost reception on short-wave receivers.	540-1600 KHz receiver complete with ferrite coil antenna.
	Kit HF61\$19.00
HF385 VHF/UHF ANTENNA PREAMP	Power Supplies
	NT415 LAB POWER SUPPLY 0-30V
250 MHz and 400-820 MHz. Gain 9-18 dB, depending on frequency.	1 amp well-regulated supply for professional use. Complete with box and
Kit 385	transformer.
Box B850	Kit NT415\$128.00
[18][18] [18] [18] [19] [19] [19] [19] [19] [19] [19] [19	NT300 LABORATORY POWER SUPPLY 2-30V
Coler assembly Kils	High quality supply, regulated 2-30V dc at 2 amps with overload protection. Complete with box and transformer.
JK01 GENERAL PURPOSE AMP 0.5w \$18.00	Kit NT300
JK02 MICROPHONE AMPLIFIER \$19.00 JK03 SINE WAVE GENERATOR 20-20,000 Hz \$30.00	AT320 ALL ROUND AC/DC REGULATOR
JK04 FM TUNER 88-108 MHz	This kit is a control unit with almost incredible possibilities. Use it as a
JK05 27 MHz RECEIVER	touch control, burglar alarm, timer, heat/cold regulator. Power supply is built-in.
JK06 27 MHz TRANSMITTER	
JK07 DUAL TONE DECODER FOR R/C MODELS \$43.00 JK08 240 Vac LIGHT OPERATED RELAY \$20.00	Kit 320
JK09 SIREN KIT inc. SPEAKER	high quality
JK10 PHOTOGRAPHIC TIMBER 240 Vac \$23.00 JK101 BURGLAR ALARM KIT	
N	.S.W.: Custom Communications, Orchardleigh Street, Yennora.
NIEWY IZITO	A.: International Communications Systems, 77 Dale Street, Port
INEW KIIS V	ic.: Eastern Communications, 898 Riversale Road, Camberwell.
	being appointed in all areas
A A A A A A A A A A A A A A A A A A A	



MAIL ORDERS enclose \$1 for P & P Dealers

being a

in all areas

**VICOM** 

68 EASTERN RD, SOUTH MELBOURNE, VIC. 3205. PH (03) 699.6700

# AMATEUR,

by Pierce Healy, VK2APQ

# RADIO



## Sydney Science Museum puts amateur station on display

Thanks to the generosity of a local electronics firm, the Sydney Museum of Applied Arts and Sciences now has a working amateur radio station on display. To be manned by volunteer operators, it should provide an excellent means of introducing amateur radio to the public.

The Sydney Museum of Applied Arts and Sciences amateur radio station, VK2BQK, will be officially opened within the next few weeks. Initial checks and operational tests conducted since early December, 1978, have been satisfactory and it is anticipated that the station will become known world wide.

Current arrangements are for the station to operate during museum hours each Saturday and Sunday. A roster of operators has been prepared by the NSW Division of the WIA, and any amateur (whether a WIA member or not) is invited to add his name to this roster. As well as helping the amateur radio cause, he will have the opportunity to operate some very modern equipment in a very pleasant environment.

In addition to the station equipment, a large area has been set aside for a static display of vintage amateur radio equipment, historical documents and photographs relating to amateur radio, and the progress of radio communication over the years.

The station equipment consists of an FT101E HF transceiver, a FT7 HF transceiver, FT227R VHF FM transceiver, FRG7 receiver, SWR meter and amateur station QTR24 clock. The HF antenna is a Hustler type 4BTV with an RM80 attachment. The VHF antenna is a Hustler type G6-144.

The equipment was presented to the museum by the Dick Smith Electronics Group, and is under the direction of Mr Jeff Sergel, VK2BQI, curator of the electronics section of the museum.

It is also desirable that the station is manned during weekday musueum hours, particularly during special visits by high school students. In this regard, any amateur who wishes to assist and obtain authority to operate the station may contact Mr Jeff Sergel at the museum during office hours or advise the Secretary, NSW division WIA, 14 Atchison Street, Crows Nest 2065.

This is an excellent opportunity to assist in publicising amateur radio and the museum authorities must be praised for their initiative and interest in setting up the station and static displays as a permanent feature for public inspection.

The amatuer radio station, VK2BQK, at the Sydney Museum of Applied Arts & Sicences. Curator, Mr Jeff Sergel, VK2BQI, is shown operating the FT101E transceiver, with the SWR meter above it and the FRG-7 receiver to the left. The VHF transceiver is hidden by the operator.

Amateurs are urged to support the project. Some 325,000 people visit the museum each year and, of these, a significant percentage would be potential amateurs. The display will be one of the best opportunities amateurs have had for a long time to recruit new members, and to educate the public generally regarding their hobby.

#### **ITU NEWS**

On November 29, 1978, I (VK2APQ) had the pleasure to attend a press con-

ference given by Mr Richard Butler, Deputy Secretary General of the International Telecommunication Union, at the United Nations Information Centre, Sydney. Mr Butler presented a paper entitled — "The Changing Communication Environment" — which was illustrated by colour slides.

The address covered man's methods of achieving international communication from the time of Julius Reuter's carrier pidgeons to the present day multi-channel microwave, ocean cable, and satellite systems. It made the point that Reuter had used carrier pidgeons to bridge gaps in the European telegraph system, caused by lack of international agreement on cross-border operation.



Obvious facets of modern communication systems — telephone, radio, television and satellites were referred to; from simple person to person telephone systems to complex satellites providing international television services and linking computer systems. Also mentioned and illustrated were the not so obvious navigational and meteorological telecommunication systems, and the even less obvious earth exploration service satellite.

These examples emphasised the need for highest international understanding and co-operation at grass roots level in order to obtain the greatest benefit from these spheres of modern technology.

Radio clubs and other organisations, as well as individual amateur operators, are cordially invited to submit news and notes of their activities for inclusion in these columns. Photographs will be published when of sufficient general interest, and where space permits. All material should be sent to Pierce Healy at 69 Taylor Street, Bankstown 2200.

## MEMO from Bail Electronic Services

To all discerning amateurs Have you read the Bail ads lately? Just take a look at the fabulous 901 series from Yaesu and Bail. Everything you need for a first class station and all matched in quality and looks. Now, take a look below.

#### PROM A WORLD LEADER -



FT-901 DM De-luxe SSB, CW, AM, FSK, FM, HF Transceiver 160-10m, P.A. 2 x 6146B, Dig. readout, freq-memory, election tuning, variable IF, audio peak filter, automatic tune-up timer, AC-DC operation etc., etc. Write to Bail for new colour leaflet on 901DM series.



SP-901 Speaker Dress up your station with the addition of the SP-901 external speaker. High quality speaker unit housed in an attractive cabinet to match the 901 styling.



FTV-901 . . . VHF/UHF OSCAR Transverter. A three-band VHF/UHF transverter from Yaesu for your FT-901 DM station. Basic unit is equipped with 144 MHz capability and option for 50 and 430 MHz plug-in modules Repeater offset for 6 and 2 meters and full duplex operation on OSCAR modes A/B/J with external receiver



FV-901DM Synthesized, Scanning External VFO

Flexibility in frequency control; PLL synthesis in 100 Hz steps; auto scan mode, which will search the band for a signal; manual mode which scan at one of three rates while you activate lever switch. Memory bank for up to 40 frequencies and clarifier for fine tuning between the 100 Hz steps, etc.




FC-901 Antenna Coupler

Efficient, compact antenna tuner for FT-901DM series. Features in-line wattmeter, SWR meter, and provision for selection of three coax-fed antennas and one single wire antenna. Presents a 50 ohm load to your FT-901 DM, all across the band.



SP-901P Phone Patch/ Speaker

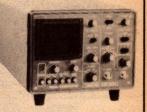Integrate your FT-901DM station with the SP-901P combination hybrid phone patch/speaker. Styling, size and interconnections match the FT-901 series of transceivers.



YO-901 Multiscope

High-performance oscilloscope, twotone generator and an optional band scope (panadaptor) for instant determination of band conditions and activity. Monitors both received and transmitted signals. Convenient interconnecting jacks for 901 series.

Ph. 450 4379

Ph. 293 2155 Ph. 44 4773 Ph. 34 6912 Ph. 44 5000 Ph. 667 1650

As the authorised Yaesu agent and factory representative for Australia since 1963, we provide after-sales services, spares availability, and 90-day warranty except power valves and semi-conductors.



**ELECTRONIC** 

FRED BAIL JIM BAIL **VK3ABA** 

60 Shannon St., Box Hill North, Vic., 3129. Ph. (03) 89 2213

Yaesu Agents in Australia since 1963

Radio amateur equipment from B.E.S. also sold by

H. R. PRIDE, 26 Lochart St., Como, 6152
WILLIS TRADING CO., 429 Murray Street, Perth 6000
FARMERS RADIO PTY, LTD., 20 Stanley Street, Plympton 5038
G. T. ELECTRONICS, 131 Westbury Road, South Launceston 7200
PRINS RADIO, 123 Argyle Street, Hobart 7000
J. D. ELECTRONICS, 64 Wentworth Street, Launceston 7250

J. D. ELECTRONICS, 64 Wentworth Street, Launceston 7250

N.S.W. Aviation Tooling, STEPHEN KUHL, 104 Robey Street, Mascot 2020

W. E. BRODIE, 23 Dalray Street, Seven Hills 2147

DIGITRONICS, 186 Parry Street, Newcastle West 2302

RIVERCOM, Sid Ward, 9 Copland Street, Wagga Wagga 2650

QLD. MITCHELL RADIO CO. 59 Albion Road, Albion 4010

TEL AIR ELECTRONICS, 187 George Street, Brisbane 4000

A.C.T. QUICKTRONIC, Jim Bland, Shop 11, Altree Court, Phillip 2606

Ph. 624 2691 Ph. 69 2040 Ph. 21 2125 Ph. 57 6830

110

## AMATEUR RADIO

Arising from questions after the address, amateur radio was discussed. Mr Butler spoke highly of the amateur service, referring in particular to the attitude of several European countries and their use of the OSCAR satellites for educational purposes.

for educational purposes.

Even the European fox hunting championships were mentioned; whereupon I was asked to explain what fox hunting, in amateur radio terms, really was (i.e., locating an expertly hidden transmitter within a given, or

shortest possible, time).

After the formal meeting Mr Butler unofficially answered a number of questions I put to him regarding the future of amateur radio. It would be ill of me to relate possibilities, good or otherwise, which have been unofficially mentioned as a possible outcome of WARC 79. Suffice it to say I was pleased to hear that there is, among officials of the ITU, a very high regard for the service amatuers can give to the community.

However, there are many problems to be solved which will need cooperation and understanding at international level. It is evident that a great deal depends on how well amatuers, through their national societies, influence and gain the co-operation of their local administrations to realise the real need for a flourishing amateur radio service.

The final paragraph of Mr Butler's address gives a forecast of the prospects for telecommunication.

"What is being shaped now for the next century goes way beyond historical issues of traffic handling, information transfer and data processing or even transmission links. In effect, what is being shaped is the nucleus of a dynamic and potentially very powerful communication system for all. It is no longer simply a telecommunication system."

## SPECIAL PREPARATORY MEETING

Some 750 scientists and engineers from 87 countries took part in a Special Preparatory Meeting in Geneva from October 23, to November 17, 1978. Over 400 documents were studied.

A 600-page report prepared by the SPM will provide the technical information likely to be needed by the World Administrative Radio Conference (WARC 79).

The results could lead the WARC to make considerable modifications to the spectrum allocation up to 300GHz.

The report is being distributed as a document for WARC 79. It cannot be bought and is not available to the public. (ITU press release 78/40 Nov 24, 1978.)

#### INTERNATIONAL AMATEUR RADIO UNION

The fourth conference of the IARU Region III Association was held in Bangkok, Thailand, on October 7, 8, 9, 1978. Member societies represented were — ARRL (USA Pacific Territories); HARTS (Hong Kong); JARL (Japan); MARTS (Malaysia); Nzart (New Zealand); PARA (Philippines); RAST (Thailand); SARTS (Singapore) and WIA (Australia).

Also present were Vic Clarke, W4KFC, president of Region II IARU (deputising for Noel Eaton, VE3C), president IARU), and the four directors of the Region III association.

The conference was formerly opened by the Deputy Undersecretary, Ministry of Communications of the Royal Thai Government, Sriphoom Suknetr, HS1SS, who assured delegates that the claims of the amatuer service for WARC 79 would be carefully borne in mind by the government of Thailand.

The conference appointed the president of the host society RAST, Kamchai Chotikul, HS1WR as honorary chairman of the conference and Fred Laun, HA1ABD, working chairman. David Rankin, 9V1RH, secretary of the Region III Association, was appointed as assistant secretary.

Considerable time was devoted to WARC 79, each society reporting on its own preparations. Several policies adopted at the Hong Kong Region III Association conference were varied to conform to WARC policies adopted by the Region I and Region II 1978 conferences. In particular, a policy, not to seek change to Article 41 of the ITU Regulations, was confirmed. That Article deals with the amateur service. The conference also adopted a paper relating to the Amateur Satellite Service submitted by Shigetake Mirimoto, JA1NET.

The IARU observer team for WARC 79 was outlined by Dick Baldwin, W1RU, secretary of IARU. The team includes Michael Owen, VK3KI, and arrangements have been made for Tom Clarkson, ZL1AZ, to participate as a special advisor to the IARU president. In addition, Dick indicated that IARU president Noel Eaton, VE3CJ, wished the Region III Association to provide a member of the team from Asia. Accordingly the conference recommended Shigetake Mirimoto, JA1NET and David Rankin 9V1RH/VK3QV, who would each be available for about half of the 10-week period of WARC.

The PARA delegate reported that J. J. Tupaz Jr, DU1JJT will be included in the Republic of the Philippines panel at WARC 79 as official delegate for the amatuer service. DU1JJT was chairman of the amateur service study group for the preparation of the Philippine paper for WARC 79.

A grant to meet the expenses of JA1NET and 9V1RH/VK3QV as members of the IARU observer team

was announced by Shozo Hara, JA1AN, president of JARL. Additional funds were also pledged by PARA and the WIA for the defence of amateur frequencies at WARC 79.

Other business included several submissions on the role of amateur radio in promoting technical education and how this could be extended. Submissions also advocated the need to emphasise self-training as a justification for the conditions being sought at WARC 79.

The next Region III Association conference will be in Manila in 1982, though the directors were asked to meet not later than May 1980 to evaluate the results of WARC and then advise member societies of the effect of those results.

(Acknowledgement to David Rankin, Secretary Region III Association for the report from which the above extract was taken.)

#### WIA NEWS

After some considerable time the P&T Department has produced a draft revision of the Handbook for Operators of Radio Stations in the Amateur Service. A draft copy has been given to WIA for comment,

The new handbook has taken into account all the concessions won by the WIA since the previous edition was printed in 1967. But it also contains a number of new provisions which will require considerable investigation by the executive of the WIA, and arrangements have been made towards that end.

A number of new definitions have been introduced as well as new material, covering examinations and provisions for club station licenses. Repeater station conditions have been set out in full. Broadcasts from club stations, third party traffic, mobile operation, emergency networks and training exercises are included with new amendments.

There are many more amendments and new material in the draft and the WIA executive, on receipt of their copy in November 1978, asked the Department for an extension of three months so that the contents and implications could be given proper consideration.

#### **WARC 79 DONATIONS**

The WIA circular to non-members inviting donations towards expenses of Region III representation at WARC 79 has brought a very pleasing response, and many of the donors wish to join the Institute. However, some 200 letters to non-members have been returned: (address unknown, left address, etc.). An adverse effect of this is that the 1979 call book information will be inaccurate as far as these people are concerned unless they notify the P&T Department of their current address.

(Note: Regulations numbered 87, 88, 89 in the current handbook relates to change of address of an amateur station.)

## **AMATEUR** RADIO

#### CENTRAL COAST FIELD DAY

The 22nd annual field day of the Central Coast Amateur Radio Club will be held on Sunday, February 18, 1979 at the Showground, Showground Road, Gosford, NSW: All amateurs, their families, and friends are invited to attend.

#### PROGRAM:

8 am-12 noon: Registration — Men \$4; Women \$2; Children 16 years and younger \$1. This includes morning and afternoon tea, outings, and entry in events. Pensioner concession is 50% on production of pensioner card.

Special note: Lunch will not be provided by the club. A takeaway food bar will be open in the showground from 10 am to 3 pm.

Tea and coffee will be available from 8 am to 5 pm in the dining room, free to anyone displaying their registration card.

8.30 am-9.00 am: Mobile scramble in two sections (a) HF; (b) VHF. Rules: No operation in the showground or 1km radius. VHF nets 1 point per contact. VHF tunable CW, AM or SSB 4 points per contact. No operation through Gosford repeaters or within 0.5km of Gosford repeater sites. Log extract to

be passed to "event recorder" before 10 am showing time of each contact, station worked, frequency mode, serial numbers in full and points claimed. In the event of tied scores neatness of log will count.

9 am: Ferry trip tickets on sale at "ticket sales" near announcer. The fare is subsidised, field day registration card must be shown. Sale of ferry tickets ceases at 12 noon, Eighty tickets only available, including children.

9 am-10 am: Bookings for equipment workshop in Dwyer Pavilion.

All items for the disposal market must be in before 9.30 am.

9.30 am: Register in Showground Road opposite to Dwyer Pavilion for 10 metre and two metre fox hunts. Registration card required.

9.45 am-10.30 am: Mobile/pedestrian fox hunt. 24.45MHz AM and 146MHz FM direction finding event. Hand held sniffer receivers will be required for location of transmitting antenna in addition to normal vehicular DF equipment. The transmitter antennas must not be disturbed.

10 am: Food bars open. Equipment workshop opens. Disposal market opens.

10 am-10.15am: Junior 2 metre AM pedestrian fox hunt for 16 year olds and younger. Frequency between 144.4MHz and 144.6MHz.

10 am-10.30 am: Children's events -races, etc.

10.30 am: Quiz sheets available return before 1.30 pm.

11 am-11.15 am: 2 metre pedestrian fox hunt. Frequency Between 144.4MHz and 144.6MHz. AM.

11 am-11.30 am: VK2 division news broadcst from VK2AFY. Broadcast to be televised on ATV.

11.30-12 noon: Children's events. 11.45-12 noon: 2 metre pedestrian fox hunt. Frequency between 144.4MHz and 144.6MHz AM.

12 noon-1 pm: Lunch break.

12.15 pm-12.30 pm: 2 metre AM pedestrian fox hunt.

12.30 pm: Departure time for ferry trip commencing at 1 pm. Transport to wharf by private cars.

1.15 pm: Departure time for Reptile Park outing.

1.20 pm: Register for 10 metre and 2 metre fox hunt.

1.30 pm: Closing time for return of quiz sheets, late entries will not be

1.30 pm-3.30 pm: Mobile/pedestrian 10 metre and 2 metre fox hunt direction finding event on 28.45MHz and 146MHz. There will be a transmitter on each frequency at two sites. A different audio tone for each site; one site will transmit tone at 30 seconds on and 30 seconds off. The other 40 seconds on and 40 seconds off. Both sites must be found. Hand held sniffer receiver will be required for location of transmitting antenna in addition to normal vehicular DF equipment. Transmitting antenna must not be disturbed.

2 pm-2.45 pm: Junior, 16 years or younger, 2 metre AM fox hunt. Frequency between 144.4MHz and 144.6MHz.

3 pm: Equipment workshop closes.

4.15 pm: Drawing of lucky numbers. If leaving early register your numbers at field day management table.

Prize presentation — advise if leaving early so as to arrange delivery of prizes.

Parking: Off street in showground, please observe directions.

Trains: From Newcastle 9.07 am and from Sydney 8.58 am and 9.52 am will be met at Gosford and transport provided to showground from Gosford railway station. For return transport in the afternoon contact the field day announcer one hour before departure time of train.

If it rains? There is plenty of shelter in the showground.

Bring your QSL card for calls present board.

A condition of entry to the showground is that there be no transmitting within the showground and the request is made that no transmitting take place within 1km of the showground.

Disposals: Items for disposal must be booked in before 9.30 am on the field day. Cataloging forms and lot numbers must be obtained in advance from Bill Smith, VK2TS, RMB 4525, Gosford 2250, or phone 043 74 1207 after hours for forms and lot numbers.

## BRIGHT STAR CRYSTALS PTY LTD

35 EILEEN ROAD, CLAYTON, VICTORIA, 546 5076 (ALL MAIL TO:- P.O. BOX 42, SPRINGVALE, VIC. 3171)

INTERSTATE AGENTS

- ROGERS ELECTRONICS ADELAIDE Phone 42 6666
- . HOSE & EQUIPMENT SYDNEY 666 8144
- DILMOND INSTRUMENTS **HOBART 47 9077**

B.S.C. TELEX AA36004



\* WESTEST ELECTRONICS PERTH 337 6393

FRED HOE & SONS PTY. LTD. **BRISBANE 277 4311** 



#### SPECIFICATIONS

- Nominal Frequency Frequency Tolerance Drive Level
- Series Resistance
- Q Factor Parabolic Curvature Constant
- Turnover Temperature Capacitance Ratio
- Storage Temperature Range
- 10. Operating Temperature Range
- 11. Aging rate 12. Shock
- 13. Package Size

+30 ppm/28° +1°C 1uW max. 31.0 kOhms max. 40,000 min.

Less than -0.04 ppm/°C (Refer Fig. 1) 28.0°C +5°C

700 max. -30°C +80°C -10°C .+60°C

Less than +5 ppm/year Less than 5 ppm for 50 cm Hammer Shock Test

DATA SHEET AVAILABLE. ALSO AVAILABLE CRYSTAL UNITS FOR QUARTZ CRYSTAL CLOCK.

## AMATEUR RADIO

A commission will be charged on all sales. Lot numbers and forms will also be available at the showground on Saturday afternoon, February 17, 1979.

Any telephone enquiries concerning the field day may be made to Ross Mudie, VK2ZRQ on 02 663 0141 between 8 am and 3 pm weekdays only.

#### RADIO CLUB NEWS

Here are two additions for your radio club director (see December 1978 issue).

Club name: North Western Branch Tasmanian Division WIA.

Club call sign: Repeater VK7RNW.

Net frequency: FM channel 40 and channel 3 repeater VK7RNW.

Contact: Secretary, PO Box 1010, Launceston, Tasmania 7250.

Club name: Geelong Radio and Electronics Society.

Club call sign: VK3ANR. Net frequency: Nil.

Contact: Secretary, GRES, VK3ANR, PO Box 962, Geelong 3220, Victoria.

GEELONG RADIO & ELECTRONICS SOCIETY: Society activities have been stapped up recently with the formation of RF and AF groups. New test equipment for members include a CRO, signal generator, GDO and some general usage tools.

general usage tools.

A printed board workshop using presensitised board is achieving excellent results. Classes for AOCP; AOLCP and AONCP amateur licence examinations are held free of charge to members on Mondays at 7.30 pm and syllabus meetings on Thursday at 8.00 pm.

Visitors are welcome at the club rooms on Breakwater Road, Belmont Common, Geelong, Victoria.

#### NORTH WESTERN BRANCH TASMANIAN DIVISION WIA:

Meetings are held in Lakins Hall, Ulverstone on the second Tuesday of each month at 8.00 pm.

When travelling through northern Tasmania on holidays, information can be obtained through the Channel 3 repeater.


SOCIETY: A meeting of the University of Wollongong staff, attended by Lyle Patison, VK2ALU, affirmed that the dish antenna should be shifted to the new site.

A secure building would be erected next to the antenna by the university authorities and the moonbounce project group would only have to install the equipment, associated wiring, and cables.

An experimental dual band disc feed for 432MHz and 1296MHz is being made and the CSIRO will test the system on their antenna test range to find out if the 432MHz radiation is
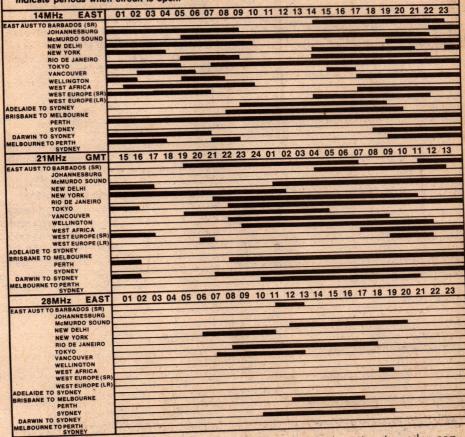
### IONOSPHERIC PREDICTIONS FOR FEBRUARY

Reproduced below are radio propagation graphs based on information supplied by the lonospheric Prediction Service Division of the Department of Science. The graphs are based on the limits set by the MUF (Maximum Usable Frequency) and the ALF (Absorption Limiting Frequency). Black bands indicate periods when circuit is open.



affected by the 1296MHz components.

The School of General Studies at Wollongong Technical College is conducting an approved course in electronics, which includes all the information and training needed for novice, limited or full amateur licence.

Enrolments to be made on the first night of the course, Friday, February 16, 1979, at Room 213, Mathews Building, commencing at 6.00 pm.

For further details contact — Brian Wade, VK2AXI. Telephone after hours (042) 84 1381.

DARLING DOWNS RADIO CLUB: As from November 2, 1978, the club's repeater, VK4RDD, formerly on channel 4/6800, has operated on channel 10/7100 (147.700MHz in and 147.100MHz out.

The change was made to eliminate inference from and to adjancent repeaters on the same channel, viz, Bundaberg and Lismore. Operators in some locations could trigger two and sometimes all three repeaters.

Further club details from the secretary, G. J. Pennycuick, VK4AGP, 38

Wentworth St, Toowoomba 4350.

WOOMERA AMATEUR RADIO CLUB:
About half of this club's members are
Americans associated with the
Woomera complex. The club is
equipped with a three element HF
beam, an 80 metre inverted "V", and an

OSCAR mode A station is under construction.

The club meets every Wednesday night at 7.30. It can be heard on 80 metres on most Wednesday nights and at least two members monitor the Port Pirie repeater on channel 2.

Further details from Andrew Squires, VK5ZWO, F100 Carriwan St, Woomera 5720.

## THE WIRELESS INSTITUTE OF AUSTRALIA

New South Wales Division

14 Atchison Street, Crows Nest, N.S.W. 2065 Telephone: 43 5796

WOULD YOU LIKE TO JOIN THE RANKS of AMATEUR RADIO ENTHUSIASTS?

The Institute conducts Courses for the A.O.C.P. or L.A.O.C.P. with the benefit of expert guidance throughout your studies.

PERSONAL CLASSES for 1979 will commence on Tuesday, February 6, at 6 p.m. at Crows Nest, and will continue for three terms to December in readiness for the February 1980 examinations. CORRESPONDENCE COURSES may be commenced at any time.

For further information, write to:

## THE COURSE SUPERVISOR, W.I.A.

14 Atchison Street, CROWS NEST, N.S.W. 2065



FT-7 Novice/Mobile/Base

You name it! Complete with mike & ready to go. Cat. D-2866.. .. .. .. .. \$535.00 Imagine - only \$54.00 deposit & as little

as \$4.60 per week

FL-110

Want the full 200 watts? Simply add this linear, NO TUNING.

Cat. D-2884

.. .. ..\$255.00



### Receivers

FRG-7 HF receiver Cat. D-2850 \$395.00 FRG-7000 deluxe HF receiver Cat. D-2848 \$695.00 Shortwave antenna kit Cat. K-3490 \$9.50

## **HF Equipment**

FT-101E transceiver Cat. D-2860 \$975.00 FL-2100B 1.2kW linear Cat. D-2546 Incredible performance \$585.00 FTV-250 2m transverter Cat. D-2894

\$339.00 FT-301 S/S 200W transceiver Cat. D-2870 Huge Reduction SAVE \$100.00! \$895.00 FP-301 AC power supply Cat. D-2872

\$195.00 FC-301 antenna tuner Cat. D-2896 \$249.00 FT-901D ultimate transceiver Cat. D-2854 \$1375.00

FC-901 new antenna tuner Cat. D-2855 \$289.00

YC-500S 500MHz counter Cat. D-2892 \$499.00

QTR-24 world clock Cat. X-1054 \$37.50 YD-148 new desk mike Cat. C-1118 \$44.50



\*\*\*\*\*\*\*\* PVC dust cover with each FRG-7, FRG-7000, FT-101E, FT-901D, FL2100B sold cat. D-9050 usually \$3.95

### \*\*\*\*\* Equipment

FT-227R 2M synthesized. Cat. D-2890

\$395.00

FT-227 RA with up /down scanner. Cat. D-2891

\$445.00 CPU-2500K 25 watts, keyboard mic,

memories & scanner. Cat D-2889 \$575.00

147 Hume Hwy, CHULLORA. Ph. 642-8922

162 Pacific Hwy, GORE HILL. Ph. 439-5311

30 Grose Street, PARRAMATTA. Ph. 683-1133

## E'VE GOT THE GEAR \*\*\*\* SPECIALS

Many reduced to below cost! Hurry - only while limited stock lasts 1978 ARRL HANDBOOK: B-2218 Now only \$8.50 SAVE \$4.25 ERB6m PREAMPS: D3806 \$6.50 save \$32.50

EXC6m CONVTR: D-3836 \$9.50 save \$26.00

#### **HUSTLER ANTENNAS..**

#### Look at these prices:

4BTV	D-4150	\$109.00	save \$35.00
MO-1 mast	D-4152	\$19.50	save \$15.50
RM-80	D-4156	\$14.50	save \$15.00
RM40	D-4158	\$9.50	save \$12.50
RM20	D-4160	\$9.50	save \$8.50
RM-15	D-4162	\$9.50	save \$14.00
RM11	D-4164	\$4.50	save \$14.50
RM10	D-4166	\$9.50	save \$9.50
SSM2 mount	D-4170	\$9.50	save \$15.00
Cowl mount	D-4180	\$2.50	save \$11.00

#### TRANSCEIVERS:

TR-7200 D-3215 \$119.00 save TR-2200 D-3210 \$99.00 save\$90.00 GORE HILL STORE ONLY: One only TS-820 with digital readout: Incredible value at \$999.50!!! Note: all units on special are sold WITHOUT WARRANTY

## Simply Incredible!



An unbelievable unit at an unbelievably low price! Has features you've probably only dreamed of. You can even work the overseas 10M FM repeaters CALL IN FOR A TEST DRIVE TODAY. 

### morse code

Economy key - value Cat. D-7105 \$1.95 Quality key - precision built Cat. D7101

\$15.75 Hi-Mound deluxe key Cat. D-7104 \$29.50 Electronic keyer kit Cat. K-3470 \$39.50 paddle only Cat. D-7103 \$17.50 Morse code trainer kit - includes oscillator key extra Cat. K-3472 \$5 90 [built up unit Cat. D-7110 \$7.90 Morse code cassettes - teach yourself - set of Cat. D-7106 only \$7.90

## What a Meter!



**NEW Dick Smith Multimeter** Even measures capacitance! 28 separate ranges. Incredible value. Cat. Q-1140 \$69.50 Value!

## Follow Oscar

Take the hassle out of satellite work. Complete kit for both OSCAR 7 and 8 - full instructions. Cat. K-3480



\$10.95

\$20.95

Dick Smith's Oscar Tables Full basic details on OSCAR, prediction tables, standard orbits and tracking details. Totally practical. Cat. B-3482 \$1.50

## Antennas

Incredibly popular mobile antennas RSE-M-2 gutter grip Cat. D-4100 \$32.50 RSE-2A 2m ¼wave stub Cat. D-4102

RSL-145 6m/2m combined whip

Cat. D-4104 \$23.95 RSL-3.5 80m mobile whip Cat. D-4110 \$19.95

RSL-7 40m mobile whip Cat. D-4112

\$19.95 RSL-14 20m mobile whip Cat. D-4114 \$20.95

RSL-21 15m mobile whip Cat. D-4116 \$20.95 RSL-28 10m mobile whip Cat. D-4118

HY-GAIN

18AVT 80-10m trapped vertical

Cat. D-4302 \$135.00 TH3JR 3 element triband beam Cat. D-4304 \$199.00

TH3MK3 large 3 element beam Cat. D-4306 \$299.00

TH6DXX 6 element thunderbird Cat. D-4308 \$399.00

BN86 balun Cat. D-4300 \$19.50 (only available with a Hi-Gain antenna purchase)

## Accessories

Shinwa 500W L.P. filter Cat. D 7080

\$19.50 Viking 5kW L.P. filter Cat. D-7086 \$37.50 Type 101 rugged coax relay Cat. D-5210

\$44.50 small egg insulators Cat. D-5300 \$0.80 large egg insulators Cat. D-5302 \$1.20 FU-400 Rotator. Now with Melamine coating. Cat. D-5000...

\$133.00 24V P/S to suit. Cat. D-5002... \$16.00

## **ECTRO**

ADELAIDE 203 Wright Street, ADELAIDE. Ph. 212-1962

399 Lonsdale Street, MELBOURNE. Ph. 67-9834 656 Bridge Road, RICHMOND. Ph. 42-1614 166 Logan Road, BURANDA. Ph. 391-6233

SHOPS OPEN 9AM to 5.30PM (Saturday 9AM – 12 noon) BRISBANE 1/2 Hour earlier.

ANY TERMS OFFERED ARE TO APPROVED APPLICANTS ONLY

Many lines available from the Dick Smith Electronics Centres at

GRACE BROS

MAIL ORDERS P.O. Box 747, Crows Nest, N.S.W. 2065. Post and packing extra.

Dealers across Australia.

Note: Prices & stock availability could change between publication deadline & on-sale date due to circumstances beyond our control. Please check with our stores for latest availability & pring

## AMATEUR

## Two items to assist the novice candidate

LEARNING MORSE CODE, by R. Black, B.A., VK2YA. Published by WIA (NSW) Education Service. Soft covers, 32 pages 200mm x 260mm, mainly text but a few illustrations. For use with two C-60 tape cassettes. Price for book and cassettes, \$6.50.

Rex Black, the author of this course, has had many years experience teaching Morse code to army, air force and amateur operators, and he has sought to bring the benefit of this experience to the presence course. He has also taken into account the fact that amateur candidates come from a wide variety of backgrounds, and have widely varying aptitudes for learning code, unlike the selected students at commercial or military level.

The first few pages of the book are devoted to the background of Morse code, the examination requirements, study techniques, slow Morse transmissions, etc, plus a certain amount of "salesmanship" aimed at convincing the student that learning

Morse is fun!

The main section consists of instructions on how to follow the course, plus practice exercises to be used in conjunction with the tapes. The course is graded from the simplest symbols (all dits) to the progressively more complex ones, with a strict routine whereby the student does not progress until each stage has been mastered.

The final section is devoted to sending; the type of key, how to hold it, wrist action, etc, plus several audio oscillator circuits. There is also a list of

"Q" codes.

The tapes are well recorded, with verbal instructions accompanying the Morse symbols. They are designed to take the student to the point where he can indulge in conventional practice to gain speed and confidence.

In summary, a well thought out course which should provide an excellent starting point for any candidate. And, at the price, extremely good

value. (PGW)

1000 QUESTIONS FOR NOVICE LICENCE CANDIDATES, by K. Hargraves, VK2AKH, D. Wilson, VK2ZCA/NMW, and R. Black, VK2YA. Published by the WIA (NSW) Education Service. Soft Covers, 109 pages, 175mm x 240mm, mainly text. Price, \$3.00 posted.

This book is also part of the study kit referred to in the previous review. As its name implies it is a series of 1000 questions aimed at testing a novice can-


didate's progress and at presenting him with the kind of questions he will encounter in a real exam.

It is emphasised that these are not the actual questions which will be asked, but are of the same standard, and presented in the same style, as in the actual exam. (There is no point in a student trying to memorise the questions, even assuming he could do so!)

It should also be realised that the book is not, in itself, an instructional text; the student will learn little from it - directly - in the technical sense. What he will learn is, firstly, what he does not know and, as a logical step from this, will be encouraged to refer to the appropriate texts until he understands that subject.

The questions are divided into 17 subject headings, ranging from electrical laws to regulations, and this classification should further assist the student to pinpoint his weak subjects. A brief appendix lists the answers to all

the questions.

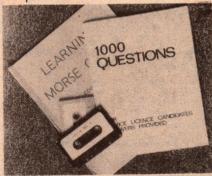

The book is well set out and printed, and obviously represents a very considerable effort on the part of the voluntary authors and others who assist them. As might be expected in a list of this size, it is possible to find a few cases where some suggested answers carry a degree of ambiguity. However, this should not detract from the book's purpose; to make the student aware of his weak points and the need to study them.

The book should also prove invaluable to instructors, providing an almost unlimited supply of typical questions for use in trial examinations.

At the other extreme, the isolated student, who must fend for himself, will find it an invaluable guide to what he needs to study.

In short, a book like this is a "must" for any prospective candidate and, equally important, it is very good value for a very modest price. (PGW)

#### BILL EDGE of ELECTRONIC AGENCIES.

115-117 PARRAMATTA ROAD, CONCORD, 2137, 747 6472

#### SLASHES KIT PRICES:

#### STROBE KIT (ETI AUG. 71)

Very popular for parties, etc. flashes up to 20 flashes/second (kit includes absolutely everything for 1st class job).

\$28

Circuit & instructions included.

#### Economy CAR ALARM kit

Works as soon as current is drawn from battery — has an LED flashing all the time to keep away would-be thieves. (No case or external h/ware.)

\$11

Circuit & instructions included.

#### KITS FOR BEGINNERS

These kits are marked right down in price to give novices a chance. In order to economise as much as possible no circuits are included with these kits. They are all available in the one volume of "Project Electronics" for only \$4.75. (No batteries or cases are included but everything is supplied to get them going.)

10% OFF

(If 10 or more kits are purchased.)

CONTINUITY TESTER	\$3.00
SOIL MOISTURE INDICATOR	4.75
500 SECOND TIMER	4.50
MORSE PRACTICE SET (LESS KEY)	3.50
MORSE KEY TO SUIT \$1.80	
BASIC AMPLIFIER	5.50
FLECTRONIC BONGOS	5.00
FLECTRONIC SIREN (less speaker)	5.50
LED DICE	5.90
BATTERY SAVER (12VDC to 9VDC)	3.90
For more information on these kits why not	buy the

book (Project Electronics \$4.75) from us & then decide which kits are most suitable to you.

E/A PLAYMASTER AM/FM DIGITAL TUNER ..... \$159.50 KIT

A comprehensive range of all electronic com-ponents & hardware is always on hand. Philips speakers & speaker kits are still one of our specialities - please give us a call.

SPECIAL FOR FEBRUARY:

Black speaker cloth (5 feet wide). (That's over 15 square feet.)

\$9 METRE ONLY LINEAR

SPECIALISTS IN ELECTRONIC COMPONENTS

## ELECTRONIC **AGENCIES**

115-117 Parramatta Road, Concord, 2137. Telephone 747 6472.

BUSINESS HOURS: 9am - 5.30pm MON-FRI; 9am - NOON SAT MAIL ORDER: PO Box 1005, Burwood North,

\$1.00 minimum pack & post plus 5% of order value. Heavy items sent "freight on".

# SHORTWAVE



by Arthur Cushen, MBE

## New TWR gospel station proves popular

The Trans World Radio organisation signed an agreement in 1975 with the Sri Lanka Broadcasting Corporation and obtained a franchise to operate a station which would be jointly programmed by the two organisations. The new 400kW transmitter is broadcasting programs from the Sri Lanka Broadcasting Corporation 7am-7pm local, and programs of Trans World Radio throughout the night. The transmitting towers are each 190 metres high, and the signals are beamed to New Delhi in India some 2000km away.

The transmitters are located 104km north of Colombo on the west side of the island, and operate on the mediumwave frequency of 891kHz. The transmissions are carried in eight Asian languages but this is expected to be expanded following the opening of recording studios in Bangladesh.

At present, studios in India and Pakistan supply the Colombo office with transcribed programs. Trans World Radio, which had its beginning in Tangier in 1954 (when we verified WTAN), is now broadcasting from all continents with stations in Monaco, Cyprus, Swaziland, Guam and Bonaire.

#### RADIO AGRICULTURA

Radio Agricultura at Santiago, Chile, is providing good reception on 9630kHz from opening at 0900GMT. Jack Buckley of Sydney, NSW, has noted this signal and the earlier sign-on time due to the fact that Chile is now on summer time. The station formerly opened at 1000GMT. There is some interference from Radio Nederland up to 0920GMT when for 10 minutes the broadcast is clearly received, but at 0930GMT Radio Sweden opens on the channel and again causes interference.

Radio Agricultura opens with a march and full identification in Spanish which includes information of other

Notes from readers should be sent to Arthur Cushen, 212 Earn Street, Invercargill, NZ. All times are GMT. Add 8 hours for WAST, 10 hours for EAST and 12 hours for NZT. In areas observing daylight time it is necessary to add one hour.

stations in the network. A news bulletin follows and then a program on agriculture for Chilean farmers. Some weeks ago the station moved temporarily to 9670kHz, but has now returned to its assigned frequency of 9630kHz.

#### **WORLD RADIO CLUB**

The popular BBC World Radio Club program, which includes information for the short-wave listener, has been retimed for the broadcast to the Pacific. The program is now heard on Sundays at 0745GMT on 7150, 9640 and 11955kHz. The World Radio Club program is repeated on Monday at 1115, Tuesday at 2100 and Wednesday at 2315GMT.

World Radio Club is written for the short-wave listener in a language that is not too technical, so that it can be understood by beginners when the session is dealing with electronics. A feature of the 15 minute program is the "Shortwave News", which is generally supplied by the BBC Monitoring Service.

#### **BRAZILIAN EXPANSION**

Brazil is fast becoming one of the most radio intensive countries in the world, with numerous new stations being reported.

The Communications Ministry has opened bids for the installation of 13 new radio stations in the country: this includes three short-wave, five medium-wave and one tropical band station.

#### **INCREASED SW COVERAGE**

The recent frequency changes for medium-wave stations in Europe, Africa, Asia and the Pacific has resulted in 9kHz station separation. Already, in Europe, the frequency moves have resulted in poorer coverage for some stations. This has been true in Germany where several of the main stations which have short-wave re-broadcasts of their programs are stepping up the power on short-wave to compensate for their loss of medium-wave coverage.

A German newspaper report

reproduced by the BBC Monitoring Service states that the Bayerrischer Rundfunk has had to make the biggest sacrifice of any German station with its move from 1602 to 801kHz. To compensate for the loss of audience abroad, plans are underway to considerably increase the power of the short-wave relay of Bayerrischer Rundfunk on 6085kHz.

Radio Bremen on 619kHz also relays a medium-wave program and this is broadcast 1000-1700 Sunday to Friday and from 0800-1100 on Saturdays. According to a letter from the station, the balance of the transmissions are a relay of Sender Freies Berlin.

#### LATIN AMERICAN NEWS

BONAIRE: Trans World Radio at Bonaire is using the new frequency of 9610kHz for the broadcast to Europe and Africa 0335-0500GMT. This gospel service is in several languages and was heard recently on 9535kHz, but on this channel suffered interference from Radio Canada International broadcasting to the United States and Central America. Trans World Radio Bonaire changed frequency to 9610kHz in mid December, and this new channel is providing much better reception.

COSTA RICA: Radio Casino, Station TIQ has made a frequency change from 5955 to 5960kHz. This station has been heard for many years but with the powerful Radio Nicaragua now using 5955kHz, TIQ was forced to make the frequency change. Our reception has been after 1100GMT but there has been some interference from Radio Moscow.

**ECUADOR:** HCJB in Quito has made a frequency change for the afternoon transmission to North America from 0030 to 0700GMT. The frequency of 9745kHz is now used for this broadcast, this outlet replacing 9560kHz which was suffering interference.

HAITI: Radio Nationale have been heard on 6156kHz at 1030GMT, according to Jack Jones in "Tropical DX". The station also announces as Radio Citadelle and has been heard as early as 1000GMT.

## SHORTWAVE SCENE

#### TWR SWAZILAND

Trans World Radio Manzini has increased its English transmissions with a broadcast to Central Africa 1630-1800GMT. Two frequencies — 9720 and 11910kHz — are used, according to a report from Colin Miller in Johannesburg. The new schedule received from the station, which confirmed our reception of 4760 and 4790kHz, indicates that English broadcasts are 0430-0630 on 3275 and 9530; 0635-0835 on 5055 and 11910; 1200-1415 on 9530; and 1800-1915GMT on 7280kHz. The address of the station is Trans World Radio, PO Box 64, Manzini, Swaziland.

#### **CHINA ENCOURAGES LISTENING**

China has lifted restrictions on listening to overseas broadcasts. Several months ago the Voice of America studios in Washington received only a trickle of mail — 5 or 6 letters a month — from listeners inside China. Today the mail is between 50 and 60 letters a day as Chinese students are encouraged to listen to the Voice of America in order to improve their English and to get a better knowledge of world events.

The Voice of America broadcasts news in English at slow speed and uses a standard vocabulary of only 1000 words. For this reason, the program is particularly appreciated by those learning English in many parts of the world. The increasing numbers of Chinese listeners listening to programs from outside their own country will do much to broaden their knowledge of the outside world, and at the same time enable the Voice of America to get a better estimation of its coverage of the Chinese mainland.

#### LISTENING BRIEFS EUROPE

**GREECE:** Athens is using a new frequency for the English broadcasts at 0215GMT. The frequency of 9515kHz is now used for the transmission which is also in Greek from 0300-0350GMT. The new frequency replaces 9690kHz.

**SWEDEN:** Radio Sweden has made a frequency change for the transmission to North America 1330-1500GMT. The station is now using 21610kHz, which replaced 21505kHz. English is heard on the new frequency at 1400GMT.

SWITZERLAND: Berne has been observed in the 13-metre band using several frequencies from 1030GMT, with an English broadcast at 1100GMT. Three frequencies have been received: 21520, 21545 and 21630kHz.

#### **AFRICA**

LYBIA: Signals from Tripoli have been heard on 5980kHz from 0600GMT, when a transmission in Arabic is heard. The broadcast commences with the national anthem and a station announcement, followed by regular programs until sign-off at 0800GMT. Douglas Doull of Auckland, NZ, reports reception of this frequency, while our reception has been a the same program on 5960kHz which also closes at 0800GMT.

UGANDA: Kampala has a new service to Europe, according to "Sweden Calling DXers". The broadcast is on 9685kHz in German till close down at 2103GMT. The transmission is on a test basis, according to announcements given by Radio Uganda at the end of the program.

#### **AMERICAS**

ARGENTINA: Radio Splendid in Buenos Aires has made a frequency move from 5985 to 6030kHz. The signal has been noted around 1000GMT but the frequency is not a good one for this area as there is some interference to the broadcast. VENEZUELA: According to the BBC Monitoring Service, a ecent government announcement from Caracas stated that the La Voz de Venezuela is to be built. The initial installation will consist of a 1MW medium-wave station, and this will be backed up by short-wave transmitters. The government already operates Radio Nacional in Caracas.



DESIGNED & MANUFACTURED IN AUSTRALIA BY

117



## **ELECTRONICS CENTRE**

BARGAIN PRICES . PERSONAL ATTENTION . SLICK MAIL ORDER SERVICE • CUSTOMER SATISFACTION •



RANK ARENA 2-WAY SPEAKER SYSTEM

> LESS THAN 1/2 PRICE

8 OHMS 10 watts teak cabinets 1814" H 11"W 91/2"D Pack & Post NSW \$2.00 VIC QLD \$3.50 SA TAS WA NT \$5.50

\$42.00 PAIR

COMPUTER GRADE ELECTROLYLICS CAN TYPE, TOP QUALITY GUARANTEED.

2900UF/40V \$5.75	6800/16V \$5.75	10000/16V	\$7.75
10000/25V \$8.25	10000/40V \$10.80	15000/25V	\$10.90
22000/25V \$11.30	22000/40V \$18.00	27000/35V	\$18.75
68000/16V \$17.80	THE REAL PROPERTY.		

CAPS TO 15000 UF P.P. NSW 75c INTERSTATE \$1.50 " P.P. NSW \$1.00 ABOVE \$1.75

#### ATTENTION COMPUTER CONSTRUCTORS

Miniwatt 12" black and white picture tube type A34-99 specs. Fil. 12V/75MA. K cut off volts 30-60. G-2. 300V. G4 Focus volts, 0-400. Anode 12KV \$9.95 P.P. NSW \$2.75. Interstate \$4.00

#### C-CORE TRANSFORMERS



LOW NOISE, HI EFFICIENCY PRIMARY 240V 50Hz

MODEL JT266 0-18V 8A \$22.95 MODEL JT235 26.0-26V4A \$21.95 MODEL JT248, 10V, 10A MODEL JT249 0-15V \$22.95 8.5-0-8 5V 4A FOR MICRO PROCESSOR \$23.95

MODEL JT274 10V 10A 2 x 12V 1A \$22 95 MODEL JT 253A 0-18V 30A PEAK \$41.95 P.P. MODEL 253A NSW \$3.50 V.Q.T. \$5.50 SA WA NT \$7.00 P.P. ALL OTHER MODELS

NSW \$2.95 V.Q.T. \$3.75 WA SA NT \$5.50

FAN	1005	MAGN	AVUX	AUSI. MAL	DE LOUD	SPEAKE	15	
MODEL	Imp	Watts	Reson	Freq Hz	V.C. Dia	Price	P.P.	
**10-40	8	40	45	30-8000	11/2"	\$25.95	\$2.50	
8-30 8"	8	30	45	30-8000	11/2"	\$19.00	\$2.25	
12WR 12"	8	16	45	30-16000	1"	\$16.90	\$2.00	
10WR 10"	8	16	45	30-16000	1"	\$16.00	\$2.00	
8WR 8"	8	16	45	30-16000	1"	\$12.95	\$2.00	
6WR 6½"	8	12	45	30-16000	1"	\$12.40	\$2.00	
6-25 61/2"	8	25	45	45-6000	11/2"	\$16.95	\$2.00	
XJ3 Dome	8/15	25	1500	2000-20000	1"	\$ 9.35	\$1.30	
	MODEL * 10-40 8-30 8" 12WR 12" 10WR 10" 8WR 8" 6WR 6½" 6-25 6½"	MODEL Imp **10-40 8 8-30 8" 8 12WR 12" 8 10WR 10" 8 8WR 8" 8 6WR 64" 8 6-25 6½" 8	MODEL 8 40 **10-40 8 40 **30-8" 8 30 12WR 12" 8 16 10WR 10" 8 16 8WR 8" 8 16 6WR 64" 8 12 6-25 61/4" 8 25	MODEL         Imp         Watts         Reson           **10-40         8         40         45           8-30 8"         8         30         45           12WR 12"         8         16         45           10WR 10"         8         16         45           8WR 8"         8         16         45           6WR 6½"         8         12         45           6-25 6½"         8         25         45	MODEL         Imp         Watts         Reson         Freq Hz           **10-40         8         40         45         30-8000           8-30 8"         8         30         45         30-8000           12WR 12"         8         16         45         30-16000           10WR 10"         8         16         45         30-16000           8WR 8"         8         16         45         30-16000           6WR 6½"         8         12         45         30-16000           6-25 6½"         8         25         45         45-6000	MODEL         Imp         Watts         Reson         Freq Hz         V.C. Dia           **10-40         8         40         45         30-8000         1½"           8-30 8"         8         30         45         30-8000         1½"           12WR 12"         8         16         45         30-16000         1"           10WR 10"         8         16         45         30-16000         1"           8WR 8"         8         16         45         30-16000         1"           6WR 6½"         8         12         45         30-16000         1"           6-25 6½"         8         25         45         45-6000         1½"	MODEL         Imp         Watts         Reson         Freq Hz         V.C. Dia         Price           **10-40         8         40         45         30-8000         1½"         \$25.95           8-30 8"         8         30         45         30-8000         1½"         \$19.00           12WR 12"         8         16         45         30-16000         1"         \$16.90           10WR 10"         8         16         45         30-16000         1"         \$12.95           8WR 8"         8         16         45         30-16000         1"         \$12.95           6WR 6½"         8         12         45         30-16000         1"         \$12.40           6-25 6½"         8         25         45         45-6000         1½"         \$16.95	**10-40

#### AM-FM STEREO TUNER



\$75.00

Expo Top Model FET-7000. Advanced solid state circuitry. Standard Aust. Freq. Bands. Modern slim line design. Slide-rule dial. Tuning metre. Sensitivity, AFC controls. Long range reception. Teak cabinet. Brushed gold aluminium front panel. Pack and post NSW \$3.50 Interstate \$5.50

#### FM WIRELESS MICROPHONES



\$32.75

\$24.75

No 2 Omnidirectional You can't trip over the mic. cable — there isn't any. The signal transmitted by FM microphones is picked up by an FM receiver, operating in the 88-106MHZ.sfreq. band. Mics can be tuned in this band. Specs. FM modulation. Field strength. 50 UV/M at 50ft max. freq. deviation + -75KHZ. Electret Condensor Mic. 2 transistors. 1.5 VDC 2.5MA

#### SUPER SPECIAL

12V 1.2AH RECHARGEABLE BATTERIES (2 SEPARATE 6V BATTERIES FOR SERIES CONNECTION)



\$10.95

PP NSW — \$1.75 INTERSTATE — \$2.50

COMPLETE WITH 240V AC PLUG-PAK BATTERY CHARGER, INCLUDING DIODES 6V 1.2AH RECHARGEABLE BATTERIES \$4 95 EA PP NSW 80c. INTERSTATE \$1.20 THE ABOVE GEL-CELL BATTERIES ARE IN FULLY SEALED. HIGH IMPACT MOULDED CASES 3'sin x 'sin x 2in

#### FLEXIBLE NYLON SCREW TERMINAL 12 WAY BLOCKS

1 MA. FSD PANEL METER

38 M/M SQ. V-U SCALE, \$1.35 EA. 2 FOR \$2.00, P.P. NSW 80c, INTERSTATE \$1.25.

525V-O-525V

1 AMP POWER TRANSFORMER

0-230, 240, 250 primary 50Hz 8" x 51/4" x 8"

\$27.50 Fon, Road Rail Air

4" L x 34" W x 56" H fully shrouded short circuit proof Box of 10 \$4.95 P.P. 95c

#### SPARK PLUG SUPPRESSORS

Straight and R-Angle available 10 for \$2.30 P.P. 60c



AWA 12" SPEAKER SPECIAL

Model 12uA 15 ohms, 30W, rms, freq. 35, 6000Hz \$17.50.

P.P. NSW \$2.00 Interstate \$2.75 N.B. 8 ohm available March

#### MOTOROLA PIEZO-ELECTRIC SUPERHORN TWEETERS



\$12.95

\$22.95



P.P. 75c 35" SO

No cross over network required. No voice coil. Super efficient. Top quality reproduction. Excellent transient response. Low harmonic distortion. Less than 1.5% high imp. over 1000 ohm at 1kHz, and still above 20 ohm at 40 kHz. Power - 40 ohm 100W. 8 ohm 50W. 16 ohm 25W. Send S.A.E. for data.

#### AT REDUCED \$\$ FERRIS CAR GEAR

LIMITED STOCKS

Model JM-3001 (the latest) stereo car cassette with AM. FM. MPX. radio. 'Auto-eject" \$129.00 PP \$3.50.

30 watts per ch. stereo power amplifier booster \$32.75 PP \$1.50. Automatic AM/FM/CB 12V motorised antenna \$17.50 P.P. \$1.50

#### OLD-BUT BRAND NEW SELENIUM RECTIFIERS

Great for battery chargers.

20V 4 AMP full wave 4 for \$2.20 P.P. \$1.00

#### SERVICE

Moderate charges — Repairs guaranteed. Radios, Tape Recorders, Cassettes. Amps.

WE REGRET THAT PRICES ARE SUBJECT TO CHANGE WITHOUT NOTICE

## **New Products**

## **HP 3467A Logging Multimeter**

Recently released by Hewlett-Packard, the 3467A Logging Multimeter is a four-function DMM that also includes a four-channel scanner, a digital thermometer, maths function, and a printer in a single instrument.

HP's 3467A Logging Multimeter measures DC volts, resistance, true RMS AC volts and temperature. Temperature can be measured simultaneously with voltage or resistance to allow convenient analysis of temperature dependent parameters. Built-in maths functions can be used to convert measured inputs into units such as deviation, scaling, ratio and dB.

DC volts are measured with a sensitivity of 10 milliohms. A front panel zero adjustment can compensate for DC offsets of up to 2mV. Similarly, lead resistance of up to 20 ohms can be nulled out. A different zero offset for each channel may be stored and automatically subtracted from the readings.

Accurate true RMS AC voltage measurements with 10uV sensitivity can be made over a 100kHz bandwidth. The

diode test function supplies a 1mA constant current to forward bias diodes without damage.

HP's new 3467A Logging Multimeter can be used to make a large number of measurements, because of its four channels and its maths capability. Measured values from the first three channels may be automatically subtracted, multiplied or divided by a manually entered constant to provide fast calculated measurements. Maths operations can also be performed on the first three channels with respect to a measured input on the fourth channel.

Direct measurements of temperature changes about ambient, frequency response of amplifiers in dB, attenuator flatness, or turns ratio of transformers are just some of the input measurements that can be made. All

four inputs are floating and protected from overload.

The built-in thermal printer with timer can automatically or manually record measured data. A manual print command initiates a print out of the selected input channels. The 3467A is easily set up for unattended measurements. It automatically scans, measures and records the selected channels with elapsed time information at selectable scan intervals from one second to three hours over a 24-hour period. A time offset can be entered, via the front panel, to synchronize the timer to the time of day.

If a momentary power failure should occur, the 3467A remembers the maths constant, elapsed time information, zero offsets and ranges.

Applications of the HP 3467A include monitoring charge/discharge cycles of batteries; monitoring output voltage drift versus time during circuit warmup; sorting resistors according to percent error; three-phase voltage measurements; and monitoring solar heating designs.

The instrument can also be used in telecommunications and audio applications, and can make dBm measurements referenced to any impedance. Amplifiers and filters can be characterized directly in dB. Hot spots on circuit boards can be measured at more than one location, and temperature changes printed directly on hard copy.

For further information contact Hewlett-Packard Australia Pty Ltd, 31-41 Joseph St, Blackburn, Victoria 3130.



Quentron's Model 158 He-Ne laser is ideal for optics and communications experiments. Output power is 0.6mW, and it may be used either modulated or unmodulated. When used for voice communications, a small audio amplifier fitted with a photodetector (to convert it to an optical receiver) is also necessary.

Input impedance of the modulation transformer of the Model 158 is 8 ohms. It may be driven from the extension speaker outlet of a cassette player or

radio.

Further information from Quentron Optics Pty Ltd, 576-578 Port Rd, Allenby Gardens, South Australia 5009.



#### MAIL ORDER

## Service

We guarantee all orders will be despatched within 24 hours of receipt of order

740	00 SE	RIES	TTL			CM	os	400	0 5	ERIE	S
7400	\$0.28	7440	\$ 0.28	7495	\$0.90	4000	\$0.30	4020	\$1.30	4050	\$0.60
7401	0.28	7442	0.65	7496	1.00	4001	0.30	4021	1.30	4051	1.20
7402	0.28	7446		74100	1.50	4002	0.30	4022	1.30	4052	1.20
7403	0.28	7447		74107	0.50	4006	1.35	4023	0.30	4053	1.20
7404	0.28	7448		74109	0.55	4007	0.30	4024	0.90	4060	1.50
7405	0.28	7450	0.28	74121	0.55	4008	1.20	4025	0.30	4066	0.85
7406	0.40	7451	0.28	74122	0.60	4009	0.70	4027	0.70	4071	0.35
7407	0.40	7453	0.28	74123	0.90	4010	0.70	4028	1.20	4072	0.35
7408	0.28	7454	0.28	74125	0.70	4011	0.30	4029	1.20	4073	0.35
7409	0.28	7460	0.28	74126	0.70	4012	0.30	4030	0.45	4075	0.35
7410	0.28	7470	0.45	74132	1.10	4013	0.55	4035	1.70	4081	0.35
7411	0.28	7472	0.45	74141	1.25	4014	1.20	4040	1.20	4082	0.35
7412	0.28	7473	0.45			4015	1.15	4042	1.10	4510	1.40
7413	0.40	7474	0.50	74145	1.10	4016	0.50	4043	1.00	4511	1.40
7414	1.00	7475 7476	0.65	74151	1.10	4017	1.20	4044	1.00	4516	1.40
7416	0.50	7476	0.90	74153	1.10	4018	1.20	4046	2.10	4518	1.40
7417	0.50	7480	1.00	74154	1.50	4019	0.45	4049	0.60	4520	1.40
7420	0.28	7483	1.00	74157	1.00						
7421	0.30	7485	1.30	74160	1.20	EDE	EI '7	0 /70	CATA	LOGU	IE.
7423 7425	0.40	7486	0.50	74164	1.50	INE		0/ 13	UAIA	LUGU	JE .
7425	0.40	7489	2.40	74165	1.50						
7420	0.40	7490	0.65	74174 74176	1.50		Exermences		604 386 6048380, 2786	WR	ITE
7430	0.28	7491	0.90	74176	1.20						
7432	0.40	7492	0.65	74177	2.20			Kaga.			
7437	0.40	7493	0.65	74185	2.20					FC	R
7438	0.40	7494	0.90	74192	1.20		-1	3			
	ECIA		₹ ☆			S.				YOU	UR
555 Ti	5V 1A Reg	ulator			\$1.30	373				00	D.V
A TANK OF STREET STREET	egulator 14	DIL			.50	3.51		1		CO	PY
1N414	8 Diode				.05	-					
	n x 115mm							THE PARTY	20.00	NO	M/I
F'gla	ass 1oz Cu	Single Sid	ed		.50					140	VV :

PACK & POST 50c MINIMUM - PLEASE ALLOW MORE FOR HEAVIER ITEMS

LINEAR CLECTRONICS MAIL ORDER ELECTRONIC COMPONENTS

P.O. BOX 254. PUNCHBOWL 2196.

## RADIO DESPATCH SERVICE

#### THE SPECIALIST STORE

869 GEORGE STREET, SYDNEY, NSW 2000. (NEAR HARRIS STREET) PHONES: 211 0816, 211 0191

#### INTERSIL SINGLE CHIP PANEL METER EVALUATION KIT. ALL THE COMPONENTS YOU NEED. KIT NO. 7106.

- PC BOARD AND HARDWARE.
- A/D CONVERTER.
- LCD DISPLAY
- RESISTORS
- CAPACITORS WIRING DIAGRAM.
- APPLICATION NOTES.
- DATA SHEET (power supply not included).
- PRICE: \$39.10 inc. s/tax.
  TI 59 CALCULATOR PRICE: \$247.00 plus s/tax
- TI PC100 PRINTER PRICE: \$213.57 plus s/tax
  TI 30 STUDENT PACK PRICE: \$20.00 plus s/tax



SEE US FOR ALL TYPES OF VALVES. WE CAN SUPPLY ETI AND EA PC BOARDS, PACK CERT. POST \$1.90

Distributors of Cannon plugs and connectors, edge connectors and Texas Calculators.

Open: Mon.-Fri. 8.00 am-5.30 pm Thursday late night shopping until 8.30 pm. Saturday 8.00 am-11.45 am.

#### **New Products**

### **HV** power scope

A new four-channel oscilloscope designed by BWD Electronics provides a safe means of displaying and measuring high voltages in the field of power engineering. The instrument is said to be the first of its kind, and patents have been taken out to cover the design concept. The BWD model 880 Powerscope is capable of measuring from 100mV to 1000V, phase angle from 0 top 359°, and time from 5ns to 100 seconds. All four channels can be viewed simultaneously.

Special attention has been given to minimizing shock hazard. The panel, knobs, shafts and input sockets are insulated. The input sockets are also deeply recessed and the probes are specially designed to provide safe connections to power lines and direct inline equipment.

The four input amplifiers are sensitive enough to monitor control signals, interference and other low level signals less than 100mV, yet can also accommodate up to 660V RMS with overload to 3kV, without the use of divider probes.



The phase measuring section of the instrument is of special interest. It will accommodate power supply frequencies from 25Hz to 2kHz, and its digitally controlled phase-locked loop (PLL) will follow unstable frequency supplies such as small uncontrolled motor generators. The circuit provides an output pulse in 1º steps, selectable from 0 to 359° via a digital display. The pulse is 1º wide and may be used either for trace bright-up or as a timebase delay trigger.

When testing multiphase circuits, the phase pulse reference can be switched in 60° steps from 0 to 300°.

The power consumption of the model 880 is low and it may be operated from the AC power lines, DC or rechargeable batteries. Accessories availale include 1:1 ans 10:1 probes with 3kV peak operating voltage, sotrage over and camera.

Further information is available from BWD Electronics Pty Ltd, Miles Street, Mulgrave, Victoria, or Box 325, P.O. Springvale, Victoria 3171. Telephone (03) 561 2888, Telex 35115.

## Capacitance meter



The new B & K model 820 digital capacitance meter combines digital accuracy with full portability. It provides 10 ranges, covering from 0.1pF to 999,900uF with a minimum resolution of 0.1pF. Because the accuracy of the instrument greatly exceeds the tolerance of most capacitors, it may thus be used for hand selection and matching of components for critical use. At the same time it is also very easy to use, even by untrained production workers.

The model 820 comes with tilt stand, detailed manual and a spare fuse. Optional accessories include the BC-28 battery charger, BP-28 rechargeable battery pack and LC-28 carrying case.

Further information from Parameters Pty Ltd, 68 Alexander St, Crows Nest, NSW 2065. Telephone (02) 439 3288.

### Miniature relay

The ITT Components type RZ miniature relay is capable of being plugged into standard DIL IC sockets, measuring only 20.2 x 9.8 x 11.2mm. However it is fitted with two changeover contact sets capable of switching 1.25A and up to 125V AC or 150V DC in dry circuits, or 60V AC/75V DC in full load circuits. Operate and release times at nominal coil voltage are less than 6ms and 3ms respectively.

Five models of the relay are available, with nominal coil voltages of 4.5, 6, 12, 24 and 48V. Contact action is very reliably, as a crossbar technique is used.

Contact resistance is 50 milliohms typical, 100 milliohms maximum. Two different contact types are available, either AgPd 50 or AgPd 50 with 20um of AuAg. Typical contact life is 1 x 106 operations at 125V AC/50VA.

Further information is available from ITT distributor Instant Component Service, which has branches in most states.

PCB push button




C & K Components has developed momentary snap-action PCB-mounting pushbuttons with anti-stress brackets for vertical mounting. Excessive force applied to the switch is absorbed by the U-shaped mount, and not transmitted to the switch casing, PCB terminals or tracks. The type V40 switches are available in both SPDT and DPDT types and offer either 1A/120VAC/28VDC rating or 0.4VA/20V(AC/DC). Electrical life is 60k cycles minimum at full load.

Further information from C & K Electronics (Aust) Pty Ltd, 2/6 McFarlane St, Merrylands, NSW or PO Box 101, Merrylands, NSW 2160. Telephone (02) 682 3144.
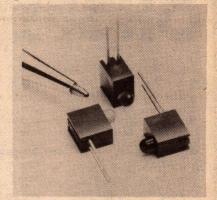
### **LED** indicators


The new Dialight 551 series of LED logic status indicators offers high reliability and long life combined with low cost and a choice of colours. Each consists of a T-1 LED packaged in a case less than 5.1m wide, designed for either PCB or panel mounting. The indicators are available with red, yellow or green LEDs, a red model also being available with a built-in series resistor for direct 5V operation.

The indicators are suitable for TTL, DTL or RTL drive, with typical operating characteristics of 1.6-2.4V at 20mA DC or 2.2V at 10mA for 2.0 mcd luminous intensity. Size of the case is 4.6 x 6.4 x 7.4mm, with the lens of the LED extended by 2.5mm to provide a wide viewing angle.



Further information from Philips Electronics Components and Materials, 67 Mars Road, Lane Cove NSW.

#### RF connectors

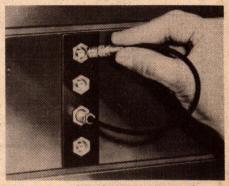

A range of Sealectro RF coaxial connectors is now available for recessed front panel presentation. Models are available in both 50 and 75 ohm.impedance and with screw or crimp type cable clamps. Clamps accept all standard coaxial cables such as RG 174/U, RG 188/AU and RG 316/U.

Full specifications, prices and other information from Acme Engineering Pty Ltd, 2-18 Canterbury Road, Kilsyth, Victoria.



## SAVE OVER \$100 ON SPEAKE

Dick Smith's amazing Playmaster hi fi speakers give you superb sound reproduction. Supplied in 'knocked down' form - incredibly easy to assemble in 2 hours.

- Three high-quality speakers (woofer, midrange, tweeter in each enclosure).
- Beautiful speaker cabinets feature wipe-clean vinyl finish - authentic timber appearance.
- Full instructions make assembly so easy your friends will never believe you built them.
- Designed by Neville Williams M.I.R.E.E. (Aust.), Editor-in-chief of Electronics Australia magazine.



IT'S SO EASY! You don't need special tools, materials or skills - just a screwdriver & a tube of wood glue! The Dick Smith Playmaster kit has all you need - precision manufactured so that everything just about 'falls into place. Simple, illustrated instructions supplied.



Illustrated above: Speaker fitted with acoustic foam grille (supplied).

**COMPLETE & MAIL OUR NO-RISK ORDER FORM TODAY!** 

12" 3-WAY (as illustrated above) KIT: \$28400 PAIR

**BUILT UP & TESTED** 

\*SAVE \$111 BY ASSEMBLING THEM YOURSELF

10" 3-WAY KIT

**BUILT UP & TESTED** 

\*SAVE \$101 BY ASSEMBLING THEM YOURSELF

8" 3-WAY KIT

## DICK SMITH

656 Bridge Road, RICHMOND. Ph. 42 1614 BRISBANE 166 Logan Road BURANDA Ph. 391 6233 147 Home Hwy, CHULLORA, Ph. 642 8922 162 Paustis Hwy, GORE HILL Ph. 439 5311 ADELAIDE 203 Wright Street, ADELAIDE Ph. 212 1962 BL Grose Street, PARRAMATTA Ph 683 1133

MAIL ORDERS P.O. Box 747, Crows Nest, N.S.W. 2065. Post and packing extra.

Note: Prices & stock availability could change between publication deadline & on-sale date due to circumstances beyond our control. Please check with our stores for latest availability & prices.

TO: Dick Smith Electronics Mail Order Centre. PO Box 747, Crows Nest, NSW 2065.

Please send me the Playmaster System(s) I have indicated below. I understand that if not completely satisfied, I may return them in good condition in original container within 14 days and receive a full refund of my money.

o 3-WAY self assembly	Kit\$149.50pair	
10" 3-WAY self assembly	kit\$224.00pair	


10". 3-WAY built up & tested......\$325.00pair 12" 3-WAY self assembly kit......\$284.00pair

12" 3-WAY built up & tested......\$395.00pair

Plus \$5.00 packing & delivery per pair

My cheque/money order for \$.....is enclosed OR charge my Bankcard No. 496.....

Expiry date.....Signature.....

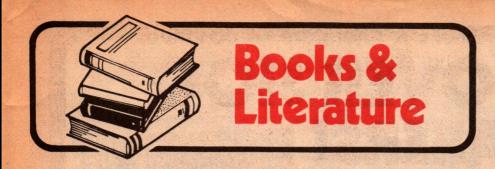

#### BASIC encyclopedia

THE BASIC HANDBOOK: An encyclopedia of the BASIC Computer Language, by David A. Lien. Compusoft Publishing, San Diego, 1978. Soft covers, 180 x 229mm, 360pp. Price in USA \$14.95.

Another book by Dr David Lien, the author of that well-known and widely acclaimed Tandy TRS-80 User's Manual which is now virtually a classic because of its excellent readability. This one seems to me very likely to become a classic also, for the same reason. Obviously Dr Lien is no ordinary technical author, but one of the few gifted with the ability to really communicate.

What he has produced in this case is a general-purpose reference manual on the BASIC language - its commands, statements, functions, operators, syntax and so on. And not just for the original



Dartmouth BASIC, but for a very large number of the "dialects" now in use on

computers big and small.

Each element of the language, in as many as possible of its known forms, is dealt with separately - but with cross references provided so you can work out how they go together. For each element you get what it does, how it is used, a sample of its usage, hints on its use, what to do if your computer/interpreter doesn't have it, known variations, and related elements to look

Sounds just what the doctor ordered, doesn't it? And it is. Just why no one thought of it before I don't know, but I think it's just as well that it had to wait for David Lien. If someone else had done it earlier, it probably wouldn't have been nearly as good, but would have stopped him doing it.

As it is, the conception is spot-on, the planning has obviously been thorough

and the execution is excellent. Every entry I checked was clearly written and eminently satisfying. It's nice to be able to write that about any book.

In short, a book which belongs alongside every computer running BASIC. And as there are more computers running BASIC than any other language, that suggests Compusoft Publishing has a real winner!

The review copy came from Dick Smith Electronics Pty Ltd, who say they hope to have stocks by the time this review is published. If you want a copy, I suggest you act fast — they're likely to go like hot cakes when word gets around. (J.R.)

#### Simple projects

ELECTRONIC PROJECTS FOR BEGINNERS, by F. G. Rayer. Bernard Babani (Publishing) Ltd, London, 1978. Soft covers, 108 pages, 112mm x 180mm, illustrated with circuits and wiring diagrams.

The term "beginner", as used in this title, is likely to be interpreted in different ways by different people, so it is probably worth commenting that the author fairly obviously intends the word to be taken literally, as judged by the simplicity of the projects. It is also significant that the first section (there are four in all) is devoted to "no soldering" projects.

The author explains this by pointing

out that some parents may feel that a soldering iron is not without its dangers in the hands of young beginners.



Again, this serves to set the level at which the book is aimed.

In addition to the "no soldering" section already mentioned the three remaining sections cover "Miscellaneous", "Radio and Audio Frequency" and "Power Supplies".

Between them they cover some 50 odd projects. There is also a useful list of equivalent semiconductors, together with drawings of typical base connections. (Unfortunately, with no indication as to whether these are above or underside views.)

To present this number of projects, with at least one and sometimes two drawings for each, in a book of this size is quite a task and, as can be imagined, does not leave a great deal of room for explanatory text. As a result, the text is almost exclusively devoted to how to build it, with little room to explain how it works. Even then, knowing the strife which beginners can encounter when working from much more detailed texts, one is forced to wonder whether the instructions are adequate.

Identification of components is also somewhat vague, such as a "300mW" or "1W" transistor, or "an output or speaker transformer", without any mention of impedance.

Another point worthy of comment is the inclusion of a project (a light dimmer) intended for direct mains connection, without a transformer. Granted, the author goes to some lengths to emphasise the need for care, but such a project seems out of place in a beginner's book.

These points aside, the book provides a useful collection of projects to hold the interest of the budding electronics enthusiast and, in conjunction with other texts, should help him put theory into practice. It would certainly make a useful addition to a beginner's library.

Our copy came direct from the publishers and the only price quoted is the English one of £1.35. No doubt it will become available through local booksellers shortly. (P.G.W.)


### Logic handbook

MASTER HANDBOOK OF DIGITAL LOGIC APPLICATIONS, by William L. Hunter. Soft covers, 390 pages, 210 x 130mm, illustrated with photographs, circuits and diagrams. Published 1976 by Tab Books, Blue Ridge Summit, Pennsylvania. Price in Australia \$10.95.

Pretentiously titled, this book could more correctly be regarded as a hand-book on the characteristics of different logic families. Even then the main
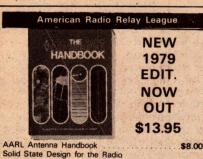
## W BOOKS

Just a few of the thousands in stock. Call in or write Prices subject to fluctuation. Correct at time of going to press



Radio Society Great Britain	
Amateur Radio Techniques, Hawker	.\$9.35
Vol. 1	\$21.85
Radio Communication Handbook	
Vol. 2	\$18.90
Test Equipment for the Radio Amateur	
— new 2nd edition 1978	\$11.75

Coil Winding Calculator: L/C/F Calculator

\$12.80

Amateur

Recent Popular Titles	
Amateur Radio Theory Course — Ameco	\$7.80
6800 Assembly Language Programming	\$12.55
Beam Antenna Handbook Orr	\$7.00
Be Your Own Television Repairman	\$2.95
Best of Creative Computing, Vol. 1	\$12.75
Best of Creative Computing, Vol. 1	\$12.75
Best of Byte Vol. 1	\$15.95
Cubical Quad Antennas, Orr	\$6.75
Ham & CB Antenna Dimension	
Charts, Noll	. \$3.90
Introduction to Microcomputers	
voi. 0 — beginners book, Adam	X
Osborne	.\$12.55
Vol. 1 — Basic Concepts, Adam	
Osborne	\$12.55
Vol. 2 — Some Real Products.	
Adam Osborne	\$21.55
Japanese Radio, Recorder Tape Player	Fall water
Schematic Servicing Manual	. \$9.90
Low & Medium Frequency Radio Scrap Book	27 EV
— Ham Radio Magazine	. \$9.85
Magazines — Byte: Interface Age; Kilobaud:	a Land
Personal Computing: — each Microcomputer Primer, a Sams	. \$4.00
Microcomputer Primer, a Sams	THE PARTY
publication	\$10.75
Personal Computing: A Beginners Guide,	242.70
Radio Amateur Antenna Handbook,	\$12.70
Hadio Amateur Antenna Handbook,	-0.00
Orr & Cowan	.\$9.90
Radio Handbook, Orr, New 20th edition Scelbi Byte Primer, Wadsworth &	.\$24.40
Scelbi Byte Primer, vvadsworth &	444.90
Helmers	\$10.00
Simple Low-Cost Wire Antennas For Radio	\$13.95
Amateurs, Orr	67.00
Truth About CB Antennas, Orr & Cowan	\$P.50
Transistor Substitution Handbook.	. 30.00
17th Ed	67.95
TTL Cookbook, Lancaster	\$12.70
VHF Handbook for Radio Amateurs.	\$12.70
Brier & Orr	60 50
World Radio TV Handbook guide to	. 30.00
the World's broadcasting & TV stations.	
1979 edition due soon!	
Reserve your copy now.	273
World DX Guide — Companion to World	
Podio TV Handbook	CO 0E
Radio TV Handbook 73 Dipole & Long-wire Antennas, Noll	. \$9.95
73 Vertical Beam & Triangle Antennas,	. \$0.75
Noll	£7.50

#### MAIL ORDERS BY RETURN

PLEASE ADD 90c per parcel postage (Vic.) \$1 70 per parcel interstate

**TECHNICAL BOOK &** MAGAZINE CO. 295-299 Swanston St., MELBOURNE 3000 Ph. 663 3951

#### **Books & Literature — continued**

emphasis is on high threshold logic and emitter-coupled logic.

Although aimed mainly at engineers and those already familiar with logic concepts, the first chapter of the book provides a brief review of basic logic circuits. The second chapter discusses the noise immunity of CMOS logic versus bipolar logic. Surprisingly, this is the only time that CMOS logic devices are discussed in the book, although the author writes mainly with industrial logic designers in mind.

The omission is even more surprising since the author devotes a complete chapter to the application of FETs in logic. He expounds their advantages of high fan-in and low power consumption, which are both possessed by CMOS logic.

Transistor-transistor-logic (TTL) is also virtually ignored.

The chapters on high-threshold logic and emitter-coupled logic are quite informative. Particularly useful in the ECL chapters is the information on design and use of micro-striplines on PCBs.

A final chapter discusses, in fair detail, some high frequency digital applications: IC crystal-controlled oscillators, a 500MHz frequency counter

and a digital frequency synthesizer. Summing up, this book will be of some use to logic designers but it certainly cannot be regarded as a comprehensive reference book. The review

copy came from Technical Book and Magazine Company, 289-299 Swanston Street, Melbourne, Victoria 3000. (L.D.S.)

#### Digital transducers


TRANSDUCERS IN DIGITAL SYSTEMS. G. A. Woolvet. Hard covers, 223 x 140mm, illustrated by photographs, circuits and diagrams. Published 1977 by Peter Peregrinus Ltd, PO Box 8, Southgate House, Stevenage, Herts. SG11HQ England. Price in UK £10.20.

According to the preface, this text provides a survey of transducers that give digital output. While it was published in 1977 and contains quite recent bibliographical entries, some of the text and diagrams appear quite dated. Transducers which are now commonly used, such as Gunn diode Doppler modules and Hall effect devices are not mentioned. LEDs are mentioned briefly but the whole area of solid state opto-electronics appears not to have been heard of. And A/D and D/A converters are treated as fairly esoteric devices available only from custom manufacturers, rather than the commonplace ICs they are now.

For this reason, the book seems likely to have only limited interest. Our review copy came direct from the publisher. (L.D.S.)
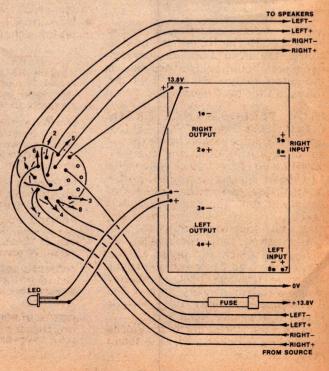
## NOTES & ERRATA

25W STEREO BOOSTER (January 1979, File No. 1/SA/61); The switch wiring diagram on page 42 was not compatible with the overlay diagram on the same page, and also implied the wrong switch rotation. A corrected diagram is reproduced here.



## INFORMATION CENTRE


COMPONENT AVAILABILITY: With respect, the article "An Electronic Thermometer" in the November, 1978 issue contains a gross error. The final paragraph says that the AD590 IC is available. I wrote to Parameters on November 4th and they referred me to a local agent etc, etc. But so far no component.

That does not seem to me a reasonable meaning of the word "available". (C.B., West Perth, WA).
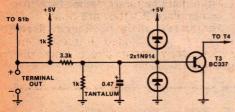
#### NOTES & ERRATA, cont.

COMPUTER TAPE INTERFACE (April 1977, File No. 2/CC/19): Readers experiencing difficulties in driving the unit with teleprinter rather than an electronic terminal may find it advantageous to change the base drive circuit of T3 so as to give a higher switching threshold.

The recommended circuit is reproduced below:



In some cases it may also be desirable to add a 1k pull-up resistor to the Q-bar output of FF3, to increase the available drive to T4.

MOVIE MIXER (September 1978, File No.1/MX/15): The 10k resistors used to convert the linear slider pots into log-law types should be connected from the rotors to ground, not from the rotors to the "top" ends.

HIGH PERFORMANCE TRAIN CONTROLLER (File No. 2/MC/16) October 1978. Some readers have expressed difficulty in obtaining the 12V 60/45W auto globe. In such instances a 12V 55W quartz halogen globe (available at auto accessory outlets) can be substituted. The only precaution necessary is to avoid touching the quartz envelope with the fingers.

Alternatively, any combination of 12V globes which add up to around 60W can be used. Typical combinations are three 12V 20W blinker indicator lamps wired in parallel, or two 12V 6/21W stop/tail lamps wired all four filaments in parallel (total 54W).

In all cases, at least one of the globes should be positioned under the 18mm hole in the PCB.

Before publishing any project in "Electronics Australia", we check first to ensure that all parts will be available. The electronic thermometer was no exception. Heavy demand did lead to a temporary shortage of the AD590, but Parameters Pty Ltd quickly imported additional stocks and the supply situation is now back to normal. The device can be obtained in Perth from W. J. Moncrieff, 176 Wittenoom St, East Perth; or from Rablec Engineering, 255 Hay St, Subiaco. Radio Despatch Service, 869 Goerge St, Sydney also carry stocks of the AD590.

MINI-SCAMP MICROCOMPUTER: I have constructed the Mini-Scamp computer and have several technical queries regarding it, and it's connection to some of the computer peripheral devices featured as constructional articles in the magazine.

Firstly, is it possible to use the NRZ cassette interface unit, described in "Getting Into Microprocessors" with Mini-Scamp? If so, how would I go about adapting it from R\$232 interfacing standards to 20mA current loop standards?

Secondly can Mini-Scamp be used in conjunction with the software-controlled Ultra Low Cost VDU? Would it be possible to generate a VMA signal from the SC/MP processor? If this VDU can be used, is more than 1k of memory required?

If extra memory is required, could the memory expansion board for the 2650 Mini-Computer be adapted? (A.P., Terrigal, NSW 2260).

• It is possible to use the NRZ recording technique with Mini-Scamp.

As far as converting the circuits published to 20mA standards are concerned, you will have to work out the exact details yourself, as this is beyond the scope of the Information Service.

Again, Mini-Scamp can be used with the software controlled VDU, but again you will have to work out the exact interfacing details yourself. Extra memory will probably be required, and the memory boards from the 2650 Mini Computer could be used to provide this.

WHISTLE FILTER: Would you please consider publishing information on how to retune the 10kHz whistle filters currently used in wide band AM tuners. With the new broadcast station spacing of 9kHz the filters will need to be reset to 9kHz. The tuner which I have is the Playmaster 123. There would probably be many others who would like this information. (MC., Cranbourne South, Victoria.)

• There's not a great deal involved in the job, M.C. In fact with some whistle filter coils it may be possible simply to re-tune to 9kHz by adjustment of the coil slug or pot-core air gap. An alternative to this for circuits which use a 100mH whistle filter coil (like the Playmaster 123 Tuner) is to simply connect a 560pF capacitor across the coil and existing capacitors, whereupon the coil should need only slight adjustment.

As Leo Simpson explains in this month's article on pages 58-59, you can set the null to 9kHz reasonably well by ear.

If you are unable to complete an "Electronics Australia" project because you missed out on your regular issue, we can usually provide emergency assistance on the following basis:

PHOTOSTAT COPIES: \$2 per project, or \$2 per part where a project spreads over multiple issues. Requests can be handled more speedily if projects are positively identified, and if not accompanied by technical queries.

METALWORK DYELINES: Available for most projects at \$2 each, showing dimensions, holes, cutouts, etc., but no wiring details.

PRINTED BOARD PATTERNS: Dyeline transparencies, actual size but of limited contrast: \$2. Specify positive or negative. We do not sell PC boards.

PROJECT QUERIES: Members of our technical staff are NOT available to discuss individual projects, either in person at our office or by telephone.

REPLIES BY POST: Limited to advice concerning projects published within the past two years. Charge \$2. We cannot provide lengthy

answers, undertake special research or discuss design changes.

BACK NUMBERS: Available only until our stocks are exhausted. Within three months of publication, face value. Four months and older, if available, \$2. Post and packing 60c per issue extra.

OTHER QUERIES: Technical queries outside the scope of "Replies by Post" may be submitted without fee, for reply in the magazine, at the discretion of the Editor.

COMMERCIAL, SURPLUS EQUIPMENT: No information can be supplied.

COMPONENTS: We do not deal in electronic components. Prices, specifications, etc., should be sought from advertisers or agents.

REMITTANCES: Must be negotiable in Australia and made payable to "Electronics Australia". Where the exact charge may be in doubt, we recommend submitting an open cheque endorsed with a suitable limitation.

ADDRESS: All requests to the Assistant Editor, "Electronics Australia", Box 163, Beaconsfield, 2014.

#### **OUR LATEST HANDBOOK**

## PROJECTS & CIRCUITS

**NUMBER TWO** 



#### 27 DO-IT-YOURSELF PROJECTS FROM ELECTRONICS AUSTRALIA

You can't afford to miss out on this exciting new book from "Electronics Australia". Here are just a few of the projects it contains: remote TV headphones, multi-band vertical aerial, roulette wheel, radar burglar alarm, model train control, voice-operated relay, transistor tester, water level alarm... plus many more. Get your copy now!

Available from

"Electronics Australia", 57 Regent St. Sydney. PRICE \$3.00 OR by mail order from "Electronics Australia", PO Box 163, Beaconsfield, 2014. PRICE \$3.60.



FREE SAMPLE LED against 20c SAE
To see is to buy. Best value in LED
in Aust. No brag just fact. Quality.
17c ea. \$12 a 100, \$110 a 1000. 40c P&P
5mm red well diffused wide viewing angle.
Clips 3c each all quantities. Diggerman
Electronics, Box 33. Coramba. NSW 2466.

### The ABC's of MODEL RAILROADING

The ideal book for beginners. \$4.50 plus \$1.50 postage and packing. SAE for complete list of Model Railway books.

P. J. P. PRODUCTIONS

20 Daly Street, Gisborne, Victoria 3437

Mail Order Specialists for Model Railway Equipment.

### TIME CLOCKS SANGAMO



LESS
DAY OMIT
DEVICE
\$13.50
WITH
DAY OMIT
DEVICE
\$16.00

240V 50 cs 15A Contacts

Used, tested and guaranteed PACK & POST N.S.W. \$2.00 Vic and QId \$2.90, W.A. \$3.40

P.O. Box 147 LINDFIELD, N.S.W. 2070

## Marketplace

#### FOR SALE

JUST ARRIVED SUPER BARGAINS!!! POPULAR SEMICONDUCTORS AT BARGAIN PRICES!! SATISFACTION GUARANTEED OR YOUR MONEY BACK!!!

IN4007 (1000v, 1A) — 10 for \$1.70, BC209 — 10 for \$1.80, BC209C — 10 for \$3.50, CMOS ICs: — 4006 — \$1.50, 4013 — 70c, 4017 — \$1.50, 4018 — \$1.50, 4024 — \$1.00, 4026 — \$2.50, 4027 — \$1, 4029 — \$2, 4035 — \$1.50, 4047 — \$1.50, 4049 — \$1, 4055 — \$2.50, More Transistors: BC204 — 10 for \$1.80, BC206 — 10 for \$1.80, 2N2219A — 60c, 2N3563 — 55c, 2N3566 — 35c, 2N3638 — 50c, 2N3639 — 50c, 2N3646 — 50c, TAA611B: — 4 watts Peak Audio IC, 12v supply into 8 ohm load (including Cct diagram) — \$1.75 ea or 4 for \$6.50.

TBA651: TUNER + IF AMP. IC RF AMP, mixer, oscillator, IF amp, and AGC control, all in single IC. Supply voltage 4.5 to 18v (incl. Cct diagram) — \$2.95 ea or 4 for \$10.

TBA810A: — 13 WATTS PEAK AUDIO IC HIGH POWER. 16 volts supply into 4 ohm load gives 13 watts peak — \$3.95 ea or 4 for \$14 (incl Cct diagram)

SUPER BARGAIN PACKS: RESISTOR PACK: (½ and 1w) — 100 for \$1. POLYESTER CAP. PACK: (High and low volt) — 100 for \$2.95. CERAMIC CAP PACK: (Disc + Tubular Caps) — 100 for \$2. POST AND PACK: (Disc + Tubular Caps) — 100 for \$2. POST AND PACK 60c or extra for heavy parcels. MICRONICS, PO Box 175. Randwick, NSW 2031.

SPEECH SCRAMBLERS, suit radio-phone or telephone. Details: Box 65, Gladesville 2111 or (02) 89 0661. SPEAKER BOXES. Hand-made, excellent acoustically Write: Sherwood Electronics, PO Sherbrooke 3789.

MAKE FRIENDS with your Tape Recorder. Join ATRA the Australian Tapespondence Club. Members in all States and overseas. All welcome. SAE to ATRA, Box 970. GPO Adelaide 5001.

AUSTRALIAN RADIO DX CLUB. Radio DXing is the ideal hobby for the young people of today. 1979 will be world DX Youth Year. The club covers shortwave, medium wave and utility DXing. So why not take up this hobby right now, it's scientific and fascinating. Listen and GSL those distant radio stations. For further details write to PO Box 67 Highett, Victoria 3100 or PO Box 79 Narrabeen, NSW 2101.

DISPLAY ADVERTISEMENTS IN MARKETPLACE are available in sizes from a minimum of 2cm x 1 col rated at \$11 per col cm.

CLASSIFIED RATES \$2 per line per insertion payable in advance. Minimum two lines.

CLOSING DATE is six weeks prior to the on-sale date. Issues are on sale the first Monday of each month

ADDRESS all classified orders, copy, enquiries, etc., to: The Advertising Manager, ELECTRONICS Australia, Box 162, Beaconsfield 2014.



## An introduction to Digital Electronics

You don't need any previous knowledge of digital electronics — the book starts you right from scratch, and covers all of the basic concepts you need.

Available from "Electronics Australia", PO Box 163 Beaconsfield, NSW 2014. Price \$3.50 plus 60c pack and post. Also from 57-59 Regent St, Sydney.

## Now available

top quality rebuilt colour picture tubes B & W also supplied Prompt service Very competitive prices

Write or phone:

## **COLOR TUBES INTERNATIONAL**

1 CARTER ROAD, BROOKVALE, NSW 2100 (Office and Factory) (02) 938 4063

## **ELECTROCRAFT** PTY. LTD.

68 WHITING STREET, ARTARMON 2064 TELEPHONE 438 4308, 438 3266

We have the largest range of TV antenna accessories in Sydney. (Check our prices)

#### TRADE AND WHOLESALE SUPPLIED

Television, complete range of Aerials — Fly Leads Splitters — Baluns — Plugs etc. Masting, 8' to 15'. Telescopic masts (not self supporting 20' \$23.55, 30' \$37.60, 40' \$51.30, 50' \$66.00. Field Strength Meter for TV TES Mc661 40-480Mhz continuous in 6 ranges, battery operated in Leather case, \$257.60. \$4.70 Spirals CB EQUIPMENT GB TM/13 UHF CB Beam 15dB forward gain (Ref Dipole) 465 to 477Mhz \$35.95. GB 1/4 wave spiral tuned base station aerial, good

skip work. SWR 1 1 1 Rotators CDE ARXL Fully approved \$124.14. CB27 Belling Lee Helical whip 5' complete with base and 3.6M of cable, \$18.

#### SWR & POWER METER

Model ME-11X. Specifications: maximum handling power 100W -SWR indication 1:1 to 3:1 - frequency range 3.5 to 150MHz. \$16.20.

FM ANTENNAS 19 68 11.55 Hills FM1 Local Hills 353 3.el Met 14.72 Matchmaster FMG/2 Semi fringe ......
Matchmaster FMG/6 Outer fringe ..... TV ANTENNAS Hills outer fringe CA.16 phase array Hills 215 (Australia's best selling high gain 8.el antenna at a new low price) . . . . Hills EFC.3 (The best of the colour 75 ohm antennas very high gain, good antiahosting Channelmaster 3111A 300-75 ohm (Best metropolitan Anti-ghosting antenna) Channelmaster 3110 300-75 ohm local anti-27.96 ghosting ...... Belling Lee plugs 0.80 Belling Lee Coaxial wall sockets . . . . . 1.75

R.F. Amplifiers, Masthead & Distribution for FM & 45.00 16dB Ecraft 25dB Ecraft

Please enclose postage with all orders

WE ARE THE EXPERTS - 30 YEARS IN THE ANTENNA BUSINESS

OPEN SATURDAY MORNINGS 8.30-12

#### DICK SMITH ELECTRONICS



### ENGINEERING MANAGER

Owing to the continuing expansion of our company, we have a position for a competent electronics engineer to take charge of our technical section.

This responsible position includes new product evaluation, some design and quality control, in fact all technical advice required for our company. Qualifications are an advantage but not as necessary as a good technical knowledge of all our products from simple kits to microcomputers.

This is a challenging position for anyone with a bit of 'get up and go'.

Apply in writing to: Dick Smith, Managing Director, Dick Smith Electronics. 24 Carlotta Street, ARTARMON. NSW. 2064.

#### MAIL ORDERING FROM US MAKES CENTS FOR YOU -

If any of these models are advertised at a lower price in this magazine, tell us and we will supply them at a lower price. Check our price on the model you want — WHY PAY MORE? We Offer — SERVICE — SATISFACTION — and SUPER SAVINGS.

#### TEXAS PROGRAMMABLE SYSTEMS

PC100A Alpha-Numeric Printer \$278 \$210 (\$234)

For Ti59 and 58 — Lists, Traces, Prints Words (64 characters). Plots Graphs, etc.

MODULES \$36 \$32 ea plug into Ti59 or 58. Pre-programmed with

approx. 5000 steps.

- Leisure Time Marine Navigation
- Real Estate and Investment
- Statistics
- Surveying
- **Business Decisions**
- Securities Analysis

#### NEW MODULES

- Maths/Utility
- Electrical Engineering

etc. (Write for details).

#### **GREATEST PACKAGE OFFER EVER!!**

A ti59 and PC100A printer \$686 only \$450 (\$503)

Desk Computers, AX1 & BX1 (basic) — floppy disk

DESK CALCULATORS/MINI COMPUTERS/

ANSWERING MACHINES/DICTATING MACHINES/CASH REGISTERS

TERMS - LEASING - EXTRA 5% OFF FOR CASH

(Also any extra modules ordered with package only \$30 ea.)

#### Ti59 \$326 \$245 (\$274)

Hills MH1 Masthead 300 ohms

Programmable to 960 steps or 100 memories, also master module with 5000 steps, magnetic cards, 3 manuals, program pad, charger, carrying cases etc.

Extra Magnetic Cards Pack of 40 and case \$15

Specialty Pakettes \$10 ea.

Programs for mag. cards - Electronic Eng • Civil Engineering • Statistics

- Programming Aids (Decoders and disassemblers ) • Securities
- Oil/gas energy Black body
   Printer utility

ALSO

Ti58 \$141 \$108 (\$120) Ti57 \$92 \$73 (\$82) Ti55 \$67 \$52 (\$58) MBA \$82 \$75 (\$83)

**NEW CANON** 

PACKING & POSTING — All LCD models \$1.50 anywhere in Australia. Otherwise \$2.00 for NSW, elsewyere \$3.00 per order for certified mail. (Another \$1.50 if you require registered.)

SALES TAX FORMS must be duly signed and stamped.

(Forms available.)

#### HEWLETT hp PACKARD

61.00

#### SPECIAL OFFER FREE! and SUPER LOW PRICES

HP 31F \$60 (\$67) (replacement for HP21)

HP 32E \$80 (\$89) (replacement for HP45)

HP 33E \$100 (\$112) (replacement for HP25)

HP 29C \$162 (\$181)

HP 19C \$210 (\$234) (a 29C with printer)

HP 38E \$120 (\$134) (programmable business)

HP 67 \$450 (\$501) (card programmable)

HP 97 \$750 (\$835) (a 67 with printer)

HP 10A \$165 (\$184) (basic funcs. & printer)

#### School and College Super Specials

(SCIENTIFIC MODELS)

CANON F41 (22 functions) \$16.90 (\$18.99) CASIO fx31 129 functions) \$19.90 (\$22.40) TEXAX Ti25 (L.C.D.) \$27 (\$30)

NATIONAL SEMICONDUCTOR NS108 (L.C.D./50 funcs.) \$36 (\$41)

#### WE WILL NEGOTIATE PRICE ON QUANTITY ORDERS

WELCOME HERE COPY OR COMPLETE: Please debit my Bankcard

NO. ..... Expiry Date .....

Signature .....

SEND A STAMPED ADDRESSED ENVELOPE FOR OUR FREE COMPLETE DISCOUNT PRICE LIST ON ALL MODELS HEWLETT PACKARD - CANON - CASIO - SANYO - SHARP - NATIONAL SEMICONDUCTOR

#### DISCOUNTS ECTRONIC CALCULATOR

Phone (02) 624 8849 (8am till 3pm) P.O. Box 106, Baulkham Hills, N.S.W. 2153

## Electronics is going digital. This book can help YOU go right along with it:

Electronic equipment now plays an important role in almost every field of human endeavour. And every day, more and more electronic equipment is "going digital"

Even professional engineers and technicians find it hard to keep pace. In order to understand new developments, you need a good grounding in basic digital conmcepts, and An Introduction to Digital Electronics can give you that grounding. Tens of thousands of people engineers, technicians, students and hobbyists - have used the first and second editions of this book to find out what the digital revolution is all about.

The new third edition has been updated and expanded, to make it of even greater value. The author is Jamieson Rowe, Editor of "Electronics Australia" magazine, a qualified engineer and



## **ONLY \$3.50**

(PLUS PACKAGE AND POSTAGE)

## Here are the chapter headings:

- 1. Signals, circuits and logic
- 2. Basic logic elements
- 2. Basic logic elements 12. Basic reador 3. Logic circuit "families" 13. Multiplexing
- 4. Logic convention and laws
- 5. Logic design: theory6. Logic design: practice
- 7. Numbers, data & codes
- 8. The flipflop family
- Flipflops in registers
- 10. Flipflops in counters

- 11. Encoding and decoding
- 12. Basic readout devices
- 14. Binary arithmetic
  - 15. Arithmetic circuits
  - 16. Timing & Control
  - 17. Memory: RAMs
  - 18. ROMs & PROMs
  - 19. CCD's & magnetic bubbles

Glossary of terms

Available from "Electronics Australia", 57 Regent St, Sydney. PRICE \$3.50 OR by mail order from "Electronics Australia", PO Box 163, Beaconsfield 2014. PRICE \$4.10.



Subscription Rates \$18.00 per year within Australia. \$A21.00 per year

Make sure you receive every copy of the magazine by ordering it from your newsagent or the publisher For publisher subscriptions post this coupon, with your remittance, to Electronics Australia Subscription Dept. John Fairfax & Sons Ltd. GPO Box 506. Sydney. 2001. Subscription will start with first available

. . . . . . . Enclosed is . . . . . . . for

## **ADVERTISING** INDEX

ADVERTISER	PAGE
A & R Soanar	117
ASP Microcomputers	89
Abacus Computer Store	100
Academy of Sound Recording Engineers	31
Ace Radio	118
Adcola Products	73
All Electronic Components Audio Engineers Pty Ltd	62 83
Audio Telex Communications Pty Ltd	107
BSR Hi-Fi	80
BWD Electronics Pty Ltd	8
Bail Electronic Services	110
Bright Star Crystals	112
Butterworths Pty Ltd C & K Electronics (Aust.) Pty Ltd	50
Cash-More Sound Systems Pty Ltd	13 70
Cema (Distributors) Pty Ltd	7
Classic Radio	30
Clock Disposal Co.	126
Colour Tubes International	126
Convoy International Pty Ltd	22
Deitch Bros	68
Dick Smith Electronic Group 20, 21, 3 71, 78, 104, 114, 122	1, 53,
Diggerman Electronics	126
Dindy Marketing (Aust.) Pty Ltd	29
E. D. & E. (Sales) Pty Ltd	62
Economic Digital Control Pty Ltd	103
Electrocraft Pty Ltd	127
Electronic & Semi Conductor Disposals	121
Electronic Agencies	67 115
Electronic Calculator Discounts	127
Elmeasco Instruments Pty Ltd	40
General Electronic Services Pty Ltd	28
Hagemeyer (Aust.)	IBC
Kenelec (Aust.) Pty Ltd Lanthur Electronics	65
Linear Electronics	75 120
110	7, 98
National Panasonic (Australia) Pty Ltd	OBC
Nomis Electronics Pty Ltd.	8
P.J.P. Productions	126
Paris Radio Electronics Pennywise Peripherals	91
Plessey Australia Pty Ltd	90
Radio Despatch Service	120
Radio Parts Group	106
Rod Irving Electronics	95
School of Electronics	31
Sheridan Electronics	74
Sontron Instruments Soundring Distributors	99
Stanton Magnetics, Inc.	70
Stewart Electronics	92
Stotts Technical College	33
	, IFC
Tandy International Electronics	57
Tasman Electronics	73
Technical Book & Magazine Co.	124
Tecnico Electronics	47
Techniparts .	87
The Byte Shop	91
/icom International	108
Vidio Technics	
	15
Warburton Franki Ltd	18
Wardrope & Carroll Engineering Pty Ltd	75
Vireless Institute of Australia	113

# The competition don't like the sound of this at all.

For quite some time, other manufacturers have been trying to produce tape with the qualities of the Maxell UD-XL. At the same time, Maxell have been quietly perfecting an even better series.

The UD-XL I and UD-XL II tapes are designed to attain maximum performance at the ferric and chrome position on your tape deck. Whichever tape position you choose, Maxell can give you a better performance.

#### UD-XLITAPE, FORFERRIC (norm.) POSITION (120us)

UD-XL I offers an excellent sensitivity of 1 dB higher than even UD-XL. MOL performance is also 1 dB higher over the entire audio frequency spectrum. The result is a new standard in ferric tape, with wider dynamic range and less distortion than ever before.

How does the UD-XL I compare then, with ordinary low-noise tapes?

Sensitivity is higher by 2.5 dB, and MOL performance by as much as 6 dB.

Yet, for all this UD-XL I requires no special bias or equalization. Simply set your tape selector as you normally would at the ferric position – but there the comparison ends.

#### UD-XLIITAPE, FOR THE CHROME POSITION (70us)

UD-XL II tape is such a dramatic improvement on most other tape that can be used in this position, that comparison is really unfair.

For example, if you're familiar with conventional chromium-dioxide tape, you'll know of the associated problems of poor output uniformity plus low maximum output level and rather high distortion.

UD-XL II tape offers you excellent MOL, sensitivity, and an output improvement of more than 2 dB over the entire frequency range.

Maxell's unique 'Epitaxial' process gives you absolute sensitivity and stability, and no drop-out problems. What's more, the shells are moulded in diamond cut dies, and made to tolerances 5 times greater than the Philips standard. And, like all Maxell tapes, UD-XL II has the 5-second cleaning leader.

In short, if you're recording in the chrome position, you can now achieve all the advantages – with none of the drawbacks.

A prospect we think you'll find very exciting – even if the competition don't.





## Yet another first for lechnics.

Technics have been the innovators of so many outstanding new concepts in audio technology. And they have done it again: the RS-M85, the world's first quartz locked directdrive flat type cassette deck. It has so many design features like the rugged two-motor tape drive including a direct-drive capstan motor; feather-touch IC logic controls; radically new style peak/VU meters; and an incredible wow and flutter rating of just 0.035% (WRMS). The bar graph FL (fluorescent) level meters are the most novel features of the RS-M85. Electronically controlled, so

response time is instantaneous,

these make conventional needle-

type meters obsolete. Highly accurate, the FL meters give direct parallel readout for instant comparison between channels.

The capstan drive has a quartz-locked servo system that keeps tape speed constant. The record/playback head is laminated with Sendust, a recently developed material which is exceptionally hard and durable. Wide frequency response and negligible distortion contribute to the high quality in sound reproduction. The RS-M85 is just one of the exciting models from the range of Technics cassette decks. See them for yourself at your dealer.



For a National Technics catalogue please write to: National Technics Advisory Service, P.O. Box 278, Kensington, N.S.W. 2033